

EE 105

Microelectronic Devices and Circuits

Bernhard E. Boser

University of California, Berkeley




boser@eecs.berkeley.edu

Copyright © 2012 by Bernhard Boser



Small & Large Signals

- Why the fuss?
 - Example: Gain
- Definitions & Nomenclature
- Simplifying life:
 - Small-signal models
- Design: break a hard problem into two simpler ones!
 - Small-signal characteristics
Usually the stuff we care about:
Gain, input/output resistance, bandwidth, ...
 - Large-signal characteristics (“biasing”)
What we need to ensure so that our circuit works as expected,
especially that it actually has all the small-signal characteristics we
care about!



Gain 1: Ideal Amplifier

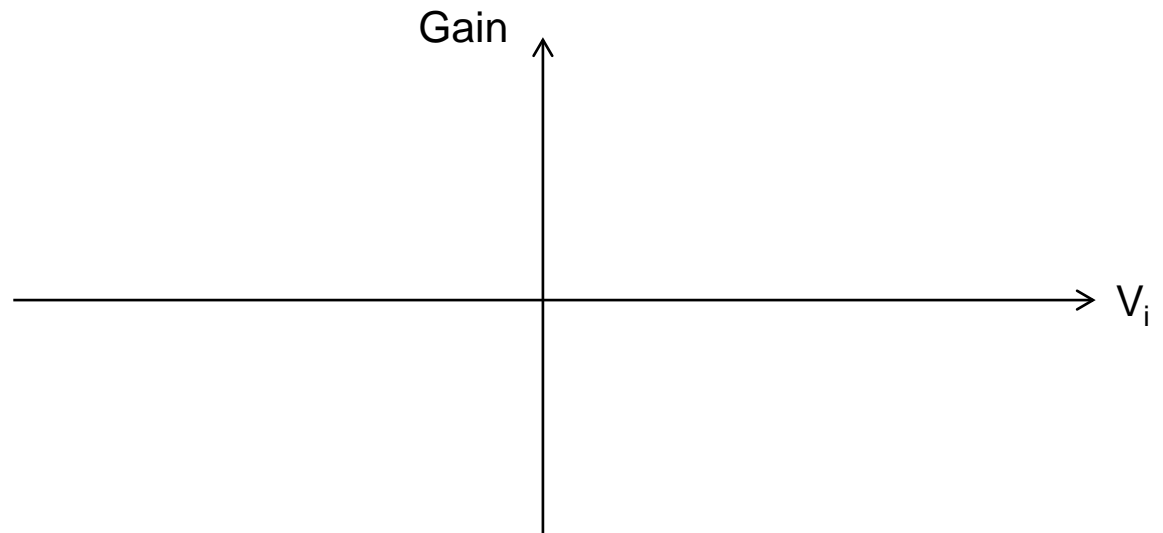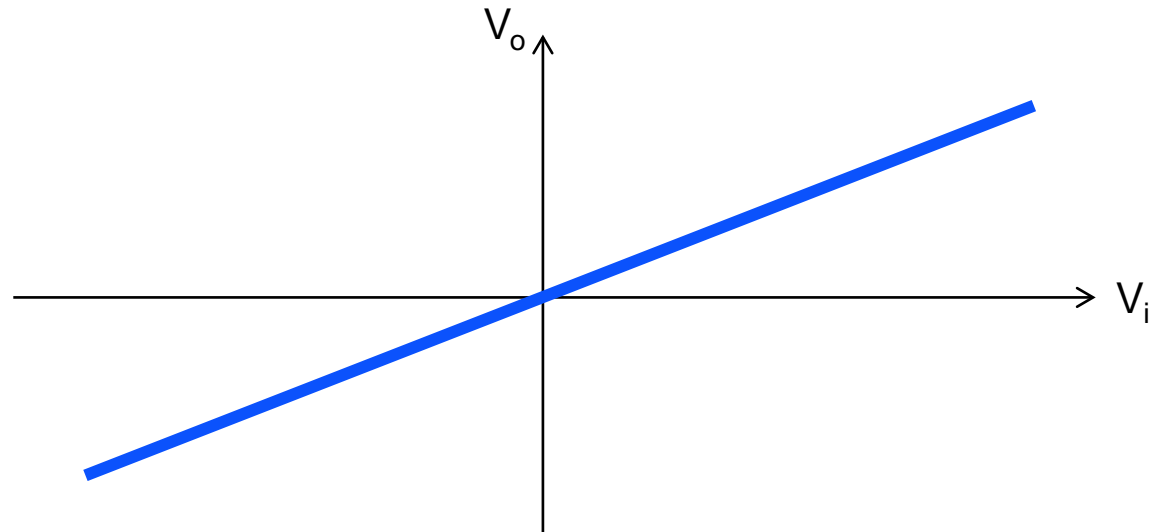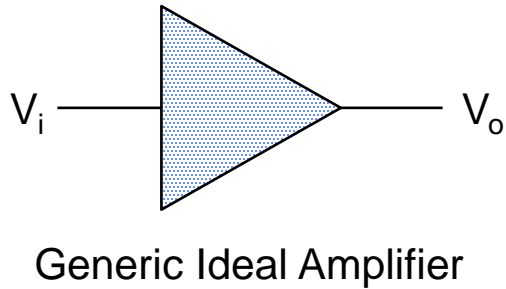


Gain 2: Practical Amplifier

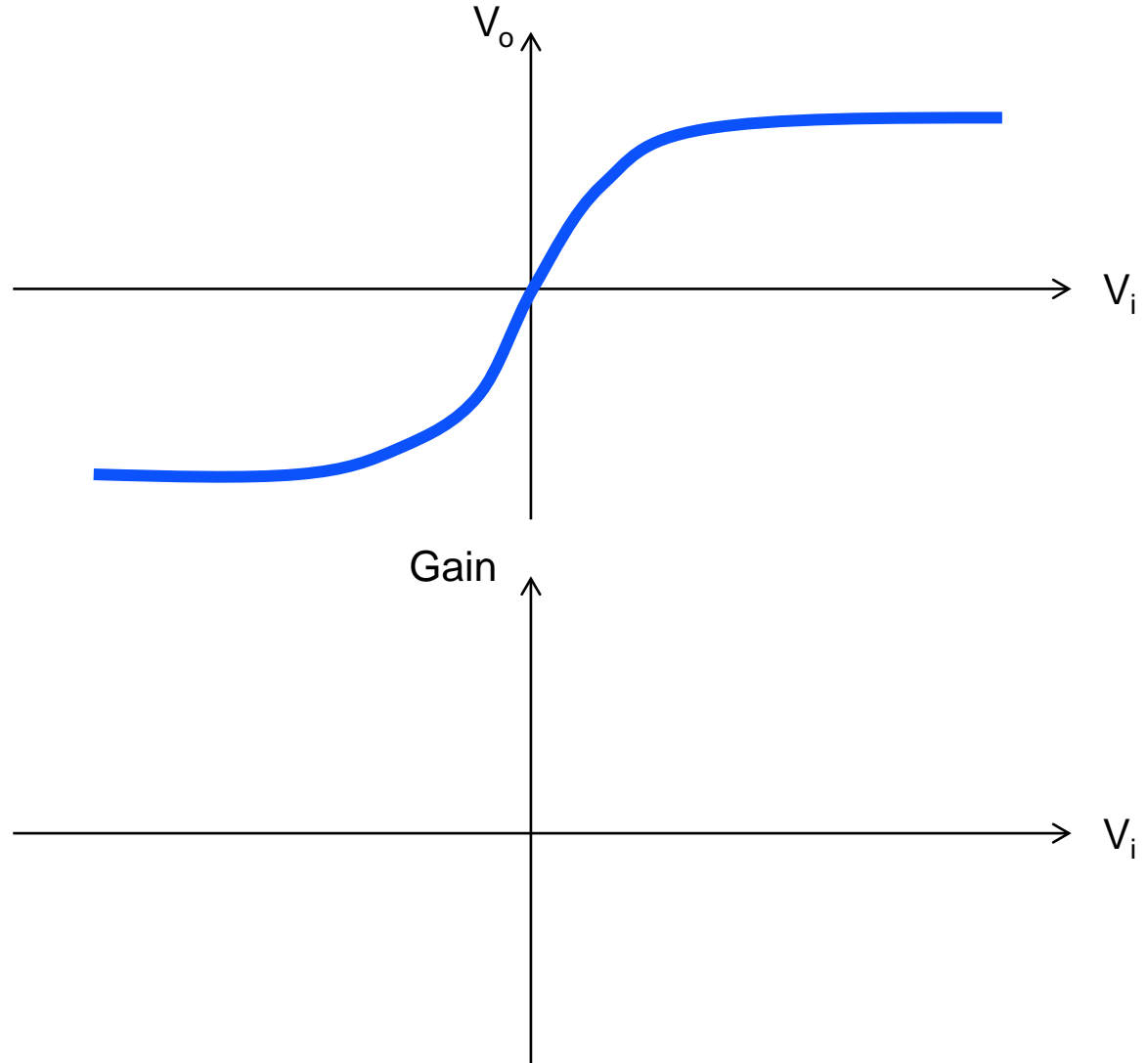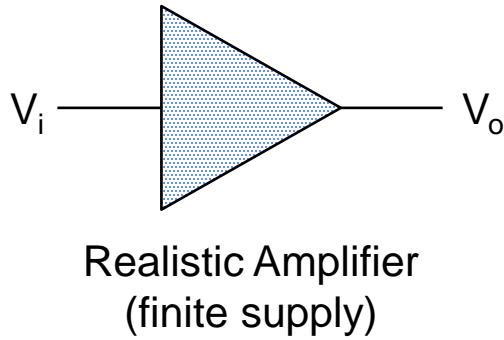

Gain 3: Common-Emitter Amplifier Example

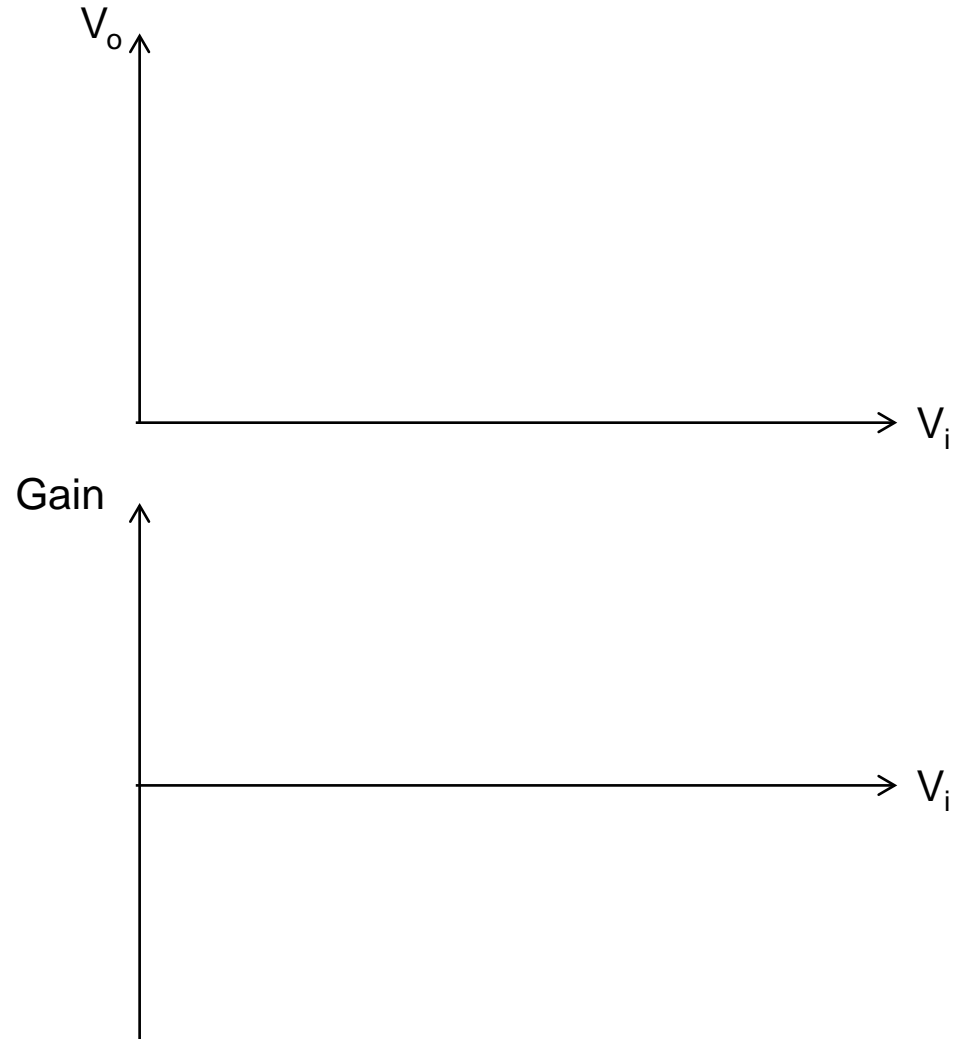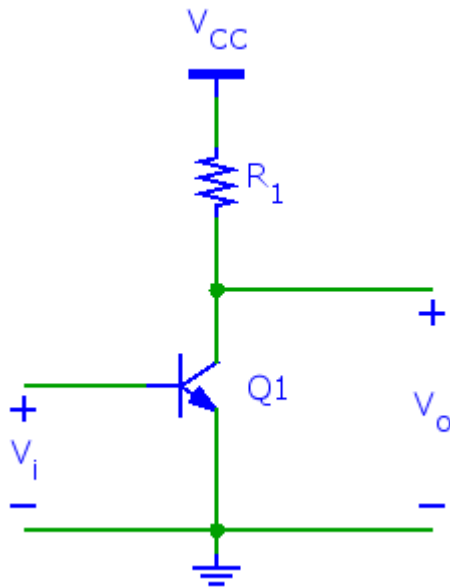

Large- and Small-Signal Definitions

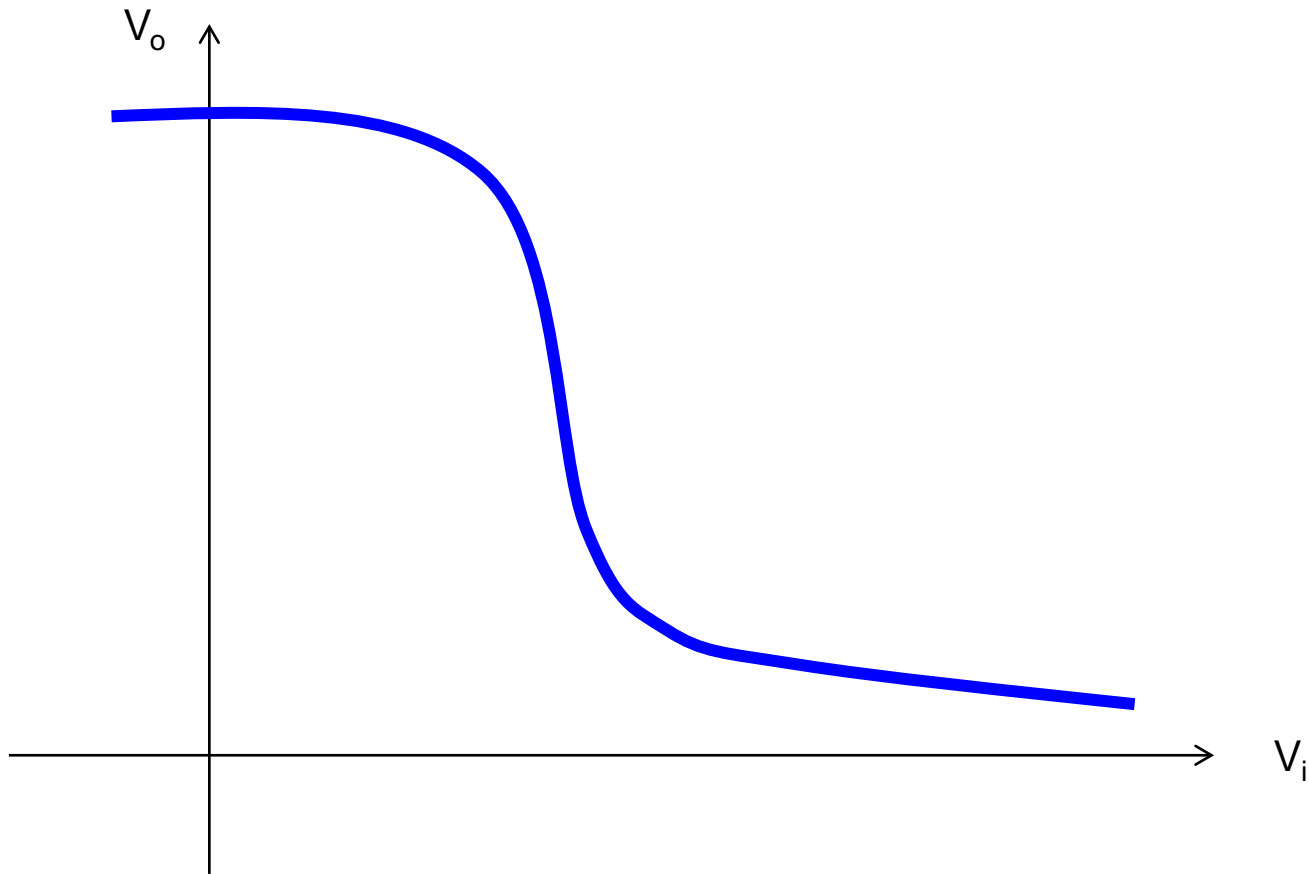

Large- and Small-Signal Nomenclature

V_x	Large Signal (rarely used) (lower case subscript)
= V_x	Bias (constant) (upper case subscript)
+ v_x	Small Signal (varying) (all lower case)

Nomenclature introduced in
Gray & Meyer, *Analysis and design of analog integrated circuits*, Wiley 1974.

Amplifier (Analog Circuit) Design

Design

small-signal characteristics


and

bias

separately

Break difficult problem into two simpler ones!

Example: voltage gain

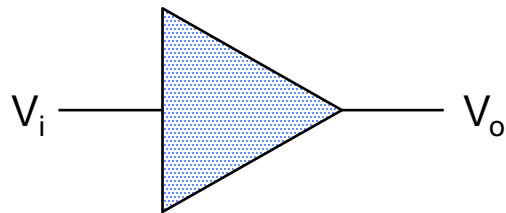

Objective:

- Design amplifier with $a_v = v_o/v_i = -2$
- $R_L = 10\text{k}\Omega$

1) Amplifier Topology


2) Small-Signal Design

3) Bias Design


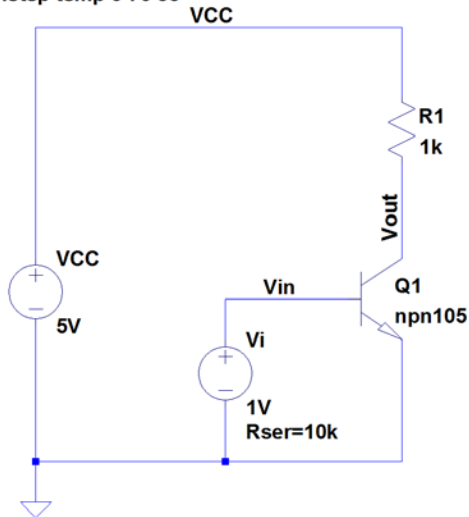
4) Verification (SPICE, lab)

Circuit


```
.model npn105 npn(is=10fA bf=100 vaf=100V)  
.dc Vi 500mV 1.4V 1mV  
.step temp 0 70 35
```



Verification

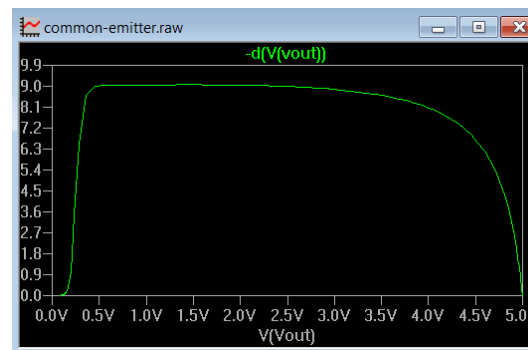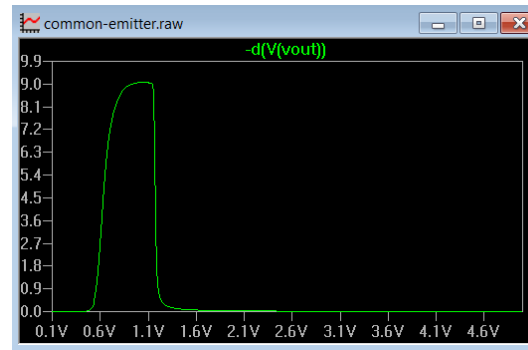

Is Circuit Robust? e.g. Temperature

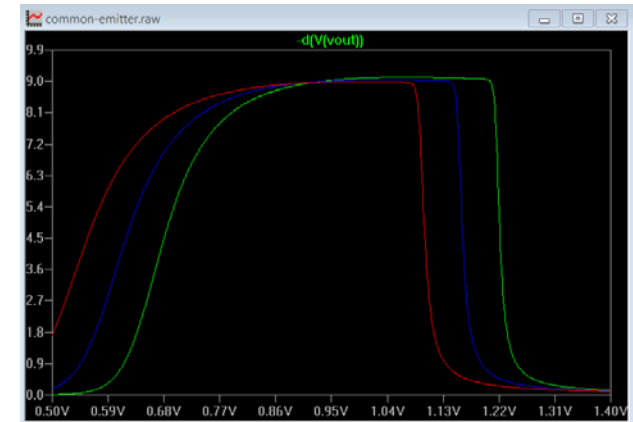


T = 0, 35, 70C

Small-Signal Circuit Models

- Linearization of device characteristics around bias point (first-order Taylor series approximation)
- Example 1: ideal (linear) resistor

Example 2: NPN BJT

Large Signal Model

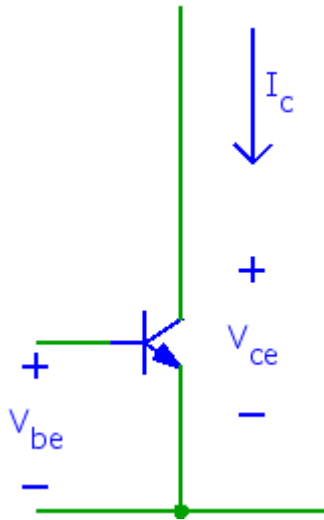

Small Signal Model

Example 3: Constant Voltage Source (e.g. Supply)

Large-Signal Circuit


Small-Signal Model

What is the small-signal model of a constant current source?

Small-Signal Circuit Models

Large-Signal Circuit

Small-Signal Model

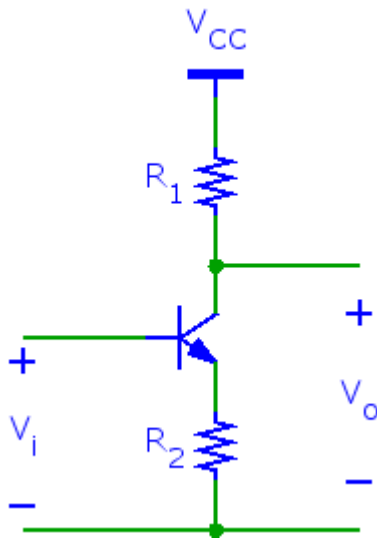

Calculate the Small-Signal Gain

Determine Bias (from Small-Signal Parameters)

Design Bias Circuit

Small & Large Signals Recap

- Why the fuss?
 - Example: Gain
- Definitions & Nomenclature
- Simplifying life:
 - Small-signal models
- Design: break a hard problem into two simpler ones!
 - Small-signal characteristics (linear)
Usually the stuff we care about:
Gain, input/output resistance, bandwidth, ...
 - Large-signal characteristics (“biasing”, nonlinear)
What we need to ensure so that our circuit works as expected,
especially that it actually has all the small-signal characteristics we
care about!