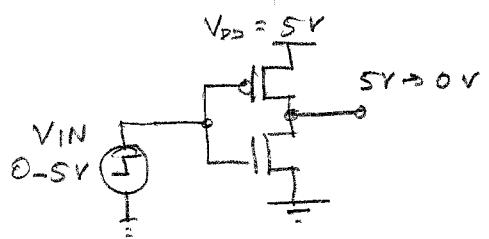




Review from last time

1. MOSFET as switch




$$V_{IN} = 5V$$

$$V_{IN} = 0V$$

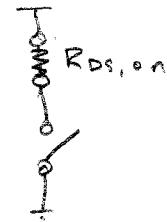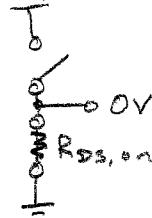


$$R_{DS(on)} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})}$$

2. MOSFET as controlled resistor

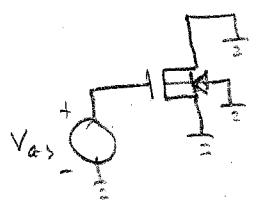


$$R_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$
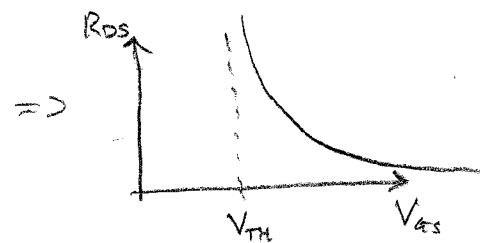
$$I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_{DS}$$



3. MOSFET as current source


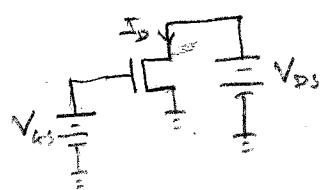


$$\text{Pinch off requirement: } V_{GD} < V_{TH} \Rightarrow V_{DS} \geq V_{GS} - V_{TH}$$

$$\text{Saturation current: } I_{DSAT} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + 2V_{DS})$$

channel length modulation

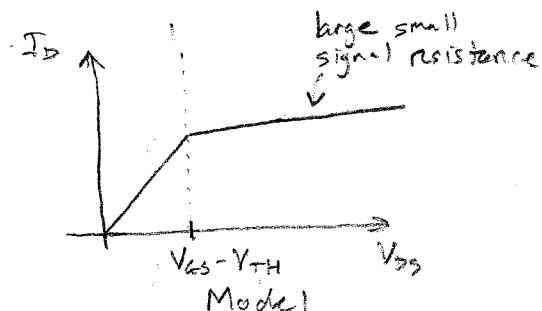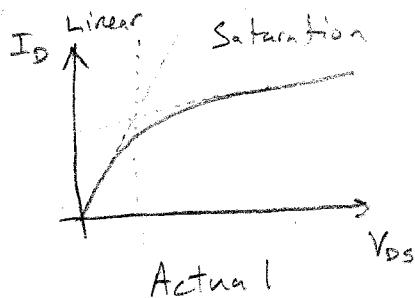② + ③ form piecewise linear model of I_D vs. V_{DS}




4. MOSFET as amplifier.

Key idea: control drain current with input voltage

Today:

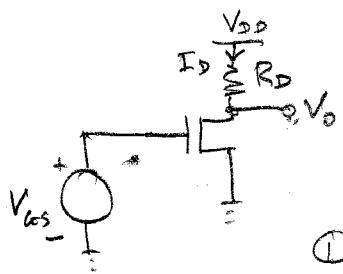- look at two topologies, common source & common drain
- design of an amplifier for a condenser microphone



Assume saturation, otherwise I_D is also a strong function of V_D .

$$\textcircled{1} \quad V_D = V_{DD} - I_D R_D$$

$$\textcircled{2} \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad (\text{ignore } \lambda \text{ for now})$$

From here we can either

1. substitute $\textcircled{2}$ into $\textcircled{1}$ for the full large signal behavior.

2. Assume V_{in} has just small changes on a nominal DC bias.

→ Taylor series

$$I_D(V_{GS}) @ V_{GS} = V_{GS0} \quad @ V_{GS0}$$

$$\frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) \Rightarrow \mu_n C_{ox} \frac{W}{L} (V_{GS0} - V_{TH}) = g_m$$

$$\frac{\partial^2 I_D}{\partial V_{GS}^2} = \mu_n C_{ox} \frac{W}{L} \Rightarrow \mu_n C_{ox} \frac{W}{L} = B$$

$$\Rightarrow I_D(V_{GS}) = \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS0} - V_{TH})^2}_{\text{DC bias}} + \underbrace{g_m (V_{GS} - V_{GS0})}_{\text{linear gain}} + \underbrace{B(V_{GS} - V_{GS0})}_{\text{nonlinearity}}$$

(BJT will have higher order terms due to exp.)




$$\text{Let } V_{in} = V_{GS} - V_{GS0} \Rightarrow V_{GS} = V_{in} + V_{GS0} \Rightarrow \begin{matrix} V_{in} \\ V_{GS0} \end{matrix} \begin{matrix} 0 \\ \vdash \end{matrix} \begin{matrix} 0 \\ V_{GS} \\ q^- \end{matrix}$$

$$I_D = I_{D0} + g_m V_{in} + B V_{in}^2$$

ignore if
 $|BV_{in}| \gg B V_{in}^2$

$$|V_{in}| \gg V_{in}^2$$

$$\boxed{|V_{in}| \gg |V_{in}|} \quad (V_{in} = V_{GS0} - V_{TH})$$

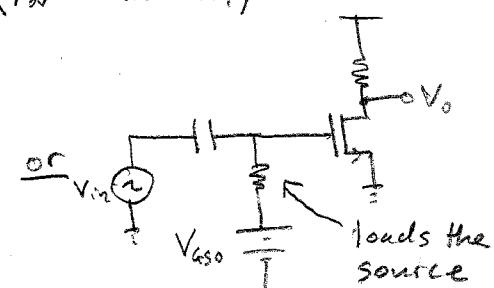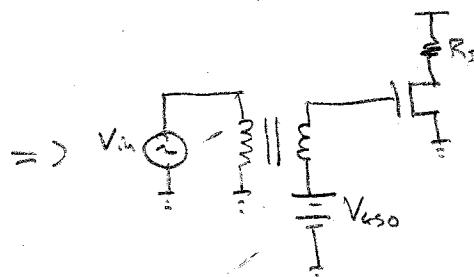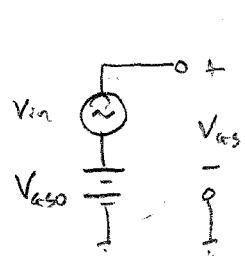


Notes:


- "small" signal and AC are not synonyms
- DC accurate amplifiers typically require differential pairs, a circuit that can take the difference of two inputs.

Single transistor amplifier stages (small signal, bias elements not shown)

Small signal model: $G \rightarrow$

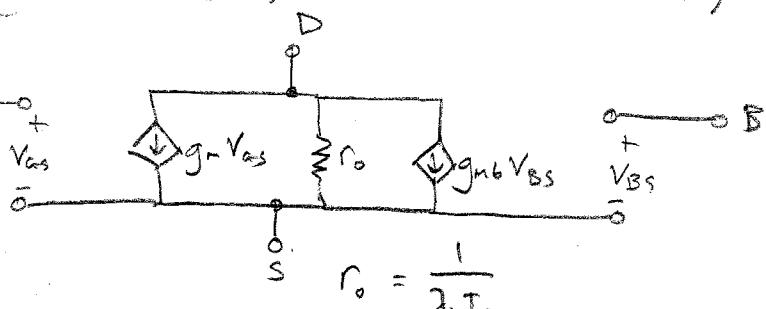

Common source

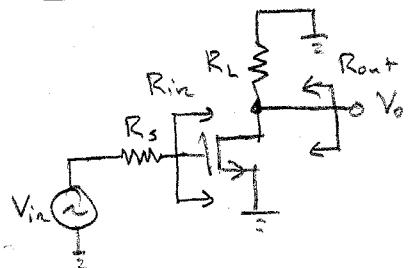


$$R_{in} = \infty \Rightarrow V_{gs} = V_m$$

$$\frac{V_o}{V_{in}} = -g_m R_{out}$$

$$R_{out} = R_L \parallel r_o$$

R_{out} calc.


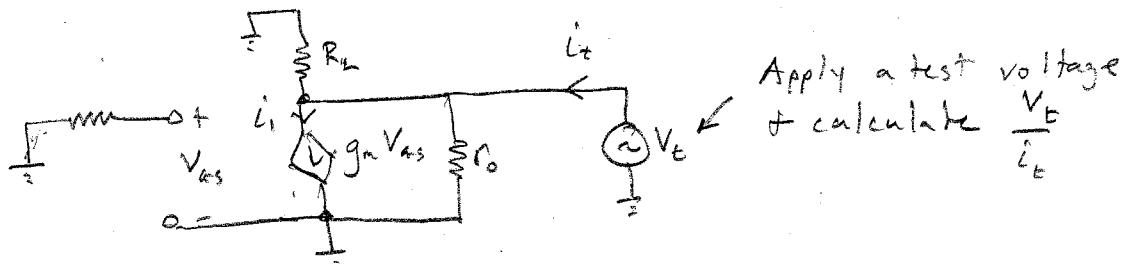
- Always set all independent sources to 0 first.



$$1. V_{AS} = 0 \Rightarrow I_d = 0$$

$$2. \frac{V_t}{I_d} = R_L \parallel r_o = R_{out}$$

Common drain (Source follower)

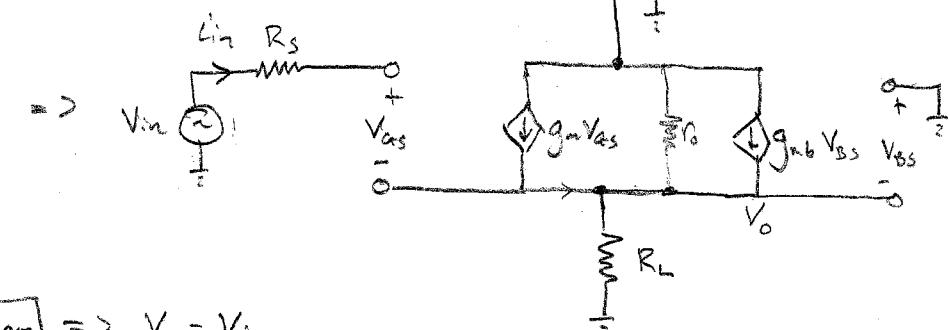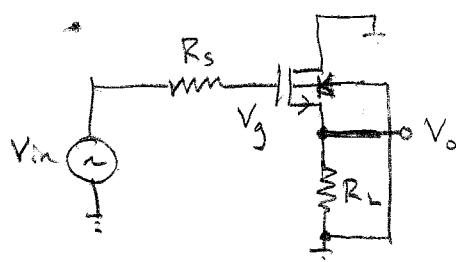

$$I_{in} = 0 \Rightarrow R_{in} = \infty \Rightarrow V_g = V_{in}$$

KCL at V_o :

$$g_m V_{as} - \frac{V_o}{r_0} + g_{mb} V_{BS} - \frac{V_o}{R_L} = 0$$

$$\begin{aligned} V_{as} &= V_{in} - V_o \\ V_{BS} &= -V_o \end{aligned} \Rightarrow g_m (V_{in} - V_o) - \frac{V_o}{r_0} + g_{mb} (-V_o) - \frac{V_o}{R_L} = 0$$


$$V_o \left(-g_m - \frac{1}{r_0} - g_{mb} - \frac{1}{R_L} \right) = V_{in} (-g_m)$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{g_m (r_0 \parallel R_L)}{(g_m + g_{mb})(r_0 \parallel R_L) + 1}}$$

$$\text{For } g_m \rightarrow \infty + g_{mb} \rightarrow 0 \Rightarrow \frac{V_o}{V_{in}} \rightarrow 1$$

g_{mb} degrades the gain! It would be nice if $\boxed{g_{mb} = 0}$, but this isn't possible in many cases due to processing restrictions. We would need many separate isolated substrates or wells.

Root

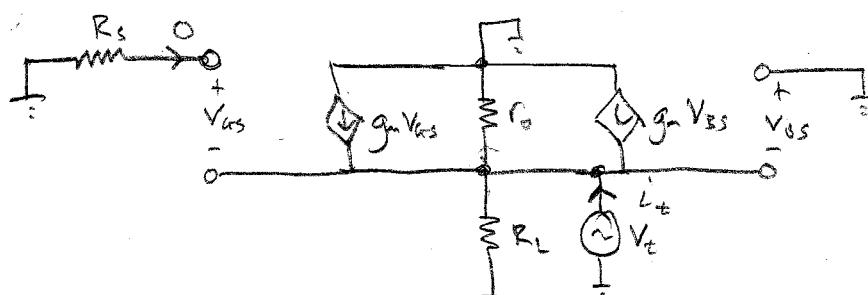

$$i_t + g_m V_{as} + g_{mb} V_{BS} - V_t \left(\frac{1}{r_0} + \frac{1}{R_L} \right) = 0$$

$$V_{as} = V_{BS} = -V_t$$

$$i_t = V_t \left(\frac{1}{r_0} + \frac{1}{R_L} + g_m + g_{mb} \right) \Rightarrow \boxed{\frac{V_t}{i_t} = r_0 \parallel R_L \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \approx \frac{1}{g_m}}$$

if $g_m \gg g_{mb}, \frac{1}{r_0}, \frac{1}{R_L}$


What is the point of a source follower?

- gain is 1. Is this useful?
- $R_{out} \ll R_{in}$.

Consider an audio amplifier for driving headphones from microphone input.

Condenser microphone: Vibrations produce changes in capacitive gap.

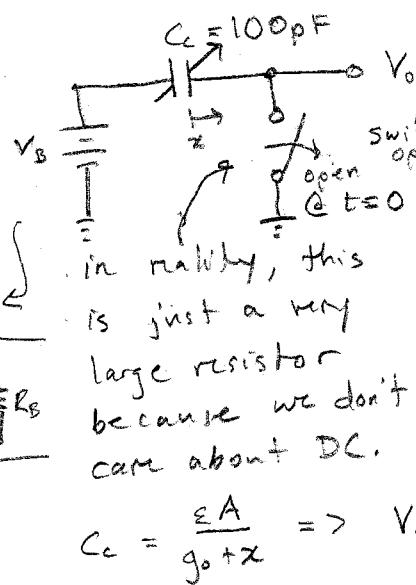- Capacitor is biased with a nominal voltage V_B , creating a charge $Q = V_B C_c$
- changes in gap cause changes in cap.



- Since charge is constant, V_o changes when cap changes.

$$Q = C_c (V_B - V_o)$$


$$V_o = \frac{C_c V_B - Q}{C_c} = V_B - \frac{Q}{C_c}$$

• Thevenin impedance is simply C_c


$$C_c = \frac{\varepsilon A}{g_o + x} \Rightarrow V_o = V_B - \frac{Q(x + g_o)}{\varepsilon A}$$

$$\text{Small signal gain } \frac{\partial V_o}{\partial x} = -\frac{Q}{\varepsilon A} = -\frac{V_B C_c}{\varepsilon A} = -\frac{V_B}{g_o}$$
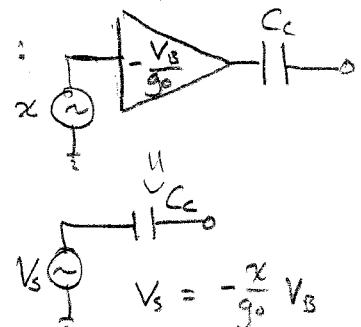
$$V_o = -\frac{x}{g_o} V_B \quad \text{small signal model:}$$




Headphones:

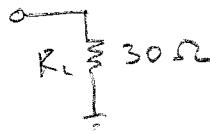


$$V_o = -\frac{x}{g_o} V_B$$

What happens if we connect the two?

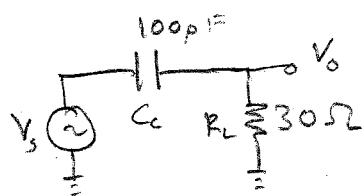


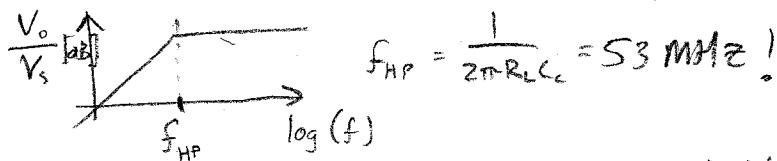- Audio is ~20 Hz to 20 kHz
- $C_c + R_L$ form a high pass filter




- Audio frequencies are greatly attenuated!

What if we use a follower?

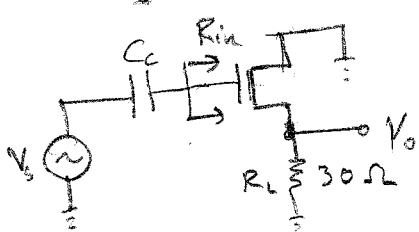


- $R_{in} = \infty$
- $V_o \approx V_s$ if $g_m R_L \gg 1$
- If we have enough g_m , we can reduce the high pass filter effect by relying on large R_{in} & small R_{out}

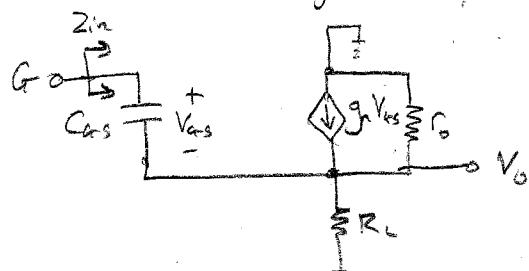Note: real MOSFETs have gate capacitance.



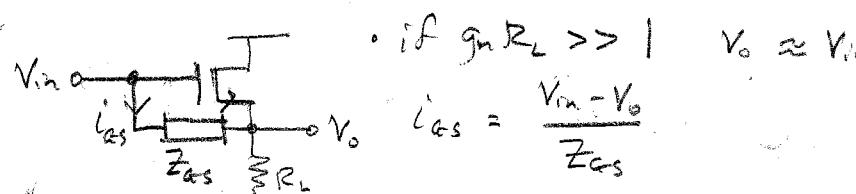- C_{as} means Z_{in} is finite. we'll study frequency response of amplifiers later.
- For source followers, there is another interesting advantage



$$\text{if } g_m R_L \gg 1 \quad V_o \approx V_{in}$$


$$I_{as} = \frac{V_{in} - V_o}{Z_{as}}$$

As $g_m R_L \rightarrow \infty$, $I_{as} \rightarrow 0$.

i. with enough $g_m R_L$, input impedance can be arbitrarily large.

• ignores 2nd order effects such as g_{nb} , other parasitic caps, etc.

What if we used CS?

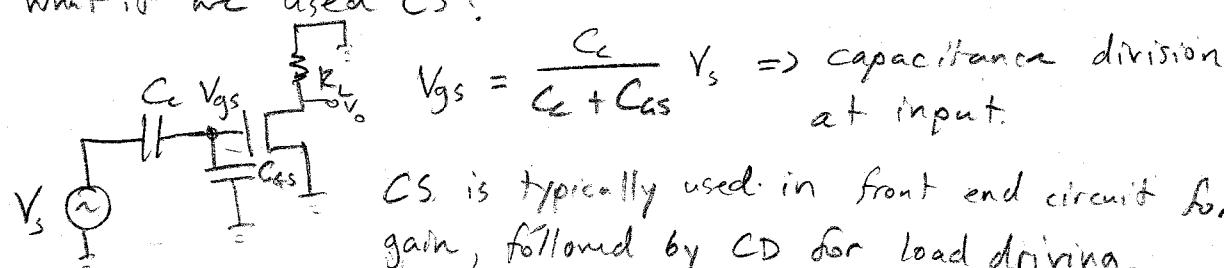


CS is typically used in front end circuit for gain, followed by CD for load driving.

$$\frac{V_o}{V_{in}} = \frac{C_c}{C_c + C_{as}} g_m R_L \Rightarrow \text{if } R_L \text{ is small, insert a second amplifier stage if more gain is necessary.}$$


Observations from mic. amp design.

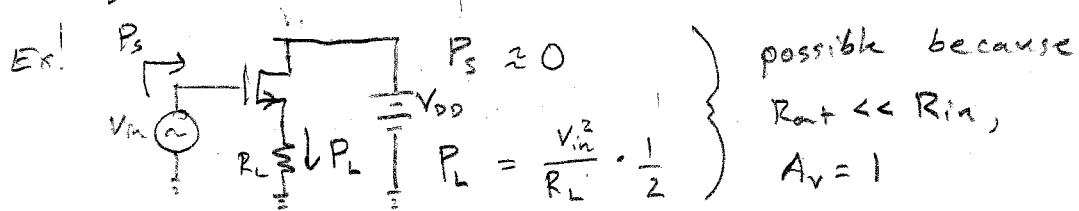- 1. Amplifiers with voltage gain of 1 can still provide Power gain.




- Does not violate energy conservation. Power comes from battery. ($P_{in} = P_{out} = P_d + P_{MOSFET}$)
- Amplification = using a small signal to modulate the operating point of a higher power circuit.

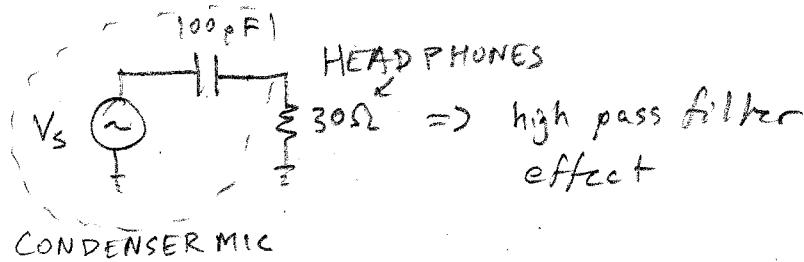- 2. Interfacing to sensors with very high impedance (large R , small C) is difficult due to loading effects.



- 3. Common drain stages offer extremely high input impedance, but cannot provide voltage gain.

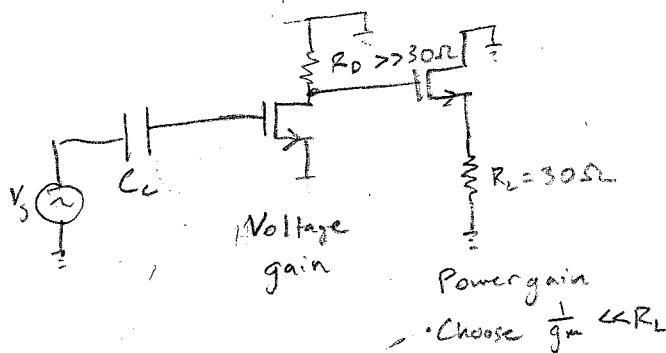- 4. Common source stages offer high input impedance + the potential for high gain if followed by a 2nd stage.



gm equations

with $V_{ds} = V_{ds0}$

gm is defined as $\frac{\partial I_D}{\partial V_{ds}}$. From $I_{Dsat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{ds} - V_{TH})^2$, we found $gm = \mu_n C_{ox} \frac{W}{L} V_{ov}$, where

$V_{ov} = V_{ds0} - V_{TH}$ is the overdrive voltage.

For BJTs, $gm = \frac{I_c}{V_T}$. We can come up with a similar expression for FETs.

$$\frac{I_{Dsat}}{gm} = \frac{1}{2} V_{ov} \Rightarrow gm = \frac{2 I_{Dsat}}{V_{ov}}$$

Also, $2 I_{Dsat} \mu_n C_{ox} \frac{W}{L} = (\mu_n C_{ox} \frac{W}{L} V_{ov})^2 = gm^2$

$$gm = \sqrt{2 I_{Dsat} \mu_n C_{ox} \frac{W}{L}}$$

The second of these equations, $gm = \frac{2 I_{Dsat}}{V_{ov}}$, is generally the most useful:

- it's independent of sizing
- V_{ov} is usually restricted by other considerations, such as linearity, noise, speed, and gain.
- It exposes the linear tradeoff between power (I_D assuming const V_{DD}) + gm .
- It allows interesting comparisons to BJTs


BJT	MOSFET
$gm = \frac{I_c}{V_T}$	$gm = \frac{2 I_D}{V_{ov}}$

Can we just make $V_{ov} < 2V_T$ in order to have a more power efficient device?

No \rightarrow the square law model breaks down for $V_{ov} < \sim 100 \text{ mV}$.

Known as weak inversion region: $I_D = I_{Se} e^{\frac{V_{ds}-V_{TH}}{nV_T}} \rightarrow n=1.2\dots 1.5$

PMOS transistor

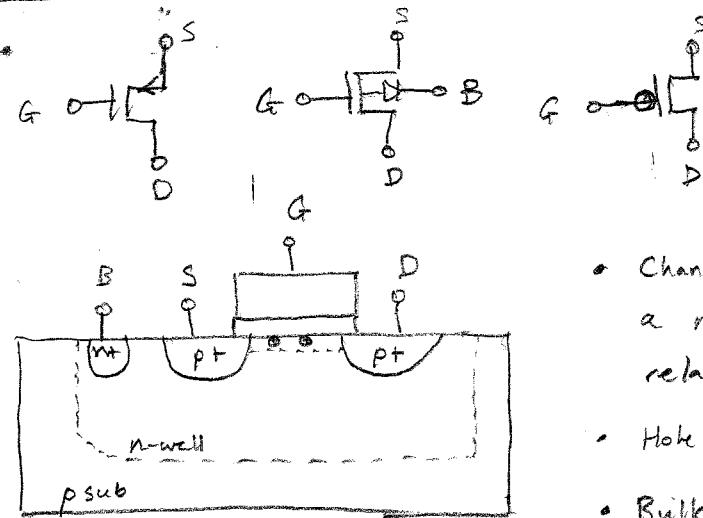

- Channel is formed by applying a negative voltage to the gate, relative to S/B.
- Holes conduct current from S \rightarrow D
- Bulk should be connected to V_{DD}
 - ensures parasitic diodes are off

$$I_{S \rightarrow D} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SD} - V_{TP})^2$$

In Si

$$\left\{ \begin{array}{l} \mu_p \leq 450 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \\ \mu_n \leq 1400 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \end{array} \right. \quad \frac{\mu_n}{\mu_p} \approx 3 \Rightarrow \text{are } 3 \text{ times more current efficient}$$

This means that NMOS transistors are 3 times more current efficient in terms of $g_m = \sqrt{2I_D \mu C_{ox} \frac{W}{L}}$ for identical sizing.

Note: V_{TN} & V_{TP} are usually different.

Remember:

S = highest potential p+ terminal in PMOS.

It is the "source" of holes.


S = lowest potential n+ terminal in NMOS.

It is the "source" of electrons.

Current is defined as the flow of positive charge, so $I_{S \rightarrow D, \text{PMOS}}$ is always positive, $I_{S \rightarrow D, \text{NMOS}}$ is always negative.

* It's much less confusing to simply label currents in a circuit with a direction that intuitively makes sense.

Ex.

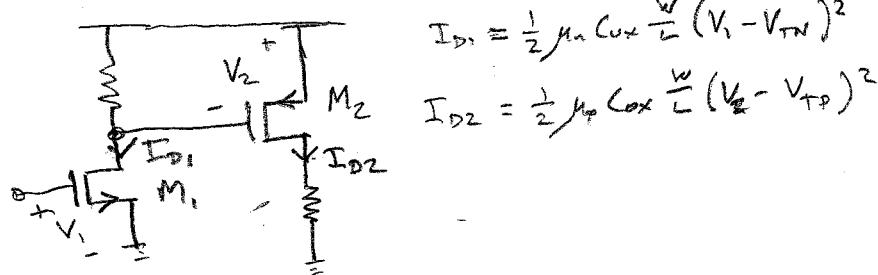

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_1 - V_{TN})^2$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_2 - V_{TP})^2$$