

Electronics for IoT

Resistance

Electronic Circuits

Bernhard E. Boser
University of California, Berkeley
boser@eecs.berkeley.edu

Last Time





- Solar powered “noise maker”
- What else could we power with the solar cell?

Outline

- Resistors
 - Electrical characteristics
 - Symbol
 - Ohm's law
- Solar cell power optimization
- Circuit analysis
 - Kirchhoff's laws
- Application:
 - LED

Resistors

- Electrical circuit component (device)

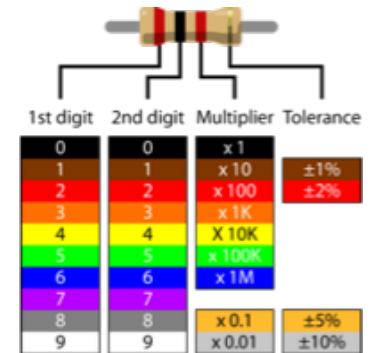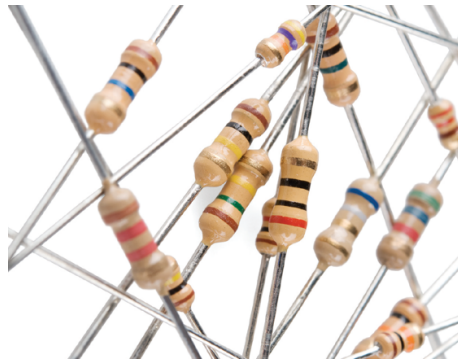


Characteristics

Ohm – Meter




Resistor I/V Relationship

Resistor Circuit Example

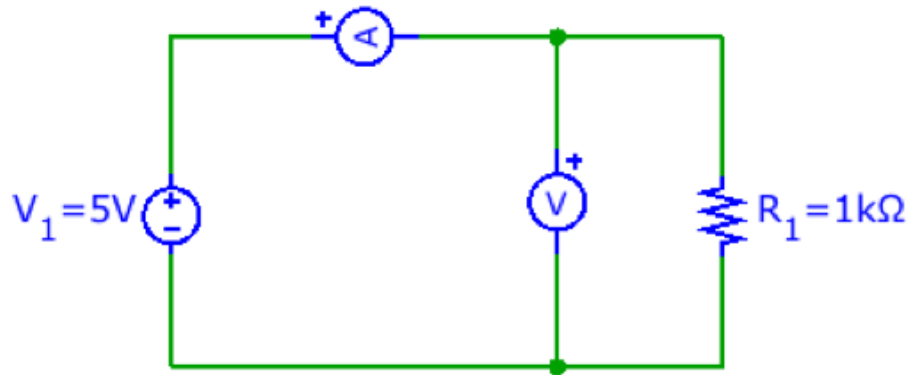


Solar Cell Power

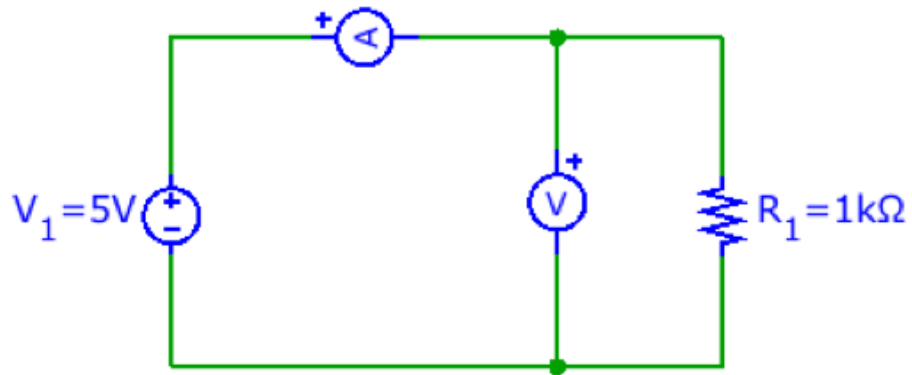


Potentiometer

- Variable resistor

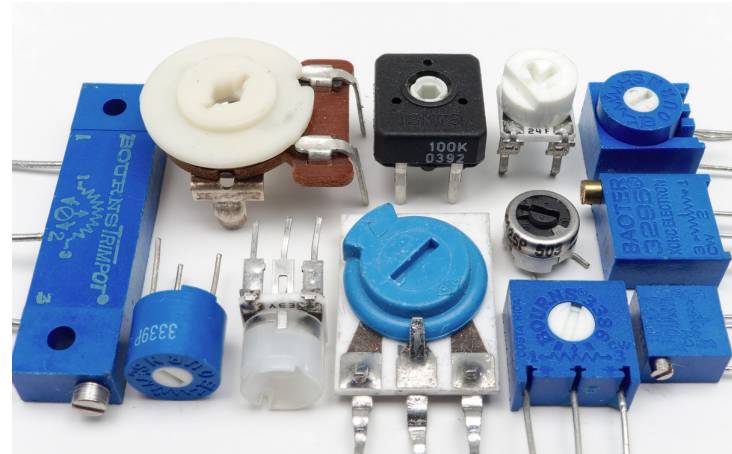


Potentiometer – How does it work?

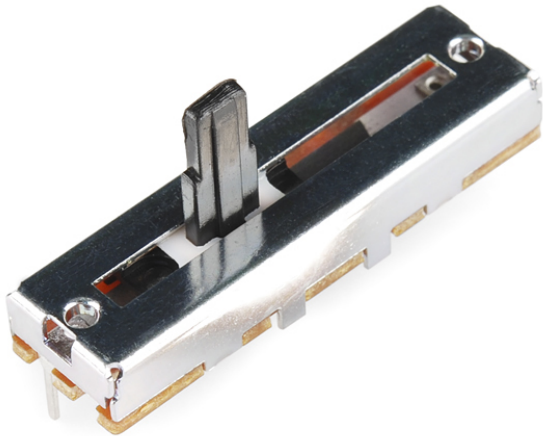


Potentiometer – Resistance

Application: Encoder

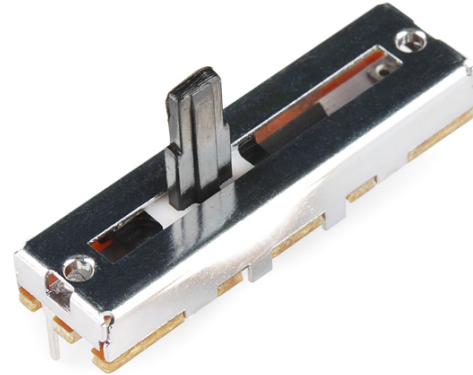

Example: Servo

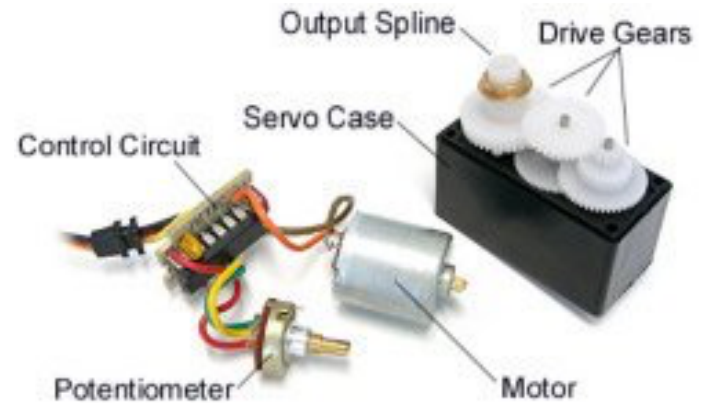


Potentiometer Symbol



Solar Power



After a little bit of work ...

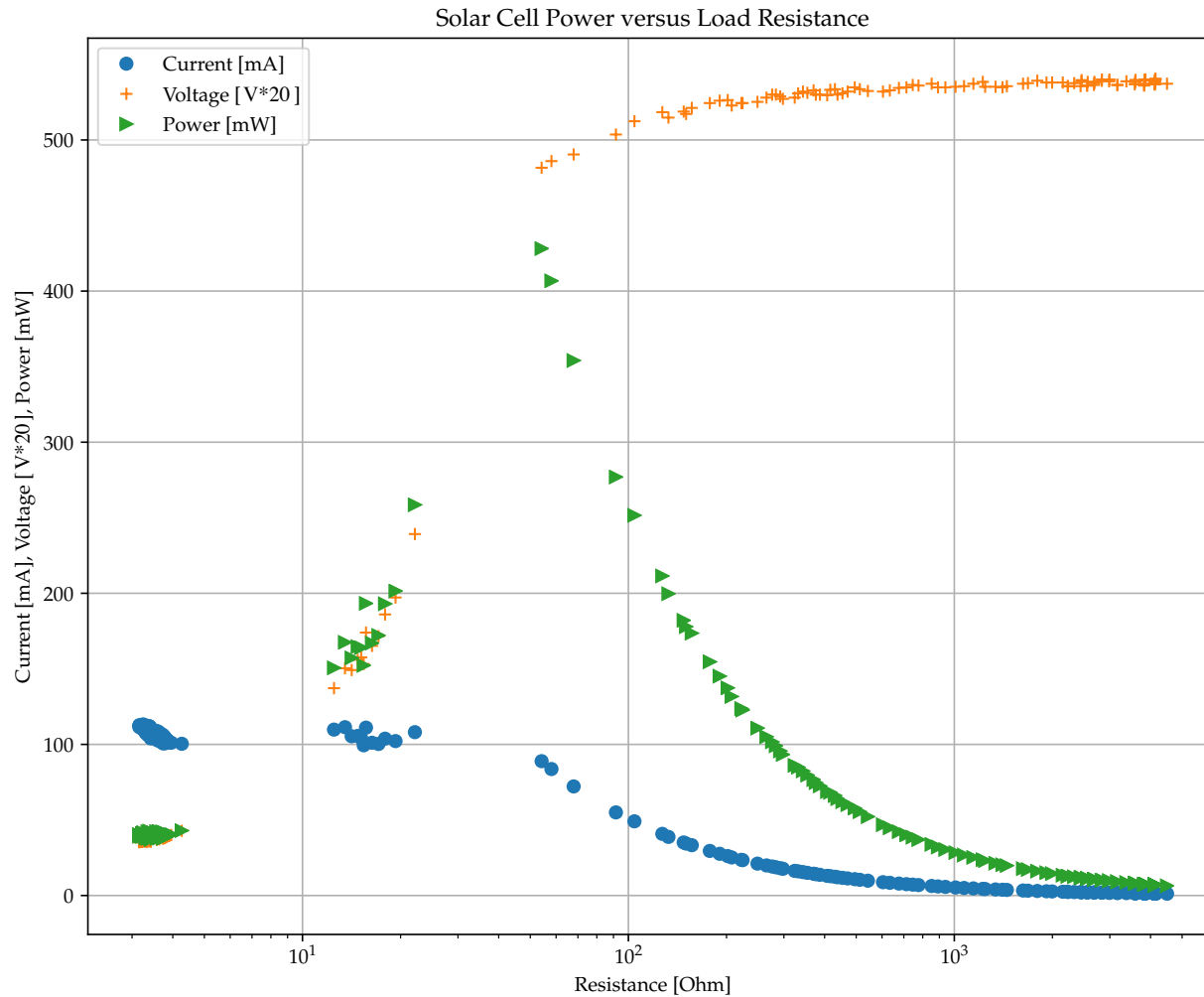

Maximum Power

- $P_{\max} = 450 \text{ mW}$
- $R = 45 \text{ Ohm}$
- $V = 5 \text{ V}$
- $I = ?$


Efficiency

- Solar power (sun overhead): $\sim 1 \text{ kW/m}^2$


Outline

- Resistors
 - Electrical characteristics
 - Symbol
 - Ohm's law
- Solar cell power optimization
- Circuit analysis
 - Kirchhoff's laws
- Application:
 - LED


Kirchhoff's Laws ...

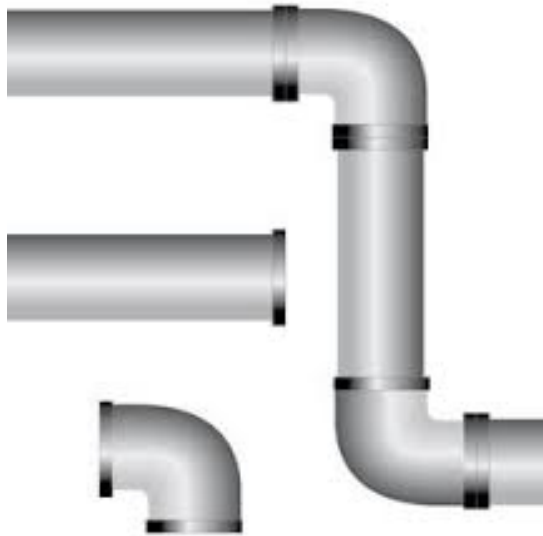


Branches

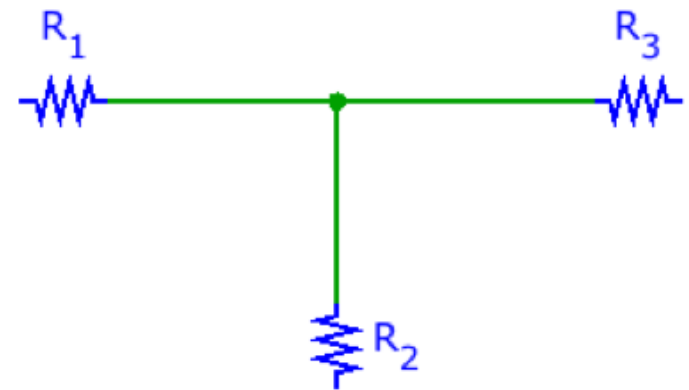


Kirchhoff's Current Law (KCL)

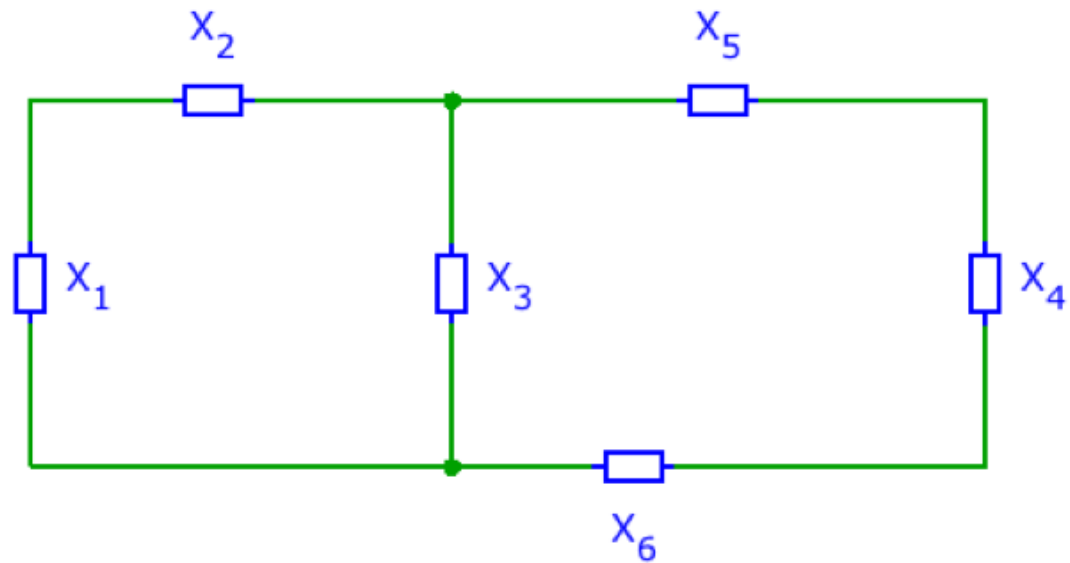


KCL Example

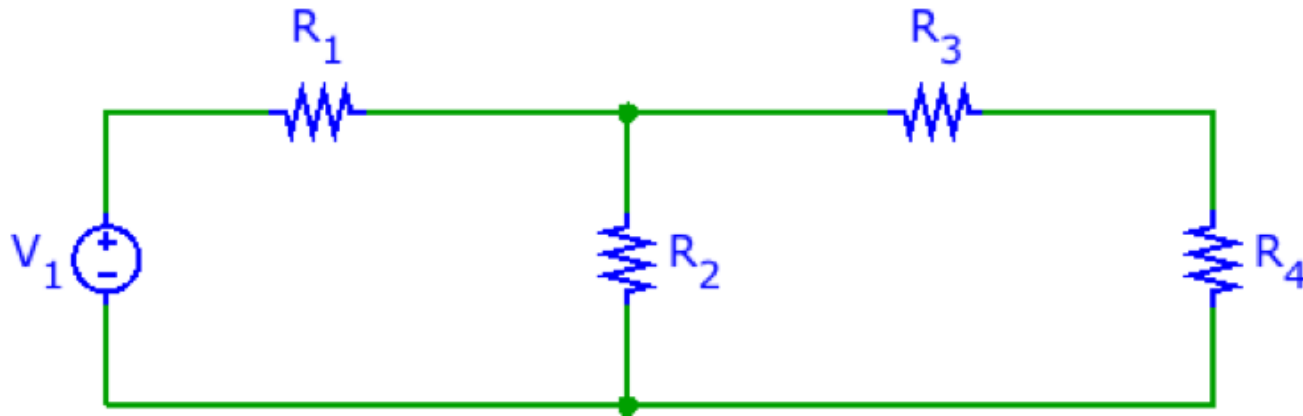


Kirchhoff's Voltage Law (KVL)

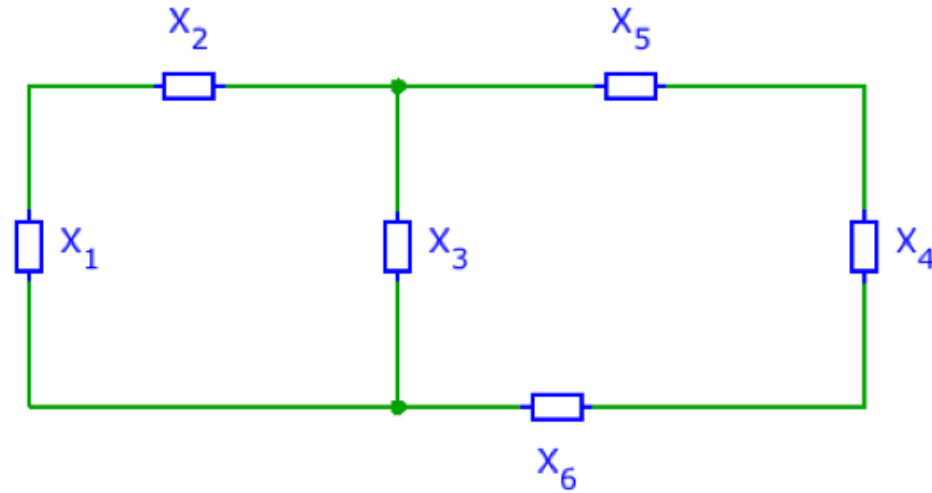

KVL Example

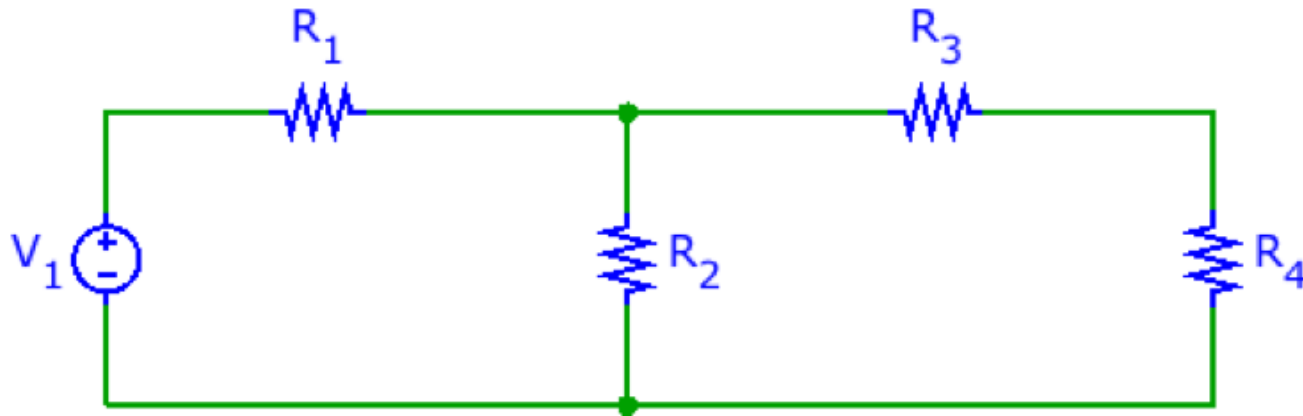

Circuit Example

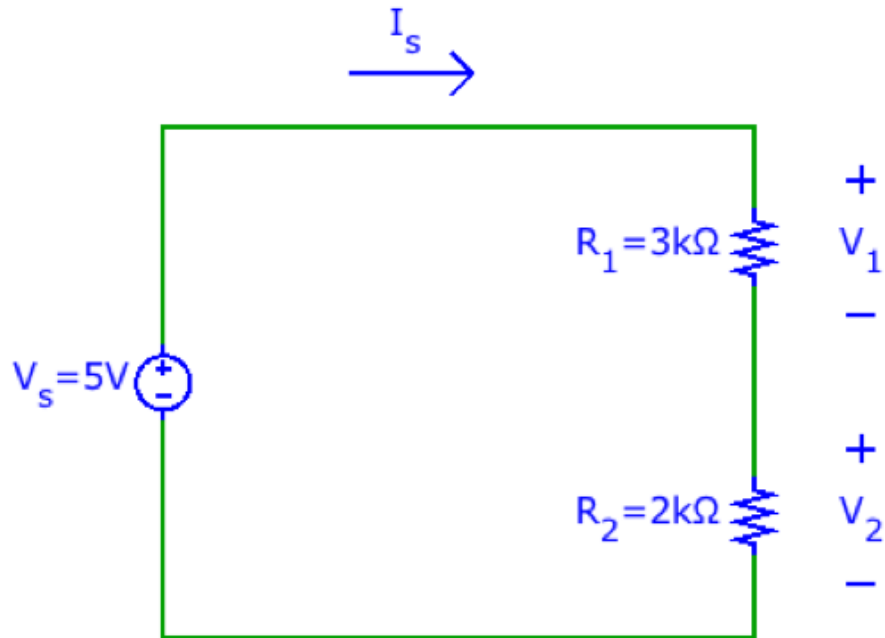


Resistors in Series

Resistors in Parallel

Design Problem


- Given:
 - 12 V battery
 - Box full of resistors
- Design circuit for
 - 5 V

LED Example

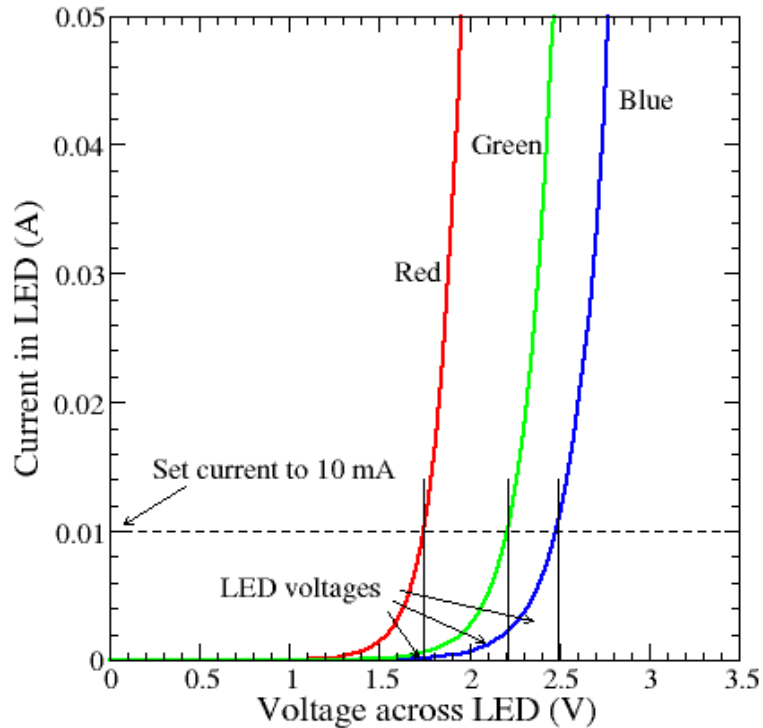

- How can we power a **Red LED** from a 5V supply?
- Direct connection ...
 - $I = ?$

10mA LED Circuit

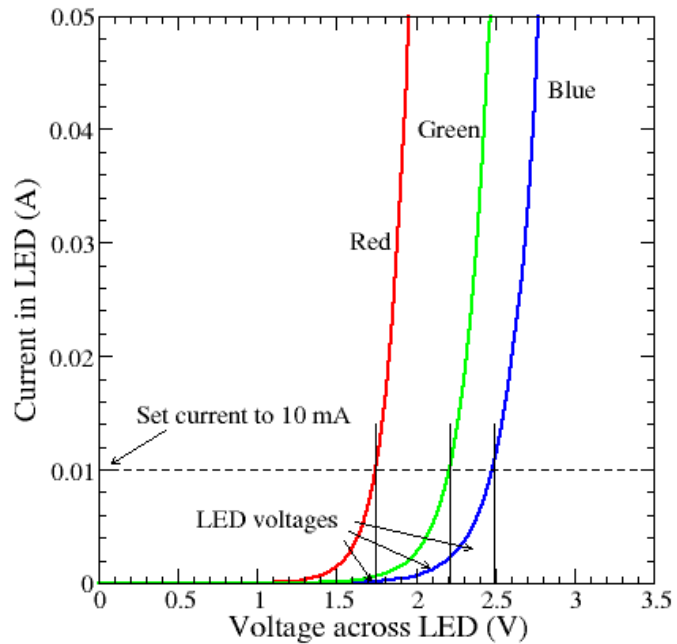


Equations, equations, ...

- KVL & KCL
 - Many more equations than we need
 - Linear dependent
- Systematic way to write just the equations needed?


Nodal Analysis

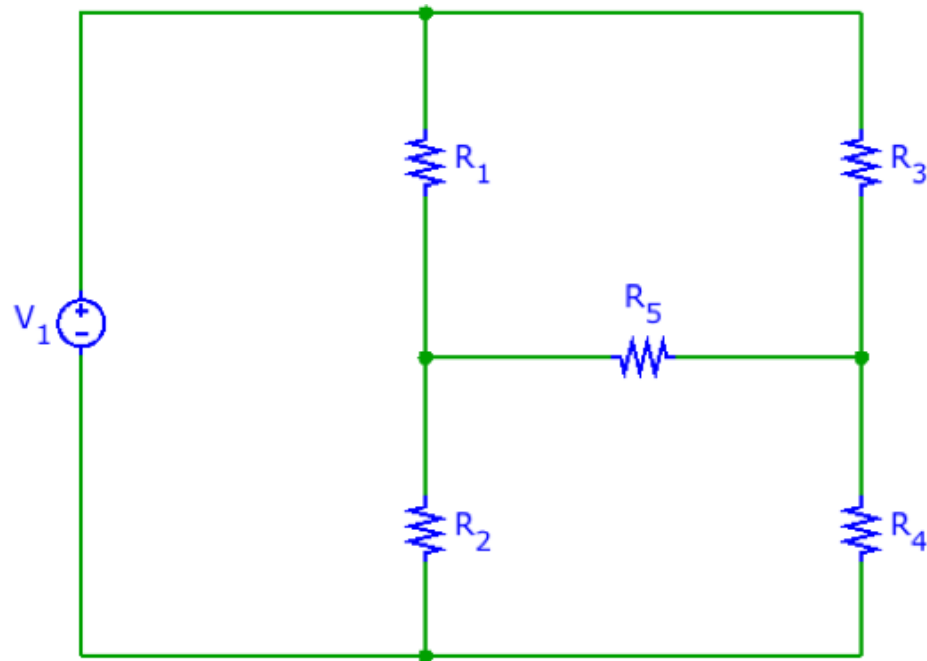- Objective
 - Find all unknown voltages in circuit




Nodal Analysis

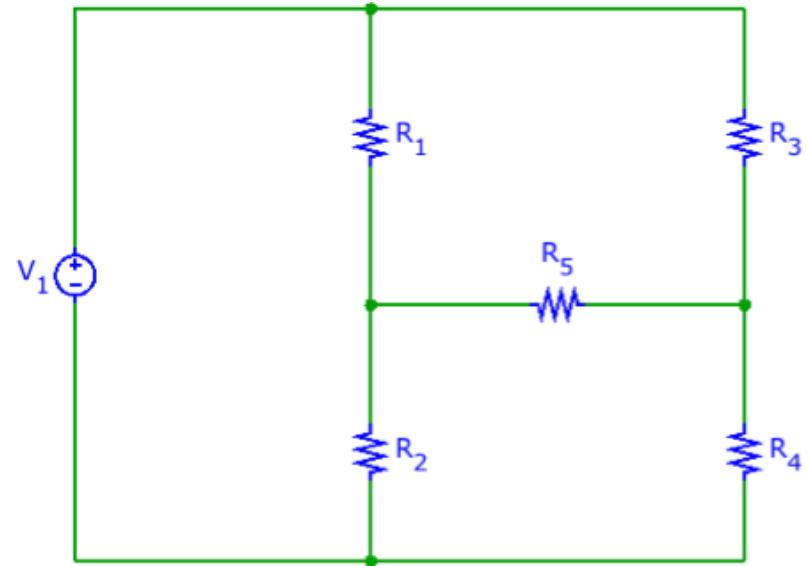1. Choose ground (GND)
2. Mark unknown node voltages
3. Write KCL equation for each unknown node
4. Solve set of equations



Nodal Analysis Example

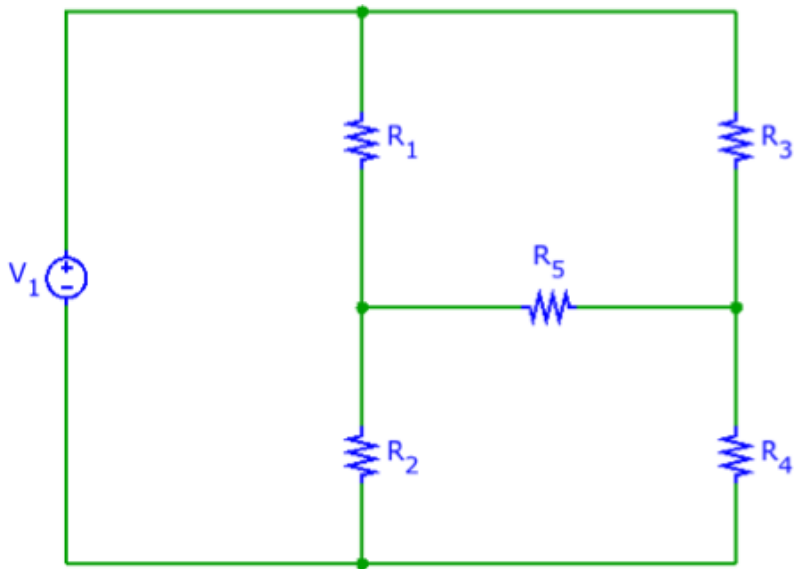

Summary

- Voltage, Current, Power
- Electrical components
 - Resistors, potentiometer
 - Solar cells, batteries, ...
- Ohm's law
- Kirchhoff's laws
 - KVL
 - KCL
- Circuit analysis: determine I , V , P , ... using
 - KVL, KCL, (nodal analysis)
 - Component characteristics

Next Time

MicroPython & Circuits
= IoT Device!