
 


 
1. In the circuit below, V_{ic} is adjusted such that $V_{oc} = 0V$.
- Draw the low-frequency small-signal differential-mode half-circuit model. Calculate the values of all low-frequency small-signal parameters (r_o 's, etc.).
 - Calculate the value of the low-frequency small-signal differential-mode gain, A_{dm} , of the circuit.
 - Draw the low-frequency small-signal common-mode half-circuit model. Specify the values of all low-frequency small-signal parameters.
 - Calculate the value of the low-frequency small-signal common-mode gain, A_{cm} , of the circuit.
 - Because of manufacturing imperfections, the values of resistors R_1 and R_2 are slightly different: $R_1 = R_0 + \Delta R/2$ and $R_2 = R_0 - \Delta R/2$ with $R_0 = 10k\Omega$ and $\Delta R = 0.05R_0$. Calculate the low-frequency small-signal common-mode to differential gain, A_{cdm} , and the common-mode rejection ratio, CMRR.
 - Describe a circuit modification resulting in at least a two-orders-of-magnitude improvement of the CMRR. You do not need to design the modification.



$$I_D = \frac{5V}{10k\Omega} = 0.5mA$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 3.79mA/V$$
 
$$r_o = \frac{1}{\lambda I_D} = 100k\Omega$$



b)

$$A_{DM} = -g_{m1} (R_1 || r_o) = 34.5$$

e)

$$A_{CDM} = \frac{\Delta R}{2R_3 + \frac{1}{g_{m1}}} = 0.117$$

d)

$$A_{cm} = \frac{g_{m1} R_1}{1 + 2g_{m1} R_3} = 2.345$$

$$CMRR = \frac{A_{DM}}{A_{CDM}} = 323.6$$

- f) Replace R_3 with a current source, source resistance at least $100 \times R_3$.

2) First try: current mirror $R_{out} = r_o = \frac{1}{\lambda I_D} = 1.275 \text{ M}\Omega$ X

$\lambda = 0.02 \text{ V}^{-1}$, $I_D = 39 \mu\text{A}$

doesn't meet spec \Rightarrow try cascode

Second try: cascode

$R_{out} = g_m r_o^2 \quad (1)$

$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2I_D}{\sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}} = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}} \quad (2)$

$r_o = \frac{1}{\lambda I_D} \quad (3)$

Combine equations (1), (2), (3):


$\lambda = 0.02 \text{ V}^{-1}$, $I_D = 39 \mu\text{A}$, $\mu_n = 300 \text{ cm}^2/\text{Vs}$

$R_{out} = 587 \text{ M}\Omega$ ✓

$C_{ox} = 10 \text{ fF}/\mu\text{m}^2$, $L = L_{min} = 180 \text{ nm}$, $W = 1 \mu\text{m}$

meets spec

 We could lower R_{out} to $10 \text{ M}\Omega$ and size W accordingly to minimize the transistor sizes.



Showing cascode biasing is important in schematic

Q3)

$$\omega_{3dB} = \frac{1}{C_s R_{in}}$$

$$R_{in} = \frac{1}{g_m}$$


$$2\pi * 500MHz = \frac{1}{10pF * R_{in}}$$

$$R_{in} = 31.8\Omega$$

$$R_{in} = \frac{1}{g_m} \Rightarrow g_m = 31.4mS$$

$$g_m = \frac{I_C}{V_T} \Rightarrow I_C = I_{dc} = 785\mu A$$
 
$$V_{0,Low Frequency} = i_s * R_X \Rightarrow R_X = 1k\Omega$$



Q4)

We know from previous that the resistance looking down from the output node is:

$$R_{0,Down} \approx g_m r_o^2$$

This resistance is probably much larger than 2k so we can assume the low frequency gain is:

$$a_v = -g_m R_L \Rightarrow g_m = \frac{10}{2k} = 5mS$$

The dominant pole is in input since the resistance is larger than output (R_L) and the cascade node ($1/g_m$). Also the capacitor is larger since there is miller effect and the gate-source capacitor.

$$\omega_{3dB} = \frac{1}{R_s(C_{gs,1} + 2C_{ov,1})}$$

$$2\pi * 800MHz = \frac{1}{R_s \left(\frac{2}{3} W L C_{ox} + W C_{ov} + 2W C_{ov} \right)}$$

$$2\pi * 800MHz = \frac{1}{10K \left(\frac{2}{3} W 0.18 * 10e^{-15} + 3W * 0.2e^{-15} \right)}$$

$$W \approx 11.05\mu m$$

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$

$$I_D = 678\mu A$$

$$V_{dsat} = \frac{g_m}{\frac{W}{L} \mu_n C_{ox}} = 270mV$$

$$V_{GS} = V_{dsat} + V_{Th} = 670mV$$


$$V_{Bias,min} = V_{dsat} + V_{GS} = 940mV$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.02 * 678e^{-6}} = 73.7k\Omega \Rightarrow g_m r_o^2 = 27.2M\Omega!$$

 5. In the circuit below, M_1 and M_2 are used as switches to control current flow between nodes V_1 and V_2 . The control voltages V_{c1} and V_{c2} are set to 0 V and 3 V to turn the switch on, and 3 V and 0 V to turn the switch off.

Determine the minimum width of M_1 and M_2 required such that the maximum resistance R_{on} between nodes V_1 and V_2 is 10Ω when the switch is on and V_1 varies between 0 V and 3 V for $V_2 \approx V_1$. Choose $L_1 = L_2 = 180 \text{ nm}$. For which value of V_1 does R_{on} reach its maximum?

Relevance: thousands of switches like this one tick along in the analog-to-digital and digital-to-analog converters used in audio and video cards, cameras, or radios.



$$R_{on} = R_{on1} \parallel R_{on2}$$

M_1, M_2 in triode:

$$R_{on,1} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_1 - V_{c1} - |V_{TH}|)} \quad V_1 - V_{c1} > |V_{TH}|$$

$$R_{on,2} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{c2} - V_1 - V_{TH})} \quad V_{c2} - V_1 > V_{TH}$$

$$R_{on} = \frac{1}{\frac{1}{R_{on1}} + \frac{1}{R_{on2}}} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_1 - 0.4 \text{ V}) + \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (2.6 \text{ V} - V_1)}$$

$$\text{Set } W_1 = 2W_2$$

$$R_{on,max} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (2.2 \text{ V})} = 10 \Omega \quad \boxed{0.4 < V_1 < 2.6 \text{ V}}$$

$$\boxed{W_2 = 27.3 \mu\text{m}, \quad W_1 = 54.5 \mu\text{m}}$$

$$(b) \quad (a) \quad \frac{I_{D1}}{I_{D2}} = \frac{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_G - V_{TH})^2}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_G - V_{TH})^2} = \frac{W_1}{W_2} = \frac{1}{10}$$

$$(b) \quad \left. \begin{aligned} I_{D1} = I_{C1} &= I_S e^{V_{BE1}/V_T} \\ I_{D2} = I_{C2} &= I_S e^{V_{BE2}/V_T} \end{aligned} \right\} \frac{I_{D1}}{I_{D2}} = \frac{1}{10} = e^{(V_{BE1} - V_{BE2})/V_T} \quad - (1)$$

$$V_{BE1} - V_{BE2} = (V_B - V_{E1}) - (V_B - 0) = -V_{E1} = I_{D1} R_1 \quad - (2)$$

Combine (1) & (2):
$$I_{D1} = \frac{kT}{qR_1} \ln(10)$$

T	V _{DD}	I _{D1}
300K	3V	59.5 μA
200K	3V	39.7 μA
300K	5V	59.5 μA

(c) The mobility dependence cancels for I_{D1}
The transistors are also at the same temperature