

☐ Reference:C:\Users\Bernhard Boser\Documents\Files\Lib\MathCAD\Default\defaults.mcd

L20: Source Follower

Given

$$\frac{v_g - v_i}{R_s} + (v_g - v_o) \cdot s \cdot C_{gs} = 0$$

$$\frac{v_o}{R_L} + (v_o - v_g) \cdot s \cdot C_{gs} - g_m \cdot (v_g - v_o) = 0$$

$$a_v = \frac{v_o}{v_i} \quad Z_i = \frac{v_i}{v_i - v_g} \cdot R_s$$

$$\text{Find}(v_g, v_o, a_v, Z_i) \text{ collect, } s \rightarrow \left[\begin{array}{l} v_i \cdot \frac{(1 + s \cdot C_{gs} \cdot R_L + g_m \cdot R_L)}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \\ R_L \cdot \frac{(s \cdot C_{gs} + g_m)}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \cdot v_i \\ R_L \cdot \frac{(s \cdot C_{gs} + g_m)}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \\ \frac{(C_{gs} \cdot R_s + C_{gs} \cdot R_L)}{C_{gs}} + \frac{(1 + g_m \cdot R_L)}{C_{gs} \cdot s} \end{array} \right]$$

$$z = \frac{g_m}{C_{gs}} = \omega_T$$

$$p = -\frac{1 + g_m \cdot R_L}{C_{gs} \cdot (R_s + R_L)} = -\frac{1}{C_{gs} \cdot \frac{R_s + R_L}{1 + g_m \cdot R_L}} \quad \text{approx} \quad R_L < R_s \quad p = \frac{g_m}{C_{gs}} \cdot \frac{R_L}{R_s} = \omega_T \cdot \frac{R_L}{R_s}$$

Given

$$\frac{v_g}{R_s} + (v_g - v_o) \cdot s \cdot C_{gs} = 0$$

$$\frac{v_o}{R_L} + (v_o - v_g) \cdot s \cdot C_{gs} - g_m \cdot (v_g - v_o) - i_t = 0$$

$$Z_o = \frac{v_o}{i_t}$$

$$\text{Find}(v_g, v_o, Z_o) \text{ collect, } s \rightarrow \left[\begin{array}{l} i_t \cdot R_L \cdot s \cdot C_{gs} \cdot \frac{R_s}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \\ \frac{R_L}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \cdot (1 + s \cdot C_{gs} \cdot R_s) \cdot i_t \\ \frac{R_L}{[(C_{gs} \cdot R_s + C_{gs} \cdot R_L) \cdot s + 1 + g_m \cdot R_L]} \cdot (1 + s \cdot C_{gs} \cdot R_s) \end{array} \right]$$

Derive by Inspection

Gain

dc gain $a_{vo} = \frac{\frac{1}{g_m}}{R_L + \frac{1}{g_m}} = \frac{1}{1 + \frac{1}{g_m \cdot R_L}}$ divider

very HF gain $a_{v_inf} = \frac{R_L}{R_s + R_L}$

zero $v_{gs} \cdot z \cdot C_{gs} = g_m \cdot v_{gs}$ $z = \frac{g_m}{C_{gs}}$ Bode Plot

pole $p = -z \cdot \frac{a_{v_inf}}{a_{vo}} = -\omega_T \cdot \frac{R_L}{R_L + R_s} \cdot \frac{1 + g_m \cdot R_L}{g_m \cdot R_L} = -\omega_T \cdot \frac{R_L}{R_s}$

Input impedance

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

low frequency $I_{in} = s \cdot C_{gs} \cdot V_{gs} = s \cdot C_{gs} \cdot (V_{in} - a_{vo} \cdot V_{in})$

$$I_{in} = \frac{s \cdot C_{gs} \cdot V_{in}}{1 + g_m \cdot R_L}$$

$$Z_{in_o} = \frac{1 + g_m \cdot R_L}{s \cdot C_{gs}}$$

very HF $Z_{in_inf} = R_s + R_L$

Output impedance

low frequency $Z_{o_o} = \text{par}\left(R_L, \frac{1}{g_m}\right) = \frac{R_L}{1 + g_m \cdot R_L}$

very HF $Z_{o_inf} = \text{par}(R_s, R_L) = \frac{R_s \cdot R_L}{R_s + R_L}$

$$\frac{Z_{o_o}}{Z_{o_inf}} = \frac{1}{1 + g_m \cdot R_L} \cdot \frac{R_s + R_L}{R_s} \quad \text{usually} < 1$$

Bode plot --> inductor