

Advanced Analog Integrated Circuits


Operational Transconductance Amplifier I & Step Response

Bernhard E. Boser



University of California, Berkeley

boser@eecs.berkeley.edu


Copyright © 2016 by Bernhard Boser

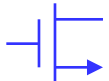



High-Level View

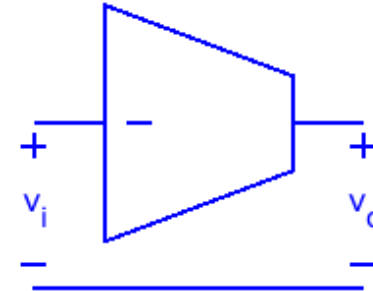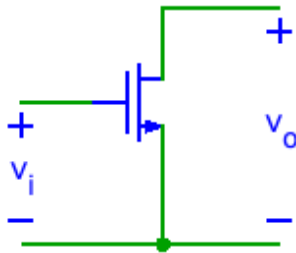


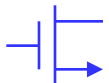
- Transistors are transconductors
- Some OTA designs consist of >40 transistors
 - Only few (typically 1 ... 2) provide the transconductance in the signal path
 - The rest is support, e.g.
 - increasing low frequency gain
 - output voltage range
 - biasing
- Hierarchical design strategies are imperative
 - Unless you like nodal equations for 40 transistors ...




Divide and Conquer

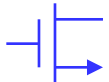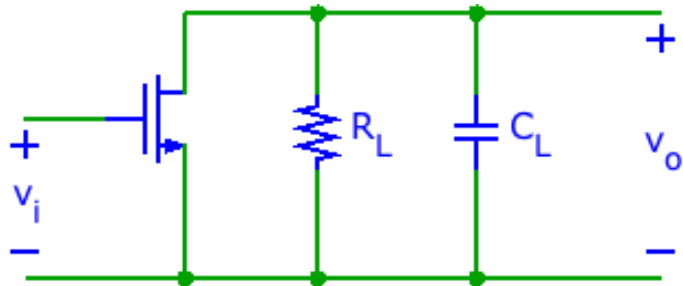



In SC Circuit

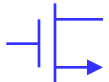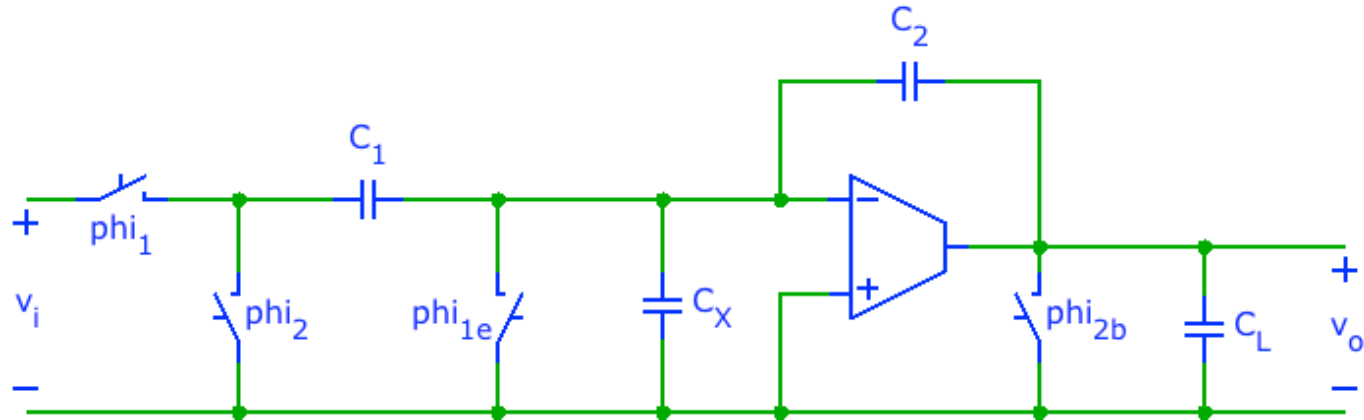


In SC Circuit

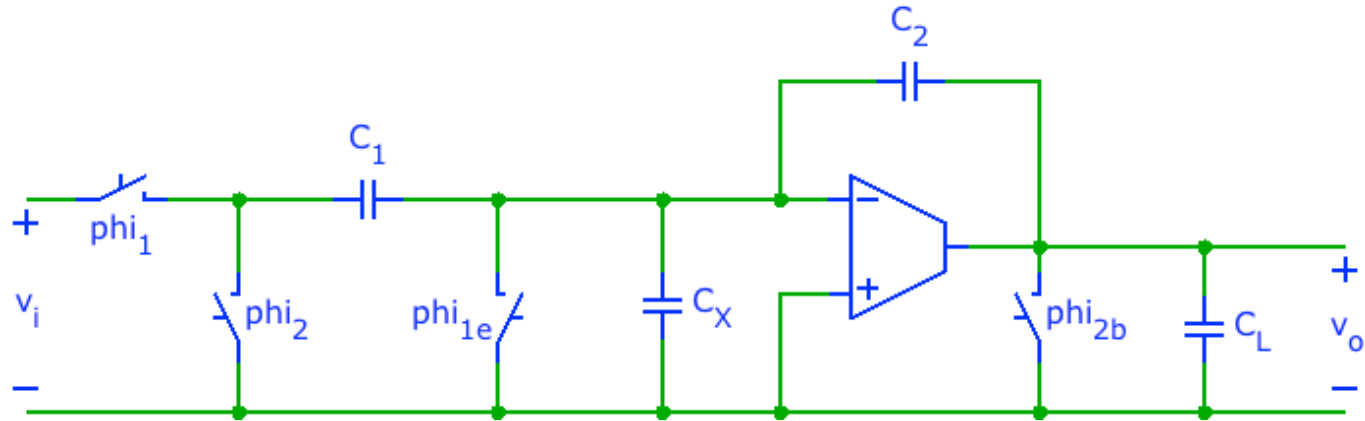


Amplifier is active only in ϕ_2 :

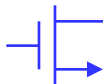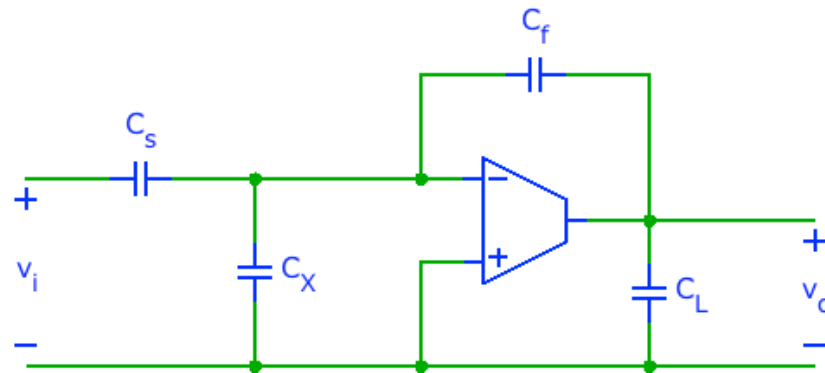


Capacitive Feedback ... Simulation

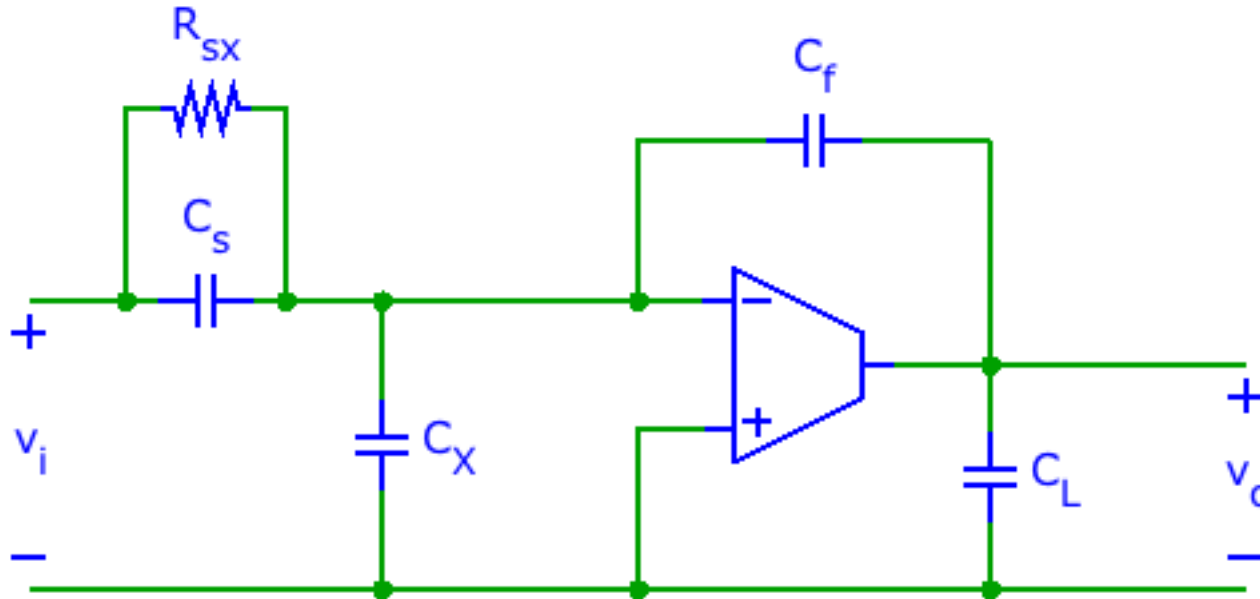


$$R_{sx} \cong 20 \text{ G}\Omega$$

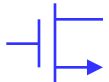

Small-Signal Model

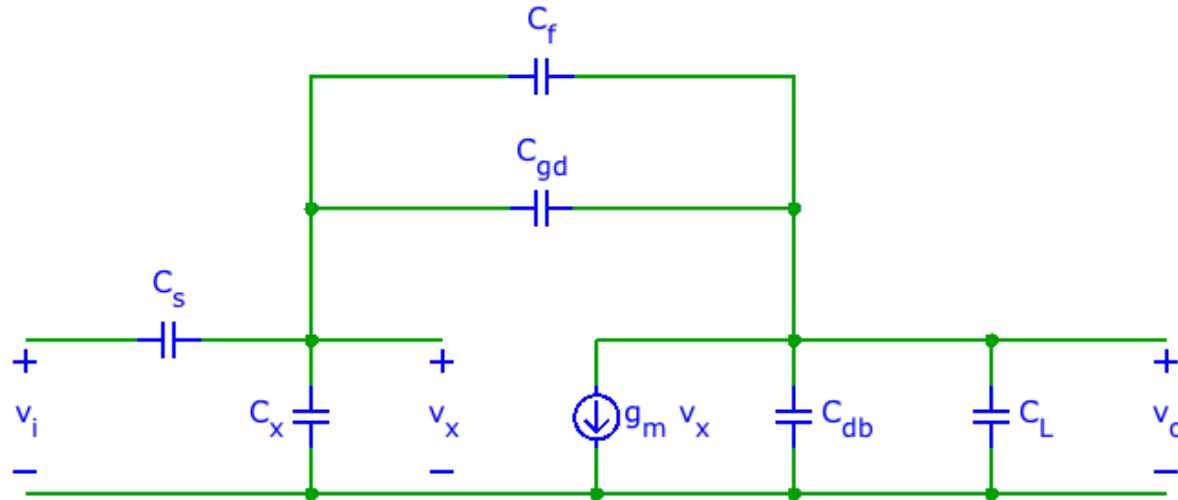

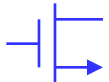Absorb C_{gd} , C_{db} , etc. in C_f , C_L , ...



Advanced Analog Integrated Circuits


Loop-Gain & Stability

Bernhard E. Boser



University of California, Berkeley

boser@eecs.berkeley.edu



Copyright © 2016 by Bernhard Boser

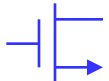


Model

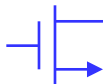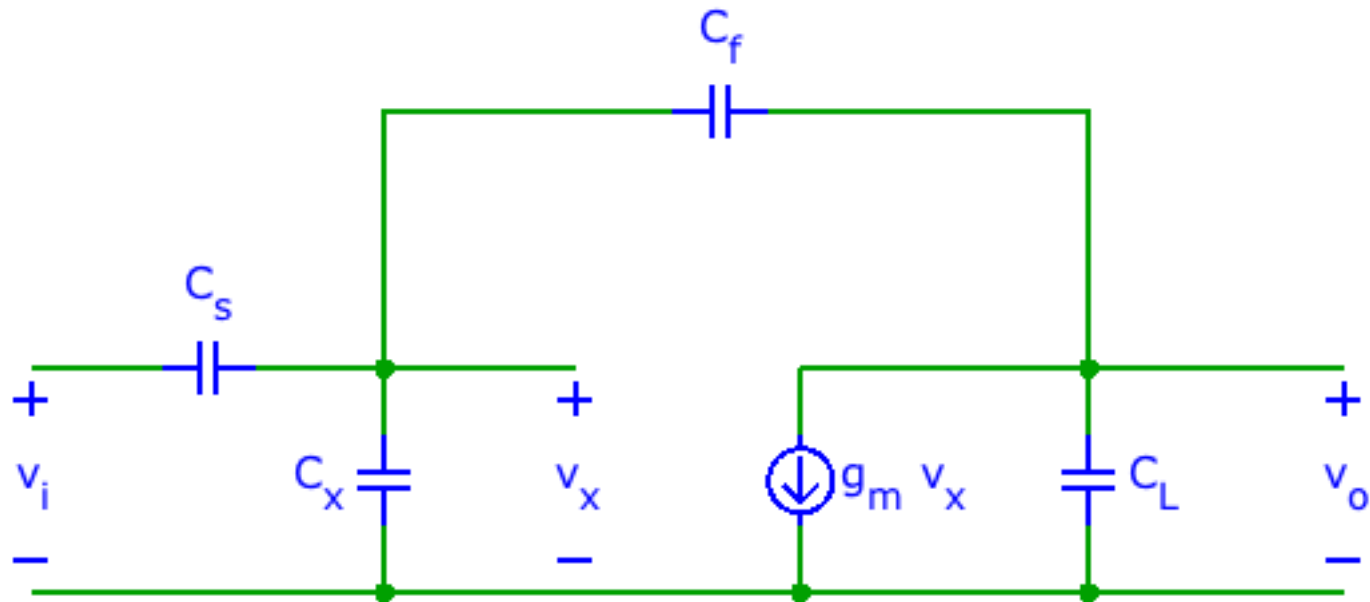

Loop-Gain Analysis

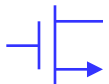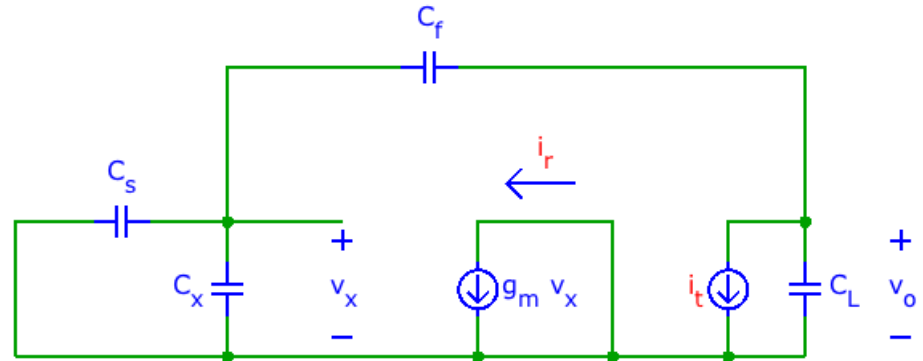


Loop-Gain $T(s)$

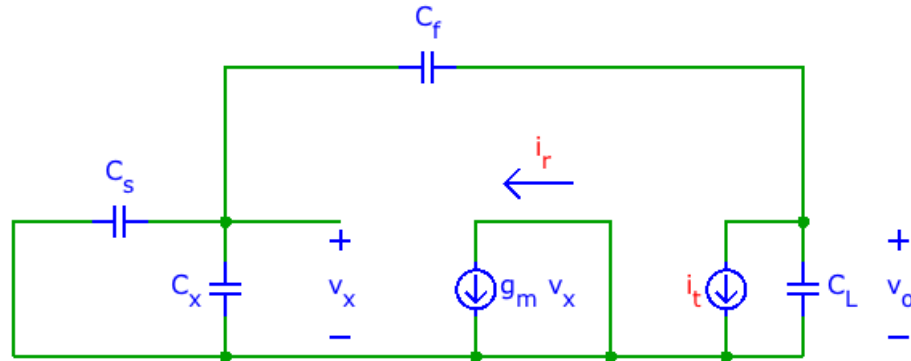

$$T(s) = \beta \frac{g_m}{s \cdot C_{Ltot}}$$



Feedback factor $\beta = \frac{v_x}{v_o} = \frac{C_f}{C_f + C_s + C_x} \neq \frac{1}{a_{vo}}$

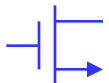Effective Load Capacitance $C_{Ltot} = C_L + (1 - \beta)C_f$



Frequency Response of T(s)
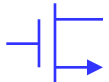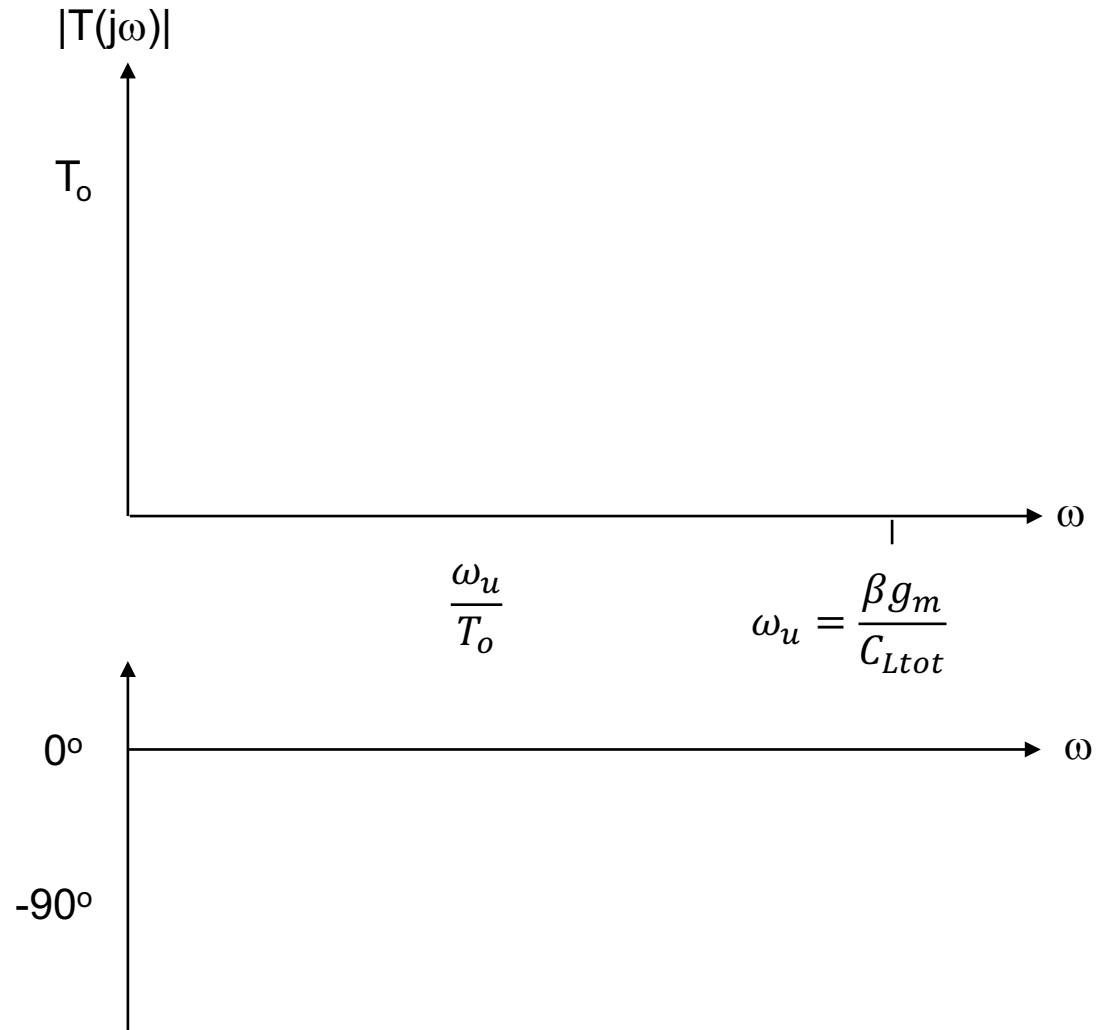
$$T(s) = \frac{\beta g_m}{s \cdot C_{Ltot}}$$



Advanced Analog Integrated Circuits


Closed-Loop Response

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

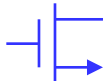


Closed-Loop Analysis


Feedback-Only Model

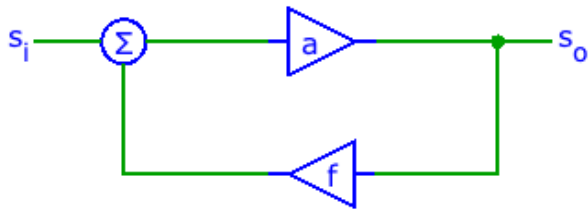


Generalized Model

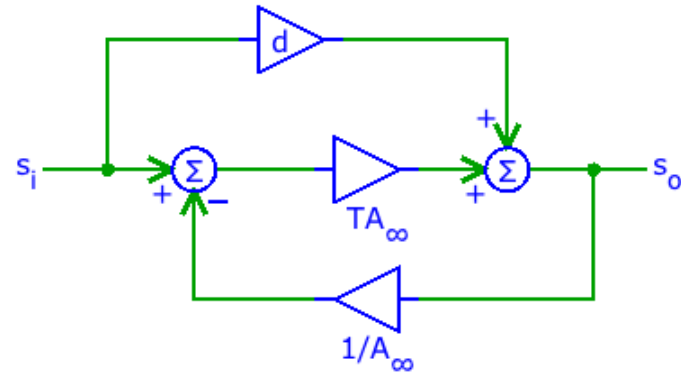


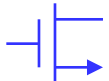
Ref: P. Hurst, "A comparison of two approaches to feedback circuit analysis," IEEE Trans. edu., Aug. 1992, pp. 253-261.





Closed-Loop Transfer Function

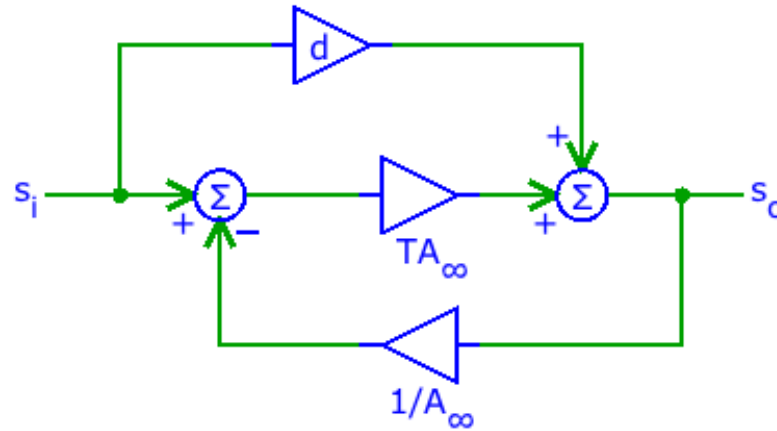


$$A_{\infty}$$

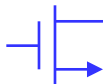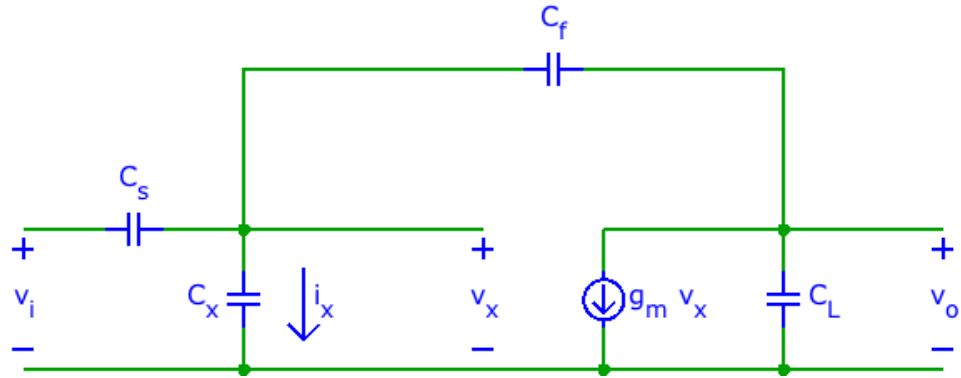

d

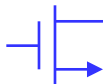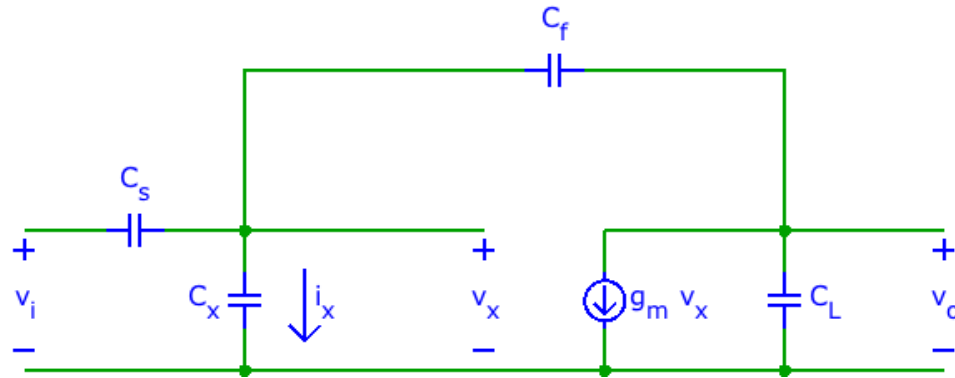


Closed-Loop Gain

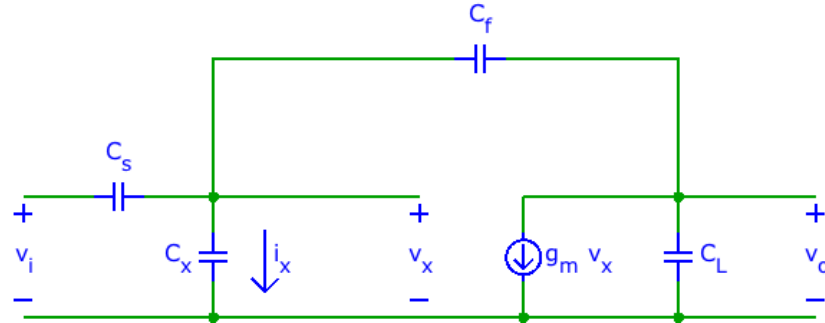

$$A(s) = A_\infty \frac{T(s)}{1 + T(s)} + \frac{d}{1 + T(s)} = -\frac{C_s}{C_f} \frac{\frac{\beta g_m}{s \cdot C_{Ltot}}}{1 + \frac{\beta g_m}{s \cdot C_{Ltot}}} + \frac{\beta \frac{C_s}{C_{Ltot}}}{1 + \frac{\beta g_m}{s \cdot C_{Ltot}}}$$

$$= -\frac{C_s}{C_f} \frac{1 - s \frac{C_f}{g_m}}{1 + s \frac{C_{Ltot}}{\beta g_m}} = -\frac{C_s}{C_f} \frac{1 - \frac{s}{z}}{1 - \frac{s}{p}}$$
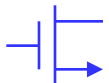
$$p = -\frac{\beta g_m}{C_{Ltot}} \quad z = +\frac{g_m}{C_f}$$



Advanced Analog Integrated Circuits


Stability and $T(s)$ with Simulator

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

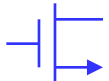


T(s) Verification with Simulator

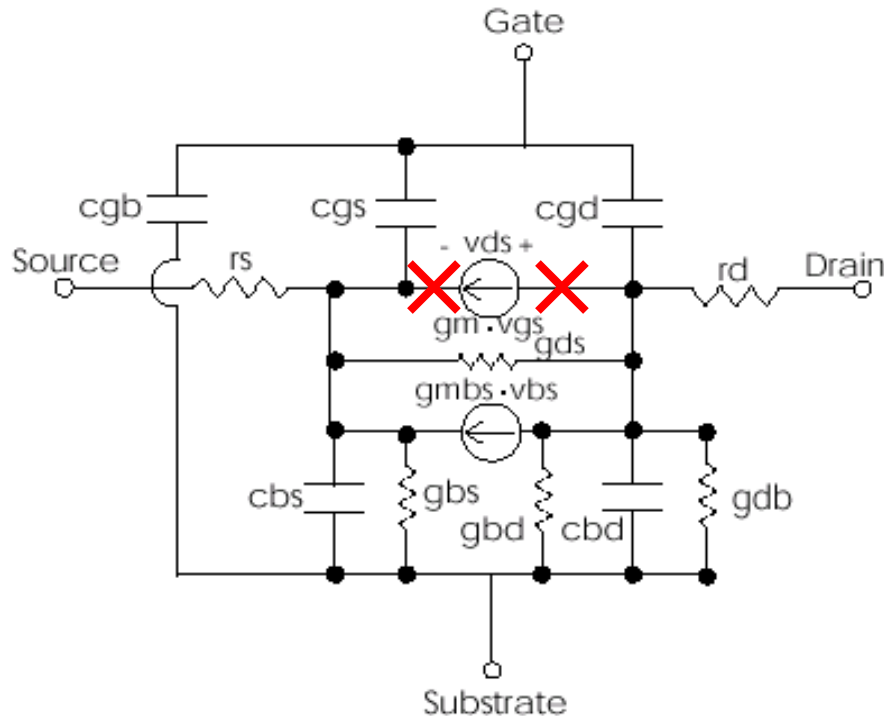
- Infinite impedance point to break loop usually not accessible
 - E.g. inside transistor




[Hspice manual]

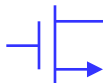

Workaround (Don't do this!)

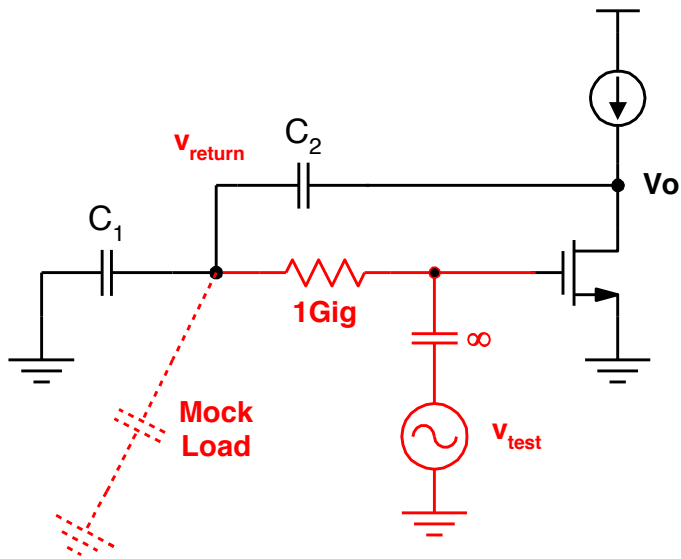


[Drawing by B. Murmann]

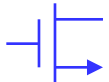

General Problem

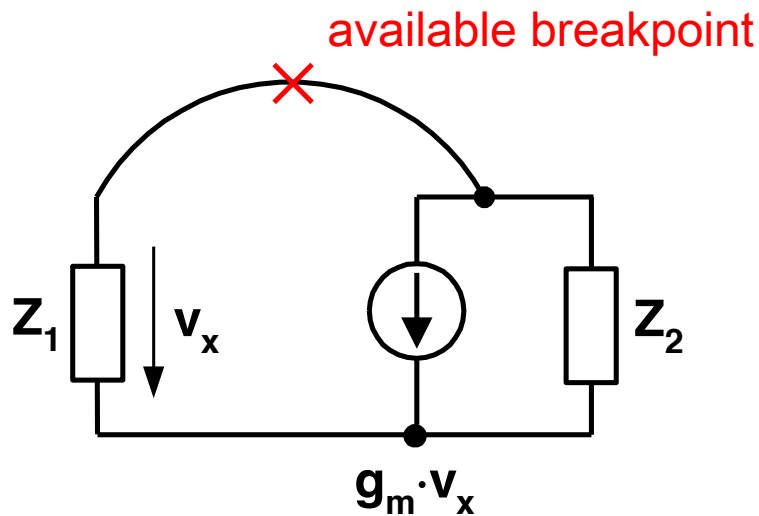Any “single loop“ feedback circuit can be represented as:




$$T(s) = g_m \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$$

[Drawing by B. Murmann]


Breakpoint at ideal source is not available.
But there is a breakpoint “between finite impedances“

Middlebrook Double Injection Method

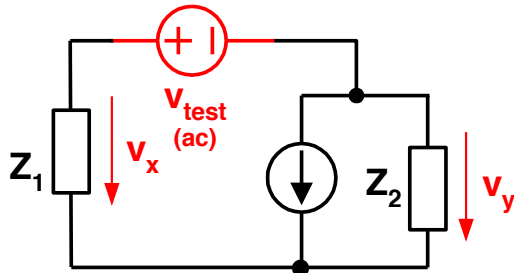

$$\frac{v_y}{v_x} \equiv T_v = g_m \cdot Z_2 + \frac{Z_2}{Z_1}$$

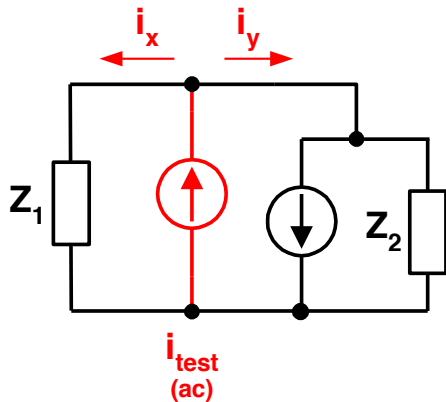True Loop Gain: $T = g_m \cdot \frac{Z_1 Z_2}{Z_1 + Z_2}$



$$\frac{i_y}{i_x} \equiv T_i = g_m \cdot Z_1 + \frac{Z_1}{Z_2}$$


[Drawing by B. Murmann]

Solving yields:


$$T = \frac{T_v T_i - 1}{T_v + T_i + 2}$$

[Middlebrook 75]

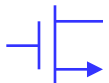- No “DC” break in the loop, all loading effects covered.
- Measure T_v and T_i , then calculate actual T
- Variant implemented in many simulators, e.g. stb-analysis in Spectre



SPICE

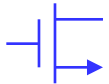


Multiple Feedback Loops

- Break all loops at a single point
- If such a point does not exist: [Bode 45]

“If a circuit is stable when all its tubes have their nominal gains, the total number of clockwise and counterclockwise encirclements of the critical point must be equal to each other in the series of Nyquist diagrams for the individual tubes obtained by beginning with all tubes dead and restoring the tubes successively in any order to their nominal gains”

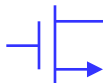– Suggestion: take a controls class if your circuit depends on this!




Nonlinearities

- Real circuits are nonlinear – frequency response depends on signal amplitude. Bode:

“... thus the circuit may sing when the tubes begin to lose their gain because of age, and it may also sing, instead of behaving as it should, when the gain increases from zero as power is supplied to the circuit ...”

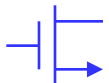- Always run a “large signal” transient analysis for a complete stability check!
 - With realistic (large) signal amplitudes including overload
 - Power supply ramping. Is a special order required?



Advanced Analog Integrated Circuits


Settling

Bernhard E. Boser



University of California, Berkeley

boser@eecs.berkeley.edu


Copyright © 2016 by Bernhard Boser

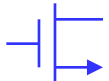

Step Response

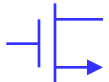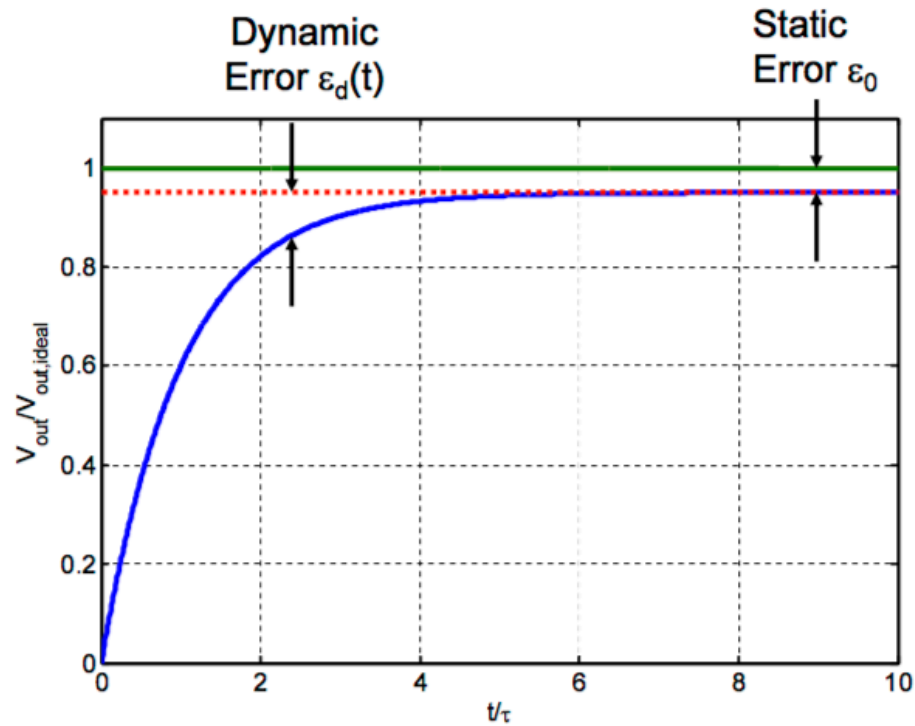

Closed-Loop Gain

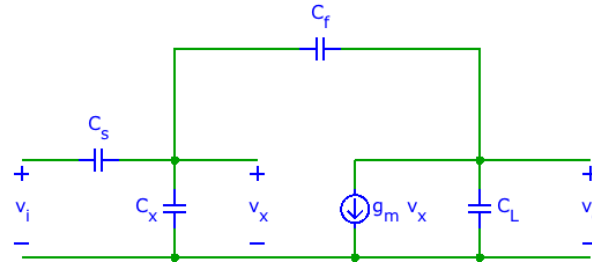

- Use favorite analysis method, e.g. return-ratio analysis*, nodal analysis, ...


$$A(s) = \frac{V_o(s)}{V_i(s)} = -\frac{C_s}{C_f} \frac{1 - s \frac{C_f}{g_m}}{1 + s \frac{C_{Ltot}}{\beta g_m}} = -\frac{C_s}{C_f} \frac{1 - \frac{s}{z}}{1 - \frac{s}{p}}$$

$$\omega_p = \frac{\beta g_m}{C_{Ltot}} \cong \omega_{-3dB} \text{ of } A(s) = \omega_u \text{ of } T(s)$$


$$\omega_z = \frac{g_m}{C_f}$$

$$\frac{\omega_z}{\omega_p} = \frac{C_{Ltot}}{\beta C_f} \quad \text{usually } \gg 1$$

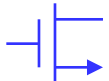
*Note: 2-port analysis ignores the feedforward path and therefore does not get the zero




Dynamic Error (no zero)

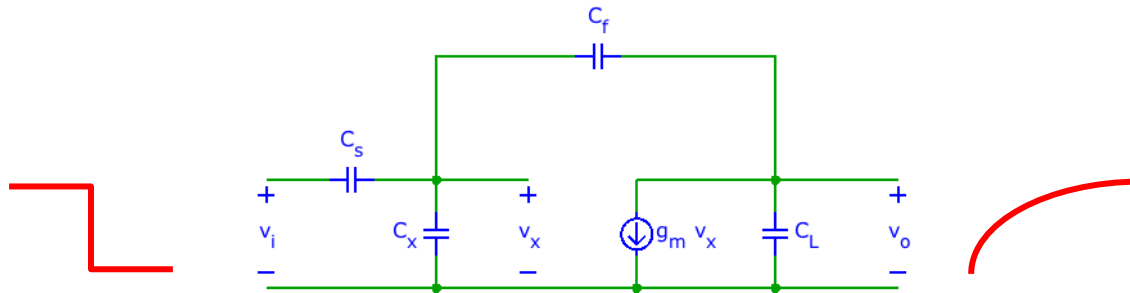

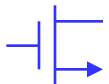Assume switch on-resistance contribution to settling is negligible




Dynamic Settling Error

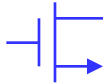


Dynamic Settling Error (single pole)

ϵ_d	t_s/τ
1%	4.6
0.1%	6.9
0.01%	9.2
10^{-6}	13.8



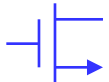


Amplifier Bandwidth versus f_s

ε_d	f_{-3dB}/f_s
1%	1.5
0.1%	2.2
0.01%	2.9
10^{-6}	4.4

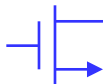

Static Settling Error

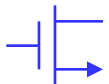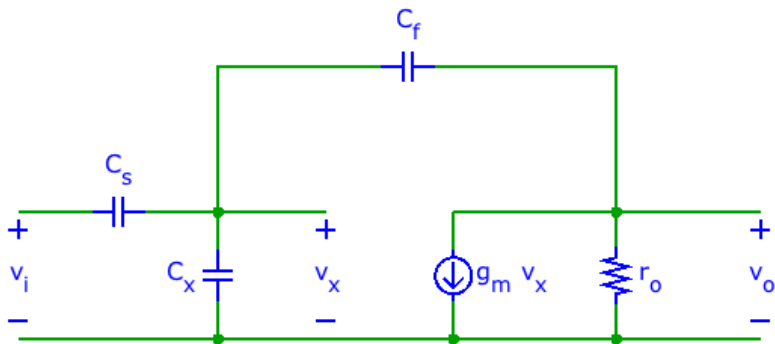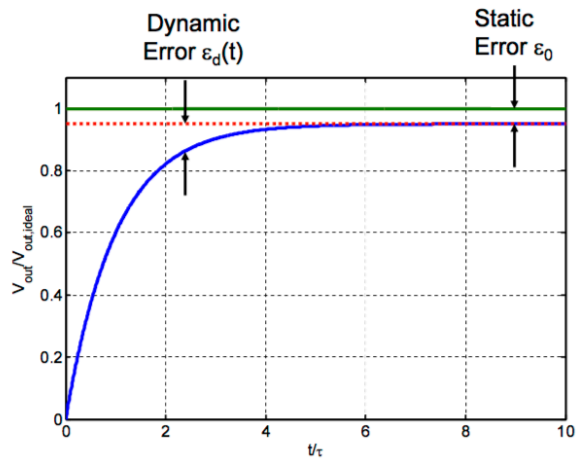


Example

$$C_s = 4\text{pF}$$


$$C_f = 1\text{pF}$$

$$C_x = 1\text{pF}$$

$$g_m r_o = 6000$$

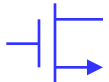


Dynamic Error (**with zero**)

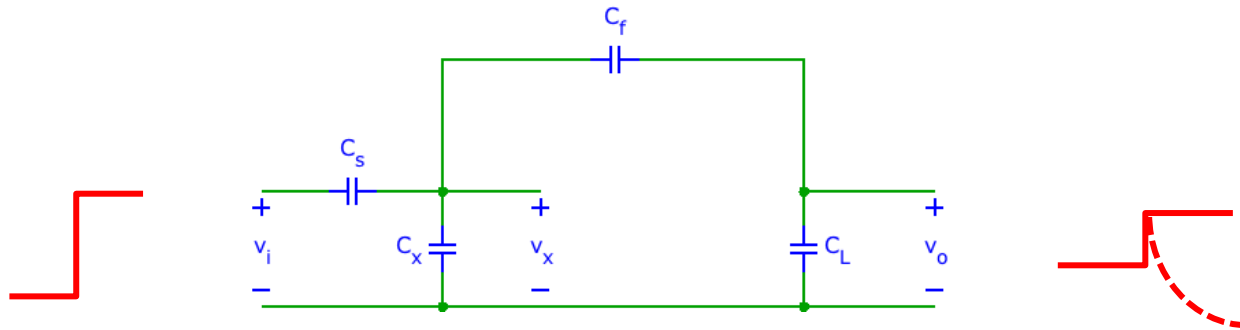

- Instant response to step determined by capacitive feed-forward

$$A(s) = \frac{V_o(s)}{V_i(s)} = -\frac{C_s}{C_f} \frac{1 - s \frac{C_f}{g_m}}{1 + s \frac{C_{Ltot}}{\beta g_m}}$$
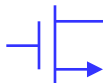
$$z = +\frac{g_m}{C_f} \quad p = -\frac{\beta g_m}{C_{Ltot}}$$




Step Response with Zero

$$v_{o,step}(t) = -V_{step} \cdot G_i \left\{ 1 - \left(1 - \frac{p}{z} \right) e^{-t/\tau} \right\}$$

$$1 - \frac{p}{z} = \frac{1}{1 - \beta \frac{C_f}{C_f + C_L}}$$
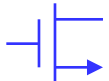
$$t_s = -\tau \cdot \ln \left\{ \varepsilon_d \left(1 - \beta \frac{C_f}{C_f + C_L} \right) \right\}$$



Advanced Analog Integrated Circuits


Phase Margin

Bernhard E. Boser



University of California, Berkeley

boser@eecs.berkeley.edu



Copyright © 2016 by Bernhard Boser

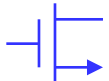


Cascode

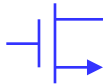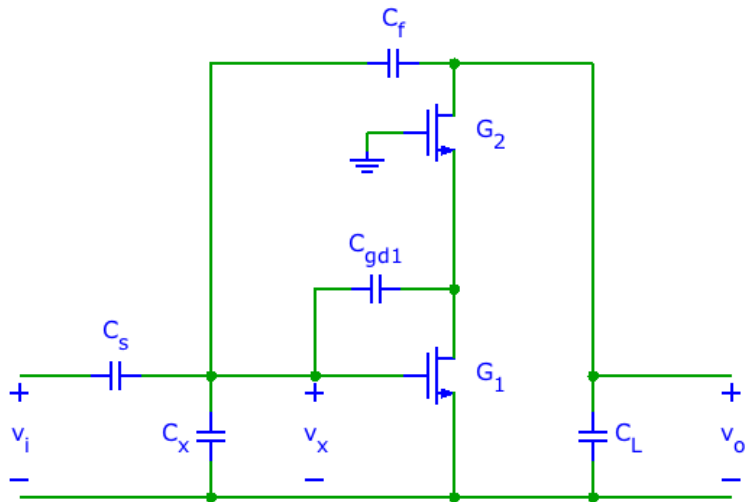



Phase Margin

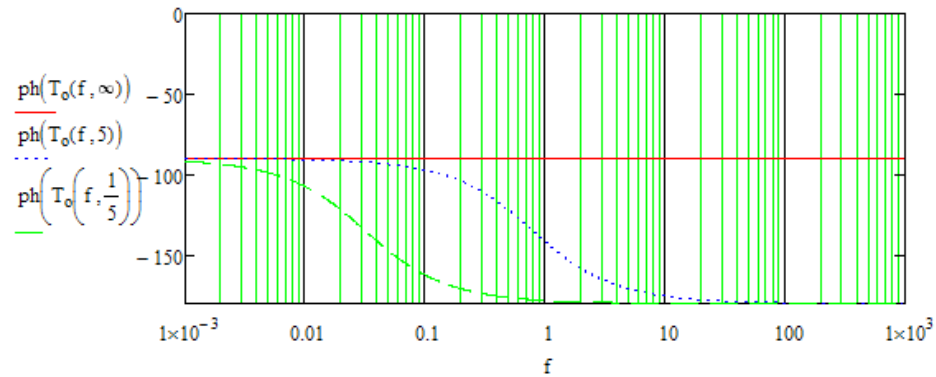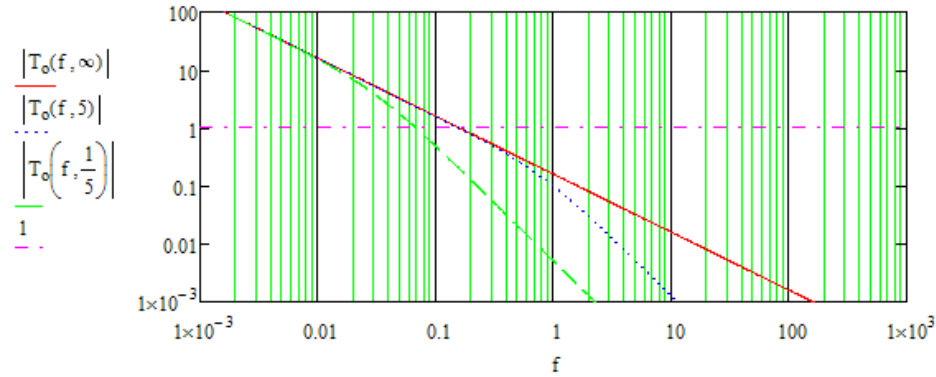



f_{p2}/f_u	Phase Margin
∞	90°
5	$\sim 80^\circ$
1/5	$\sim 28^\circ$

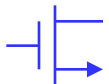

Step Response

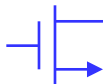
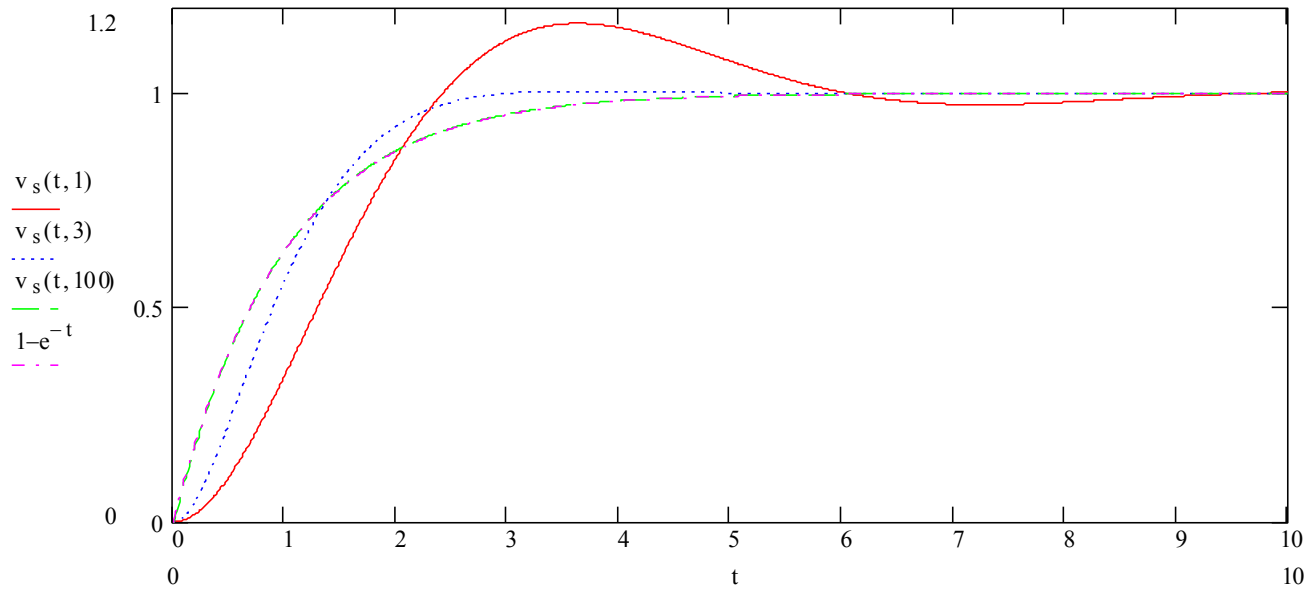


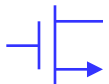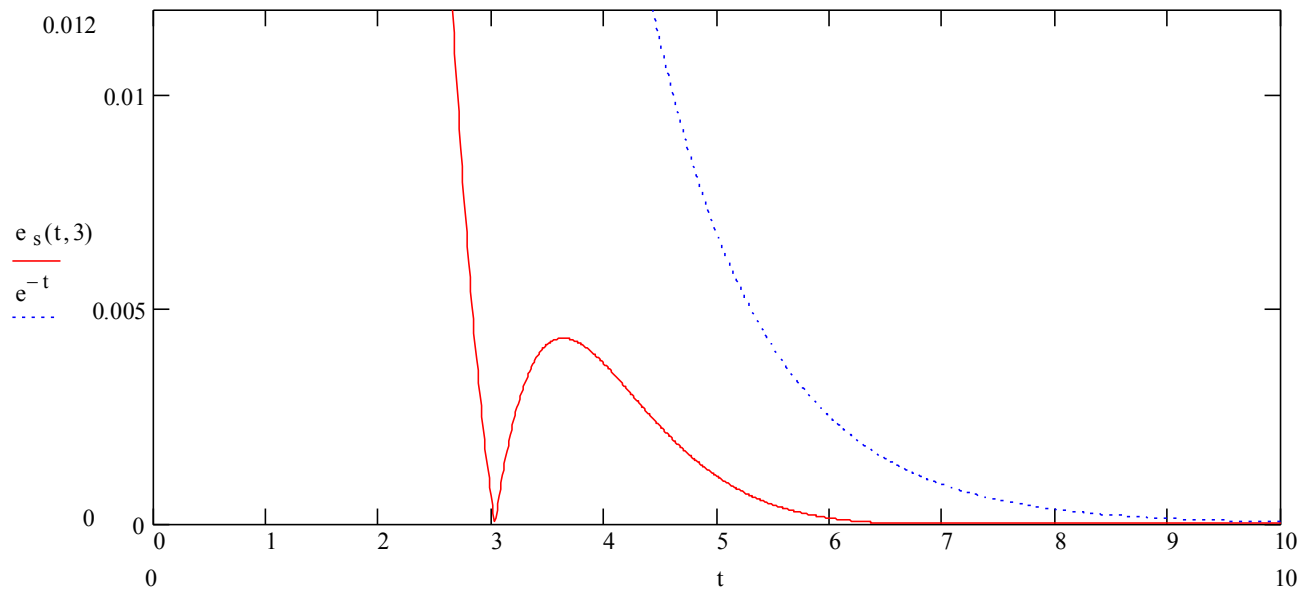Relative Settling Error for $f_{p2}/f_u = 3$




Settling Time versus f_{p2}/f_u


$$\varepsilon_d = 0.1\%$$

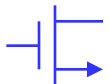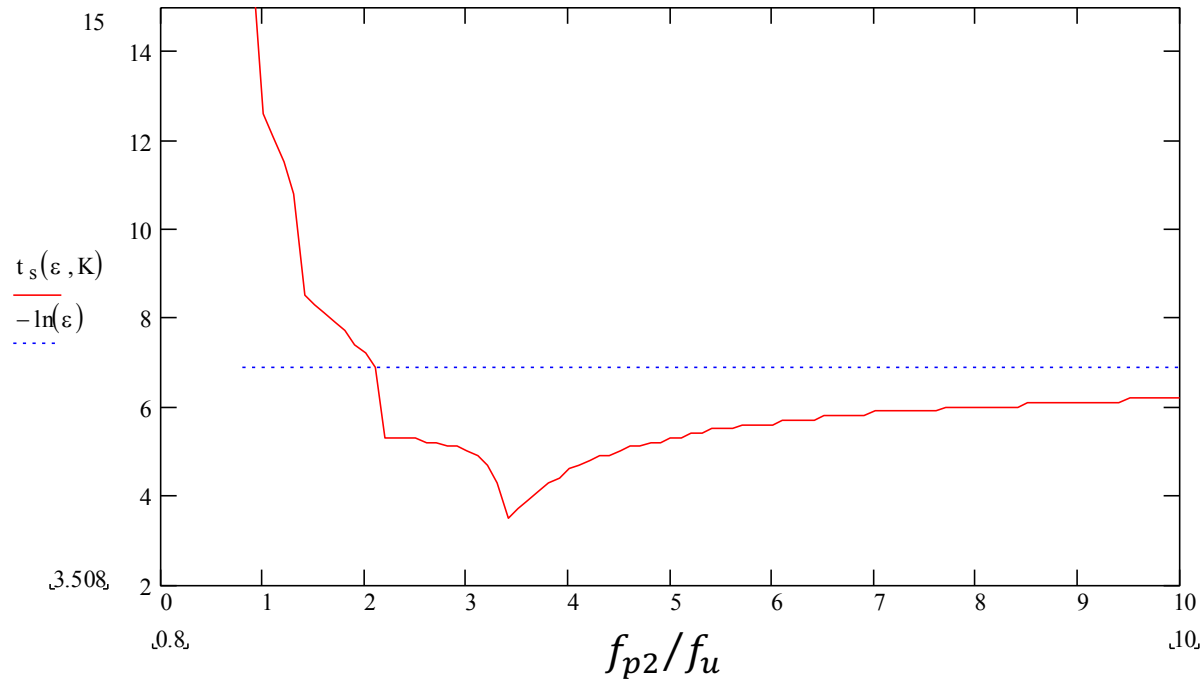

Noise

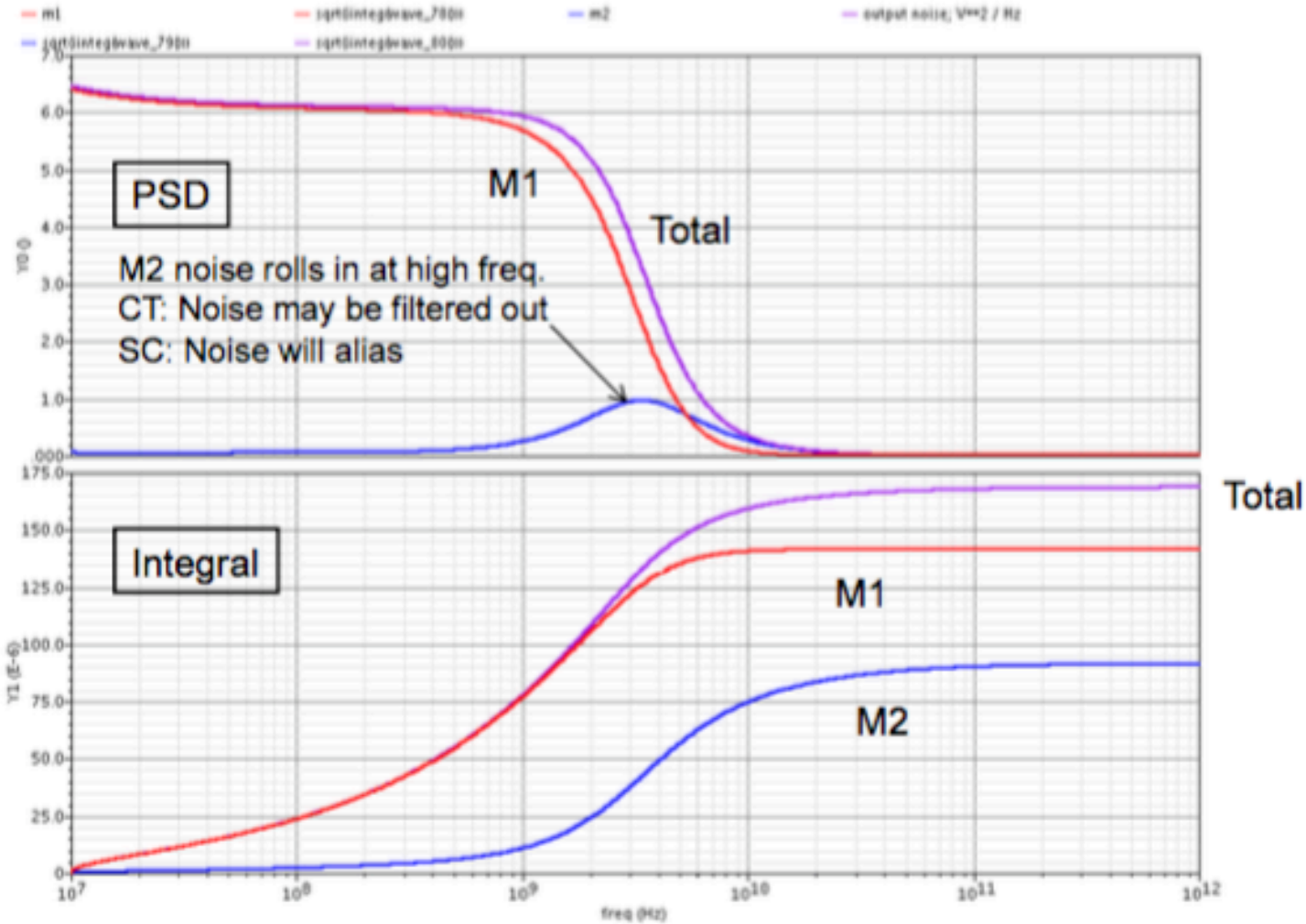

[B. Murmann]

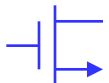

Advanced Analog Integrated Circuits


Design Example

Bernhard E. Boser

University of California, Berkeley

boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

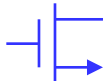

Design Example: Specification

Closed-loop gain (magnitude):

$$A_{vo} := 2$$

Settling time:

$$t_s := 5 \text{ ns}$$

$$f_{s_max} := \frac{1}{2 \cdot t_s} = 100 \text{ MHz}$$

Dynamic settling accuracy:

$$\varepsilon_d := 0.02\%$$

Static settling accuracy:

not specified (later)

Dynamic range at output:

$$\text{DR} := 10^7$$


$$10 \cdot \log(\text{DR}) = 70 \text{ dB}$$

Supply voltage:

$$V_{dd} := 1.8 \text{ V}$$

Power:

minimum

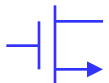

Design: Gain & Feedback Factor


Sampling capacitance: $C_s := 4\text{pF}$ set by previous stage / iterate ...

Feedback capacitance: $C_f := \frac{C_s}{A_{vo}}$ $C_f = 2 \cdot \text{pF}$

"Maximum" input capacitance: $C_{x_max} := 0.7 \cdot (C_s + C_f)$ $C_{x_max} = 4.2 \cdot \text{pF}$

Actual input capacitance (iterate): $C_x := 0.7\text{pF}$

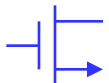Feedback factor: $\beta := \frac{C_f}{C_f + C_s + C_x}$ $\beta = 0.299$



Design: Dynamic Range

Available output voltage range:

$$V_{\text{opp}} := V_{\text{dd}} - 400\text{mV}$$

Total noise at output:

$$N_{\text{ot}} := \frac{\frac{1}{2} \cdot \left(\frac{V_{\text{opp}}}{2}\right)^2}{\text{DR}} \quad \sqrt{N_{\text{ot}}} = 156.525 \cdot \mu\text{V}$$

Total noise at output:

$$N_{\text{ot}} = \frac{k \cdot T}{\beta} \cdot \left(\frac{1}{C_f} + \frac{\alpha}{C_{\text{Ltot}}}\right)$$

OTA noise factor (topology & bias):

$$\alpha := 4$$

Sampling noise (phase 1):

$$\sqrt{\frac{k_B \cdot T_r}{\beta} \cdot \frac{1}{C_f}} = 81.89 \cdot \mu\text{V} \quad <? \quad \sqrt{N_{\text{ot}}} = 156.525 \cdot \mu\text{V}$$

Total load capacitance:


$$C_{\text{Ltot}} := \frac{\alpha}{N_{\text{ot}} \cdot \frac{\beta}{k_B \cdot T_r} - \frac{1}{C_f}} \quad C_{\text{Ltot}} = 3.015 \cdot \text{pF}$$

Total load capacitance:

$$C_{\text{Ltot}} = C_{\text{L}} + (1 - \beta) \cdot C_f$$

Load capacitance:
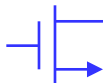
$$C_{\text{L}} := C_{\text{Ltot}} - (1 - \beta) \cdot C_f \quad C_{\text{L}} = 1.612 \cdot \text{pF}$$



Design: Settling

Settling time (single pole, no slewing):

$$t_s = -\tau \cdot \ln \left[\epsilon_d \cdot \left(1 - \beta \cdot \frac{C_f}{C_f + C_L} \right) \right]$$

Settling time constant:


$$\tau := \frac{-t_s}{\ln \left[\epsilon_d \cdot \left(1 - \beta \cdot \frac{C_f}{C_f + C_L} \right) \right]} = 574.854 \cdot \text{ps}$$

Settling time constant:

$$\tau = \frac{C_{L\text{tot}}}{\beta \cdot g_m} \quad f_u := \frac{1}{2 \cdot \pi \cdot \tau} = 276.862 \text{ MHz}$$

Transconductance:
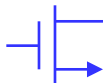
$$g_m := \frac{C_{L\text{tot}}}{\beta \cdot \tau} = 17.57 \cdot \text{mS}$$



Design: Power Dissipation

Minimum cutoff frequency:

$$f_T := \frac{1}{2 \cdot \pi} \cdot \frac{g_m}{C_x} = 3.995 \cdot \text{GHz}$$

Channel length:

$$L_1 := 250\text{nm}$$

Current density:

$$V_{\text{star}} := 120\text{mV}$$

Actual f_T :


$$f_{T_actual} := 6\text{GHz} \quad >? \quad f_T = 3.995 \text{GHz}$$

Actual C_x (update):


$$C_{x_actual} := \frac{g_m}{2 \cdot \pi \cdot f_{T_actual}} = 0.466 \text{pF} \quad <? \quad C_x = 0.7 \text{pF}$$

Bias current:
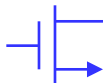
$$I_d := \frac{g_m \cdot V_{\text{star}}}{2} = 1.054 \cdot \text{mA}$$



Could we go Faster?

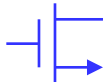

Advanced Analog Integrated Circuits


Gain Boosting

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

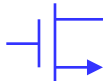



Openloop Gain

$$a_{vo} = g_m R_o$$


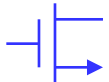


Openloop Gain

$$a_{vo} = g_m R_o$$

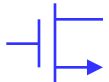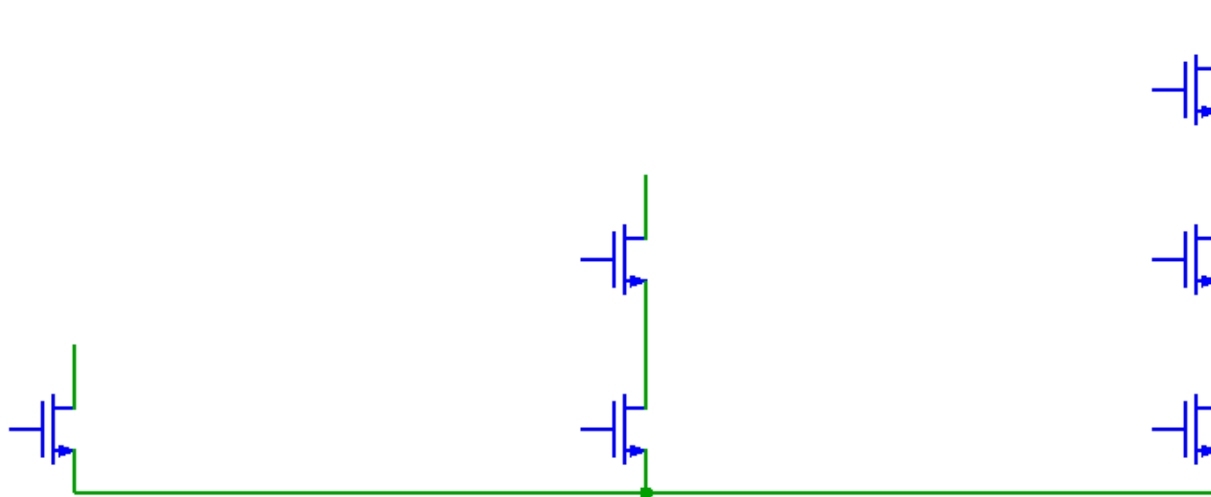

Gain Boosting

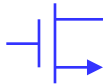
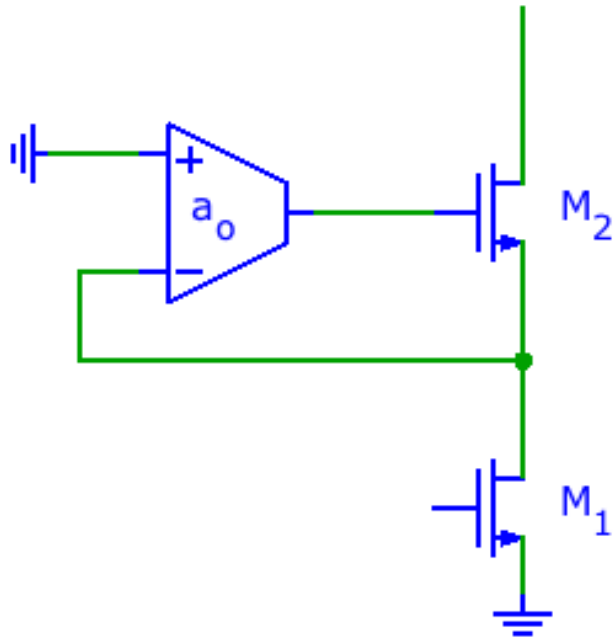


Gain Boosting



- Use feedback to boost low-frequency output resistance

- References

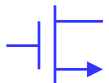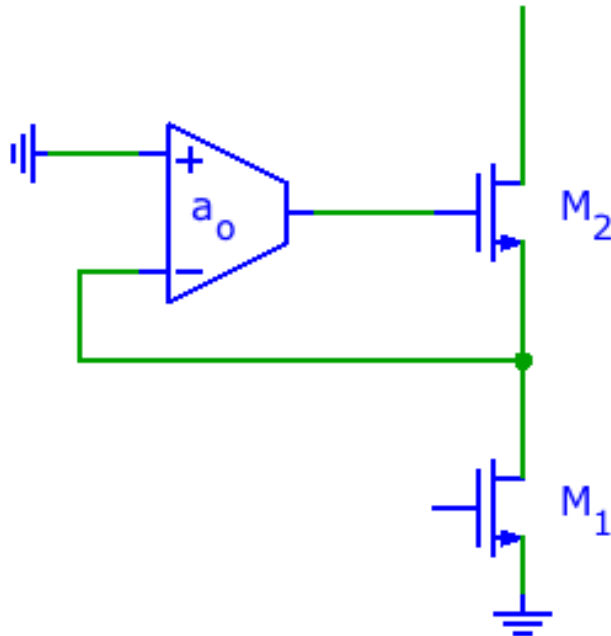
- B. J. Hosticka, “Improvement of the gain of MOS amplifiers,” JSSC, Dec. 1979 , pp. 1111-4.
- E. Sackinger and W. Guggenbuhl, “A high-swing high-impedance MOS cascode circuit”, JSSC, Feb. 1990, pp. 289-298.
- K. Bult, G. Geelen, “A fast-settling CMOS op-amp for SC circuits with 90-dB DC gain,” JSSC, Dec. 1990 , pp. 1379-84.




High Frequency Analysis

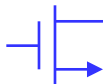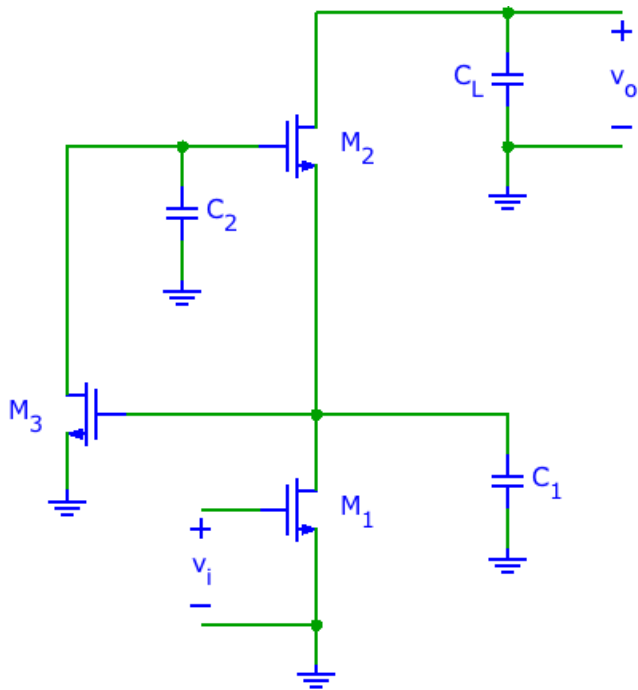

Overall Amplifier Response

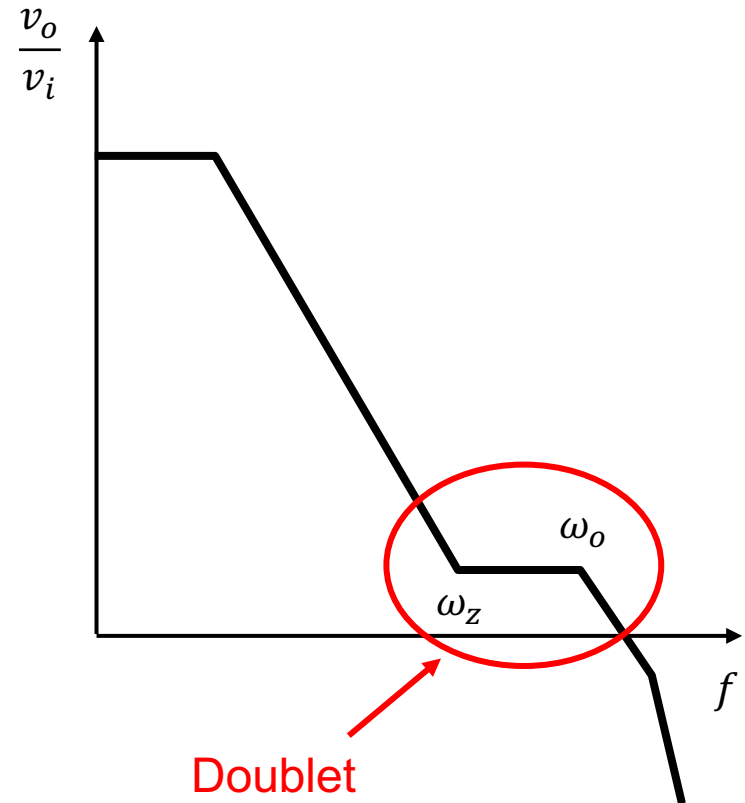

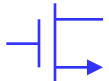Ref: M. Das, "Improved design criteria of gain boosted CMOS OTA with high-speed optimizations," IEEE CAS II, March 2002, pp. 204-7.



Advanced Analog Integrated Circuits


Pole-Zero Doublets

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

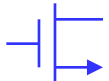

Pole-Zero Doublets

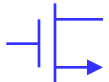Ref: Y. Kamath, R. G. Meyer, and P. R. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE J. Solid-State Circuits*, pp. 347–352, Dec. 1974.




Doublet Settling

- Amplifier model: replace G_{mo} with

$$G_m(s) = G_{mo} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

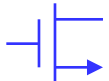Notation from Y. Kamath, R. G. Meyer, and P. R. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE J. Solid-State Circuits*, pp. 347–352, Dec. 1974.



Doublet Settling


- Amplifier model: replace G_{mo} with

$$G_m(s) = G_{mo} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \quad \text{with} \quad \begin{aligned} \omega_p &= \beta \omega_{-3dB}, & \omega_{-3dB} & \text{ is bandwidth of } T(s) \\ \omega_z &= \frac{\omega_p}{\alpha} \\ \alpha &= 1 + \varepsilon & \text{ with } |\varepsilon| & \ll 1 \end{aligned}$$

- Closed-loop response

$$\frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m(s)}} \cong -\frac{c}{1 + \frac{s}{\omega_{-3dB}}} \left(\frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_{pp}}} \right) \quad \text{with} \quad \begin{aligned} \omega_{-3dB} &= \frac{FG_{mo}}{C_{Leff}} \\ \omega_{pp} &\cong \omega_p \end{aligned}$$

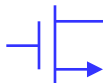Notation from Y. Kamath, R. G. Meyer, and P. R. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE J. Solid-State Circuits*, pp. 347–352, Dec. 1974.




Doublet Step Response

$$v_{o,step}(t) = -cV_{step} \left(1 + Ae^{-t\omega_{-3dB}} + Be^{-t\omega_{pp}} \right)$$


with

$$A \cong -1$$


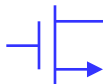
$$B \cong \varepsilon \frac{\beta}{1 - \beta^2}$$



Doublet Example

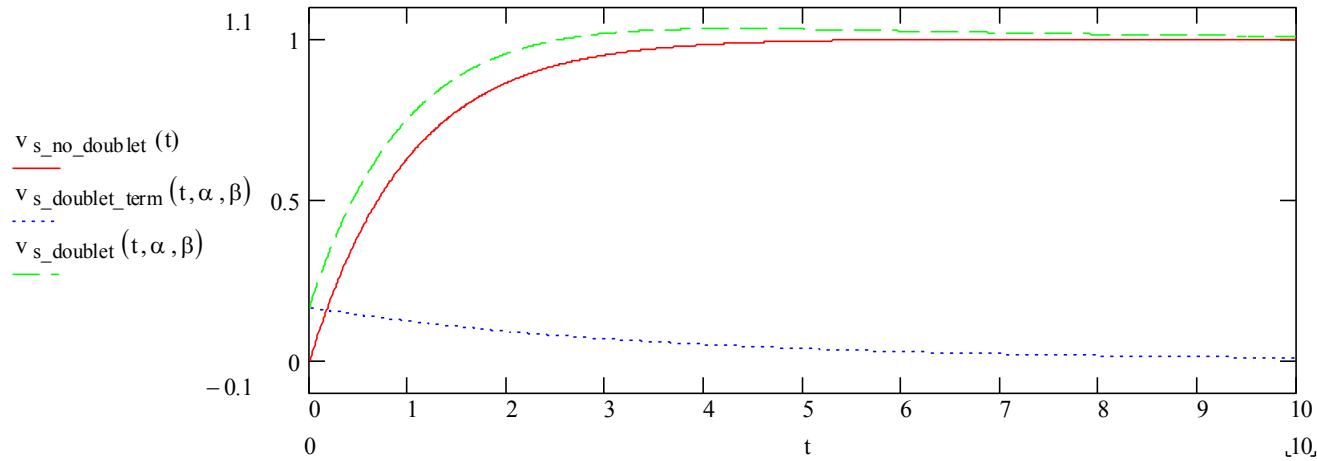

$$\alpha = 1.5$$
$$\beta = 0.3$$

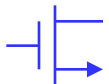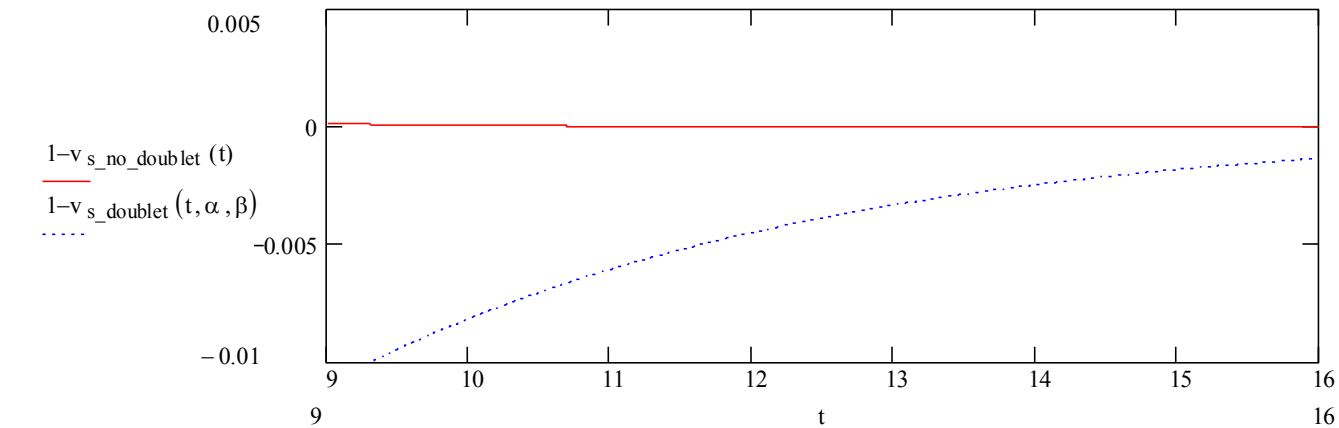

Gain Boosting – Doublets

