

Reference: W:\Lib\MathCAD\Default\defaults.mcd

1. Objective

a. Motivation

- . Finite circuit speed, e.g. amplifier - effect on signals
- . E.g. how "fast" an amp do we need for audio? For video? For RF?
- . How do we characterize "fast"?
- . Check response for "every possible" input is not practical
- . Solution: check response for "representative signals"
that stand in for "every possible" signal

b. What is Frequency domain analysis?

- . Analysis technique
- . Not a new circuit element, it's applies to the circuit we already know
- . Widely used in engineering (not just circuits)
 - e.g. EE 20 ++
 - Underlying math: Laplace & Fourier transform, (phasors)

2. Analysis with sinusoids

- . cascadable (shape retained)
- . efficient: phasor analysis
- . universal: Fourier analysis
- . Demo: <http://www.falstad.com/fourier> (live!)

3. Phasor / Laplace

- 0. Motivation: time domain diff eqs, trigonometry: math problem
- a. Represent sinusoids with complex numbers
- b. Signals are not complex
- c. RC LPF example steady state analysis
- d. Impedance, Admittance
 - . RLC
 - . generalized

4. Bode plot

- a. Ratios, dB (why logarithmic)
- b. Bode plot
- c. Techniques

5. Power (NR Ch 10)

- . instantaneous, average
- . rms
- . complex

Lecture 25: Sinusoidal Steady State (see also ppt)

Motivation

- circuits 'deform' changing signals
- e.g. digital signals do not retain their "square" shape
- amps also cannot keep up with rapidly changing signals (capacitors inside!)
- how determine e.g. if amplifier is fast enough?
- how do we even characterize how "fast" an amplifier is?
- what's a good metric? We don't want to deal at the component (schematic) level (not very hierarchical)

Problem

Example: RC LPF, (ideal) amp, RC HPF
 square wave input (for simplicity)
 "exponentials" after LPF
 even more complicated waveform after HPF
 How to analyze this???

Demo

Conclusion: sinusoids retain shape --> modular!!!

Sinusoidal Response (AC analysis)

Sinusoids:

- sin or cos
- amplitude
- frequency (f or omega)
- phase

Initial transient

Example: RL HPF (see NR text), **calculate V_R**

$$V_m := 1V \quad f := 1\text{MHz} \quad \omega := 2\pi \cdot f \quad R := 5k\Omega \quad L := 1\text{mH} \quad \tau := \frac{L}{R} \quad \tau = 200\text{ns}$$

$$T := \frac{1}{f}$$

input: $v_s(t) := V_m \cdot \cos(\omega \cdot t)$ for $t \geq 0$, 0 otherwise


KVL: $L \cdot \frac{di(t)}{dt} + R \cdot i(t) = v_s(t)$

solution: $\phi := \text{atan}\left(\frac{\omega \cdot L}{R}\right) \quad \phi = 51.488 \text{ deg}$

$$V_{R_steady}(t) := \frac{V_m \cdot R}{\sqrt{R^2 + \omega^2 \cdot L^2}} \cdot \cos(\omega \cdot t - \phi) \quad \frac{R}{\sqrt{R^2 + \omega^2 \cdot L^2}} = 0.623$$

$$v_{R_trans}(t) := \frac{-V_m \cdot R}{\sqrt{R^2 + \omega^2 \cdot L^2}} \cdot \cos(\phi) \cdot e^{-\frac{t}{\tau}}$$

$$v_R(t) := v_{R_trans}(t) + v_{R_steady}(t)$$

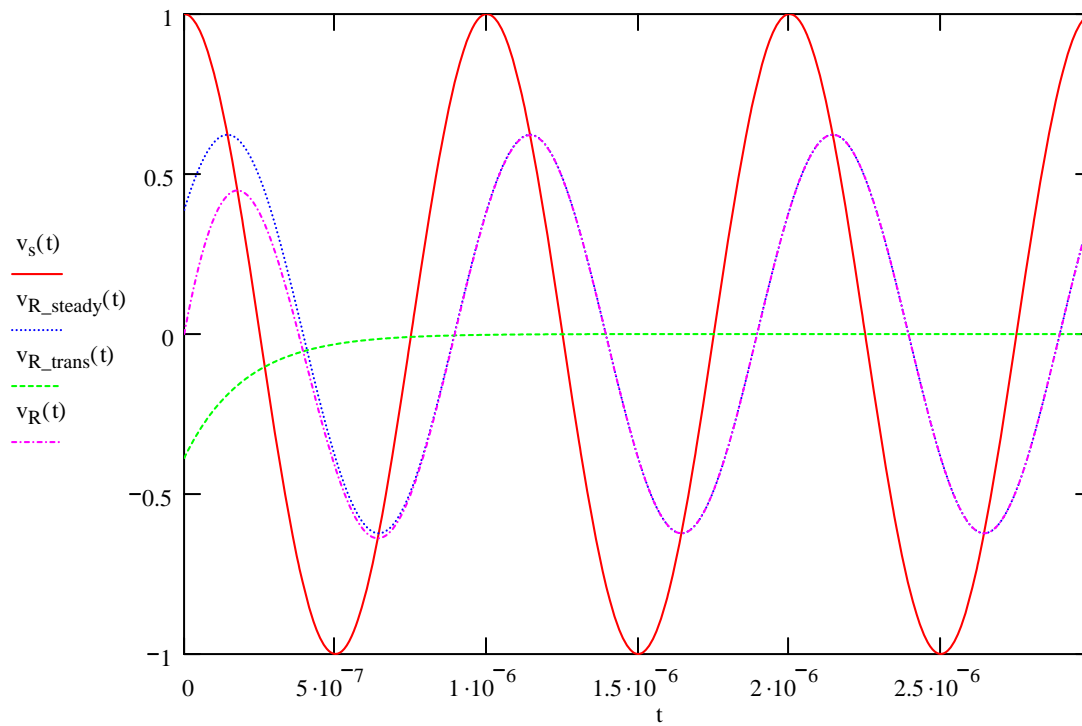

Lecture 26: Phasors

Analysis technique:

- . efficiently analyze sinusoidal steady state response
- . linear differential equations --> linear algebraic equations
- . uses complex numbers (signals are real)

Sinusoidal signal:

$$v(t) = V_m \cdot \cos(\omega \cdot t + \phi)$$

$$v(t) = \operatorname{Re} \left[V_m \cdot e^{j(\omega t + \phi)} \right] = \operatorname{Re} \left(V_m \cdot e^{j\phi} \cdot e^{j\omega t} \right) = \operatorname{Re} \left(V(j \cdot \omega) \cdot e^{j\omega t} \right)$$

Phasor

$$V(j \cdot \omega) = V_m \cdot e^{j\phi}$$

- abbreviation $s := j \cdot \omega$
- more compact equations without j
 - complex numbers show up in numeric result
 - phasor analysis is special case of Laplace transform, --> consistency with other texts on subject

Example: inductor

diff eq analysis

$$i_L(t) = I_{Lm} \cdot \cos(\omega \cdot t)$$

$$v_L(t) = L \cdot \left(\frac{d}{dt} i_L(t) \right) = -L \cdot I_{Lm} \cdot \sin(\omega \cdot t)$$

phasor analysis

$$i_L(t) = \operatorname{Re} \left(I_L(s) \cdot e^{st} \right)$$

$$v_L(t) = L \cdot \frac{d}{dt} \operatorname{Re} \left(I_L(s) \cdot e^{st} \right) = \operatorname{Re} \left(L \cdot I_L(s) \cdot s \cdot e^{st} \right)$$

$$v_L(t) = \operatorname{Re} \left(V_L(s) \cdot e^{st} \right)$$

with $V_L(s) = s \cdot L \cdot I_L(s)$

e.g. $L := 1\text{mH}$ $I_{Lm} := 1\text{mA}$ $f := 1\text{MHz}$ $\omega := 2 \cdot \pi \cdot f$ $s := j \cdot \omega$

$I_L(s) := I_{Lm}$ $V_L(s) := s \cdot L \cdot I_L(s)$ $V_L(s) = 6.283i \text{ V}$

Impedance:

$$Z_L(s) = \frac{V_L(s)}{I_L(s)} = s \cdot L$$

- universal! Treat L, C like "resistors"
- complex number
- units: ohm!

Admittance:

$$Y_L(s) = \frac{I_L(s)}{V_L(s)} = \frac{1}{s \cdot L}$$

e.g. $s \cdot L = 6.283i \text{ k}\Omega$

$$\frac{1}{s \cdot L} = -159.155i \mu\text{S}$$


Let class derive admittance of a capacitor.

Lecture 27: Network analysis with phasors

- KVL and KLC still hold (with phasors)
- represent signals with phasors (complex numbers)
- Restance becomes Impedance, generalizable to L, C!
- Ditto Admittance
- Generalized ohm-meters exist also: LCR meters, impedance / network analyzers

$$Z_R = R \quad Z_L = s \cdot L \quad Z_C = \frac{1}{s \cdot C}$$

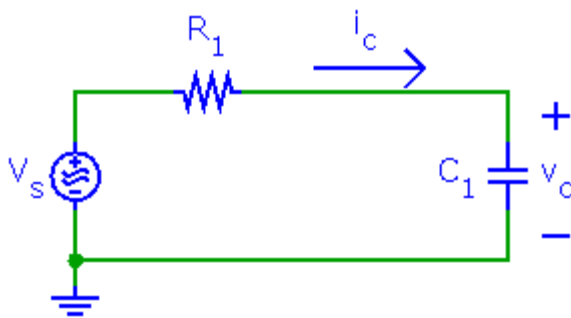Example: calculate magnitude and phase of i_c , v_c



$$Z_{\text{tot}}(s) = Z_{R1}(s) + Z_{C1}(s)$$

$$Z_{\text{tot}}(s) = R_1 + \frac{1}{s \cdot C_1} = \frac{1 + s \cdot R_1 \cdot C_1}{s \cdot C_1}$$

$$I_c(s) = \frac{V_s(s)}{Z_{\text{tot}}(s)} = V_s(s) \cdot \frac{s \cdot C_1}{1 + s \cdot R_1 \cdot C_1}$$

with $V_{\text{sm}} := 1\text{V}$ $R_1 := 10\text{k}\Omega$ $C_1 := 1\text{pF}$ $R_1 \cdot C_1 = 10\text{ns}$ $\tau_1 := R_1 \cdot C_1$

$$V_s(s) := V_{\text{sm}} \quad I_c(s) := V_s(s) \cdot \frac{s \cdot C_1}{1 + s \cdot R_1 \cdot C_1}$$

$$I_{c1} := I_c(2j \cdot \pi \cdot 10\text{MHz}) \quad I_{c1} = 28.304 + 45.048i \mu\text{A} \quad |I_{c1}| = 0.053 \text{ mA}$$

$$\arg(I_{c1}) = 57.858 \text{ deg}$$

KVL, KCL, node voltage, divider - whatever, we get:

$$V_c(s) = \frac{V_s(s)}{1 + s \cdot R_1 \cdot C_1} \quad H_1(s) = \frac{V_c(s)}{V_s(s)} = \frac{1}{1 + s \cdot R_1 \cdot C_1} \quad H_1(s) := \frac{1}{1 + s \cdot R_1 \cdot C_1}$$

$$H_a := H_1(2j \cdot \pi \cdot 0\text{MHz}) \quad |H_a| = 1 \quad \arg(H_a) = 0 \text{ deg}$$

$$H_a := H_1(2j \cdot \pi \cdot 1\text{MHz}) \quad |H_a| = 0.998 \quad \arg(H_a) = -3.595 \text{ deg}$$



$$H_a := H_1(2j \cdot \pi \cdot 10\text{MHz}) \quad |H_a| = 0.847 \quad \arg(H_a) = -32.142 \text{ deg}$$

$$H_a := H_1(2j \cdot \pi \cdot 100\text{MHz}) \quad |H_a| = 0.157 \quad \arg(H_a) = -80.957 \text{ deg}$$


$$H_a := H_1(2j \cdot \pi \cdot 1\text{GHz}) \quad |H_a| = 0.016 \quad \arg(H_a) = -89.088 \text{ deg}$$


Lecture 28: Frequency Response
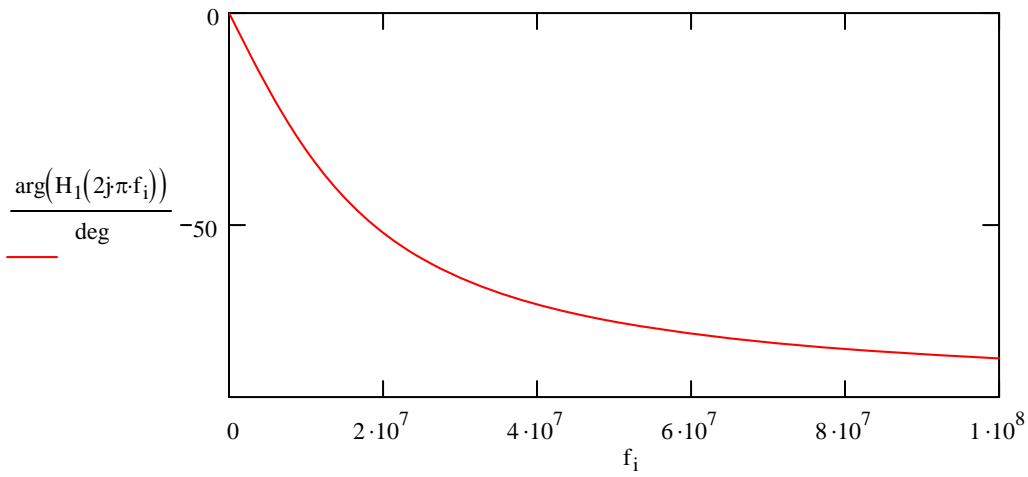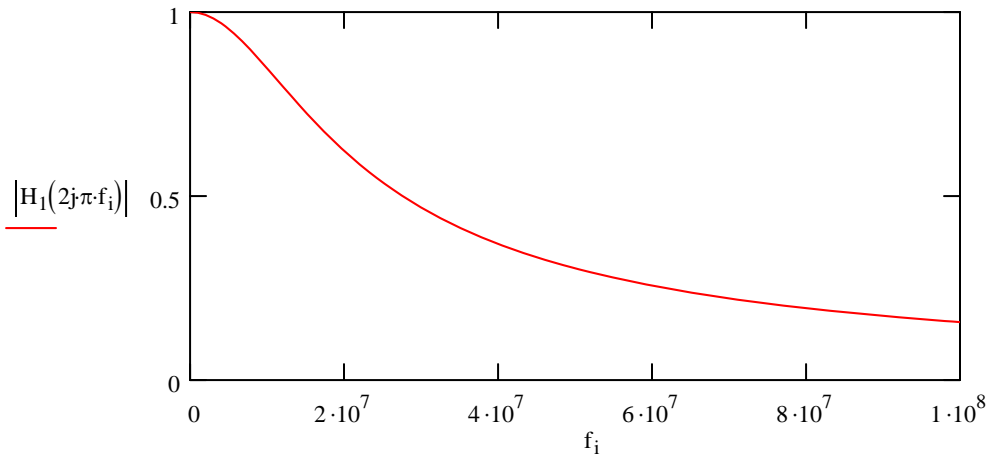
`N := 100` `i := 0..N - 1` `f := linrange(0Hz, 100MHz, N)`


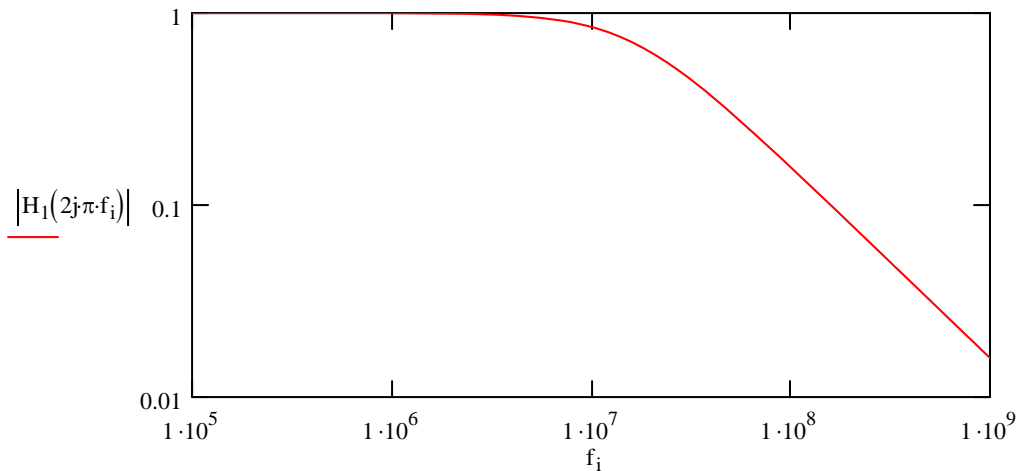
`N := 100` `i := 0..N - 1` `f := logrange(100kHz, 1GHz, N)`



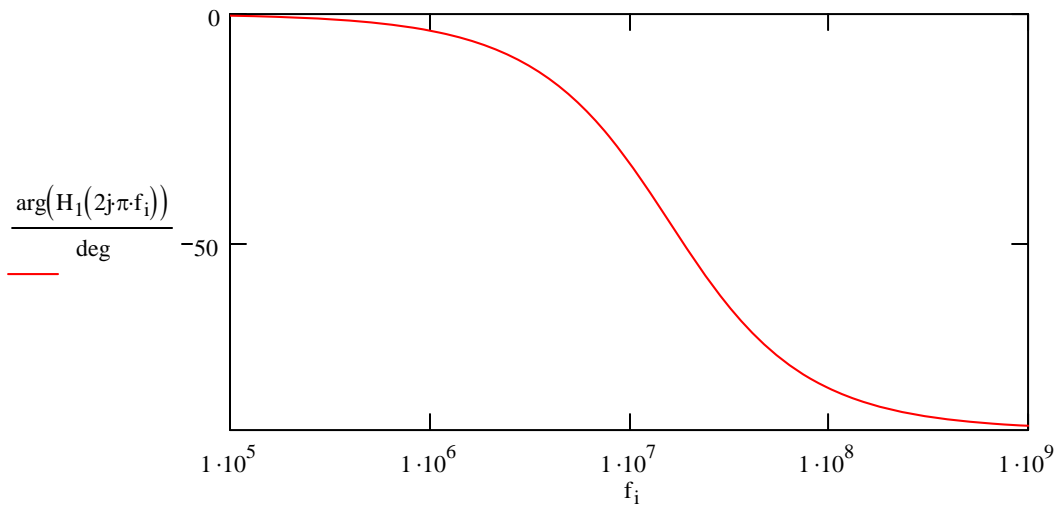

Logarithmic axis:

- more informative:
 - . 1Hz resolution at low frequencies, but not at 1GHz!
 - . many processes are logarithmic (cf. octave)
- for frequency - beware of label log f; usually the freq and not the log is specified
- amplitude
- phase scale is always linear

Interpretation

$$H_{1\text{abs}}(\omega) := \frac{1}{\sqrt{1 + (\omega \cdot \tau_1)^2}}$$

$$\text{phi}_1(\omega) := -\text{atan}(\omega \cdot \tau)$$


$$V_{\text{in}} := 1\text{V}$$

$$v_{\text{in}}(\omega, t) := V_{\text{in}} \cdot \cos(\omega \cdot t)$$

$$V_{\text{out}}(\omega) := V_{\text{in}} \cdot H_{1\text{abs}}(\omega)$$

$$v_{\text{out}}(\omega, t) := V_{\text{out}}(\omega) \cdot \cos(\omega \cdot t + \text{phi}_1(\omega))$$

$$\omega_1 := \frac{25}{\tau}$$

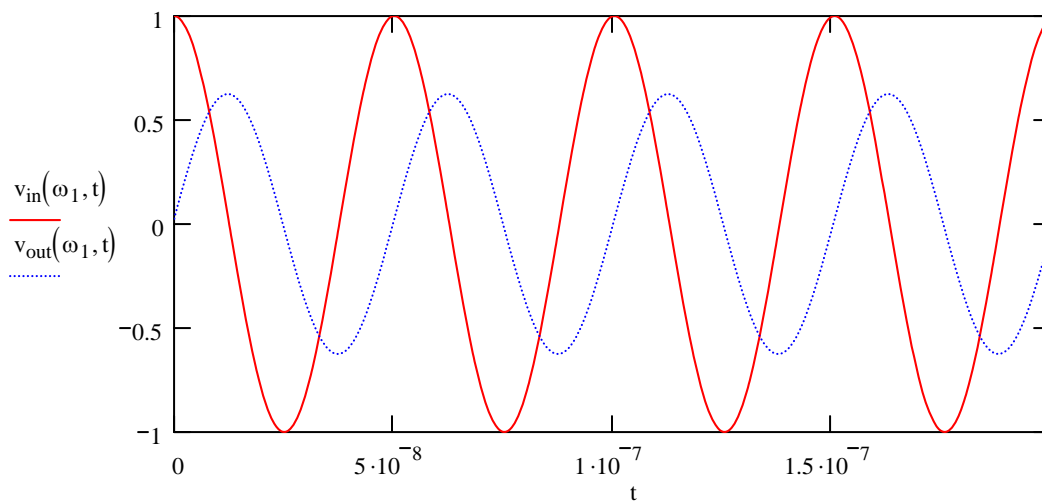

deci-Bel

- for power ratios $dB(r) := 10 \cdot \log(|r|)$

e.g. $P_{antenna} := 1\mu W$ $P_{ref} := 1mW$ $dB\left(\frac{P_{antenna}}{P_{ref}}\right) = -30 \text{ dB (dBm)}$

$$P_{antenna} = \frac{V_{antenna}^2}{R_{antenna}} \quad P_{ref} = \frac{V_{ref}^2}{R_{antenna}} \quad dB\left(\frac{P_{antenna}}{P_{ref}}\right) = dB\left(\frac{V_{antenna}^2}{V_{ref}^2}\right) = 20 \cdot \log\left(\frac{V_{antenna}}{V_{ref}}\right)$$



- for voltage ratios $dB(r) := 20 \cdot \log(|r|)$

e.g. $H_1(2j \cdot \pi \cdot 100MHz) = 0.025 - 0.155i$ $dB(H_1(2j \cdot \pi \cdot 100MHz)) = -16.072 \text{ dB}$

$dB(1) = 0$ $dB(10) = 20$ $dB\left(\frac{1}{10}\right) = -20$

$dB(2) = 6.021$ $dB(0.5) = -6.021$ $dB(20) = 26.021$

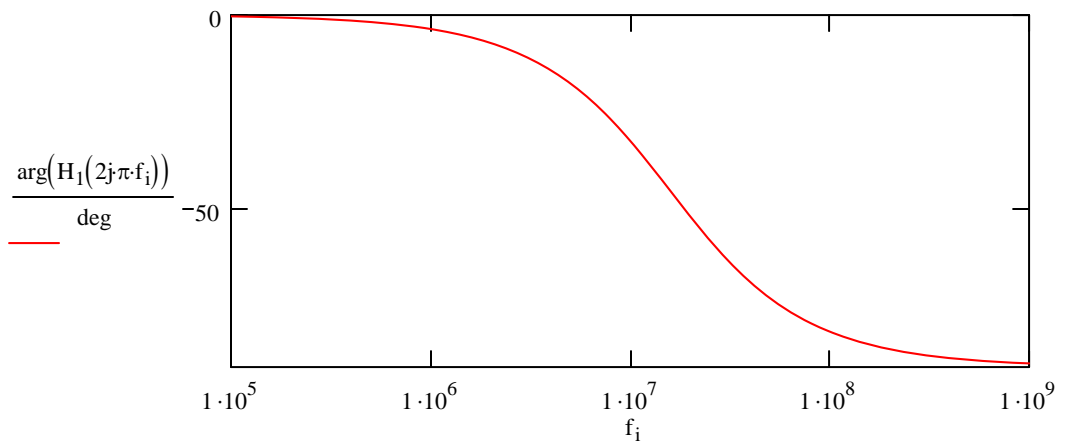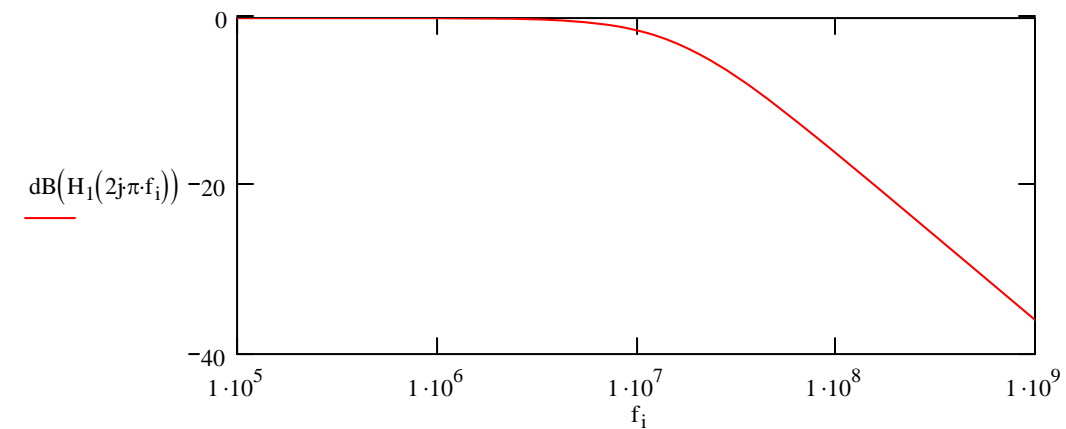$N := 100$ $i := 0..N - 1$ $f := \text{logrange}(100kHz, 1GHz, N)$



Construct Bode-plot (single pole) from equation. Pole. 3dB Bandwidth.

Filters LPF, HPF, BPF, BNF ideal, practical (approximate shapes)


Example: PWM DAC

$$V_{dac} = D_{dac} \cdot V_{ref} \quad D_{dac} = \frac{0..255}{256} \quad t_1 = D_{dac} \cdot T \quad (\text{time when } V_{out} = V_{ref})$$

worst case ripple for $t_1 = \frac{T}{2}$ (50% duty cycle) $V_{ref} := 1V$ $\omega_1 := 2 \cdot \pi \cdot 1MHz$

$$v_{out}(t) := \frac{V_{ref}}{2} + \frac{2 \cdot V_{ref}}{\pi} \cdot \sum_{n=0}^{20} \frac{\sin[(2 \cdot n + 1) \cdot \omega_1 \cdot t]}{2 \cdot n + 1}$$
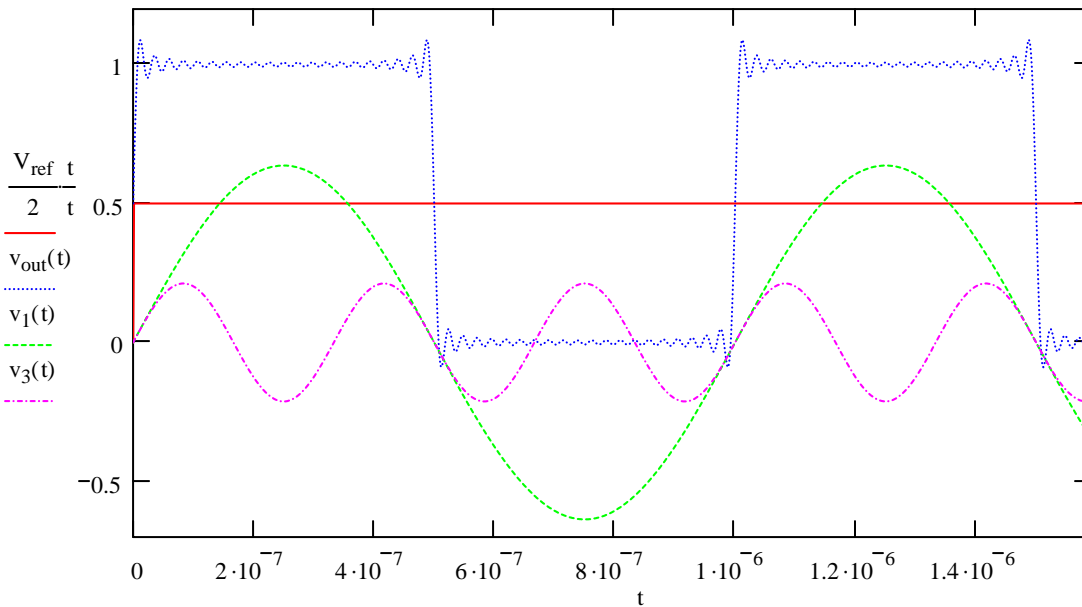
$$v_1(t) := \frac{2 \cdot V_{ref}}{\pi} \cdot \sin(\omega_1 \cdot t) \quad v_3(t) := \frac{2 \cdot V_{ref}}{\pi} \cdot \frac{\sin(3 \cdot \omega_1 \cdot t)}{3}$$



Goal: amplitude of ripple < r * v_ref $r := 10\%$

Ripple dominated by v_1 $A_1 := \frac{2 \cdot V_{ref}}{\pi}$ $\frac{A_1}{V_{ref}} = 0.637 < r$

Attenuation required $a := \frac{A_1}{V_{ref}} \cdot \frac{1}{r}$ $a = 6.366$ $dB(a) = 16.078$ dB

a) graphical solution (from Bode diagram, determine $\omega_p = 1/RC$ from ω_1 and a)

b) algebraic

$$|H(j \cdot \omega_1)| = \frac{1}{\sqrt{1 + (\omega_1 \cdot R \cdot C)^2}} = a \quad RC := \frac{\sqrt{a^2 - 1}}{\omega} \quad RC = 1.001 \mu s$$

$$C := 1nF \quad R := \frac{RC}{C} \quad R = 1.001 k\Omega$$


Pole of RC LPF: $\omega_p := \frac{1}{RC}$ $\frac{\omega_p}{2\pi} = 159.054 \text{ kHz}$ $f := \frac{\omega_p}{\omega_1}$ $f = 0.159$

uC output:
$$v_s(t) := \frac{V_{\text{ref}}}{2} + \text{Im} \left[\frac{2 \cdot V_{\text{ref}}}{\pi} \cdot \sum_{n=0}^{20} \left[\frac{e^{j \cdot (2n+1) \cdot \omega_1 t}}{2 \cdot n + 1} \right] \right]$$


RC LPF:
$$H_f(s, f) := \frac{1}{1 + \frac{s}{\omega_1 \cdot f}}$$

Filter output:
$$v_o(t, f) := \frac{V_{\text{ref}}}{2} + \text{Im} \left[\frac{2 \cdot V_{\text{ref}}}{\pi} \cdot \sum_{n=0}^{20} \left[H_f[j \cdot (2 \cdot n + 1) \cdot \omega_1, f] \cdot \frac{e^{j \cdot (2n+1) \cdot \omega_1 t}}{2 \cdot n + 1} \right] \right]$$

$$v_n(t, n) := \text{Im} \left[\frac{2V_{\text{ref}}}{\pi} \cdot \left[H_f[j \cdot (2 \cdot n + 1) \cdot \omega_1, f] \cdot \frac{e^{j \cdot (2n+1) \cdot \omega_1 t}}{2 \cdot n + 1} \right] \right]$$

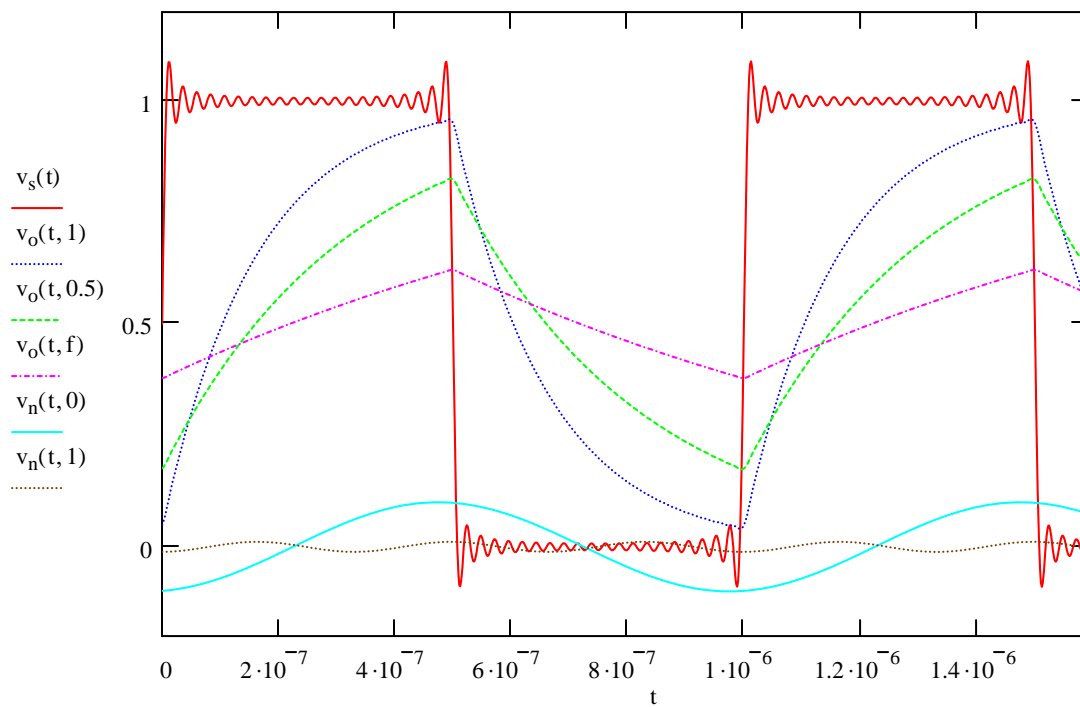

Lecture 29: Bode Plot

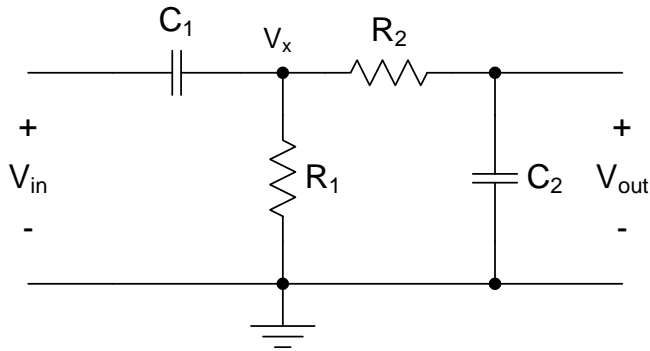

Given

$$(V_x - V_{in}) \cdot s \cdot C_1 + \frac{V_x}{R_1} + \frac{V_x - V_{out}}{R_2} = 0$$

$$\frac{V_{out} - V_x}{R_2} + V_{out} \cdot s \cdot C_2 = 0$$

$$\text{Find}(V_x, V_{out}) \rightarrow \left[\begin{array}{l} s \cdot C_1 \cdot R_1 \cdot \text{volt} \cdot \frac{(1 + s \cdot C_2 \cdot R_2)}{\left(s \cdot C_1 \cdot R_1 + s^2 \cdot C_1 \cdot R_1 \cdot R_2 \cdot C_2 + 1 + s \cdot C_2 \cdot R_2 + R_1 \cdot s \cdot C_2 \right)} \\ s \cdot C_1 \cdot R_1 \cdot \frac{\text{volt}}{\left(s \cdot C_1 \cdot R_1 + s^2 \cdot C_1 \cdot R_1 \cdot R_2 \cdot C_2 + 1 + s \cdot C_2 \cdot R_2 + R_1 \cdot s \cdot C_2 \right)} \end{array} \right]$$

e.g.

$f_1 := 100\text{Hz}$	$f_2 := 10\text{MHz}$	$\omega_{p1} := 2\pi \cdot f_1$	$\omega_{p2} := 2\pi \cdot f_2$
$R_1 := 100\text{k}\Omega$	$C_1 := \frac{1}{2 \cdot \pi \cdot f_1 \cdot R_1}$	$C_1 = 15.915 \text{ nF}$	
$R_2 := 1\text{k}\Omega$	$C_2 := \frac{1}{2 \cdot \pi \cdot f_2 \cdot R_2}$	$C_2 = 0.016 \text{ nF}$	

Given

$$1 + s \cdot (R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2) + s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2 = 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \cdot \omega_{p2}}$$

$$\text{Find}(\omega_{p1}, \omega_{p2}) = \left(\begin{array}{l} 99.899 + 2.583i \times 10^{-6} \\ 1.001 \times 10^7 \end{array} \right) \text{Hz} \cdot 2\pi$$

$$H(s) = \frac{s \cdot R_1 \cdot C_1}{\left(1 + \frac{s}{\omega_{p1}} \right) \cdot \left(1 + \frac{s}{\omega_{p2}} \right)} = \frac{s \cdot R_1 \cdot C_1}{1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \cdot \omega_{p2}}}$$



Pole splitting: $\omega_{p1} \ll \omega_{p2}$

$$H(s) := \frac{s \cdot R_1 \cdot C_1}{1 + s \cdot (R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2) + s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2} \quad H(s) := \frac{s \cdot R_1 \cdot C_1}{\left(1 + \frac{s}{\omega_{p1}} \right) \cdot \left(1 + \frac{s}{\omega_{p2}} \right)}$$

Bode Plot

$$N := 200 \quad i := 1..N \quad f := \text{logrange}\left(\frac{f_1}{100}, 100 \cdot f_2, N\right)$$

3dB bandwidth

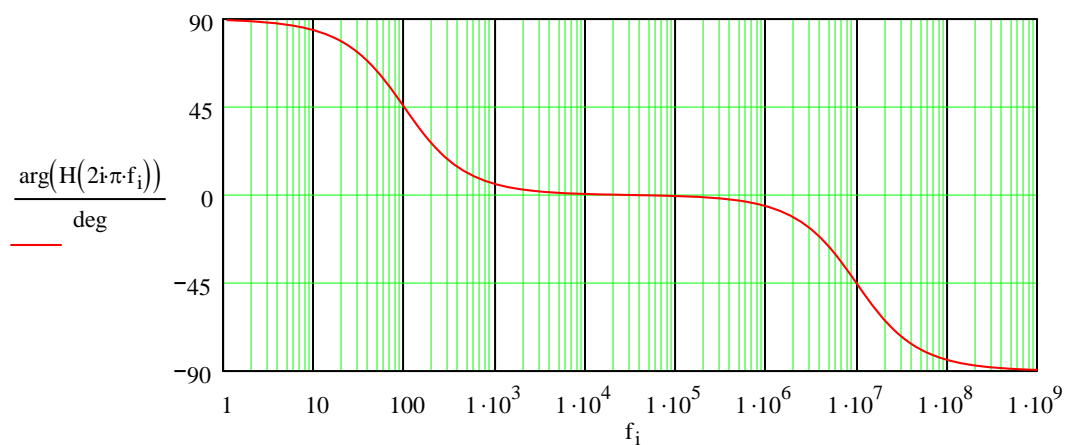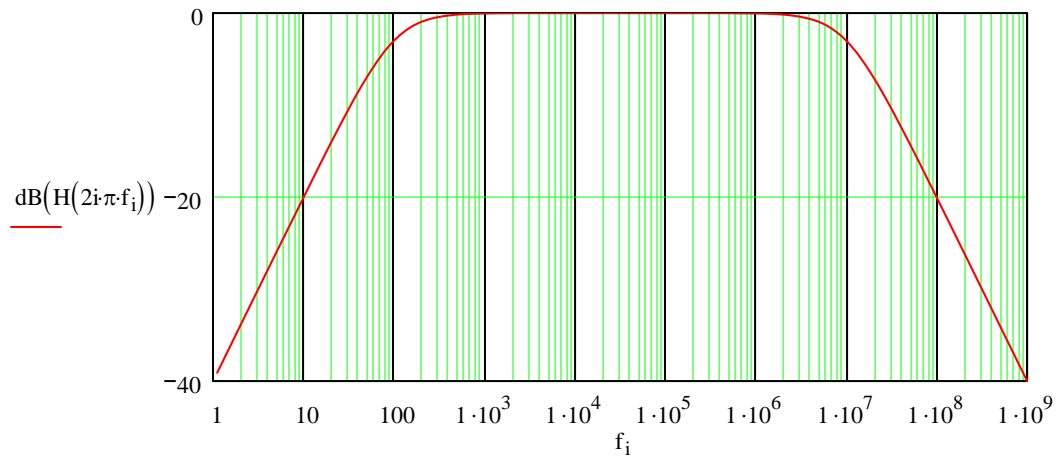

Bandpass characteristic:
 rejects low and high frequency, passes mid-band

Bode plots capture significant information about behavior of circuit.
 Need efficient way to construct and draw them.

Application: Phone Basspand from 300Hz ... 3kHz

Lecture 30: Constructing Bode Plots

Transfer functions: $H(s) = \frac{N(s)}{D(s)}$

Need roots of N (zeros of H) and roots of D (poles of H) for Bode Plot.
 Zeros and poles capture many important characteristics of systems
 (see other courses).

Then rewrite H(s) with poles and zeros explicitly:

1. Standard form

$$H(s) = K \cdot s^r \cdot \frac{\prod_m \left(1 - \frac{s}{z_m}\right)}{\prod_n \left(1 - \frac{s}{p_n}\right)}$$

z_m zeros of H(s)
 p_n poles of H(s)

2. Magnitude response

$$H_m(\omega) = \text{dB}(|H(j \cdot \omega)|) = 20 \cdot \log \left[\left| K \cdot s^r \cdot \frac{\prod_m \left(1 - \frac{s}{z_m}\right)}{\prod_n \left(1 - \frac{s}{p_n}\right)} \right| \right] \quad s = j \cdot \omega$$

$$H_m(\omega) = 20 \cdot \log(|K|)$$

$$\blacksquare + 20 \cdot r \cdot \log(\omega)$$

$$\blacksquare + 20 \cdot \sum_m \log \left(\left| 1 + j \cdot \frac{\omega}{z_m} \right| \right)$$

$$\blacksquare - 20 \cdot \sum_n \log \left(\left| 1 + j \cdot \frac{\omega}{z_n} \right| \right)$$

sum individual terms
 (thanks to log!)

3. Phase response

$$\phi(\omega) = 0 + (r \cdot 90\text{deg}) + \sum_m \phi \left(\left| 1 - j \cdot \frac{\omega}{z_m} \right| \right) - \sum_n \phi \left(\left| 1 - j \cdot \frac{\omega}{p_n} \right| \right)$$

sum individual terms

Example 1: R := 10kΩ C := 1pF

$$H(s) = \frac{1}{1 + s \cdot R \cdot C} = \frac{K}{1 - \frac{s}{p_1}} \quad K = 1 \quad p_1 := -\frac{1}{R \cdot C} \quad f_1 := \left| \frac{p_1}{2 \cdot \pi} \right| \quad f_1 = 1.592 \times 10^4 \text{ kHz}$$


Magnitude response: $H_m(\omega) := -20 \log \left(\left| 1 - j \cdot \frac{\omega}{p_1} \right| \right)$ $H_m(\omega) := -10 \cdot \log \left[1 + \left(\frac{\omega}{p_1} \right)^2 \right]$

for $\omega \ll p_1$: $H_{m_low}(\omega) := 0$

for $\omega \gg p_1$: $H_{m_high}(\omega) := -20 \log \left(\frac{\omega}{p_1} \right)$

at $\omega = p_1$: $H_m(p_1) = -3.01$

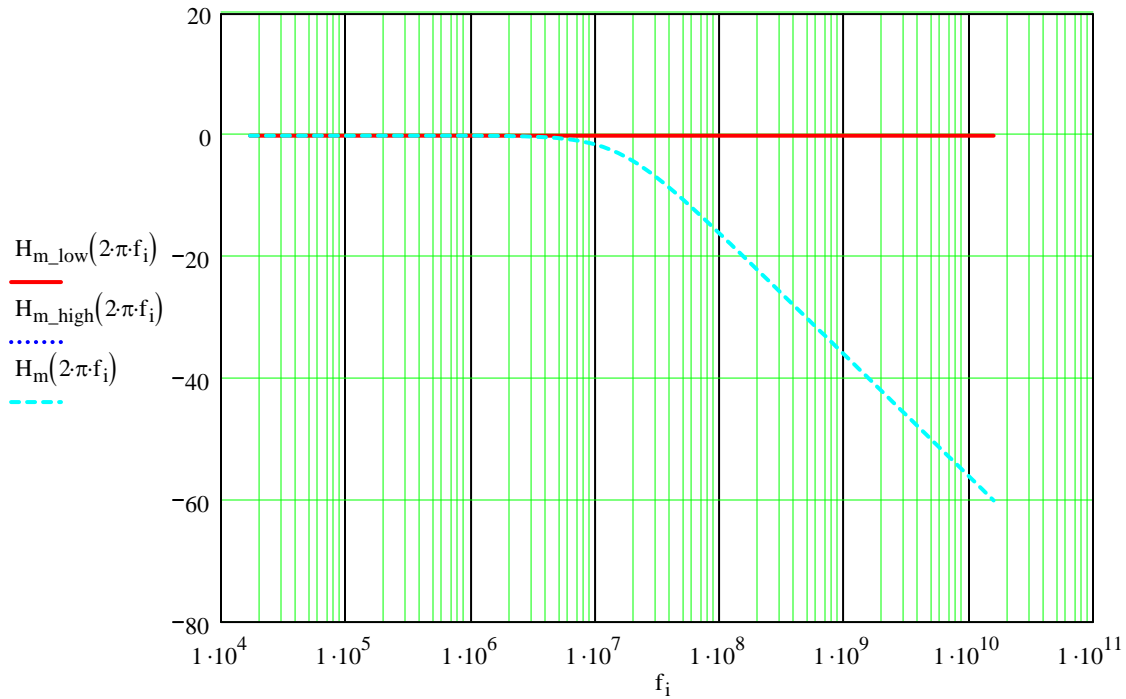N := 200 i := 1..N f := logrange $\left(\frac{f_1}{1000}, 1000 \cdot f_1, N \right)$




Straight line approximation: lines intersect at $p_1/2\pi$

Phase response:

$$\phi(\omega) := -\arg\left(1 - \frac{j \cdot \omega}{p_1}\right)$$
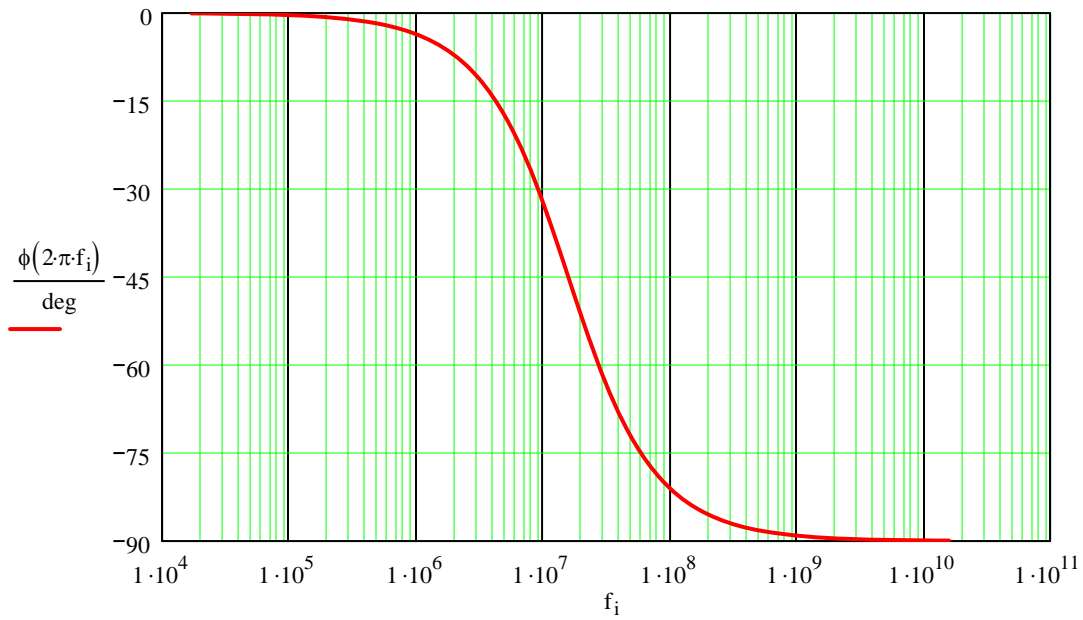
$$\phi(\omega) := \operatorname{atan}\left(\frac{\omega}{p_1}\right)$$



Straight line approximation: 90 deg over 2 decades, -45 deg @ f_1

Example 2:

$$H(s) := \frac{K}{s}$$


$$K := 2 \cdot \pi \cdot 100\text{Hz}$$

$$H_m(\omega) := \frac{K}{\omega}$$

$$N := 200$$

$$i := 1..N$$

$$f := \operatorname{logrange}(1\text{Hz}, 100\text{kHz}, N)$$

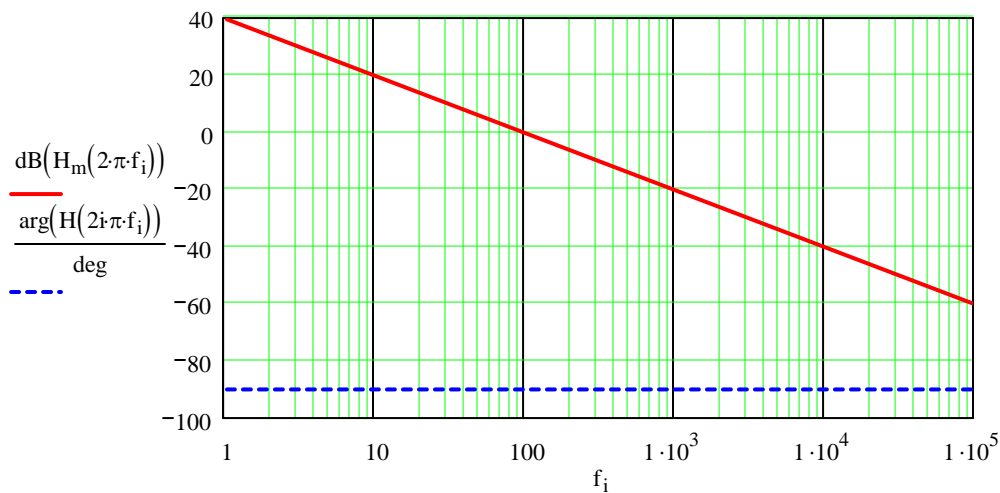

Example 3:

$$H(s) := \frac{s \cdot R_1 \cdot C_1}{1 + s \cdot (R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2) + s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2}$$

Find roots of denominator:


$$1 + s \cdot (R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2) + s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2 = 0$$

$$a := R_1 \cdot R_2 \cdot C_1 \cdot C_2 \quad a = 2.533 \times 10^{-11} \text{ s}^2$$

$$b := R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2 \quad b = 1.593 \times 10^{-3} \text{ s}$$

$$p_1 := \frac{-b + \sqrt{b^2 - 4 \cdot a}}{2 \cdot a} \quad f_1 := \left| \frac{p_1}{2 \cdot \pi} \right| \quad f_1 = 99.9 \text{ Hz}$$

$$p_2 := \frac{-b - \sqrt{b^2 - 4 \cdot a}}{2 \cdot a} \quad f_2 := \left| \frac{p_2}{2 \cdot \pi} \right| \quad f_2 = 10.01 \text{ MHz}$$

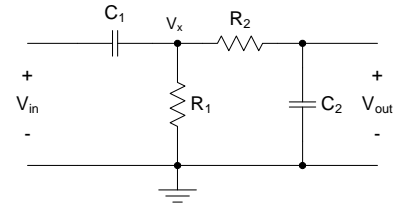

check roots:

$$D(s) := 1 + s \cdot (R_1 \cdot C_1 + R_1 \cdot C_2 + R_2 \cdot C_2) + s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2$$

$$D(p_1) = 1.694 \times 10^{-12} \quad \text{should be (nearly) zero}$$

$$D(p_2) = -2.91 \times 10^{-11}$$

standard form:



$$H(s) := R_1 \cdot C_1 \cdot s \cdot \frac{1}{\left(1 - \frac{s}{p_1}\right)} \cdot \frac{1}{\left(1 - \frac{s}{p_2}\right)} \quad r = 1$$

$$K = R_1 \cdot C_1$$

$$H_1(s) := s \cdot R_1 \cdot C_1 \quad H_2(s) := \frac{1}{\left(1 - \frac{s}{p_1}\right)} \quad H_3(s) := \frac{1}{\left(1 - \frac{s}{p_2}\right)}$$

$$\frac{1}{2 \cdot \pi \cdot R_1 \cdot C_1} = 100 \text{ Hz}$$

$$N := 3000 \quad i := 1..N \quad f := \text{logrange}\left(\frac{f_1}{100}, 900 \cdot f_2, N\right)$$

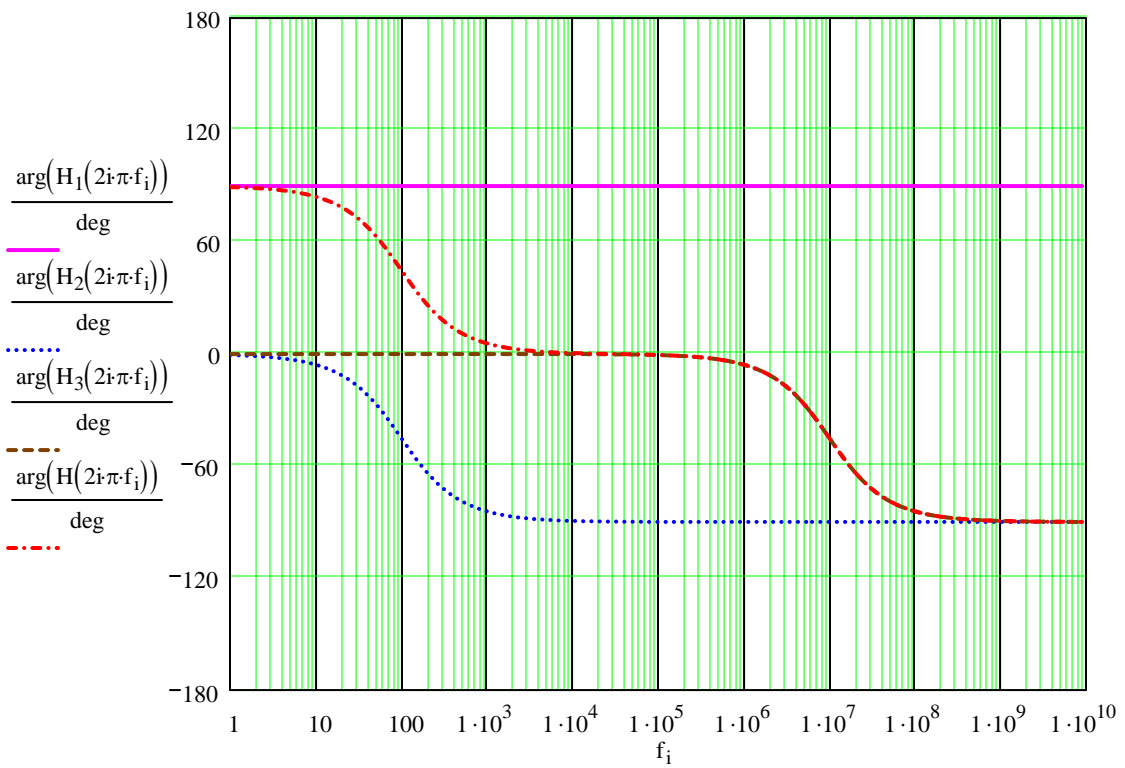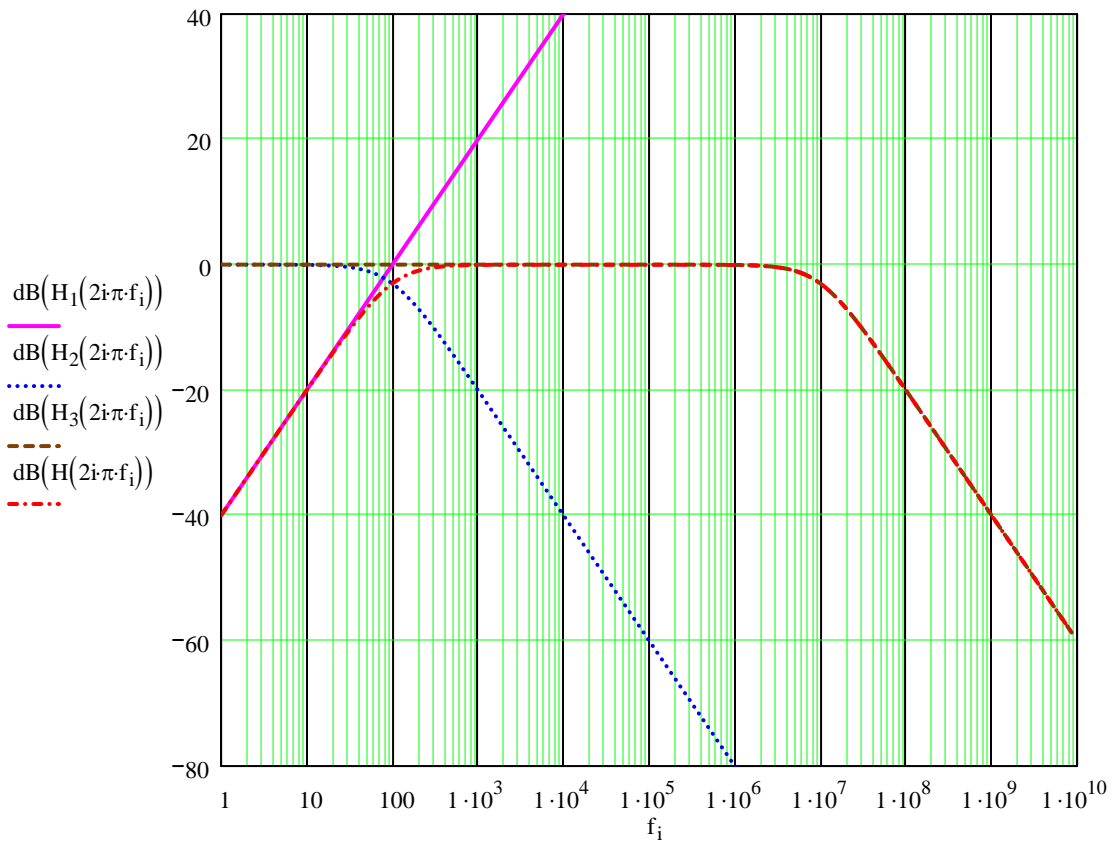


Lecture 31: Power

Resistive load

$$V_1 := 1V \quad f_1 := 60\text{Hz} \quad \omega_1 := 2\pi \cdot f_1 \quad R_1 := 1\Omega \quad T_1 := \frac{1}{f_1}$$
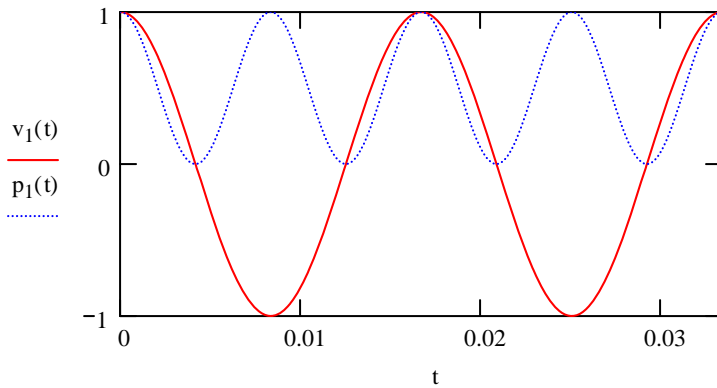
$$v_1(t) := V_1 \cdot \cos(\omega_1 \cdot t) \quad p_1(t) := \frac{v_1(t)^2}{R_1}$$




$$P_{\text{rms}} = \frac{1}{T_1} \cdot \int_0^{T_1} p_1(t) dt = \frac{1}{T_1} \cdot \int_0^{T_1} \frac{(v_1(t))^2}{R_1} dt = \frac{V_{\text{rms}}^2}{R_1}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \cdot \int_0^T (V_1 \cdot \cos(\omega \cdot t))^2 dt} = \frac{V_1}{\sqrt{2}} \quad V_{\text{rms}} := \frac{V_1}{\sqrt{2}} \quad P_{\text{rms}} := \frac{V_{\text{rms}}^2}{R_1}$$

Capacitive Load

$$P_{\text{rms}} = 0.5 \text{ W}$$
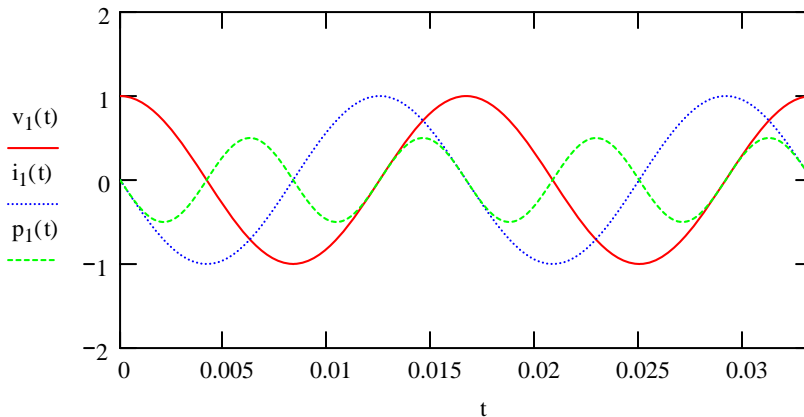
$$C_1 := \frac{\text{farad}}{\omega_1} \quad i_1(t) := C_1 \cdot \frac{d}{dt} v_1(t) \quad p_1(t) := v_1(t) \cdot i_1(t)$$



Power Analysis

$$V_1 := 1V \quad I_1 := 0.7A \quad \phi_1 := 70\text{deg}$$


Phase: $\phi_1 = \Delta\phi = \phi_v - \phi_i$

$$v_1(t) := V_1 \cdot \cos(\omega_1 \cdot t) \quad i_1(t) := I_1 \cdot \cos(\omega_1 \cdot t - \phi_1)$$

$$p_{1a}(t) := V_1 \cdot I_1 \cdot \cos(\omega_1 \cdot t - \phi_1) \cdot \cos(\omega_1 \cdot t)$$

after some work ...
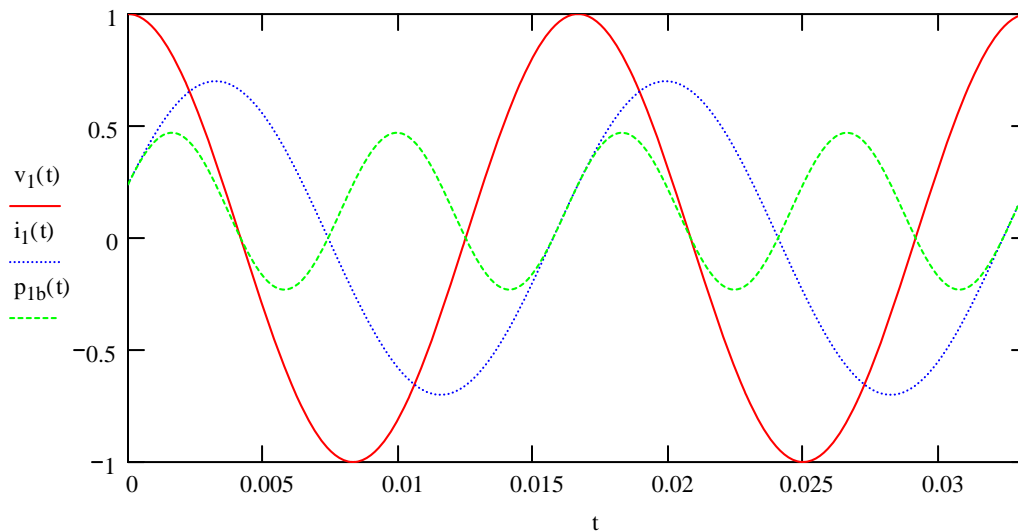
$$p_{1b}(t) := \frac{V_1 \cdot I_1}{2} \cdot [\cos(\phi_1) \cdot (1 + \cos(2 \cdot \omega_1 \cdot t)) + \sin(\phi_1) \cdot \sin(2\omega_1 \cdot t)]$$



Nomenclature

Average (real) power: $P_1 := \frac{V_1 \cdot I_1}{2} \cdot \cos(\phi_1)$ power factor $\text{pf} := \cos(\phi_1)$ $\text{pf} = 0.342$

Reactive power: $Q_1 := \frac{V_1 \cdot I_1}{2} \cdot \sin(\phi_1)$ $\text{rf} := \sin(\phi_1)$ $\text{rf} = 0.94$

$$\text{pf}^2 + \text{rf}^2 = 1$$

$$p_1(t) := P_1 \cdot (1 + \cos(2 \cdot \omega_1 \cdot t)) + Q_1 \cdot \sin(2 \cdot \omega_1 \cdot t)$$

a) Purely resistive circuits

$$\phi_1 := 0\text{deg} \quad P_1 := \frac{V_1 \cdot I_1}{2} \quad Q_1 = 0 \quad [\text{W}] \quad P_1 = 350\text{mW}$$

Actually dissipated in load (has a 2w1 ripple on top of average).

b) Purely reactive circuits

$$\phi_1 := 90\text{deg} \quad P_1 = 0 \quad Q_1 := \frac{V_1 \cdot I_1}{2} \quad [\text{VAR}] \quad Q_1 = 350\text{mW}$$

Average is zero. Only heats wires (which add a resistive component).

Complex Power

Efficient way to calculate P & Q.

Complex power: $S = P + j \cdot Q$ [VA]

Apparent power: $|S| = \sqrt{P^2 + Q^2}$ [VA]

Power handling capacity of distribution network (e.g. power cord).

... some math ...

$$S(s) = \frac{1}{2} \cdot V(s) \cdot \overline{I(s)} \quad (\text{complex conjugate of current})$$

Example 1: computer supply R // C

$$V_1 := 110V \cdot \sqrt{2} \quad V_1 = 155.563 \text{ V} \quad f_1 := 60\text{Hz} \quad \omega_1 := 2 \cdot \pi \cdot f_1$$

$$R_1 := 1\text{k}\Omega \quad C_1 := 20\mu\text{F} \quad Z_1(s) := \frac{R_1}{1 + s \cdot R_1 \cdot C_1} \quad \text{drops at high freq!!!}$$

$$V_1(s) := V_1 \quad I_1(s) := \frac{V_1(s)}{Z_1(s)} \quad \text{increases at high frequency!}$$

$$S_1(s) := \frac{1}{2} \cdot V_1(s) \cdot \overline{I_1(s)}$$

$$S_1(0\text{Hz}) = 12.1 \text{ W} \quad \text{only resistive part matters}$$

$$\text{VA} := \text{W} \quad \text{mVA} := \text{mW}$$

$$S_1(j \cdot \omega_1) = 12.1 - 91.232i \text{ VA}$$

$$\text{kVA} := \text{kW}$$

$$\text{VAR} := \text{W}$$

$$|S_1(j \cdot \omega_1)| = 92.031 \text{ VA} \quad (!!!)$$

$$\text{Re}(S_1(j \cdot \omega_1)) = 12.1 \text{ W} \quad \text{Im}(S_1(j \cdot \omega_1)) = -91.232 \text{ VAR}$$

$$|V_1(j \cdot \omega_1)| = 155.563 \text{ V} \quad |I_1(j \cdot \omega_1)| = 1.183 \text{ A} \quad (!!!)$$

$$\frac{V_1(0\text{Hz})}{R_1} = 155.563 \text{ mA}$$

Current dominated by reactive part

Example 2: loudspeaker with(out) series capacitor

$V_{dc} := 5V$ $V_1 := 2V$ $f_1 := 440Hz$ $\omega_1 := 2\pi \cdot f_1$

$L_1 := \frac{8\Omega}{\omega_1}$ $L_1 = 2.894 \text{ mH}$ $R_1 := 1\Omega$

$Z_1(s) := R_1 + s \cdot L_1$ $I_1(s) := \frac{V_1}{Z_1(s)}$ $S_1(s) := \frac{1}{2} \cdot V_1 \cdot \overline{I_1(s)}$

$S_1(0Hz) = 2 \text{ VA}$ just heats speaker! (nobody can hear DC)

$S_1(j \cdot \omega_1) = 30.769 + 246.154i \text{ mVA}$ audio power is much smaller (than heat)



with series capacitor: $C_1 := 5mF$

$Z_{1c}(s) := R_1 + s \cdot L_1 + \frac{1}{s \cdot C_1}$ $I_{1c}(s) := \frac{V_1}{Z_{1c}(s)}$ $S_{1c}(s) := \frac{1}{2} \cdot V_1 \cdot \overline{I_{1c}(s)}$

$S_{1c}(j \cdot 10^{-20} \cdot Hz) = 0 \text{ VA}$ no heat (DC term)

$S_{1c}(j \cdot \omega_1) = 31.325 + 248.33i \text{ mVA}$ same as w/o C1!

$N := 300$ $i := 1..N$ $f := \text{logrange}(10Hz, 1kHz, N)$

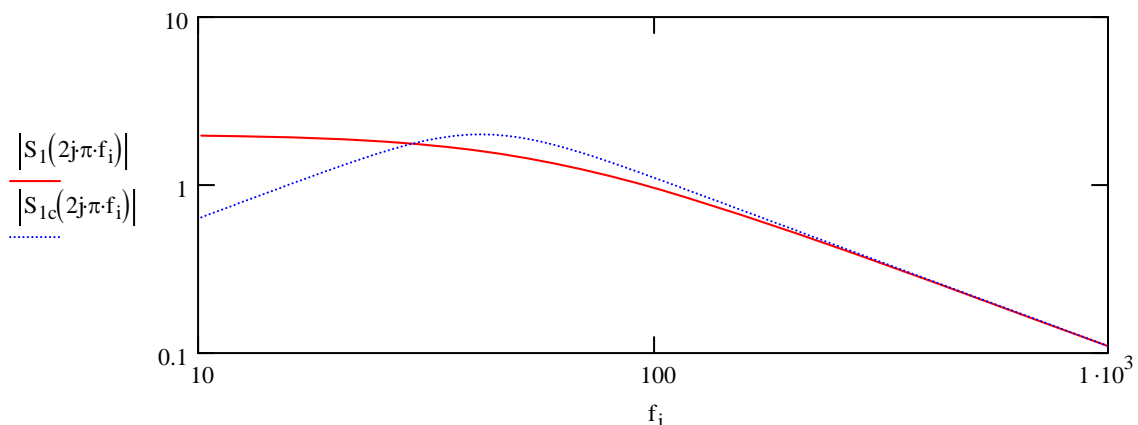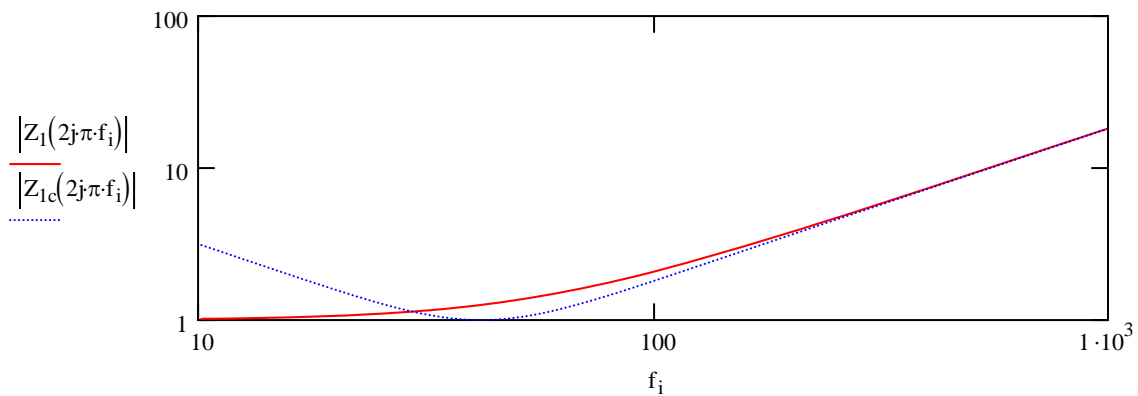

Example 3: correcting the power factor (zero reactive power)

$$V_1 := \sqrt{2} \cdot 110\text{V}$$

$$\omega_1 := 2\pi \cdot 60\text{Hz}$$

Inductive load

$$Z_L := 40\Omega + j \cdot 20\Omega$$

without correction:

$$S_a := \frac{V_1^2}{Z_L}$$

$$S_a = 484 + 242i \text{ VA}$$

$$I_a := \frac{V_1}{Z_L}$$

$$I_a = 3.111 - 1.556i \text{ A} \quad |I_a| = 3.479 \text{ A}$$

with correction:

$$Y_c := -\text{Im}\left(\frac{1}{Z_L}\right)$$

$$Z_c := \frac{1}{Y_c \cdot j} \quad Z_c = -100i\Omega \quad \text{capacitor!}$$

$$Z_{\text{tot}} := \frac{Z_L \cdot Z_c}{Z_L + Z_c}$$

$$Z_{\text{tot}} = 50\Omega$$

$$S_b := \frac{V_1^2}{Z_{\text{tot}}}$$

$$S_b = 484 \text{ VA}$$

Example 4:

voltage drop in inductive power supply wiring
(model current as sinusoid at fs)

Lecture 32: Finite Opamp Bandwidth

Model: $a(s) = \frac{\omega_b}{s}$ $|a(j \cdot \omega_b)| = 1$


$|a(0)| = \infty$

like ideal opamp

Note: can model finite gain and bw simultaneously

- more complicated math

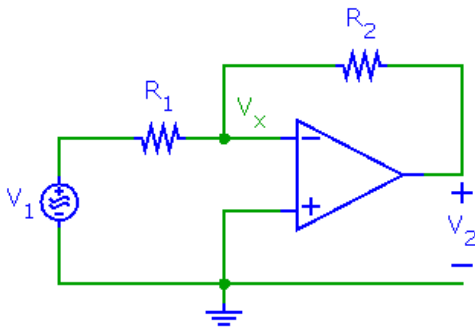- rather use superposition for small errors (system linear)



Given

$$\frac{V_x - V_1}{R_1} + \frac{V_x - V_2}{R_2} = 0$$

$$V_2 = -\frac{\omega_b}{s} \cdot V_x$$

Find(V_2, V_x) →


$$\left[\begin{array}{l} -\omega_b \cdot R_2 \cdot \frac{V_1}{(R_2 \cdot s + s \cdot R_1 + \omega_b \cdot R_1)} \\ R_2 \cdot V_1 \cdot \frac{s}{(R_2 \cdot s + s \cdot R_1 + \omega_b \cdot R_1)} \end{array} \right]$$

$$A(s) = \frac{V_2(s)}{V_1(s)} = \frac{-\omega_b \cdot R_2}{s \cdot (R_1 + R_2) + R_1 \cdot \omega_b}$$

$$A(s) = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{s}{\omega_b} \cdot \frac{R_1 + R_2}{R_1}} = -A_o \cdot \frac{1}{1 + \frac{s}{\omega_b} \cdot (1 + A_o)} = \frac{-A_o}{1 + \frac{s}{\omega_p}} \quad \omega_p = \frac{\omega_b}{1 + A_o}$$

$$A(s, A_o, f_p) := \frac{-A_o}{1 + s \cdot \frac{A_o + 1}{2 \cdot \pi \cdot f_p}} \quad \text{dB}(A(2j \cdot \pi \cdot 100\text{kHz}, 10, 1\text{MHz})) = 16.556 \quad \text{dB}$$

N := 300 i := 1..N f := logrange(10Hz, 10MHz, N)

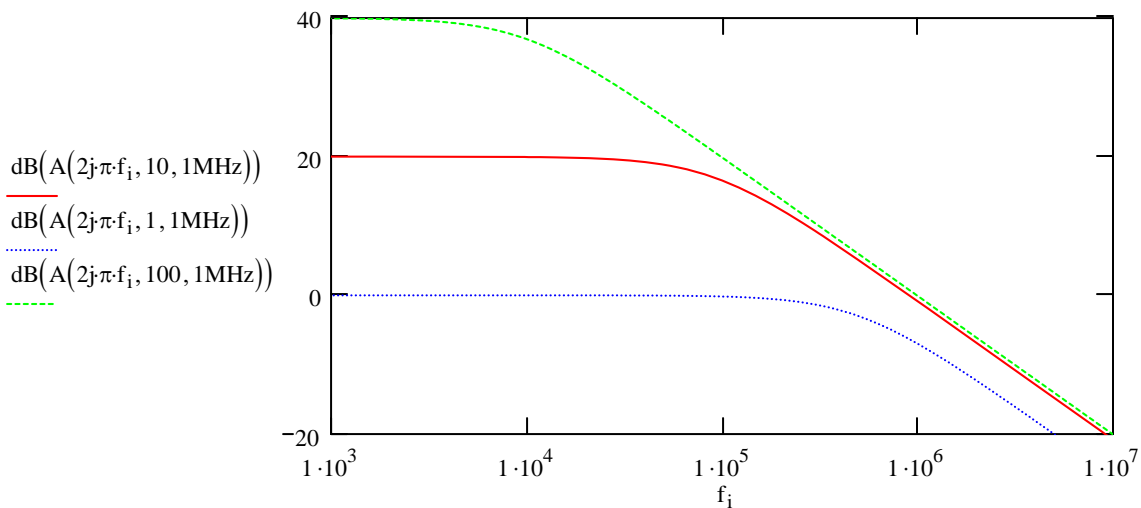


Lecture 33: Electronic Noise

Digital: finite # bits limits resolution

Analog: many errors, interference etc --> shield or use other methods to reduce
 ultimate: finite charge of electrons

Lecture 34: Filters

Example: Sampling

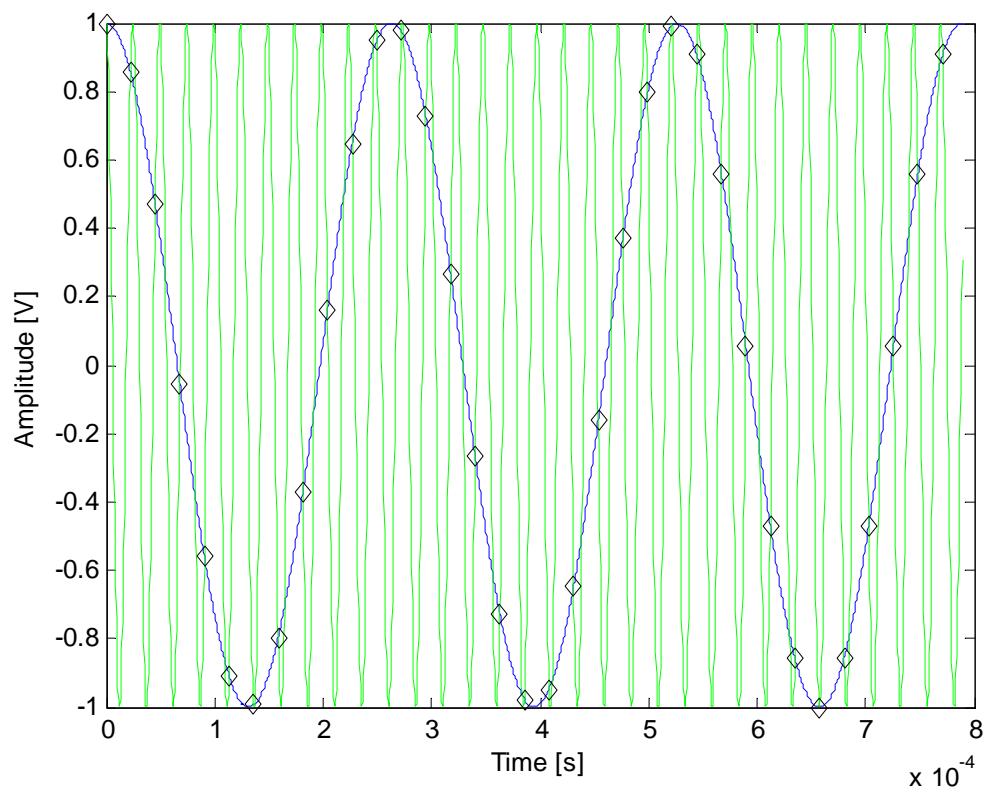

Show spectrum of input signal and alias.

Sampling theorem: frequencies $> f_s/2$ alias --> filter out!

$$f_s := 44.1\text{kHz}$$

$$B := 20\text{kHz}$$

$$\omega_p := 2 \cdot \pi \cdot B$$

3dB bandwidth


$$H(s) := \frac{1}{1 + \frac{s}{\omega_p}}$$

$$\left| H\left(2j \cdot \pi \cdot \frac{f_s}{2}\right) \right| = 0.672$$

$$\text{dB}\left(H\left(2j \cdot \pi \cdot \frac{f_s}{2}\right)\right) = -3.455$$

http://www.maxim-ic.com/appnotes.cfm/an_pk/1762 see also MAX 274/5

Sallen Key:

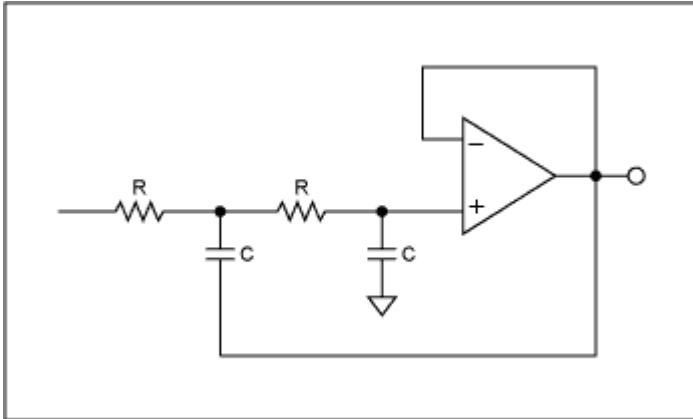

$$H(s) = \frac{1}{1 + s \cdot \tau + (s \cdot \tau)^2}$$

Given

$$1 + s \cdot \tau + (s \cdot \tau)^2 = 0$$

$$\text{Find}(s) \rightarrow \left[\frac{\left(\frac{-1}{2} + \frac{1}{2} \cdot i \cdot \sqrt{3} \right)}{\tau} \quad \frac{\left(\frac{-1}{2} - \frac{1}{2} \cdot i \cdot \sqrt{3} \right)}{\tau} \right]$$