

- Redo practice problem 14.3 in Alexander and Sadiku, 5h Edition for $H(\omega) = \frac{4(j\omega+3)}{j\omega(j\omega+20)}$.
- (D-95) Complete the table below. Do not use a pocket calculator!

Voltage ratio x	dB(x)
2	6 dB
4	
32	
10	
40	
100	
0.001	
1.6	
	120
	-26
	-3

3. (D-98)

- a) Draw the Bode Plot of $H(s) = \frac{V_2(s)}{V_1(s)}$ for $R_1 = 6.9 \text{ k}\Omega$ and $C_1 = 2.7 \text{ nF}$. What is the response at the following frequencies?

Frequency Magnitude [dB], Phase [deg]

1 Hz

1 kHz

1 MHz

- b) Repeat with the positions of the resistor and capacitor exchanged. What mathematical operation does this circuit perform?

Frequency Magnitude [dB], Phase [deg]

1 Hz

1 kHz

1 MHz


- c) Draw the Bode Plot of the circuits from parts (a) and (b) in series.

Frequency Magnitude [dB], Phase [deg]

1 Hz

1 kHz

1 MHz

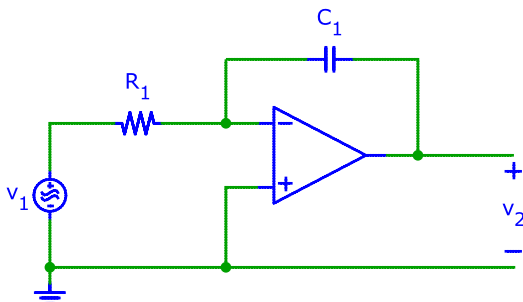


4. (D-99) Draw the Bode plot (piecewise linear approximation) from 1 Hz to 1 MHz for the following transfer function:

$$H(s) = \frac{s \left(1 + \frac{s}{z_1}\right)}{z_0 \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

with $s = j\omega$ and $z_0 = 2\pi \times 10$ Hz, $z_1 = 2\pi \times 10$ kHz, $p_1 = 2\pi \times 1$ kHz, $p_2 = 2\pi \times 100$ kHz. Label the axes!

5. (D-100) For the circuit below, calculate the magnitude $Z(s)$ between terminals (a,b). Use $R_1 = 6.3$ k Ω , $L_1 = 4.9$ nH, $C_1 = 9.8$ nF and $C_2 = 4.9$ pF.

Frequency	Magnitude [Ω], Phase [deg]
1 Hz	<input type="text"/>
1 kHz	<input type="text"/>
1 MHz	<input type="text"/>

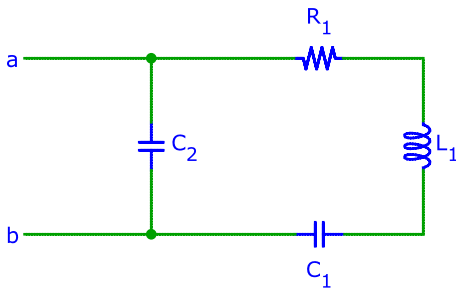

6. Figure 1 shows the frequency response of the voltage gain of some amplifier. For each of the following input voltages, find the steady-state output voltage.
- $v_{in}(t) = \sin(t + 1)$
 - $v_{in}(t) = 10$
 - $v_{in}(t) = 10 \cos^2(5t)$ Hint: Write $\cos^2(\cdot)$ as a sum of sinusoids.
7. Let \mathbb{I}_{in} and \mathbb{I}_{out} in Figure 2 be the phasors of the input current I_{in} and the output current I_{out} respectively.
- Find the current gain of the circuit.
The current gain $G(\omega)$ is the ratio of the phasors $\mathbb{I}_{out} / \mathbb{I}_{in}$.
 - With $R_1 = 1$ k Ω , $R_2 = 5$ k Ω , $L = 100$ mH, $C = 3$ μ F, sketch the magnitude frequency response of the current gain, i.e. plot $|G(\omega)|$ versus ω .
 - Is this a low/high/band pass filter?

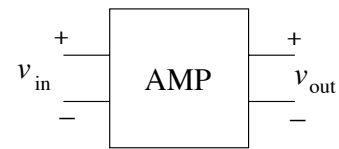
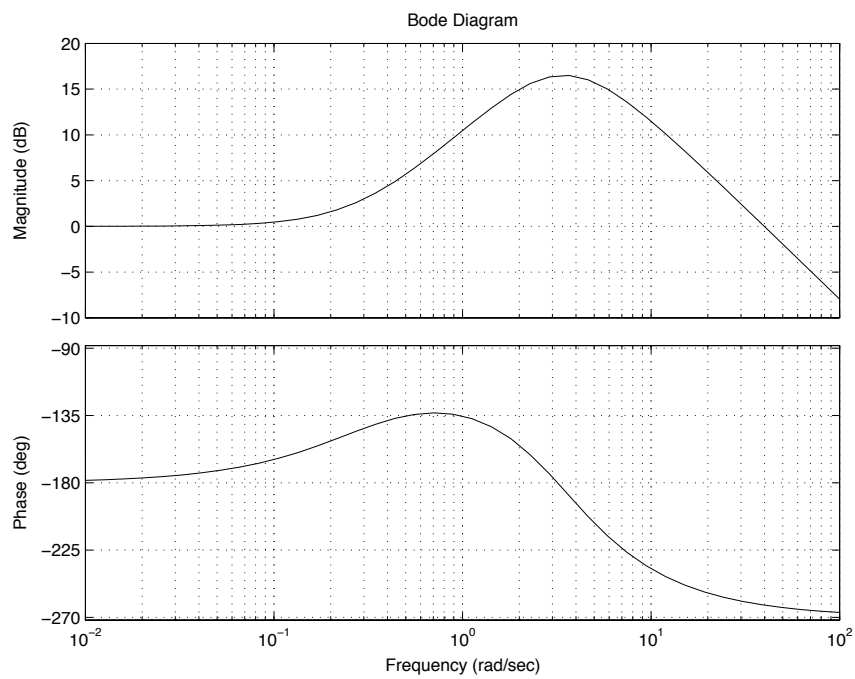


Figure 1 Bode Diagram

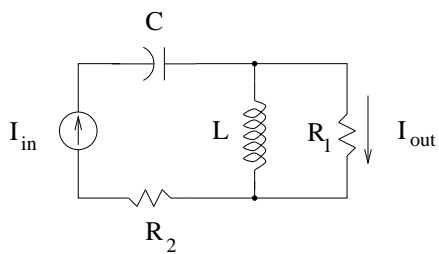


Figure 2 RLC Circuit.