

---


# Delay Modeling and Static Timing Verification

Prof. Kurt Keutzer  
Michael Orshansky  
EECS  
University of California  
Berkeley, CA

1


## RTL Synthesis Flow

---

 


2


# Design Process

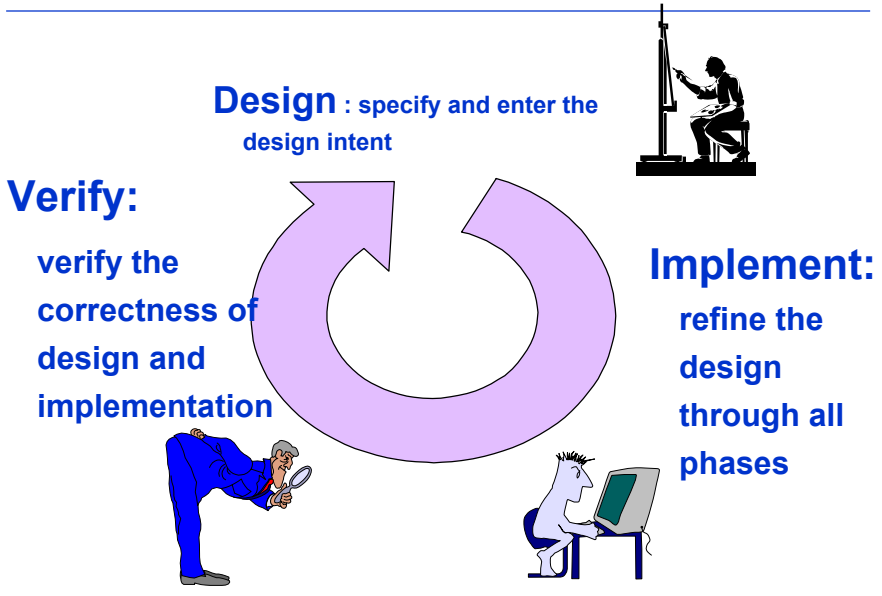

# Implementation Verification

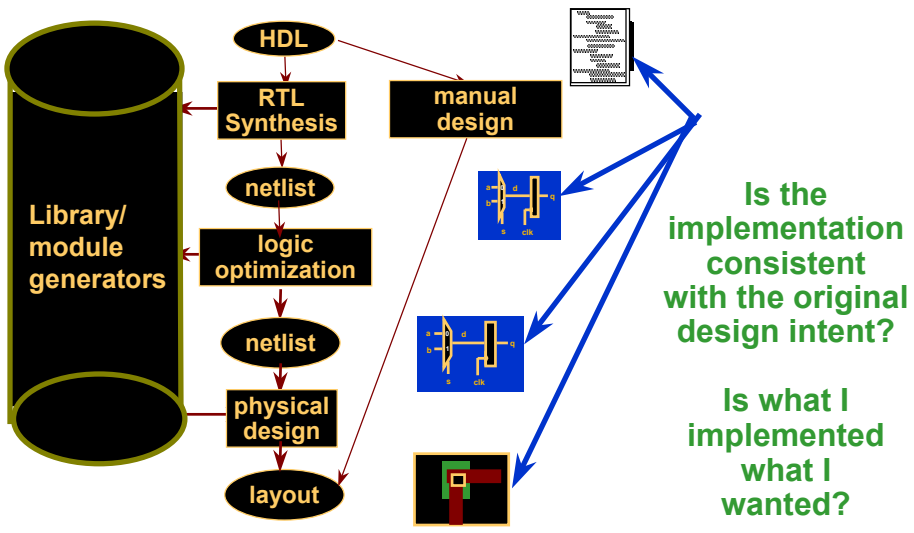

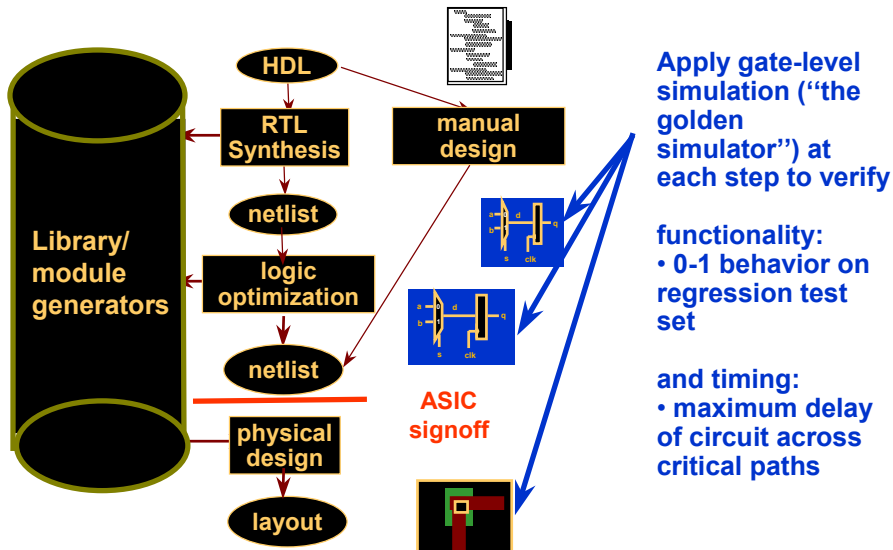
## Implementation verification for ASIC's



5

## Software Simulation

 

### Advantages of gate-level simulation


- verifies timing and functionality simultaneously
- approach well understood by designers

### Disadvantages of gate-level simulation

- computationally intensive - only 1 - 10 clock cycles of 100K gate design per 1 CPU second
- incomplete - results only as good as your vector set - easy to overlook incorrect timing/behavior

6

## Alternative - Static Sign-off

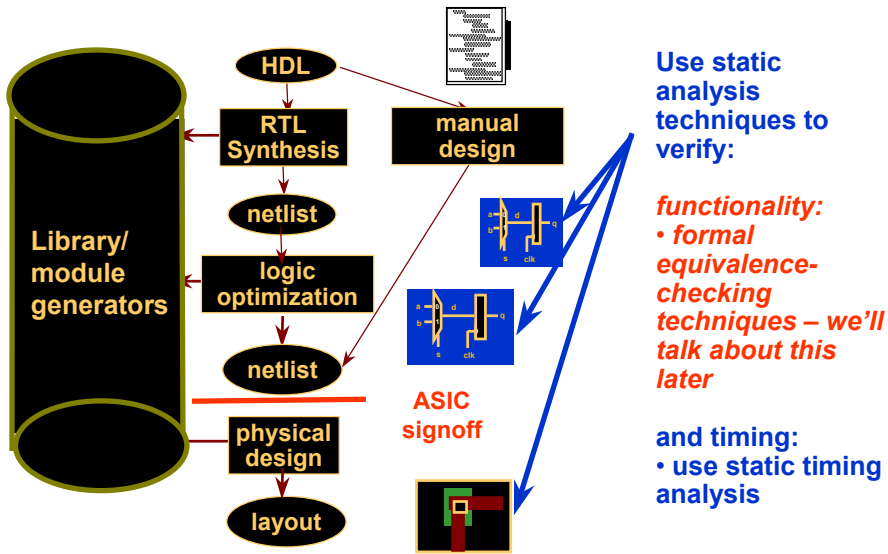

7

## Different Roles of Timing Analysis

Optimization is only relevant when there exists an objective function

For many circuits the primary objective function is speed

Timing verification


- Before fabrication, ensure a chip meets its timing requirements

Timing-driven optimization – give fast accurate timing information to guide tools as they evolve the chip

- Logic synthesis
- Placement
- Routing

8
 
## Approach of Static Timing Verification



- determine fastest permissible clock speed (e.g. 100MHz) by determining delay (including set-up and hold time) of longest path from register to register (e.g. 10ns.)

- largely eliminates need for gate-level simulation to verify the delay of the circuit

9


## Cycle Time - Critical Path Delay

Cycle time ( $T$ ) cannot be smaller than longest path delay ( $T_{max}$ )


Longest (critical) path delay is a function of:

Total gate, wire delays

- logic levels

 

$$T_{max} \leq T$$

 


10

 
## Cycle Time - Setup Time

For FFs to correctly latch data, it must be stable during:

- Setup time ( $T_{\text{setup}}$ ) before clock arrives


 
$$T_{\text{max}} + T_{\text{setup}} \leq T$$




11

 
## Cycle Time - Clock-skew

If clock network has unbalanced delay – clock skew

Cycle time is also a function of clock skew ( $T_{\text{skew}}$ )


 
$$T_{\text{max}} + T_{\text{setup}} + T_{\text{skew}} \leq T$$




12

 
## Cycle Time - Clock to Q

Cycle time is also a function of propagation delay of FF ( $T_{clk-to-Q}$ )

$T_{clk-to-Q}$ : time from arrival of clock signal till change at FF output)


 
$$T_{max} + T_{setup} + T_{skew} + T_{clk-to-Q} \leq T$$




13

## Min Path Delay - Hold Time


For FFs to correctly latch data, data must be stable during:

- Hold time ( $T_{hold}$ ) after clock arrives

 Determined by delay of shortest path in circuit ( $T_{min}$ ) and clock skew ( $T_{skew}$ )




$$T_{min} \geq T_{hold} + T_{skew}$$

 

14

## One more time

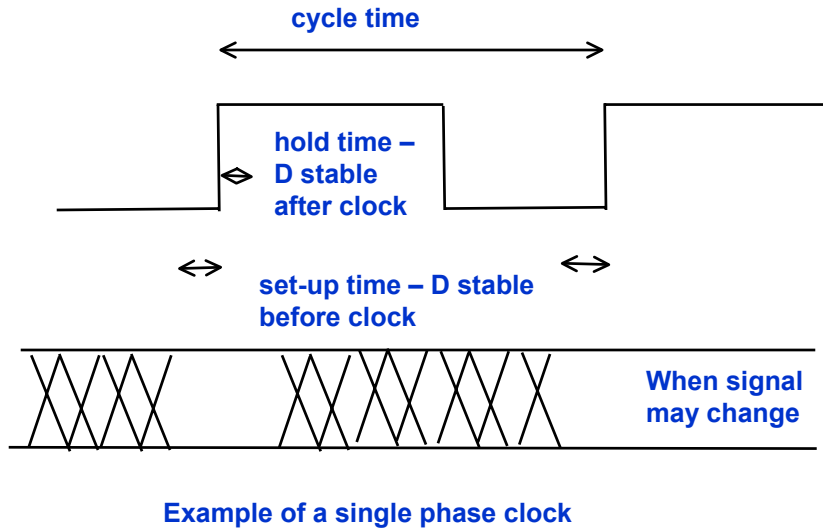

15

## Elements of Timing Verification

### To verify circuit timing need

- Accurate delay calculation
- Timing analysis engine

### Delay calculation

- Delay numbers for gates
- Delay numbers for wires

### Timing analysis engine


- Circuit path analysis
- Integrating clock network and FF/latches

16




## Delay Modeling and Delay Computation

### Single path delay computation

 

To simulate complex circuits, need accurate models of

- Gate delay
- Interconnect delay

 

Path delay = sum of 50% propagation delays

17

## Gate Delay Modeling Requirements

### Fast delay evaluation

- To enable full chip simulation
- Analytical models and look-up tables

### Conservative delay models


- STA determines longest path delay under *all possible* conditions

To enable fast tractable computation, have to give up on many modeling details

- Input pattern dependencies
- Complex dynamic behavior is captured through tables

18

## Gate Timing Characterization

 

“Extract” exact transistor characteristics from layout

- Transistor width, length, junction area and perimeter
- Local wire length and inter-wire distance

Compute all transistor and wire capacitances


19

## Cell Timing Characterization

Delay tables generated using a detailed transistor-level circuit simulator SPICE (differential-equations solver)

For a number of different input slews and load capacitances simulate the circuit of the cell

 - Propagation time (50% Vdd at input to 50% at output)
- Output slew (10% Vdd at output to 90% Vdd at output)



20

# Scope of Variation

Inter-Die Variation  
Intra-Die Variation

- As an ASIC vendor we must ensure that our chips work across this range of variation
- This is a *very restrictive condition and will be responsible for many conservative assumptions throughout timing analysis*


Lot-to-Lot




Wafer-to-Wafer (or within Lot)



Within Wafer

 


Intradie

 

# Device Worst Case Model

## Comparison Corner vs Real Data

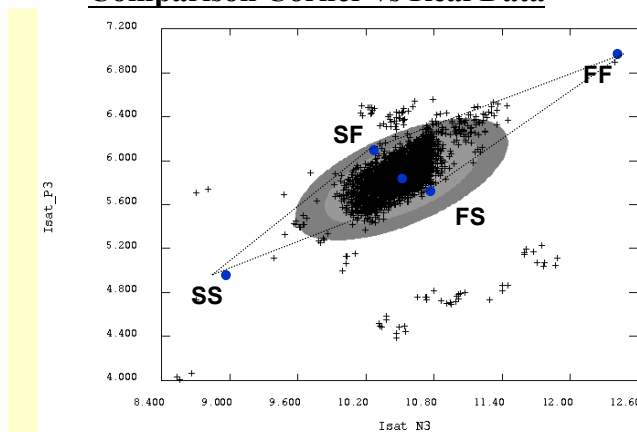

**FF: Fast NMOS & Fast PMOS**

**SF: Slow NMOS & Fast PMOS**

**3 corner Model: TT, SS, FF**

- Corners from SPICE document

**5 corner model: all**

**Must use worst case assumptions for Slow/set-up and Fast/hold analysis**


## How Is Gate Delay Computed? Non-linear effects reflected in tables

$$D_G = f(C_L, S_{in}) \text{ and } S_{out} = f(C_L, S_{in})$$

- Non-linear

Interpolate between table entries

 Interpolation error is usually below 10% of SPICE






23
   
## Conservatism of Gate Delay Modeling

True gate delay depends on input arrival time patterns

- STA will assume that only 1 input is switching
- Will use worst slope among several inputs



24

## Elements of Timing Verification

### To verify circuit timing need

- Accurate delay calculation
- Timing analysis engine

### Delay calculation


- Delay numbers for gates
- Delay numbers for wires

### Timing analysis engine

- Circuit path analysis
- Integrating clock network and FF/latches

25

## Interconnect Impact on Chip

 

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic

26

## Wire-Dominated Chips


Wiring requirements grow dramatically

Number of interconnect layers (6-8)

Interconnect effects

- Large RC and RLC delays
- Inter-wire coupling

 Interconnect becomes a dominant factor in limiting chip performance




TSMC Copper Process

27
 
## Wire Delay Modeling


Lumped RC model

- Simple:  $R$  – total resistance,  $C$  – total capacitance
- Pessimistic and inaccurate
- Spurious oscillations



Distributed RC model

 - Required for longer interconnect lines
- Exact solution requires solving “diffusion equation”
- No closed-form solution - approximations




28

## Wire Delay Modeling: Elmore Constant
 
### Elmore Delay Constant

- Dominant time constant for step input
- Works for branch-less distributed RC networks
- No floating caps, grounded resistors



$$\tau_N = \sum_{i=1}^N C_i \sum_{j=1}^i R_j = C_1 R_1 + C_2 (R_1 + R_2) + \dots + C_i (R_1 + R_2 + \dots + R_i)$$

29

## Wire Delay Modeling: AWE

AWE (Asymptotic Waveform Evaluation) is a  $q^{\text{th}}$ -order extension of the Elmore delay for general RLC circuits

### A generalized approach to linear RLC network response approximations

- Floating cap, grounded resistors, inductors
- Non-zero input transition times
- Initial conditions

### Produces a reduced $q^{\text{th}}$ order model of transient response

- Trade-off between model order (complexity) and model accuracy

The  $q$  unknown time- constants, or poles, of the circuit, are obtained through a moment matching technique (a Padé approximation)

A first-order AWE approximation reduces to RC tree methods

30


## Constructing RC Network

Resistance estimation (extraction) is easy

$$R_w = \rho \frac{L_w}{W \cdot T}$$


Capacitance estimation (extraction) is difficult

 - Analytically
- Using electromagnetic 3D simulators / extractors



31

## Capacitance: The Parallel Plate Model

 

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

$$S_{Cwire} = \frac{S}{S \cdot S_L} = \frac{1}{S_L}$$

32



## Interwire Capacitance

 


33

## Deriving Capacitance Information

### Wire delays determined by layout

- Wire-to-wire spacing
- Wire-length

 

**Problem: wire-to-wire capacitance and wire-length not known until placement and routing of all circuit components**

### Two modes of evaluating wire delay

- Post P&R: 2, 2&1/2 or 3-D interconnect parasitic extraction (e.g. capacitance and resistance), distributed RC delay models
- Synthesis: tabular data based on prior chips

34

## Wire Load Models


---

Synthesis must produce circuits that meet the designer's timing constraints

Wire delay based on gathered empirical data from past chips or estimated by typical (average) wirelength given by Rent's rule – see extra slides at the end of the lecture

- Function of FO
- Function of block size

Lumped RC model used

 

35

## Delay Modeling: Review

---

Components of cycle time

- Critical path delay, setup time, clock skew, clock-to-Q

Gate delay modeling

- Fast delay evaluation: look up tables
- Conservative models: worst-case assumptions
- Derived by running SPICE simulations of cells in the library

Wire delay modeling

More accurate

- Elmore model, RC tree, AWE
  - Statistical wirelength modeling
- Typically table look ups – or extracted values are used

36

## ***Library (.lib) Embodies Gate/Wire Delay Info***


---

Contains for each cell:

- Functional information:  $cell = a * b * c$
- Timing information: function of
  - input slew
  - intrinsic delay
  - output capacitancenon-linear models used in tabular approach
- Physical footprint (area)
- Power characteristics

Wire-load models - function of

- Block size
- Fan-out

 

37

## ***Elements of Timing Verification***

---

To verify circuit timing need

- Accurate delay calculation
- Timing analysis engine

Delay calculation


- Delay numbers for gates
- Delay numbers for wires

Timing analysis engine

- Considering clock network and FF/latches
- Circuit path analysis

38
 
## Elements of Static Timing Verification - 2




### Clocking issues

- Regimes: single-phase, two-phase, multi-phase
- overlapping, non-overlapping
- qualified clocks, clock skew

39
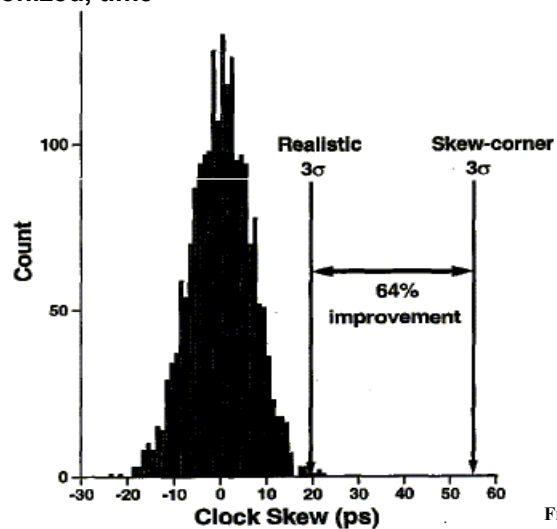
## Clock Skew


The clock may be delivered to each FF at a different, unsynchronized, time



From Dennis Sylvester

40
 
## Elements of Static Timing Verification - 3



### Delay calculation procedure

- Longest graphical path
- Longest true delay

### Method of calculation

- ``Batch mode''
- Incremental

41

## Typical Simplifications

### Clocking issues

- clocking regime treated as orthogonal issue

### Delay modeling

- gate - fixed pin-to-pin delays,
- interconnect - non-linear effects captured in tables
- Process-voltage-temperature - worst-case values used

### Delay calculation

- ``extract'' combinational logic from sequential circuit
- Choose for accuracy
  - Simple ``longest-path analysis''
  - Boolean analysis excluding false paths

42

## Elements of Timing Verification

---

To verify circuit timing need

- Accurate delay calculation
- Timing analysis engine

Delay calculation

- Delay numbers for gates
- Delay numbers for wires


Timing analysis engine

- Considering clock network and FF/latches
- **Circuit path analysis**
  - Topologically/graphically based
  - Including Boolean/functional pruning

43

## Approach -reduce to combinational

---

 


## Each combinational block

Arrival time in green

Interconnect delay in red

Gate delay in blue

 

What's the right mathematical object to use to represent this physical object?

45

## Problem formulation - 1

Use a labeled directed graph


$G = \langle V, E \rangle$

Vertices represent gates, primary inputs and primary outputs

Edges represent wires

Labels represent delays


Now what do we do with this?

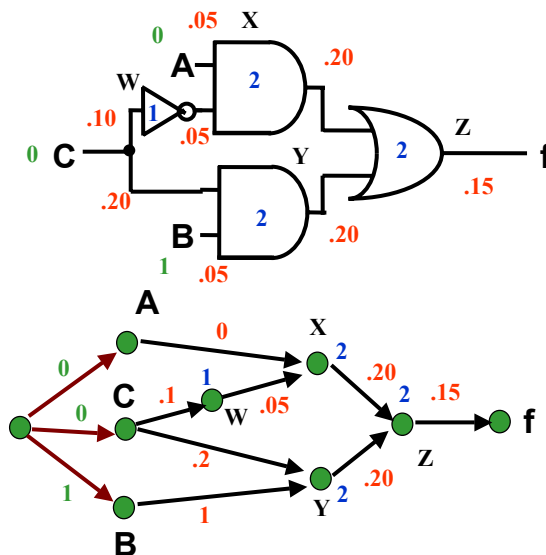

46
 
## Problem formulation - Arrival Time

Arrival time  $A(v)$  for a node  $v$  is time when signal arrives at node  $v$



$$A(v) = \max_{u \in FI(v)} (A(u) + d_{u \rightarrow v})$$

where  $d_{v \rightarrow u}$  is delay from  $v$  to  $u$ ,  $FI(u) = \{X, Y\}$ , and  $v = \{Z\}$ .


47

## Problem formulation - 2

Use a labeled directed graph

$G = \langle V, E \rangle$

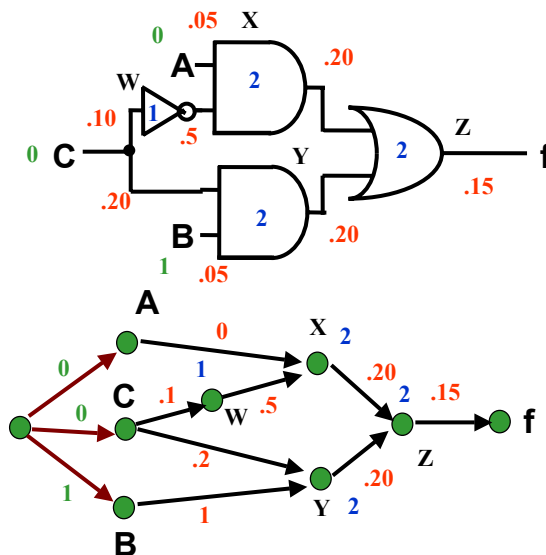
Enumerate all paths  
- choose the longest?



48



## Problem formulation - 3

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

49

## Algorithm Execution

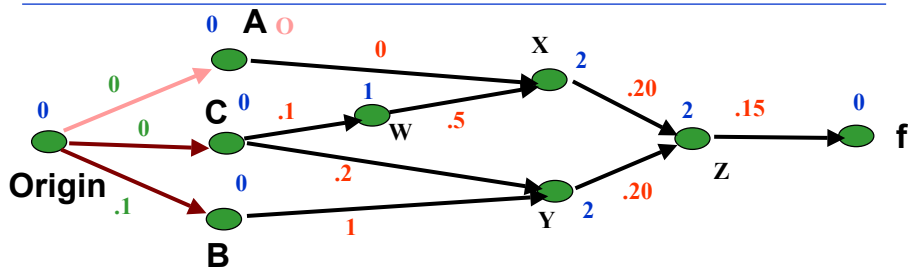

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

50

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

51

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

52

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

53

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

54

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

55

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

56

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

57

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

58

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

59

## Algorithm Execution

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay* is set of labels, *Origin* is the super-source of the DAG)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }


Longest path( $G$ )

  Forward\_prop(Origin)

}

60

## Critical Path (sub-graph)

 

Compute the longest path in a graph  $G = \langle V, E, \text{delay}, \text{Origin} \rangle$  (*delay is set of labels, Origin is the super-source of the DAG*)

Forward-prop( $W$ ) {

  for each vertex  $v$  in  $W$

    for each edge  $\langle v, w \rangle$  from  $v$

$\text{Final-delay}(w) = \max(\text{Final-delay}(w), \text{delay}(v) + \text{delay}(w) + \text{delay}(\langle v, w \rangle))$

      if all incoming edges of  $w$  have been traversed

        add  $w$  to  $W$

  }

Longest path( $G$ )

  Forward\_prop(Origin)

}

61


## Timing for Optimization: Extra Requirements

Longest-path algorithm computes arrival times at each node

If we have timing constraints, need to propagate slack to each node

- A measure of how much timing margin exists at each node
- Can optimize a particular branch

 
Can trade slack for power, area, robustness



62
 
## Required Time

Required time  $R(v)$  is the time before which a signal must arrive to avoid a timing violation



Required time is user defined at output:

$$R(v) = T - T_{\text{setup}}$$


Then recursively

$$R(v) = \min_{u \in FO(v)} (R(u) - d_{v \rightarrow u})$$

where  $FO(v) = \{Y, Z\}$  and  $v = \{X\}$

63

## Required Time Propagation: Example

 

Assume required time at output  $R(f) = 5.80$

Propagate required times backwards

64



## Timing Slack

From arrival and required time can compute slack. For each node  $v$ :

$$S(v) = R(v) - A(v)$$

Slack reflects criticality of a node

Positive slack

- Node is not on critical path. Timing constraints met.

Zero slack

- Node is on critical path. Timing constraints are barely met.


Negative slack

- There is a timing violation

Slack distribution is key for timing optimization!

65

## Timing Slack Computation: Example

 

Compute slack at each node

$$S(v) = R(v) - A(v)$$

66

## Timing Slack Properties

R. Nair et al, "Generation of Performance Constraints for Layout", TCAD 1989.

Path through a timing graph:  $\rho = \langle v_1, v_2, \dots, v_k \rangle$

Path slack:  $S(\rho) = R(v_k) - A(v_1) - \sum_{i=1}^{k-1} d_{v_i \rightarrow v_{i+1}}$

Path slack reflects slack at output assuming no other path in circuit is active


**Lemma 1:** For any path  $\rho = \langle v_1, v_2, \dots, v_k \rangle$  through circuit,  $S(v_i) \leq S(\rho)$ , for  $1 \leq i \leq k$

**Lemma 2:** For each cell  $v \in V$  there is some path  $\rho_v$  such that  $S(v) = S(\rho_v)$

By increasing delay on only one cell in the path, can set path slack to zero  $\rightarrow$  other cells also have zero slack.

67
 
## Approach of Static Timing Verification



- computing longest path delay
  - full path enumeration - potentially exponential
  - longest path algorithm on DAG (Kirkpatrick 1966, IBM JRD) ( $O(v+e)$  or  $O(g+p)$ )
- Currently in successful application on even the largest (>10M gate) circuits
- has two challenges:
  - asynchronous sub-circuits - limited gate-level simulation
  - false paths - ubiquitous and problematic

68

## Elements of Timing Verification

To verify circuit timing need

- Accurate delay calculation
- Timing analysis engine

Delay calculation

- Delay numbers for gates
- Delay numbers for wires

Timing analysis engine


- Considering clock network and FF/latches
- Circuit path analysis
  - Topologically/graphically based
  - Including Boolean/functional pruning

69

## Interesting Example: Carry Bypass Adder

$p_i$ : carry propagate from state  $i$


$P_i$ :  $a_i$  XOR  $b_i$

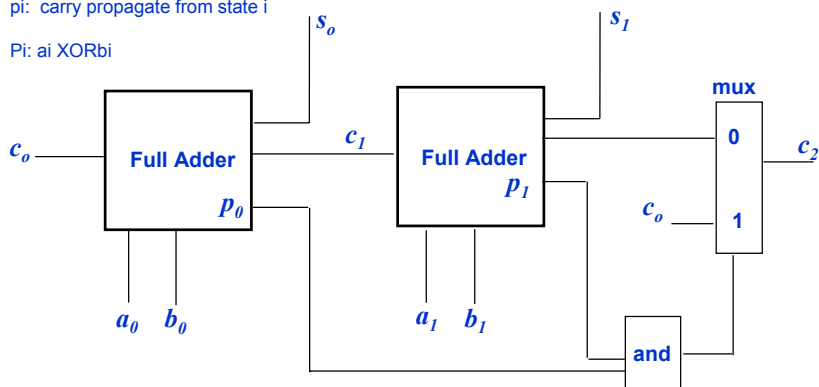

Lehman, Birla - IRETrans. Electron. Comput. , 1961  
V. Oklobdzija - JrnI. of VLSI Signal Processing, 1991

70

## Inside Carry Bypass Adder - 1

 


Longest graphical/topological path runs along carry chain from stage to stage

Longest path analysis would identify red path as critical

71

## Inside Carry Bypass Adder - 2

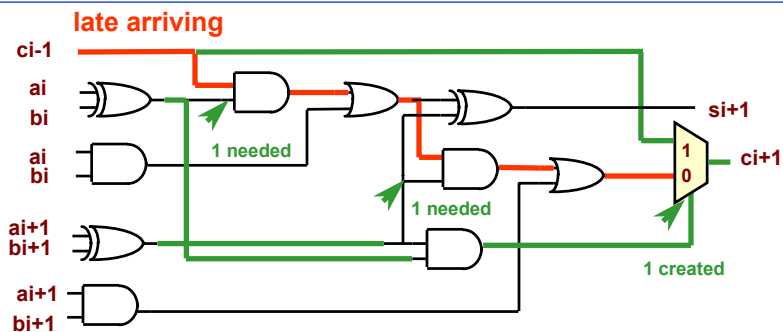

To sensitize red path we need:  $a_i \oplus b_i \ \&\& \ a_{i+1} \oplus b_{i+1}$

But: red path is false because when this condition is true MUX selects "1" input, i.e. directly from  $c_{i-1}$

Instead shorter green paths are sensitized and red path is not the critical path of the circuit

False paths first observed by V. Hrapcenko (Soviet Math. Dokl. 1978 )

72

## ***Capturing Functional Behavior in Analysis***

---

**Failure to remove false paths leads to conservative delay estimation**

**Looking for a path delay calculation approach that :**

- Is conservative
- Is not (overly) pessimistic
- Incorporates functional (Boolean) behavior
  - Eliminates false paths from analysis

**Two approaches to false path elimination**

- User-specified path exceptions (still mainstream)
- Automatic false-path detection

73

## ***False Path Detection***

---

**Sensitization criterion: a condition under which a signal transition at gate input will propagate to the gate output**

**Two-vector (transition mode) condition**

- More complex: two-vector condition with ( $2^n * 2^n$ ) vs. single vector condition ( $2^n$  space)
- Does not satisfy monotone speedup property
  - Path delay increased when gate delay decreases

**One-vector (floating mode) condition**

- Previous node value is (conservatively) indeterminate

74

## Chen-Du Path Sensitization Condition

---

Path from a gate input to the gate output is true iff the input gives

1. The earliest controlling value
2. The latest non-controlling value if all inputs are non-controlling



### Functional timing analysis

- Test each path for falsity
- Implicit path delay sensitization (PODEM)

75

## Enhancements of STA – project ideas

---

Incremental timing

Incorporation of deep sub-micron effects - crosstalk

Incorporation of physical variation → timing variation – statistical timing

76

## ***Current Status of Static Timing Verification***

---

Static timing verification is now the principal method for verifying timing in the majority of digital circuits

- ASICs:
  - Gate-level models from Semiconductor vendors
  - Driven by fast interpolation from tables
  - Estimated (wire-load model) or back-annotated capacitances
- Custom (e.g. Intel microprocessor)/COT (e.g. nVidia, ATI graphics chips)
  - Mixture of above and transistor-level static-timing verification
  - Transistor level based on extracted device and wiring attributes
  - Simulation of each transistor network builds accurate model

77

## ***Extras***

---

Rent's rule

RC Models


78

## Statistical Wire Length Estimation

Before P&R, need to predict wire length for each net

Can predict average (typical) wirelength based on empirical statistical regularities

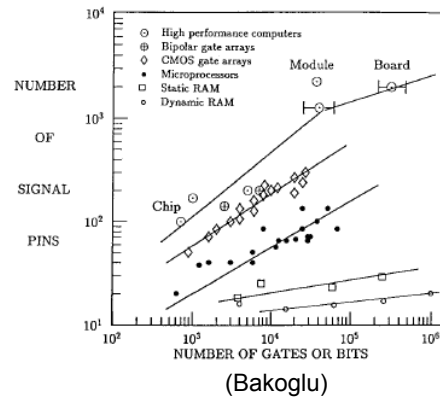Early on data showed that there exist strong correlation between number of IO terminals and number of gates in the block



79

## Rent's Rule

In 1960, E.F.Rent showed that

$$N_p = K(N_g)^\beta$$

where  $N_p$  = no. of external signal connections on a block,  $N_g$  = no. of logic gates in a block,  $K$  accounts for # of pins per gate, and  $\beta$  is Rent's constant – is a measure of many of the gates in a circuit block need to communicate with the outside world.

Rent's Rule is very circuit-fabric (architecture) specific

| Chip Type      | Rent's constant | Proportionality Constant K |
|----------------|-----------------|----------------------------|
| Static Memory  | 0.12            | 6                          |
| Microprocessor | 0.45            | 0.82                       |
| Gate Array     | 0.5             | 1.9                        |

Typical values of Rent's Coefficient (Bakoglu)

80



## Statistical Wirelength Estimation


Estimate average wiring length for point-to-point nets by applying Rent's rule recursively:

- Partition the chip into hierarchical divisions
- Estimate the connections between partitions by Rent's Rule

$$L_{avg} = f(N_g, \beta)$$

Wire length also depends on fan out of the net

 
$$L_{avg}(FO) = L_{avg}(1 + 0.4(FO - 1))$$



81
 
## Wire Delay Modeling: RC Trees

For RC trees (branching networks), delay can be estimated using Rubinstein-Penfield Theorem



If a single dominant time-constant exists, then

$$\tau_i \propto \sum_{k=1}^N C_k R_{i,k}$$


where  $R_{i,k} = \sum R_j \Rightarrow (R_j \in [\text{path}(i \rightarrow s) \cap \text{path}(k \rightarrow s)])$

E.g.  $\tau_i = C_1 R_1 + C_2 R_1 + C_3 (R_1 + R_3) + C_4 (R_1 + R_3) + C_i (R_1 + R_3 + R_i)$

82
 
## Wire Delay Modeling: RC Trees

The theorem also establishes precise bounds on voltage waveforms



Same limitations as for Elmore constant

- RC- tree topologies (not applicable with inter-nodal capacitances)
- Instantaneous input transition times