

Manufacture Testing of Digital Circuits

Prof. K-T Cheng

UC Santa Barbara

Prof. Srinivas Devadas

MIT

Prof. Kurt Keutzer & Sanjit Seshia

Mukul Prasad

University of California

Berkeley, CA

1


Design Process

Design : specify and enter
the design intent



Verify:

 verify the
correctness of
design and
implementation




Implement:

refine the
design
through all
phases




2

Design Verification

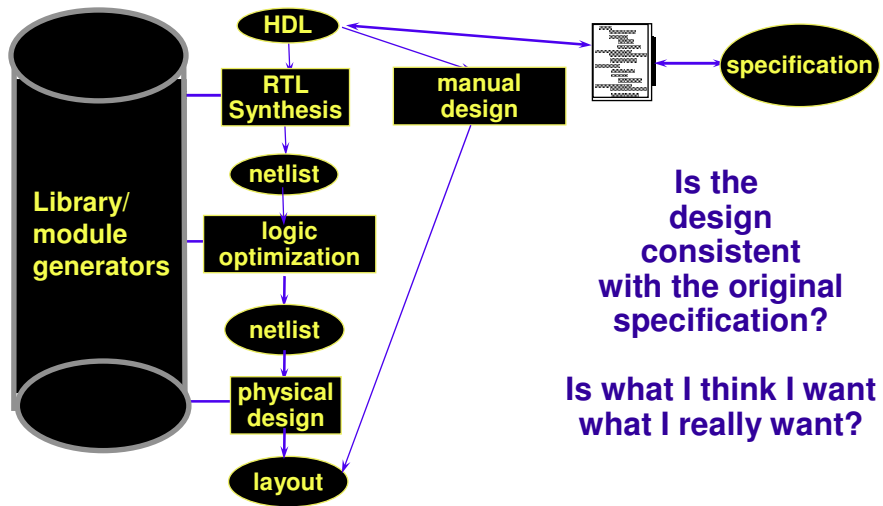


3

Implementation Verification

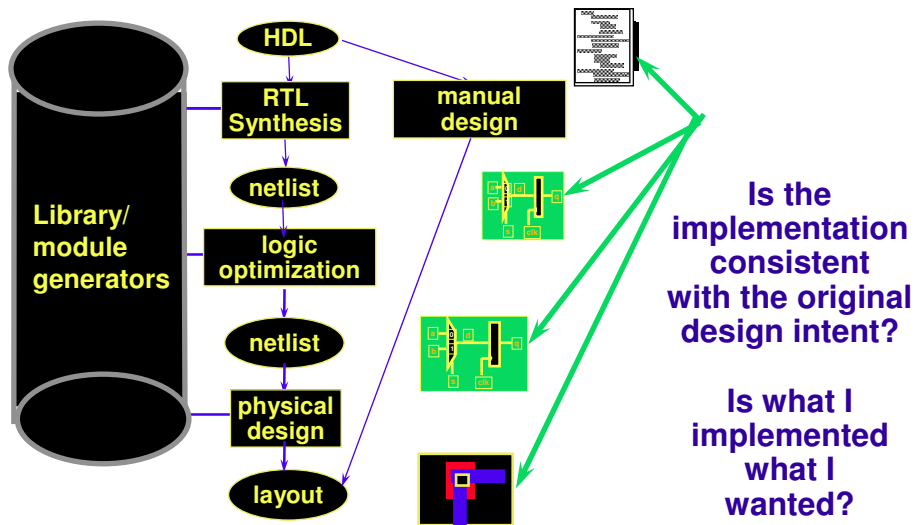

4


Manufacture Verification (Test)

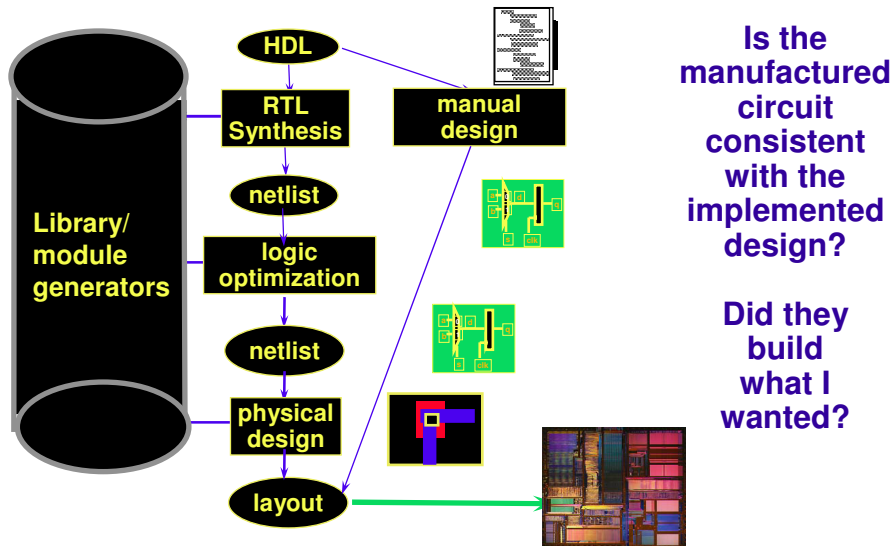

5

Testing

 - Apply a sequence of inputs to a circuit
- Observe the output response and compare the response with a precomputed or "expected" response
- Any discrepancy is said to constitute an error, the cause of which is a physical defect



6

Defects and Fault models

Manufacturing defects can manifest in a variety of ways:[See Ch. 5 of book]

- Bridging
- Contaminants
- Shorts
- Opens
- Transistors stuck-open

These need to be reduced to models:


- Single stuck-at-1, stuck-at-0
- Multiple stuck-at-1, stuck-at-0
- Delay fault models:
 - Gate
 - Path
 - x {hazard-free, hazard-free robust}

Presently:

- single-stuck-at fault model ubiquitous
- some use of delay fault modeling

7

Defect Model: Stuck-At Faults

 

Any input or internal wire in circuit can be stuck-at-1 or stuck-at-0


Single stuck-at-fault model: In the faulty circuit, a single line/wire is S-a-0 or S-a-1

Multiple stuck-at fault model: In the faulty circuit any subset of wires are S-a-0/S-a-1 (in any combination)

9

Reduce to Combinational Logic Problem

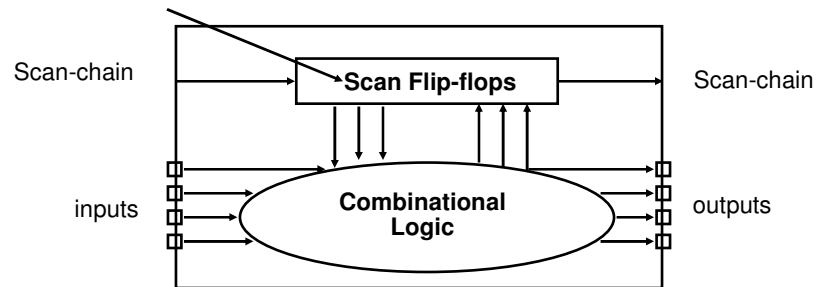add additional state to flip-flops
(15 - 20% area overhead)



10

Outline of Topics

- **Basics & Terminology**
- **PODEM technique**
- **Boolean Satisfiability-based technique**

11

Test Generation

Choose a fault model, e.g., single stuck-at fault model

Given a combinational circuit which realizes the function $f(x_1, x_2, \dots, x_n)$, a logical fault alters it to $f_\alpha(x_1, x_2, \dots, x_n)$

Inputs detecting α are $f \oplus f_\alpha (= 1)$



Interested in one vector

$$A = (a_1, a_2, \dots, a_n) \in f \oplus f_\alpha$$

12

Single Stuck-At Faults

  A fault is assumed to occur only on a single line.




This model is used because it has been found to be statistically correlated with defect-free circuits

13

Activation and Path Sensitization

 In order for an input vector X to detect a fault h s-a-1, $j = 0,1$ the input X must cause the signal h in the normal (fault-free) circuit to take the value \bar{j} .




The condition is necessary but not sufficient. Error signal must be propagated to output.

14

Fault Activation

 The faulty signal must be propagated along some path from its origin to an output




How to activate the fault?

15

Fault Activation

 The faulty signal must be propagated along some path from its origin to an output




h s-a-1, for h to be 0, need $x_2 = x_3 = 0$ ($\overline{x_2} \overline{x_3}$)

16

Fault Propagation

 The error signal must be propagated along some path from its origin to an output




h s-a-1, for h to be 0, need $x_2 = x_3 = 0$ ($\overline{x_2} \overline{x_3}$)

How to propagate the fault?

17

Fault Propagation

 The error signal must be propagated along some path from its origin to an output



h s-a-1, for h to be 0, need $x_2 = x_3 = 0$ ($\overline{x_2} \overline{x_3}$)

Only one path G_3, G_5

In order to propagate an error through AND gate G_3 , other input $x_1 = 1$. To propagate through G_5 , need $G_4 = 0, x_1 + \overline{x_4}$


18

Single Path Sensitization (SPS)

1. Activate: Specify inputs so as to generate the appropriate value (0 for s-a-1, 1 for s-a-0) at the site of the fault.
2. Propagate: Select a path from the site of the fault to an output and specify additional signal values to propagate the fault signal along this path to the output (error propagation).
3. Justify; Specify input values so as to produce the signal values specified in (2) (line justification).

19

Sensitization Example

 


$h s-a-1$

Activate?

20

Sensitization Example

 


$h s-a-1$

Activate: To generate $h = 0$, need $A = B = C = 1$

Propagate?

21

Sensitization Example

 

h s-a-1

To generate $h = 0$, need $A = B = C = 1$

Have a choice of propagating through G_5 or via G_6 .

Propagating through G_5 requires $G_2 = 1$


$\Rightarrow A = D = 0$ **Contradiction**

Propagating through G_6 requires $G_4 = 1 \Rightarrow C = 1, E = 0$.

A valid test vector is $ABCE$

22

Line Justification

 

E s-a-1 $\Rightarrow E = 0$


$C = D = 1$ to propagate through G_1 .

To propagate through G_4 , need $G_2 = G_3 = 1$

How do we justify these values?

23

Line Justification - 2

 

Attempt to line justify $G_2 = G_3 = 1$

$G_3 = 1$ possible if $A = F = 1$ or $B = H = 1$

If $A = C = 1$, then $G_2 = 0$.

$G_3 = 1 \Rightarrow B = H = 1$


$G_2 = 1$ needs $A = 0$ or $F = 0$

Tests are $\overline{!}ABCD\overline{!}EH, BCD\overline{!}E\overline{!}FH$

24

Redundancy

 
Existence of a fault does not change the functionality of a circuit \Rightarrow redundant fault



A test generation algorithm is deemed **complete** if it either finds a test for any fault or proves its redundancy, upon terminating.

25

Completeness of SPS method ?

 

$d \text{ s-a-}0 \Rightarrow A = B = 1$

Propagate along $G_3, G_6 \Rightarrow C = 1$

$G_2 = G_4 = G_5 = 1$


For $G_4 = 1$ either $G_1 = 0$ or $E = 0$

If $G_1 = 0$ fault is not activated

If $E = 0$ (B must be 1) $\Rightarrow G_5 = 0$ **Inconsistency**

26

Completeness of SPS? - 2

 


Propagation along G_4, G_6 also results in inconsistencies by symmetric argument

Is there no test?

27

Multiple Path Sensitization

 

Error propagates down two paths G_3, G_6 and G_4, G_6 to output

It's natural to work backwards (justifying) and forwards (propagating) from point of fault activation but this focuses on sensitizing a single path

Attempting to sensitize a single path will not find a test for this fault


28

First notation: D-Algebra/ D-calculus

Need to be able to deal with multiple "errors" at the inputs to a gate

D represents a signal which has value 1 in normal circuit, and value 0 in faulty circuit.

$\bar{D} \equiv 0/1$

 

D, \bar{D} behave like Boolean variables

29

Outline of Topics

- Basics & Terminology
- **PODEM technique**
- Boolean Satisfiability-based technique

30

Podem strategy – Goel (1981)

Podem

- Path Oriented Decision Making
- uses a simplification to avoid the single-path sensitization trap - only primary inputs are assigned a value

Values are assigned to primary inputs, then propagated forward – need a compatibility between required value and PI value

Continue to assign PI values one at a time

- Implicate values forward
- check to see if the faulty value has propagated to an output – if so then you have a test


If at any point there is a conflict between the PIs and

- Exciting the faulty value
- Propagating the faulty value forward

backtrack – but only at the primary inputs, if you have tried all combinations then halt with failure to find test

31

Podem decision procedure

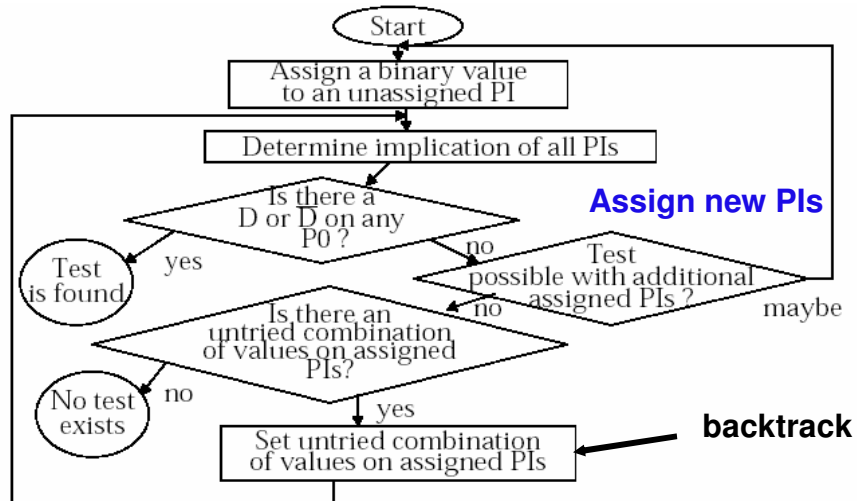


Try a new value on existing PIs

Cf. Fig 5, Goel 1981

32


Flowchart of Backtrace (not backtrack!)

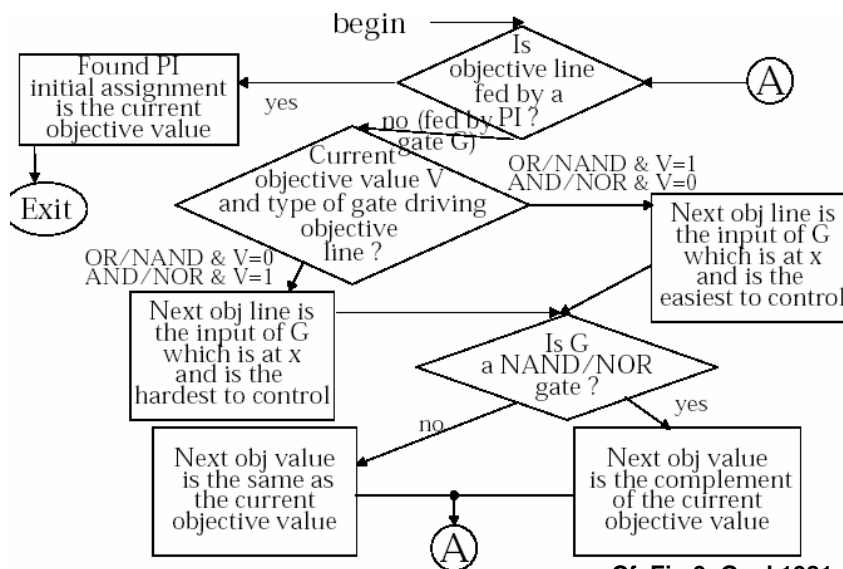

Cf. Fig 9, Goel 1981

33

PODEM Example

 

Initial objective: $(0, G_2)$

Backtrace to PIs: $x_2 = 1$


Objective: $(0, G_2)$

Backtrace: $x_3 = 1$

Implication: $G_2 = \bar{D}$

34

Podem Example – 2a

 

D-frontier is $\{G_5, G_6\}$


Attempt to propagate through G_5

Require $x_1 = 1$

Implication?

35

Podem Example – 2b

 

D-frontier is $\{G_5, G_6\}$


Attempt to propagate through G_5

Require $x_1 = 1$

Implication $G_1 = 0, G_4 = 1, G_5 = D$

36

Podem Example – 3a

 

Attempt to propagate D through G_8 .


Objective $(1, G_6)$

Backtrace to set $x_4 = 0$

Implication produces $G_3 = 1, G_7 = 0, G_8 = 1$
failed in propagating error

37

Podem Example – 3b

 


Attempt to propagate D through G_8 .

Objective $(1, G_6)$

Backtrace

38

Podem Example - 4

 

BACKTRACK to most recent assignment x_4

Try alternative value $x_4 = 1$

Implication results in $G_3 = 0, G_6 = D, G_8 = \bar{D}$

Generated test 1111

39

Status on Podem

Podem approach very successful

At the core of most ATPG systems today

Spawned many additional innovations

- FAN – Fujiwara – sophisticated backtrace
- Socrates – Schulz – learning

But if we had it all to do over ...

40

Outline of Topics

- Basics & Terminology
- PODEM technique
- **Boolean Satisfiability-based technique**

41

Another approach to ATPG (Larrabee, 1989)

The ATPG problem


The CIRCUIT-SAT problem

The Boolean Satisfiability (SAT) problem



42


The ATPG problem

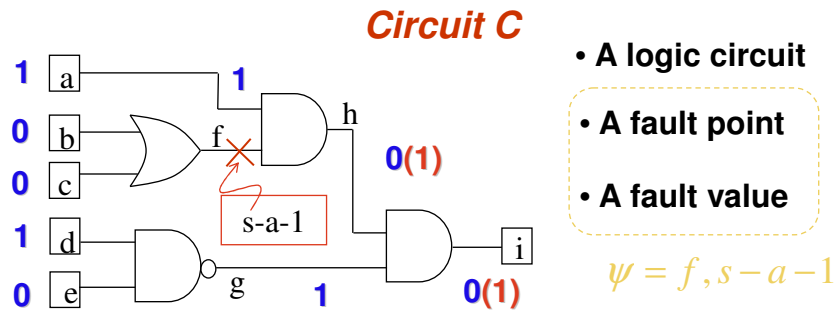

Does there exist a value assignment to the primary inputs which distinguishes the faulted and correct circuits ?

43

The CIRCUIT-SAT problem

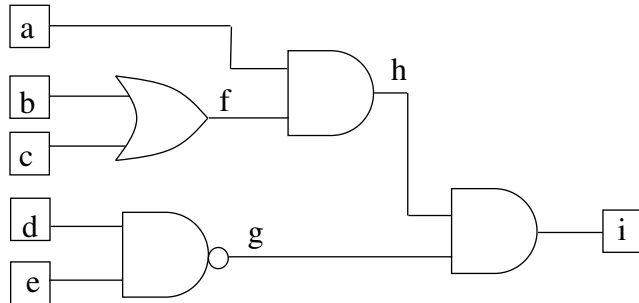


Does there exist a value assignment to the primary inputs which causes the primary output to assume logic value '1' ?

44

ATPG as a CIRCUIT-SAT problem

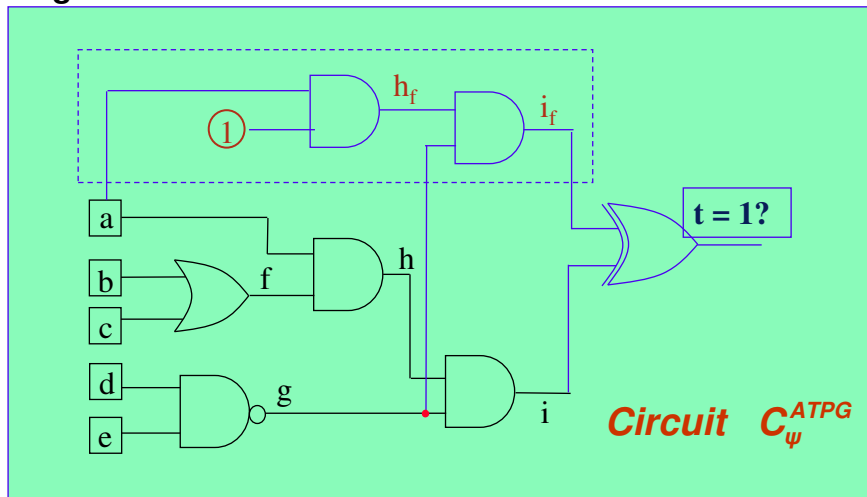Can we find an input value in which the faulty circuit and the good circuit differ?



45

The Boolean Satisfiability (SAT) problem

Given a formula, f :

- ❖ Defined over a set of variables, V (a, b, c)
- ❖ Comprised of a conjunction (AND) of clauses (C_1, C_2, C_3)
- ❖ Each clause is a disjunction (OR) of literals of the variables V

Does there exist an assignment of Boolean values to the variables, V which sets at least one literal in each clause to '1' ?

Example : $(a+b+\bar{c})(\bar{a}+c)(a+\bar{b}+c)$ $a=b=c=1$


$\underbrace{\hspace{2em}}_{C_1}$ $\underbrace{\hspace{2em}}_{C_2}$ $\underbrace{\hspace{2em}}_{C_3}$

46

CIRCUIT-SAT as a SAT problem

A set of clauses representing the functionality of each gate

 A unit literal (i) clause asserting the output to be '1'




47

Algorithm for SAT [DPLL-62]

We have reduced ATPG to SAT- but then what?

Given : CNF formula $f(v_1, v_2, \dots, v_k)$, and an ordering function *Next_Variable*
 
```
Is_SAT(f, A)
{
  if Eval_1(f, A) return SAT
  if Eval_0(f,A) return NOT_SAT
  v = Next_Variable(f, A)
  if Is_SAT(f, (A,v=0)) return SAT
  if Is_SAT(f, (A,v=1)) return SAT
  return UNSAT
}
```



48

DPLL Algorithm – Unit Clause Rule

- **Unit Literal Propagation** rule (Boolean Constraint Propagation, BCP)

$$\begin{array}{cc} (a + b + c) & \implies & c = 1 \\ \parallel & & \\ 0 & & 0 \end{array}$$

49

DPLL Algorithm – Pure Literal Rule

- **Pure-Literal rule:** a

$(a + \dots)$ $(\bar{a} + \dots)$
 $(a + \dots)$ $(\bar{a} + \dots)$
 \vdots
 $(a + \dots)$ $(\bar{a} + \dots)$


⇒ **Assign $a = 1$,
Skip $a = 0$**

50

Tegus Performance on Real Circuits

Results :

 - Of the 11,000 instances generated, 90% were solved in less than 1/100th of a second
- The remaining exhibited roughly a cubic growth in execution time



Why is ATPG easy, inspite of being NP-Complete?

(see paper by Prasad, Chong, Keutzer in the reader)

51

Current Status on Manufacture Test

Practical approach to test: use scan – achieve 99%+ stuck-at coverage

Single stuck-at-fault testing for combinational logic is a “solved problem”

- Despite the fact that it is NP-complete
- After 20+ years of research
- Results applied to combinational-equivalence checking

Single stuck-at-fault testing for sequential circuits is an intractable problem

- Time-frame expansion used in state-space search

Principal research focus is on ATPG for enhanced fault models

- Delay fault testing

Other approaches

- BIST