

Logic Synthesis with VHDL

Combinational Logic

Bob Reese
Electrical Engineering Department
Mississippi State University

Logic Synthesis

- ⇒ Use of Logic Synthesis has become common industrial practice. The advantages are many:
 - Technology portability
 - Design Documentation
 - Constraint Driven Synthesis
- ⇒ Two major languages are Verilog and VHDL. This tutorial will cover logic synthesis via VHDL.
- ⇒ We will split the tutorials into three parts:
 - Introduction to VHDL via combinational synthesis examples
 - Sequential synthesis examples (registers, finite state machines)
 - System examples (combined datapath and control)

Tutorial Caveats

- ⇒ Tutorial examples have been made as simple and portable as possible.
 - Will stay away from topics such as parameterization which may involve vendor-dependent features.
 - Will also stay away from coding styles which involve type conversion as this tends to add extra complications.
- ⇒ Examples have been tested with the Synopsys and Viewlogic synthesis tools; most of the synthesized schematics shown in the slides are from the Viewlogic synthesis tool. Some of the more complex examples are only compatible with the Synopsys environment
- ⇒ In these tutorials, the suggested styles for writing synthesizable VHDL models come from my own experience in teaching an ASIC design course for Senior/Graduate EE students.
- ⇒ Coverage of VHDL packages will be light; the *block structural* statements and VHDL *configurations* are skipped. *Generics* are not mentioned until late in the tutorial since support from a synthesis point of view is vendor dependent.
- ⇒ This tutorial is no substitute for a good, detailed VHDL textbook or the language reference manual. Get one or both!!!

VHDL Synthesis Subset

- ⇒ The VHDL language has a reputation for being very complex - that reputation is well deserved!
- ⇒ Fortunately, the subset of VHDL which can be used for synthesis is SMALL - very easy to learn.
- ⇒ Primary VHDL constructs we will use for synthesis:
 - signal assignment
 - nextstate <= HIGHWAY_GREEN
 - comparisons
 - = (equal), /= (not equal),
 - > (greater than), < (less than)
 - <= (less than or equal), >= (greater than or equal)
 - logical operators
 - (**and, xor, or, nand, nor, xnor, not**)
 - 'if' statement
 - if** (presentstate = CHECK_CAR) **then**
 - end if** | **elsif**
 - 'for' statement (used for looping in creating arrays of elements)
 - Other constructs are '**when else**', '**case**', '**wait**'. Also **:=** for variable assignment.

General Comments on VHDL Syntax

- ⇒ Most syntax details will be introduced on an 'as-needed' basis.
 - The full syntax of a statement type including all of its various options will often NOT be presented; instead, these will be introduced via examples as the tutorial progresses.
 - There are many language details which will be glossed over or simply skipped for the sake of brevity.
- ⇒ Generalities:
 - VHDL is not case sensitive.
 - The semicolon is used to indicate termination of a statement.
 - Two dashes ('—') are used to indicate the start of a comment.
 - Identifiers must begin with a letter, subsequent characters must be alphanumeric or '_' (underscore).
 - VHDL is a strongly typed language. There is very little automatic type conversion; most operations have to operate on common types. Operator overloading is supported in which a function or procedure can be defined differently for different argument lists.

Combinational Logic Examples

- ⇒ We will go through some combinational examples to introduce you to the synthesizable subset of VHDL. Usually, we will demonstrate multiple methods of implementing the same design.
- ⇒ Examples are:
 - 2 to 1 Mux
 - 8-level priority circuit
 - 3 to 8 Decoder
 - Synthesis boundary conditions
 - Ripple-carry adder

Model Template

entity *model_name* is

```
port
(
    list of inputs and outputs
);
end model_name;
```

```
architecture architecture_name of model_name is
begin
```

```
    ...
    VHDL concurrent statements
    ....
```


```
end architecture_name ;
```

2-to-1 MUX — Using *when else*

```
library IEEE;
use IEEE.std_logic_1164.all;

— vhdl model for 2 to 1 mux, 8-bits wide
entity mux2to1 is
port
(
    signal s:          in  std_logic;
    signal zero,one:  in  std_logic_vector(7 downto 0);
    signal y:          out std_logic_vector(7 downto 0)
);
end mux2to1;

 architecture behavior of mux2to1 is
begin
    y <= one when (s = '1') else zero;
end behavior;
```



Standard Logic 1164

```
library IEEE;
use IEEE.std_logic_1164.all;
```

- ⇒ The LIBRARY statement is used to reference a group of previously defined VHDL design units (other entities or groups procedures/functions known as 'packages').
- ⇒ The USE statement specifies what entities or packages to use out of this library; in this case 'USE IEEE.std_logic_1164.all' imports all procedures/functions in the *std_logic_1164* package.
- ⇒ The *std_logic_1164* package defines a multi-valued logic system which will be used as the data types for the signals defined in our examples.
 - The VHDL language definition had a built-in bit type which only supported two values, '1' and '0' which was insufficient for modeling and synthesis applications.
 - The 1164 standard defines a 9-valued logic system; only 4 of these have meaning for synthesis:
 - '1', '0', 'Z' (high impedance), '-' (don't care).
- ⇒ The 1164 single bit type *std_logic* and vector type *std_logic_vector* (for busses) will be used for all signal types in the tutorial examples.

2/1 MUX Entity Declaration

```
entity mux2to1 is
port
(
  signal s:      in  std_logic;
  signal zero,one: in  std_logic_vector(7 downto 0);
  signal y:      out std_logic_vector(7 downto 0)
);
end mux2to1;
```

- ⇒ The *entity* declaration defines the external interface for the model.
- ⇒ The port list defines the external signals. The signal definition consists of the signal name, mode, and type.
 - For synthesis purposes (and for this tutorial), the mode can be either *in*, *out* or *inout*.
- ⇒ In this tutorial, the signal types will be either *std_logic* (single bit) or *std_logic_vector* (busses).
- ⇒ The array specification on the *std_logic_vector* type defines the width of signal:

<i>std_logic_vector</i> (7 downto 0)	(descending range)
<i>std_logic_vector</i> (0 to 7)	(ascending range)

 Both of these are 8-bit wide signals. The descending/ascending range declaration will affect assignment statements such as:


```
y <= "11110000";
```

 For descending range, y(7) is '1'; for ascending range y(0) is '1'.

2/1 MUX Architecture Declaration

architecture *behavior* of *mux2to1* is
begin

```
y <= one when (s = '1') else zero;
```

end *behavior*;

⇒ The architecture block specifies the model functionality.


→ The architecture name is user-defined. Multiple architectures can be defined for the same entity. VHDL *configurations* can be used to specify which architecture to use for a particular entity.

→ This tutorial will only use one architecture per entity and it will always be called *behavior*.

⇒ The 'when ... else' statement is a conditional signal assignment statement. 'When ... else' statements can be chained such as:

```
signal_name <= value1 when condition1 else
               value2 when condition2 else,
               ..... value N when conditionN else default_value;
```

 ⇒ The 'when ... else' statement is a particular type of statement known as a *concurrent* statement as opposed to a *sequential* statement. The differences between *concurrent* and *sequential* statements will be discussed in more detail later.



2/1 MUX Architecture Using Booleans

architecture *behavior* of *mux2to1* is
 signal *temp*: std_logic_vector(7 downto 0);

```
begin
  temp <= (s, s, s, s, others => s);
  y <= (temp and one) or (not temp and zero);
```

end behavior;

⇒ Boolean operators are used in an assignment statement to generate the mux operation.

⇒ The *s* signal cannot be used in a boolean operation with the *one* or *zero* signals because of type mismatch (*s* is a std_logic type, *one/zero* are std_logic_vector types)

→ An internal signal of type std_logic_vector called *temp* is declared. Note that there is no mode declaration for internal signals. The *temp* signal will be used in the boolean operation against the *zero/one* signals.

⇒ Every bit of *temp* is to be set equal to the *s* signal value. An array assignment will be used; this can take several forms:

```
temp <= (others => s); 'others' keyword gives default value
temp <= (s, s, s, s, s, s, s, s); positional assignment, 7 downto 0
temp <= (4=>s, 7=>s, 2=>s, 5=>s, 3=>s, 1=>s, 6=>s, 0=>s);
named assignment
or combinations of the above.
```

2/1 MUX Architecture Using a Process

architecture *behavior* of *mux2to1_8* is
 begin

```
  comb: process (s, zero, one)
  begin
    y <= zero;
    if (s = '1') then
      y <= one;
    end if;
  end process comb;
end behavior;
```

⇒ This architecture uses a *process* block to describe the mux operation.

→ The process block itself is considered a single concurrent statement.

→ Only sequential VHDL statements are allowed within a process block.

→ Signal assignments are assumed to occur sequentially so that an assignment can supercede a previous assignment to the same signal.

→ 'if ... else', 'case', 'for ... loop' are sequential statements.


⇒ The list of signals after the process block is called the *sensitivity* list; an event on any of these signals will cause the process block to be evaluated during model simulation.

8-level Priority Encoder

- vhdl model for 8 level priority circuit
- IO Interface Declaration

```
entity priority is
port (
  signal y1, y2, y3, y4, y5, y6, y7: in std_logic;
  signal vec: out std_logic_vector(2 downto 0)
);
end priority;
```

 
```
— Architecture body
architecture behavior of priority is
begin
  process (y1,y2,y3,y4,y5,y6,y7)
  begin
```



```
  if (y7 = '1') then vec <= "111";
  elsif (y6 = '1') then vec <= "110";
  elsif (y5 = '1') then vec <= "101";
  elsif (y4 = '1') then vec <= "100";
  elsif (y3 = '1') then vec <= "011";
  elsif (y2 = '1') then vec <= "010";
  elsif (y1 = '1') then vec <= "001";
  else vec <= B"000";
  end if;
```

```
end process;
end behavior;
```

Uses 'elsif' construct for logic

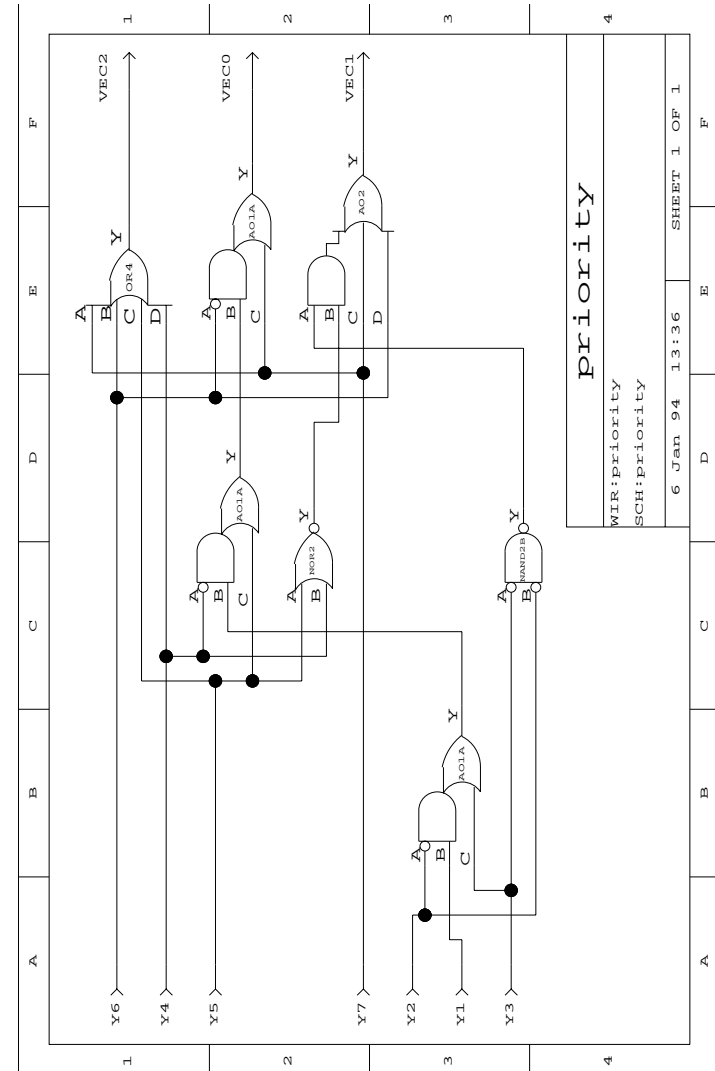

priority

WIR:priority
SCH:priority

6 Jan 94 13:36 SHEET 1 OF 1

Priority Encoder again.....

⇒ In a process, the ordering of sequential statements which affect a common output define the priority of those assignments.

→ By using normal 'if' statements and reversing the order of the assignments we achieve the same results as with the chained 'elsif' statements.

```
— Architecture body
architecture behavior of priority is
begin
  process (y1,y2,y3,y4,y5,y6,y7)
  begin
```

```
    vec <= "000";
    if (y1 = '1') then vec <= "001"; end if;
    if (y2 = '1') then vec <= "010"; end if;
    if (y3 = '1') then vec <= "011"; end if;
    if (y4 = '1') then vec <= "100"; end if;
    if (y5 = '1') then vec <= "101"; end if;
    if (y6 = '1') then vec <= "110"; end if;
    if (y7 = '1') then vec <= "111"; end if;
```

```
  end process;
end behavior;
```

Since 'y7' is tested last it will have highest priority.

3 to 8 Decoder Example

```
entity dec3to8 is port (
  signal sel: in std_logic_vector(2 downto 0); — selector
  signal en: in std_logic; — enable
  signal y: out std_logic_vector(7 downto 0) — outputs are low true
); end dec3to8;
```

architecture behavior of dec3to8 is

```
begin
```

```
  process (sel,en)
```

```
  begin
```

```
    y <= "11111111";
```

```
    if (en = '1') then
```

```
      case sel is
```

```
        when "000" => y(0) <= '0';
```

```
        when "001" => y(1) <= '0';
```

```
        when "010" => y(2) <= '0';
```

```
        when "011" => y(3) <= '0';
```

```
        when "100" => y(4) <= '0';
```

```
        when "101" => y(5) <= '0';
```

```
        when "110" => y(6) <= '0';
```

```
        when "111" => y(7) <= '0';
```


```
      end case;
```

```
    end if;
```

```
  end process;
```

```
end behavior;
```

'case' statement used for implementation

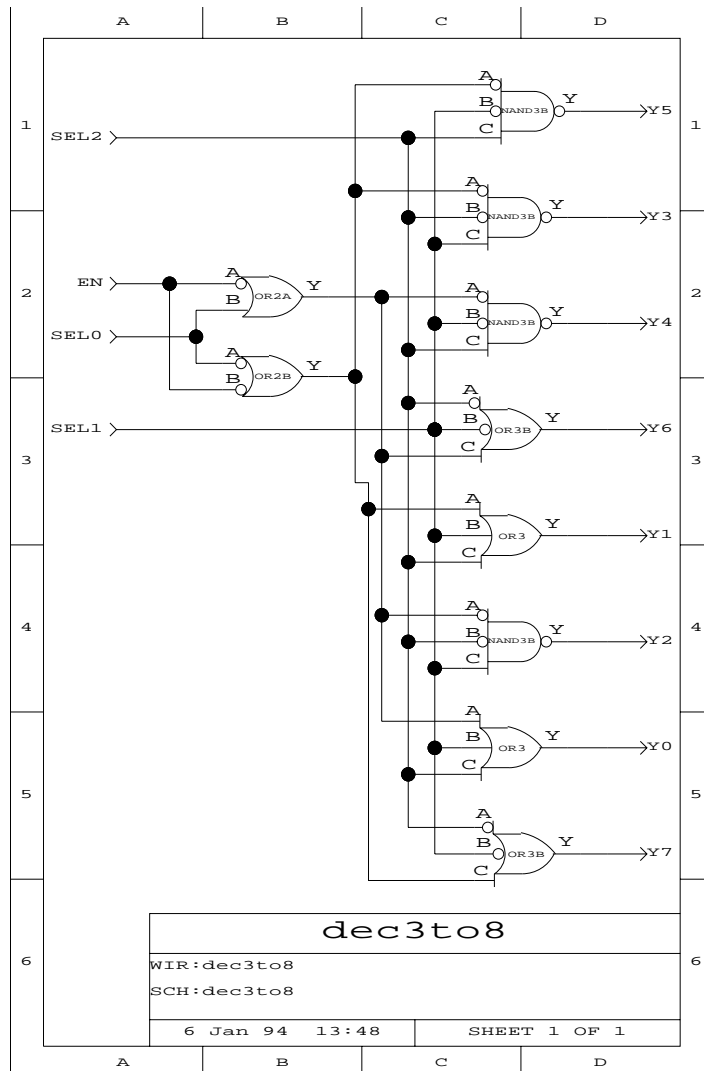

A Common Error

⇒ When using processes, a common error is to forget to assign an output a default value. ALL outputs should have DEFAULT values!!!!

→ If there is a logical path in the model such that an output is not assigned any value then the synthesizer will assume that the output must retain its current value and a latch will be generated.


⇒ Example: In *dec3to8.vhd* do not assign 'y' the default value of B"11111111". If *en* is 0, then 'y' will not be assigned a value!

```

process (sel,en)
begin
  y <= "11111111";
  if (en = '1') then
    .....
  
```

Comment out the default assignment to 'y'.

⇒ In the new synthesized logic, all 'y' outputs are latched!

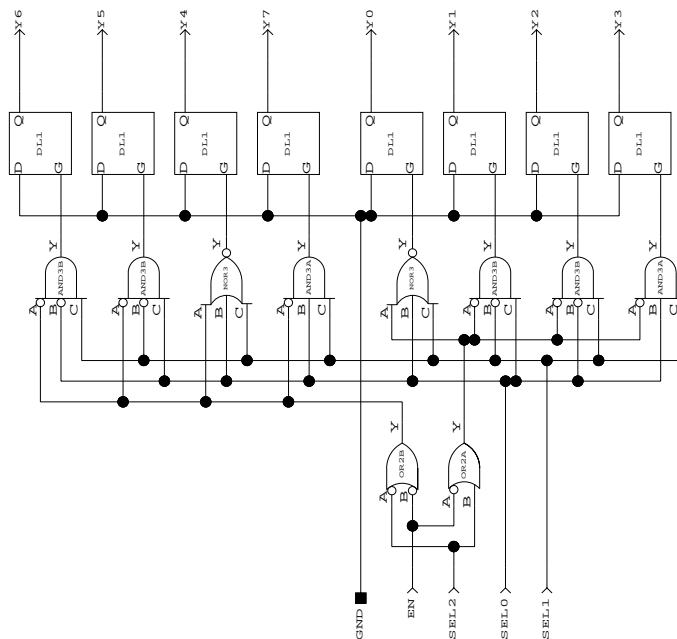

Alternative 3-to-8 Decoder

- vhdl model for the 3 to 8 decoder
- uses conditional signal assignments
- which are concurrent statements

entity dec3to8_alt is

port (

 signal sel: in std_logic_vector(2 downto 0); — selector

 signal en: in std_logic; — enable

 signal y: out std_logic_vector(7 downto 0) — outputs are low true

);

end dec3to8_alt;

architecture behavior of dec3to8_alt is

begin

y(0) <= '0' when (en = '1' and sel = "000") else '1';

y(1) <= '0' when (en = '1' and sel = "001") else '1';

y(2) <= '0' when (en = '1' and sel = "010") else '1';

y(3) <= '0' when (en = '1' and sel = "011") else '1';

y(4) <= '0' when (en = '1' and sel = "100") else '1';

y(5) <= '0' when (en = '1' and sel = "101") else '1';

y(6) <= '0' when (en = '1' and sel = "110") else '1';

y(7) <= '0' when (en = '1' and sel = "111") else '1';

end behavior;

*Conditional signal
assignment used
for each output bit.*

Generic Decoder

⇒ Shown below is an architecture block for a generic decoder:

architecture behavior of *generic_decoder* is

```
begin
  process (sel, en)
  begin
    y <= (others => '1');
    for i in y'range loop
      if (en = '1' and bvtoi(To_Bitvector(sel)) = i) then
        y(i) <= '0';
      end if;
    end loop;
  end process;
end behavior;
```

⇒ This architecture block can be used for any binary decoder (2 to 4, 3 to 8, 4 to 16, etc).

⇒ The 'for ... loop' construct is used to repeat a sequence of statements.

→ The *y'range* is the range of values for loop variable 'i'. The *'range* attribute of the signal 'y' is defined as the array range of the signal. In this case, 'i' will vary from 7 to 0 if the array range of 'y' was defined as "7 downto 0".

→ Other attributes useful for synthesis are: 'LEFT, 'RIGHT (left, right array indices); 'HIGH, 'LOW (max, min array indices); 'EVENT (boolean which is true if event occurred on signal).

Generic Decoder (cont.)

```
....
for i in y'range loop
  if (en = '1' and bvtoi(To_Bitvector(sel)) = i) then
    y(i) <= '0';
  end if;
```

⇒ In order to compare loop variable *i* with the value of *sel*, a type conversion must be done on *sel* to convert from *std_logic_vector* to *integer*.

→ The Standard Logic 1164 package defines a conversion from *std_logic_vector* to *bit_vector* (*bit_vector* is a primitive VHDL type).

⇒ Unfortunately, the VHDL language standard does not define type conversions between *bit_vector* and *integer*; these conversion functions are vendor dependent.

→ 'bvtoi' is the Synopsys *bit_vector* to *integer* conversion function; 'vlb2int' is the Viewlogic equivalent; the Cypress WARP equivalent is 'bv2i'.

Synthesis Boundary Conditions

What happens when:

Two outputs are reduced to the same logic equation?

An output is reduced to '0', '1' or to a primary input?

— synthesis 'boundary' conditions..

entity boundtest is

port (

 signal a,b,c: in std_logic;

 signal w, x, y, z_low, z_high: out std_logic

); end boundtest;

architecture behavior of boundtest is

begin

— x and y reduce to the same logic equation

— the w output should be just a wire from c...

— the z_low output will be '0', the z_high will be '1'

x <= a or b;


y <= a or ((b and not c) or (b and c));

w <= (c and b) or (c and not b);

z_low <= b and not b;

z_high <= b or not b;

end behavior;

 

Ripple Carry Adder

```

Library IEEE;
use IEEE.std_logic_1164.all;

entity adder4 is port (
  signal a,b: in std_logic_vector (3 downto 0);
  signal cin: in std_logic;
  signal sum: out std_logic_vector(3 downto 0);
  signal cout: out std_logic
);
end adder4;

```

*Explicit CarryIn
and CarryOut*


```

architecture behavior of adder4 is
  signal c: std_logic_vector(4 downto 0);
begin
  process (a,b,cin,c)
  begin
    c(0) <= cin;
    for i in 0 to 3 loop
      sum(i) <= a(i) xor b(i) xor c(i);
      c(i+1) <= (a(i) and b(i)) or
        (c(i) and (a(i) or b(i)));
    end loop;
    cout <= c(4);
  end process;
end behavior;

```

*Temporary signal
to hold internal
carries.*

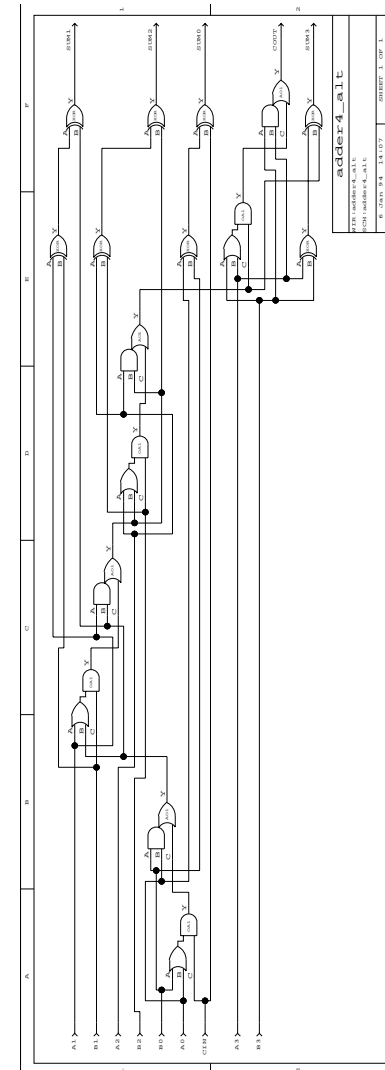*Use Looping construct to
create logic for ripple carry
adder.*



Ripple Carry Adder Comments

- ⇒ The *Standard Logic 1164* package does not define arithmetic operators for the *std_logic* type.
- ⇒ Most vendors supply some sort of arithmetic package for 1164 data types.
 - Some vendors also support synthesis using the '+' operation between two *std_logic* signal types (Synopsis). Others provide an explicit function call (Viewlogic).
 - For code portability, it is best to avoid use of vendor-specific arithmetic functions.

Summary

- ⇒ Logic synthesis offers the following advantages:
 - Faster design time, easier to modify
 - The synthesis code documents the design in a more readable manner than schematics.
 - Different optimization choices (area or speed)
- ⇒ Several combinational VHDL examples were examined.
 - Both concurrent and sequential statements can be used to specify combination logic – which you use is up to individual preference.


Logic Synthesis with VHDL

Sequential Circuits

Bob Reese
Electrical Engineering Department
Mississippi State University

Sequential Circuits

 ⇒ Logic which contains both combinational logic and storage elements form sequential circuits. All sequential circuits can be divided into a combinational block and a storage element block.



Single Phase Sequential System

⇒ The above diagram shows a single-phase sequential system. In a single-phase system the storage elements are edge-triggered devices (flip-flops).

→ *Moore*-type outputs are a combinatorial function of PresentState signals.

→ *Moore*-type outputs are a combinatorial function of both PresentState and external input signals.

⇒ Multiple-phase design is also supported since latches can be synthesized as the storage elements.

Sequential Template

library declarations

```
entity model_name is
port
(
    list of inputs and outputs
);
end model_name;
```

architecture behavior of *model_name* is

internal signal declarations

```
begin
    — the state process defines the storage elements
    state: process ( sensitivity list — clock, reset, next_state inputs )
    begin
        vhdl statements for state elements
    end process state;

    — the comb process defines the combinational logic
    comb: process ( sensitivity list — usually includes all inputs )
    begin
        vhdl statements which specify combinational logic
    end process comb;
end behavior;
```

8-bit Loadable Register with Asynchronous clear

```
library ieee;
use ieee.std_logic_1164.all;

entity reg8bit is port (
    signal clk, reset, load:      in std_logic;
    signal din:                   in std_logic_vector(7 downto 0);
    signal dout:                  out std_(7 downto 0)
);
end reg8bit;

architecture behavior of reg8bit is
    signal n_state,p_state : std_logic_vector(7 downto 0);
    begin
        dout <= p_state;

        comb: process(p_state,load,din)
        begin
            n_state <=p_state;
            if (load='1') then n_state <= din; end if;
        end process comb;


        state: process(clk, reset)
        begin
            if (reset = '0') then p_state <= (others => '0');
            elsif (clk'event and clk = '1') then
                p_state <= n_state;
            end if;
        end process state;
    end behavior;
```

reg8bit State Process

```

state: process(clk, reset)
begin
if (reset = '0') then p_state <= (others => '0');
elsif (clk'event and clk = '1') then
    p_state <= n_state;
end if;
end process state;
    
```

- ⇒ The *state* process defines a storage element which is 8–bits wide, rising edge triggered, and had a low true asynchronous reset.
- The output of this process is the *p_state* signal.
- Note that the *reset* input has precedence over the clock in order to define the asynchronous operation.
- The *'event* attribute is used to detect a change in the clock signal; comparing the current clock value against '1' implies that *p_state* gets the *n_state* value on a 0 to 1 transition (rising edge).
- The state holding action of the process arises from the fact that *p_state* is not assigned a value is reset is not asserted and a rising clock edge does not occur.

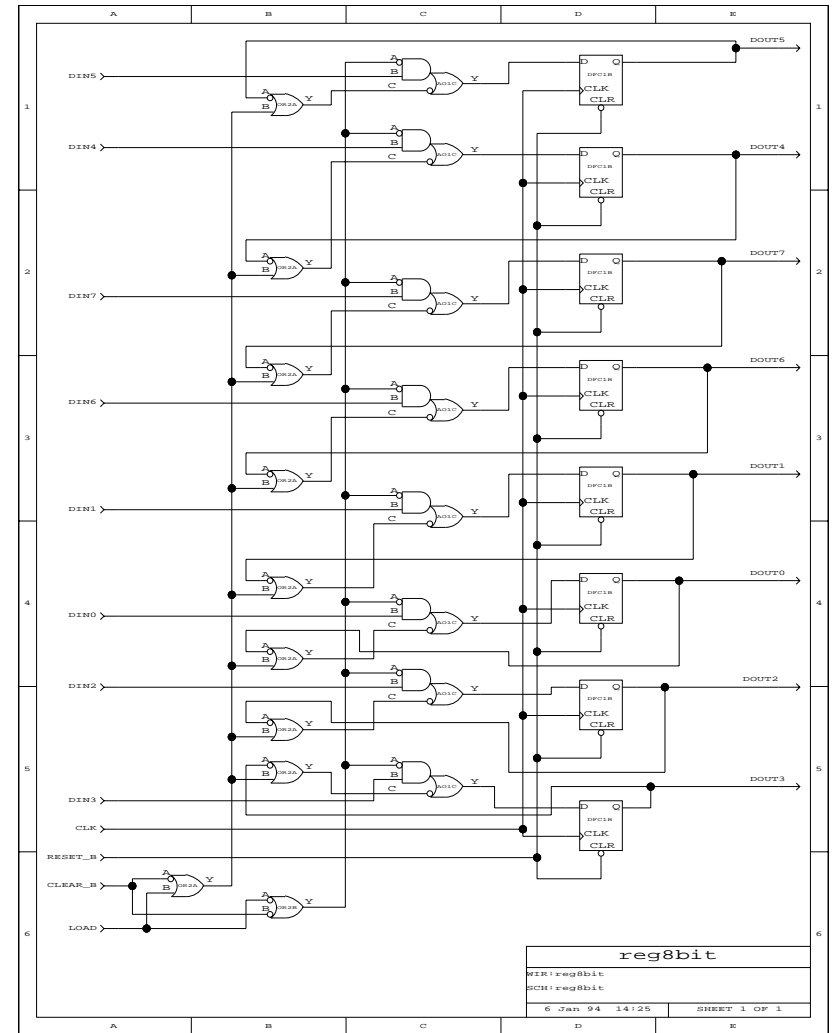

wait Statement

⇒ An alternative method of specifying the storage elements is shown below:

```
state: process
begin
wait until ((clk'event and clk = '1') or (reset = '0'));
if (reset = '0') then p_state <= (others => '0');
else
p_state <= n_state;
end if;
end process state;
```

⇒ The *wait* statement is a sequential statement.

⇒ The *wait* statement causes a suspension of a process or procedure until the condition clause is satisfied.


⇒ The signals used in the condition clause form an implicit sensitivity list for the *wait* statement.

→ Can use 'wait on *sig1*, *sig2*, ..*sigN* until *condition_clause*' to explicitly specify the sensitivity list.


→ Note that the process has no sensitivity list.

⇒ 'if' statements used with processes generally give more flexibility and control than 'wait' statements .

Finite State Machine Example

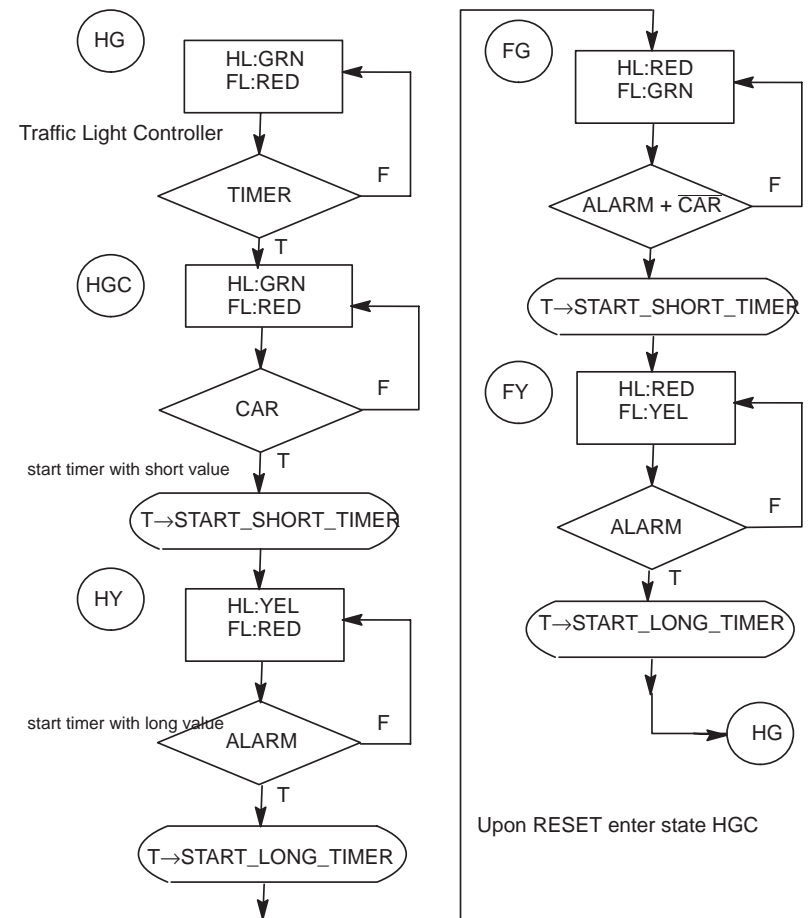

Traffic Light Controller Block Diagram

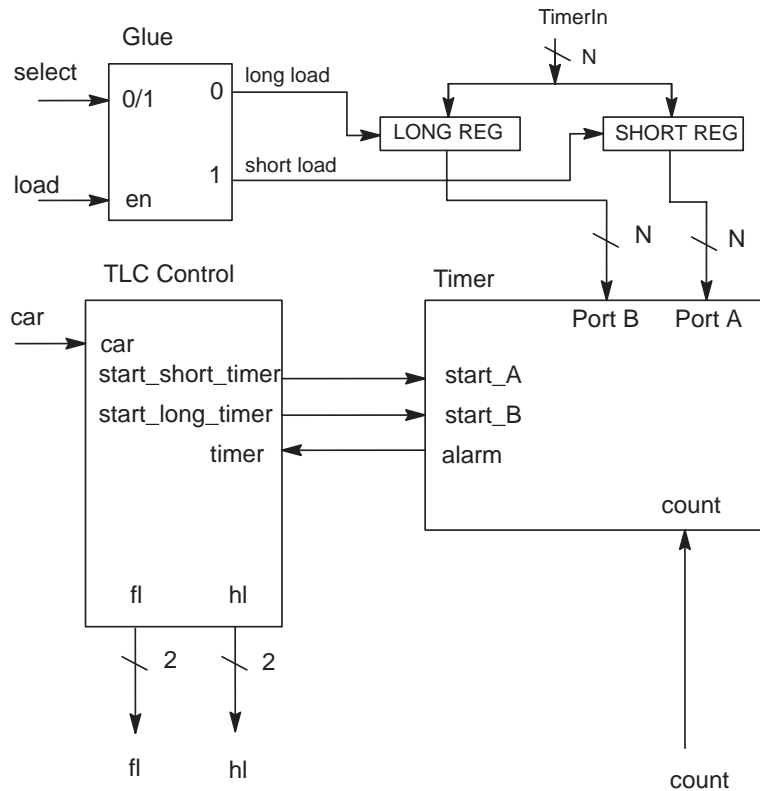

VHDL For Traffic Light FSM Control

```

library ieee;
use ieee.std_logic_1164.all;
-- vhdl model for the Traffic Light Control, sync reset, encoded states
entity tlc_enc is port(
    signal reset, car, timer, clk: in std_logic;
    signal stateout: out std_logic_vector(2 downto 0);
    signal highway_light, farm_light: out std_logic_vector(1 downto 0);
    signal start_short_timer, start_long_timer: out std_logic );
end tlc_enc;
architecture behavior of tlc_enc is

```

State assignments

```

    constant HGC: std_logic_vector(2 downto 0) := "000";
    constant HY: std_logic_vector(2 downto 0) := "001";
    constant FG: std_logic_vector(2 downto 0) := "010";
    constant FY: std_logic_vector(2 downto 0) := "011";
    constant HG: std_logic_vector(2 downto 0) := "100";

    constant GREEN: std_logic_vector(1 downto 0) := "00";
    constant YELLOW: std_logic_vector(1 downto 0) := "01";
    constant RED: std_logic_vector(1 downto 0) := "11";

```

```

    signal p_state, n_state : std_logic_vector(2 downto 0);

```

```

begin
    stateout <= p_state;
    statereg: process(clk, reset)
        if (reset = '0') then p_state <= HGC;
        elsif (clk'event and clk = '1') then p_state <= n_state; end if;
    end process statereg;

```

VHDL For Traffic Light FSM (cont)

```
comb:process(car, timer, p_state)
```

```
begin
```

```
— default assignments — VERY IMPORTANT
```

```
start_short_timer <= '0';
```

```
start_long_timer <= '0';
```

```
— by default, stay in same state!!!
```

```
n_state <= p_state;
```

```
highway_light <= GREEN; farm_light <= RED;
```

```
if p_state = HG then
```

```
highway_light <= GREEN; farm_light <= RED;
```

```
if (timer = '1') then n_state <= HGC; end if;
```

```
end if;
```

```
if p_state = HGC then
```

```
highway_light <= GREEN; farm_light <= RED;
```

```
if car = '1' then
```

```
n_state <= HY; start_short_timer <= '1'; end if;
```

```
end if;
```

```
if p_state = HY then
```

```
highway_light <= YELLOW; farm_light <= RED;
```

```
if timer = '1' then
```

```
n_state <= FG; start_long_timer <= '1'; end if;
```

```
end if;
```

All outputs should be assigned default values!! If you do not assign default values then outputs may get synthesized with output latches!

Use 'if' statements to enumerate states.

Start timer with short timeout value (yellow light).

Start timer with long timeout value.

VHDL For Traffic Light FSM Control (cont.)

```
if p_state = FG then
```

```
highway_light <= RED; farm_light <= GREEN;
```

```
if timer = '1' or car = '0' then
```

```
n_state <= FY; start_short_timer <= '1'; end if;
```

```
end if;
```

```
if p_state = FY then
```

```
highway_light <= RED; farm_light <= YELLOW;
```


```
if timer = '1' then
```

```
n_state <= HG; start_long_timer <= '1'; end if;
```

```
end if;
```

```
end process comb;
```

```
end behavior;
```

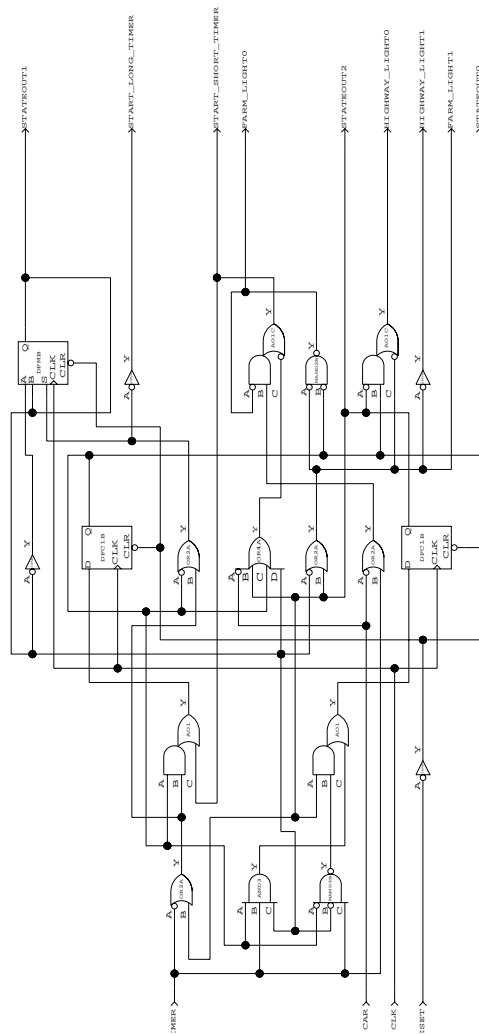

One-Hot Encoding for FSMs

- ⇒ One-Hot encoding of FSMs uses one flip-flop per state.
 - Only one flip-flop is allowed 'on' at anytime.
 - E.G., states are "00001", "00010", "00100", "01000", "10000" for a five state FSM. All other states are illegal.
- ⇒ One-Hot encoding trades combinational logic for flip-flops.
 - Good for 'flip-flop' rich implementation technologies.
 - Because the combinational logic is reduced, the length of the critical path can be reduced resulting in a faster FSM. Speed increase is more significant for larger finite state machines.

One Hot Encoding for TLC

```
library IEEE; use IEEE.std_logic_1164.all;
```

```
entity tlc_onehot is port (
  signal reset, car, timer, clk:      in std_logic;
  signal stateout:                    out std_logic_vector(4 downto 0);
  signal highway_light, farm_light: out std_logic_vector(1 downto 0);
  signal start_long_timer, start_short_timer: out std_logic
); end tlc_onehot;
```

architecture behavior of tlc_onehot is

```
constant HG: integer := 0;
constant HGC: integer := 1;
constant HY: integer := 2;
constant FG: integer := 3;
constant FY: integer := 4;
```

State assignments now specify bit positions in the state FFs

```
constant GREEN: std_logic_vector(1 downto 0) := "00";
constant YELLOW: std_logic_vector(1 downto 0) := "01";
constant RED: std_logic_vector(1 downto 0) := "11";
```

```
signal p_state, n_state : std_logic_vector(4 downto 0);
```

```
begin
  stateout <= p_state;
```

```
state: process(clk, reset)
```

Initial state is '00010'

```
begin
  if (reset = '0') then p_state <= (HGC => '1', others => '0');
  elsif (clk'event and clk = '1') then
    p_state <= n_state;
  end if;
end process state;
```

One Hot Encoding for TLC

```
comb:process(car, timer, p_state)
```

```
begin
```

— default assignments — VERY IMPORTANT

```
start_long_timer <= '0'; start_short_timer <= '0'; start <= '0';
n_state <= p_state;
highway_light <= GREEN; farm_light <= RED;
```

```
if p_state(HG) = '1' then
  highway_light <= GREEN; farm_light <= RED;
  if (timer = '1') then
    n_state(HG) <= '0'; n_state(HGC) <= '1';
  end if;
end if;
```

When changing states you must turn off current state FF and turn on next state FF.

```
if p_state(HGC) = '1' then
  highway_light <= GREEN; farm_light <= RED;
  if car = '1' then
    n_state(HGC) <= '0'; n_state(HY) <= '1';
    start_short_timer <= '1';
  end if;
end if;
```

```
if p_state(HY) = '1' then
  highway_light <= YELLOW; farm_light <= RED;
  if timer = '1' then
    n_state(HY) <= '0'; n_state(FG) <= '1';
    start_long_timer <= '1';
  end if;
end if;
```

One Hot Encoding for TLC


```

if p_state(FG) = '1' then
  highway_light <= RED; farm_light <= GREEN;
  if timer = '1' or car = '0' then
    n_state(FG) <= '0'; n_state(FY) <= '1';
    start_short_timer <= '1';
  end if;
end if;

if p_state(FY) = '1' then
  highway_light <= RED; farm_light <= YELLOW;
  if timer = '1' then
    n_state(FY) <= '0'; n_state(HG) <= '1';
    start_long_timer <= '1';
  end if;
end if;

end process comb;
end behavior;

```

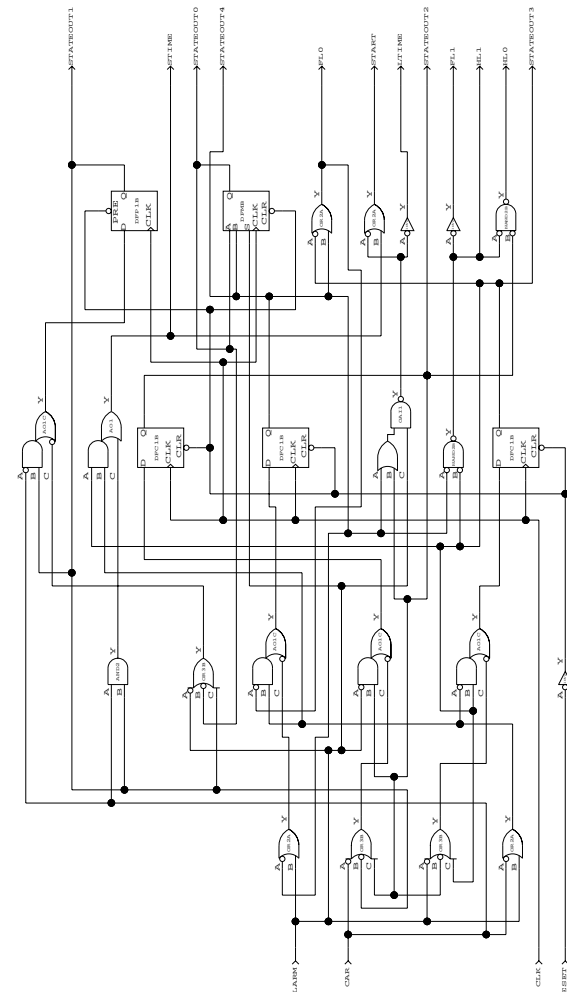

Simple 4-bit Shift Register

```
library IEEE; use IEEE.std_logic_1164.all;
```

'din' is serial input

```
entity shift4 is port(
  signal clk, reset:   in std_logic;
  signal din:          in std_logic;
  signal dout:        out std_logic_vector(3 downto 0)
); end shift4;
```

MSB of 'dout' is the serial output

architecture behavior of shift4 is

```
signal n_state, p_state : std_logic_vector(3 downto 0);
```

```
begin
dout <= p_state;
state: process(clk, reset)
begin
if (reset = '0') then p_state <= (others => '0');
elsif (clk'event and clk = '1') then
  p_state <= n_state;
end if;
end process state;
```

Assign serial input 'din' to the 'data' input of the first flip-flop


```
comb:process (p_state,din)
begin
  n_state(0) <= din;
  for i in 3 downto 1 loop
    n_state(i) <= p_state(i - 1);
  end loop;
end process comb;
end behavior;
```


Use 'for' loop to connect output of previous flip-flop to input of current flip-flop

Loop function for Shift Register

```
comb:process (p_state,din)
begin
  n_state(0) <= din;
  for i in 3 downto 1 loop
    n_state(i) <= p_state(i - 1);
  end loop;
```

```
end process comb;
```

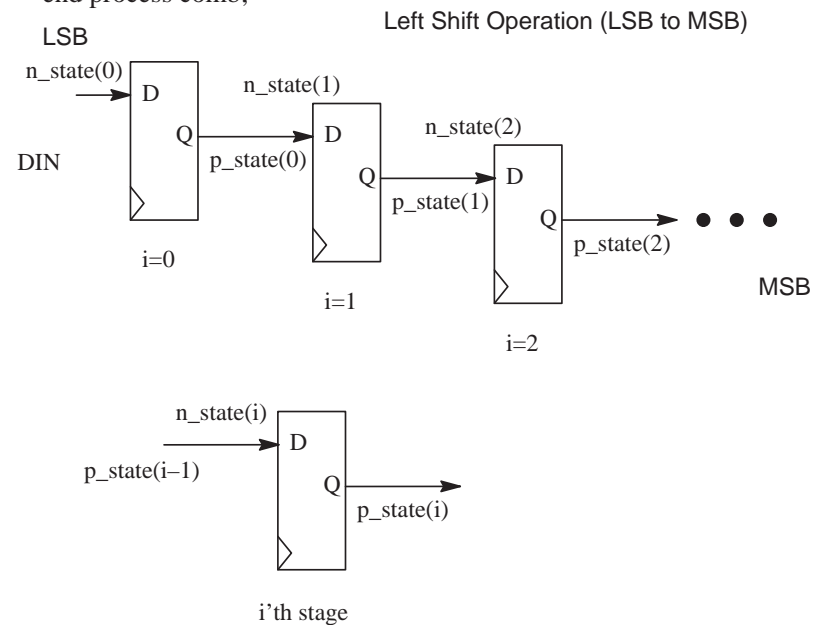

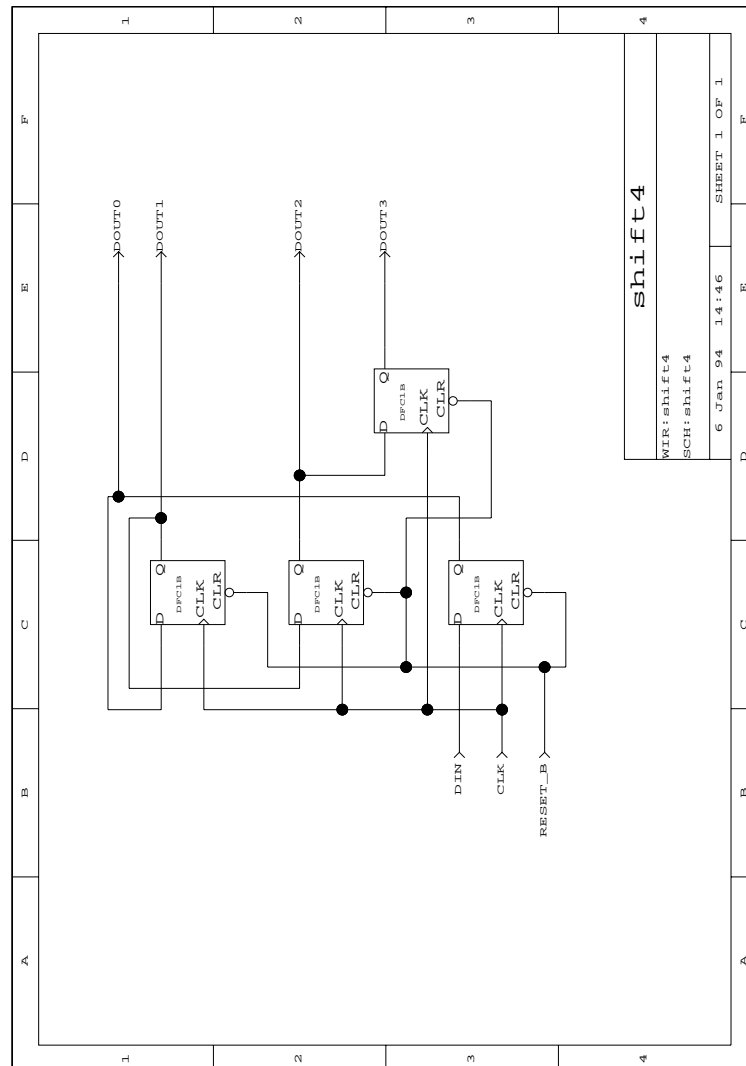

Scan Path Synthesis

⇒ The 'for-loop' VHDL construct can be used to create a scan-path in your design. A scan path is a design technique used for improving the testability of a design.

→ A scan path requires three extra pins on the design: 'scan', 'scan_in', and 'scan_out'.

→ When 'scan' is asserted, all flip-flops in the design act like a serial shift register; the 'scan_in' pin is the serial input and the 'scan_out' pin the serial output. When 'scan' is negated the design functions normally.

→ Because all flip-flops in the design are on the scan path the circuit can be placed in any desired state.

⇒ To enter a test vector via the scan path do:

→ Assert 'scan'.

→ Apply the test vector serially to the 'scan_in' input; this requires N clocks if N flip-flops are on the scan path.

→ Negate 'scan', clock the circuit once. This will allow the circuit to operate normally for one clock cycle; the result of the test vector will be loaded into the flip-flops.

→ Assert 'scan'; clock N times to clock out the test vector result and to clock in the next test vector. Thus, each test vector requires N+1 clocks.

4-bit Register with Scan Path

```
entity scanreg4 is port (
  signal clk, reset_b, load:      in std_logic;
  signal scan, scan_in:         in std_logic;
  signal din:                     in std_logic_vector(3 downto 0);
  signal dout:                    out std_logic_vector(3 downto 0)
); end scanreg4;
```

'scan', 'scan_in'
signals

architecture behavior of scanreg4 is
signal n_state, p_state : std_logic_vector(3 downto 0);

'scan_out' will be
MSB of 'dout'; don't
need an extra pin
for 'scan_out'.

```
begin
  dout <= p_state;
  state: process(clk, reset)
  begin
    if (reset = '0') then p_state <= (others => '0');
    elsif (clk'event and clk = '1') then
      p_state <= n_state;
    end if;
  end process state;
```

When 'scan' is
asserted the scan
path is active.

```
process (scan,scan_in,load,p_state,din)
begin
  n_state <= p_state;
  if (scan = '1') then
    n_state(0) <= scan_in;
    for i in 3 downto 1 loop
      n_state(i) <= p_state(i - 1);
    end loop;
  elsif (load = '1') then
    n_state <= din;
  end if;
end process;
end behavior;
```

Register functions
normally when
'scan' is negated.

Adding Scan to *tlc_onehot.vhd*

⇒ Add 'scan', 'scan_in' to port list. 'scan_out' will be MSB of port 'stateout'.

```
entity tlc_onehot_scan is port (
  signal reset, car, timer, clk:      in std_logic;
  signal scan, scan_in:              in std_logic;
  signal stateout:                   out std_logic_vector(4 downto 0);
  signal highway_light,farm_light:   out std_logic_vector(1 downto 0);
  signal start_long_timer, start_short_timer: out std_logic
); end tlc_onehot_scan;
```

⇒ Add 'scan', 'scan_in' to sensitivity list of *process: state_machine*.

```
state_machine:process(scan, scan_in, reset, car, timer, p_state)
```

⇒ Add scan path in Architecture body:

```
if (scan = '1') then
  n_state(0) <= scan_in;
  for i in 4 downto 1 loop
    n_state(i) <= p_state(i - 1);
  end loop;
else
  if p_state(HG) = '1' then
    highway_light <= GREEN; farm_light <= RED;
    .... etc...
```

Register with TriState Output

```

library IEEE; use IEEE.std_logic_1164.all;

entity tsreg8bit is port ( signal clk, reset, load, en in std_logic;
    signal din:      in std_logic_vector(7 downto 0);
    signal dout:     out std_logic_vector(7 downto 0)
);
end tsreg8bit;

architecture behavior of tsreg8bit is
    signal n_state, p_state : std_logic_vector(7 downto 0);


begin
    dout <= p_state when (en = '1')
    else "ZZZZZZZZ";

    state: process(clk, reset)
    begin
        if (reset = '0') then p_state <= (others => '0');
        elsif (clk'event and clk = '1') then
            p_state <= n_state;
        end if;
    end process state;

    comb: process (p_state, load, din)
    begin
        n_state <= p_state;
        if (load = '1') then n_state <= din;
        end if;
    end process comb;
end behavior;
    
```

Make Z assignment to specify tristate capability.

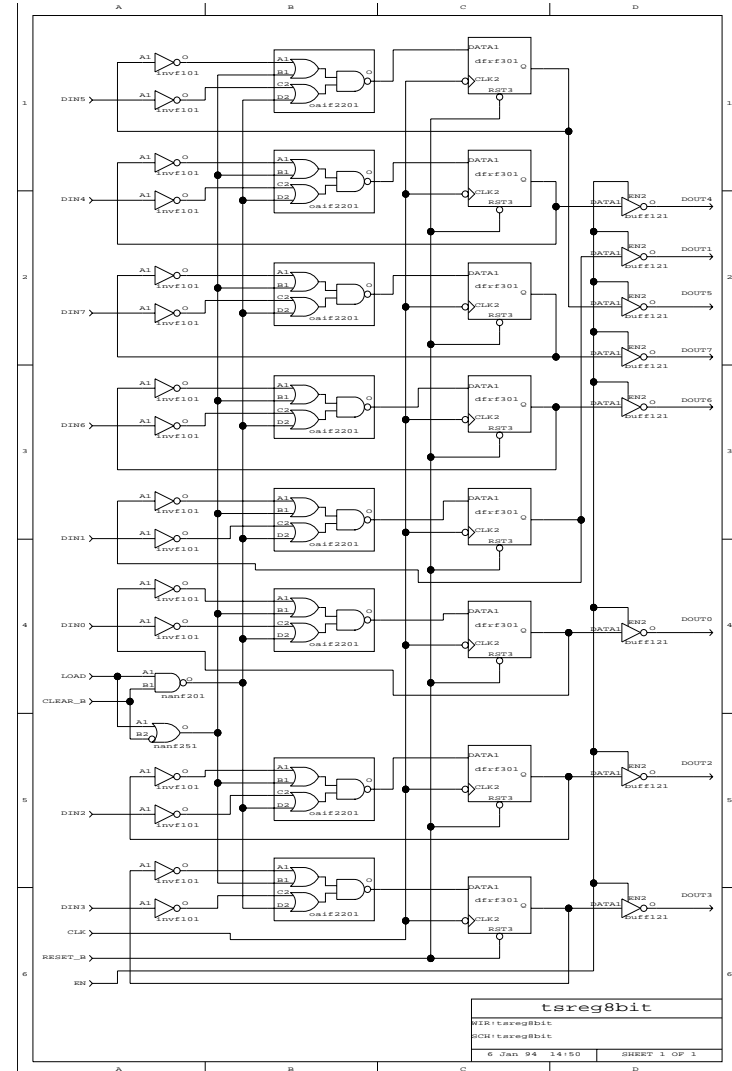Mapped to ITD stdcell library because Actel ACT1 does not have tristate capability.



Logic Synthesis with VHDL

System Synthesis

Bob Reese
Electrical Engineering Department
Mississippi State University

VHDL Packages

⇒ A VHDL *package* is a mechanism for collecting procedures, functions, constants, and components for future re-use.

⇒ A package contains a package *declaration* followed by a package *body*.

→ Package declaration

```
package package_name is
```

```
    { external constant, procedure, function,  
      component declarations }
```

```
end package_name;
```

→ Package body

```
package body package_name is
```

```
    { constant, procedure, function, component  
      definitions }
```

```
end package_name;
```

⇒ Any items in the package declaration are available for external use. There can be items in the package body which are not in the package declaration; these items are only available for use within the package.

Example VHDL Package

```

Library IEEE; use IEEE.std_logic_1164.all;

package iscas is

    procedure ripple_adder (a,b: in std_logic_vector; cin: in std_logic;
        sum: inout std_logic_vector; cout: out std_logic);

end iscas;

package body iscas is

    function xor3 (a,b,c: in std_logic) return std_logic is
    begin
        return (a xor b xor c);
    end xor3;

    procedure ripple_adder (a,b: in std_logic_vector; cin: in std_logic;
        sum: inout std_logic_vector; cout: out std_logic) is

        variable c: std_logic_vector((a'high-a'low+1) downto 0);
    begin
        c(0) := cin;
        for i in 0 to (a'high-a'low) loop
            sum(i+sum'low) := xor3 (a(i+a'low), b(i+b'low), c(i) );
            c(i+1) := (a(i+a'low) and b(i+b'low)) or
                (c(i) and (a(i+a'low) or b(i+b'low)));
        end loop;
        cout := c(c'high);
    end ripple_adder;

end iscas;

```

VHDL Functions

⇒ General form:

```

function function_name ( parameter list) return return_type is
    {variable declarations}
begin
    {sequential statements}
end function_name;

```

```

function xor3 (a,b,c: in std_logic) return std_logic is
begin
    return (a xor b xor c);
end xor3;

```

⇒ A VHDL function computes a return value based upon its parameter list.

- All parameters passed to a VHDL function must be of mode *in*; i.e, the function is not allowed to modify any of the function parameters.
- The default class of the elements in a parameter list for either procedures or functions is *variable*.
- Signals can be passed in the parameter list; in this case the parameter list would look like:
(signal a, b, c: std_logic)
- More on the difference between variables and signals will be given later.

VHDL Procedures

⇒ General form:

```
procedure procedure_name ( parameter list) is
  {variable declarations}
begin
  {sequential statements}
end procedure_name;
```

⇒ The **ripple_adder** procedure implements the ripple carry adder used in previous examples.

⇒ The ripple_adder procedure uses the local **xor3** function defined within the package.

```
sum(i+sum'low) := xor3 (a(i+a'low), b(i+b'low), c(i) );
```

⇒ For generality, the input parameters 'a' and 'b' as well as the output 'sum' are declared as *unconstrained* array types; i.e., no array bounds are given for the *std_logic_vector* type.

→ Allows any width vector to be passed as a parameter.

→ Array indices must be computed using the 'low attribute as an offset in order to achieve independence from the actual array indices which are passed in.

Signals vs Variables

⇒ Only signals are used as the connection ports for VHDL entities.

→ Variables are declared within process blocks, procedures, and functions.

→ Signals can only be declared within architecture bodies; they can be passed as parameters to functions and procedures.

⇒ Signals are assigned via "<=""; Variables are assigned via ":="".

⇒ From a simulation point of view:

→ Signals have events occurring on them and this event history is tracked via an internal event list.

→ Signal assignment can be delayed such as:

```
a <= '1' after 10 ns
```

→ Variable assignment is always immediate.

```
a <= '1';
```

→ Signals require more overhead in terms of storage and simulation time than variables. A general rule of thumb is to use variables wherever possible.

⇒ From a synthesis point of view, both variables and signals can turn into internal circuit nodes.

Carry_Select_Adder Procedure

```

procedure carry_select_adder
  (groups: iarray; a,b: in std_logic_vector; cin: in std_logic;
   sum: inout std_logic_vector; cout: out std_logic) is

  variable low_index, high_index :integer;
  variable temp_sum_a, temp_sum_b : std_logic_vector(sum'range);
  variable carry_selects :std_logic_vector(groups'range);
  variable carry_zero :std_logic_vector(groups'low to (groups'high-1));
  variable carry_one :std_logic_vector(groups'low to (groups'high-1));

begin
  low_index := 0;
  for i in groups'low to groups'high loop
    high_index := (groups(i)-1) + low_index ;
    if (i = 0) then      — first group, just do one ripple-carry
      ripple_adder (a(high_index downto low_index), b(high_index downto low_index),
        cin, sum(high_index downto low_index), carry_selects(0) );
    else
      — need to do two ripple carry adders then use mux to select
      ripple_adder (a(high_index downto low_index), b(high_index downto low_index),
        '0', temp_sum_a(high_index downto low_index), carry_zero(i-1));

      ripple_adder (a(high_index downto low_index), b(high_index downto low_index),
        '1', temp_sum_b(high_index downto low_index), carry_one(i-1));
    if (carry_selects(i-1) = '0') then
      sum(high_index downto low_index) := temp_sum_a(high_index downto low_index);
    else
      sum(high_index downto low_index) := temp_sum_b(high_index downto low_index);
    end if;
    carry_selects(i) := (carry_selects(i-1) and carry_one(i-1) ) or carry_zero(i-1);
  end if;
  low_index := high_index + 1;
end loop;
cout := carry_selects(groups'high);
end ripple_adder;

```

iscas Package Declaration

```

Library IEEE;
use IEEE.std_logic_1164.all;

package iscas is

  type IARRAY is array (natural range <>) of integer;

  procedure ripple_adder (a,b: in std_logic_vector; cin: in std_logic;
    sum: inout std_logic_vector; cout: out std_logic);

  procedure carry_select_adder
    (groups: iarray; a,b: in std_logic_vector; cin: in std_logic;
     sum: inout std_logic_vector; cout: out std_logic);
end iscas;

⇒ We need to declare an array type for integers; call this IARRAY.
  This type will be used to pass in an integer array to the carry_select_adder procedure; the integer array will be define the stage sizes for the adder.

⇒ Since xor3 is to be local to the iscas package; it is not in the package declaration. However, if it was to be made externally available, its declaration would be:

  function xor3 (a,b,c: in std_logic) return std_logic;

```

Using the *carry_select_adder* Procedure

```

Library IEEE;
use IEEE.std_logic_1164.all;
use work.iscas.all;

entity adder_cs is
port (
  signal a,b: in std_logic_vector (15 downto 0);
  signal cin: in std_logic;
  signal sum: out std_logic_vector(15 downto 0);
  signal cout: out std_logic
);
end adder_cs;

```

architecture behavior of adder_cs is

begin

process (a,b,cin)

variable temp_sum: std_logic_vector (sum'range);

variable temp_cout: std_logic;

constant groups: iarray(0 to 2) := (4,5,7); ←

begin

carry_select_adder(groups,a,b,cin,temp_sum, temp_cout);


sum <= temp_sum;

cout <= temp_cout;

end process;

end behavior;

 Define local constant array of integers to define the stage sizes for the adder. 4 + 5 + 7 = 16 bits. Must be a constant array so that stage sizes are known at compile time.



VHDL Generic lists

```
Library IEEE;
use IEEE.std_logic_1164.all;
use work.iscas.all;
```

```
entity adder_test is
generic ( N : integer := 16);
```

```
port (
  signal a,b: in std_logic_vector (N-1 downto 0);
  signal cin: in std_logic;
  signal sum: out std_logic_vector(N-1 downto 0);
  signal cout: out std_logic
);
end adder_test;
```

architecture behavior of adder_test is

```
begin
  process (a,b,cin)
    variable temp_sum: std_logic_vector (sum'range);
    variable temp_cout: std_logic;
    begin
      ripple_adder(a, b, cin, temp_sum, temp_cout);
      sum <= temp_sum;
      cout <= temp_cout;
    end process;
```

```
end behavior;
```

Generic declaration which is used to define the a,b,sum signal widths.

Default value is specified as 16.



VHDL Generic lists (cont.)

⇒ VHDL *generic* lists are used in entity declarations for passing static information.

→ Typical uses of generics are for controlling bus widths, feature inclusion, message generation, timing values.

⇒ A generic will usually have a specified default value; this value can be overridden via VHDL configurations or by vendor-specific back-annotation methods.

→ Generics offer a method for parameterizing entity declarations and architectures. Because the method of specifying generic values (other than defaults) can be vendor specific, generics will not be covered further in this tutorial.

Operator Overloading

Library IEEE; use IEEE.std_logic_1164.all;

package genmux is

— **2/1 version, 1 bit inputs**

function **mux** (a,b: std_logic; sel: std_logic) return std_logic;

— 2/1 version, N bit inputs

function **mux** (a,b: std_logic_vector; sel: std_logic) return std_logic_vector;

— **3/1 version, 1 bit inputs**

function **mux** (a,b,c: std_logic; sel: std_logic_vector) return std_logic;

— **3/1 version, N bit inputs**

function **mux** (a,b,c: std_logic_vector; sel: std_logic_vector) return std_logic_vector;

— **4/1 version, 1 bit inputs**

function **mux** (a,b,c,d: std_logic; sel: std_logic_vector) return std_logic;

— **4/1 version, N bit inputs**

function **mux** (a,b,c,d: std_logic_vector; sel: std_logic_vector) return std_logic_vector;

end genmux;

package body genmux is

function **mux** (a,b: std_logic; sel: std_logic) return std_logic is

variable y: std_logic;

begin

y := a;

if (sel = '1') then y := b; end if;

return(y);

end mux; — 2/1 version, 1 bit inputs

function **mux** (a,b: std_logic_vector; sel: std_logic) return std_logic_vector is

variable y: std_logic_vector(a'range);

begin

y := a;

if (sel = '1') then y := b; end if;

return(y);

end mux; — 2/1 version, N bit inputs

Operator Overloading (cont.)

function **mux** (a,b,c: std_logic; sel: std_logic_vector) return std_logic is
variable y: std_logic;

begin

y := '-'; — **Don't care for default state**

if (sel = "00") then y := a; end if; if (sel = "01") then y := b; end if;

if (sel = "10") then y := c; end if;

return(y);

end mux; — 3/1 version, 1 bit inputs

function **mux** (a,b,c: std_logic_vector; sel: std_logic_vector) return std_logic_vector is
variable y: std_logic_vector(a'range);

begin

y := (others => '-'); — **Don't care for default state**

if (sel = "00") then y := a; end if; if (sel = "01") then y := b; end if;

if (sel = "10") then y := c; end if;

return(y);

end mux; — 3/1 version, N bit inputs

function **mux** (a,b,c,d: std_logic; sel: std_logic_vector) return std_logic is
variable y: std_logic;

begin

y := d;

if (sel = "00") then y := a; end if; if (sel = "01") then y := b; end if;

if (sel = "10") then y := c; end if;

return(y);

end mux; — 4/1 version, 1 bit inputs

function **mux** (a,b,c,d: std_logic_vector; sel: std_logic_vector) return std_logic_vector is
variable y: std_logic_vector(a'range);

begin

y := d;

if (sel = "00") then y := a; end if; if (sel = "01") then y := b; end if;

if (sel = "10") then y := c; end if;

return(y);

end mux; — 4/1 version, N bit inputs

end genmux;

Test of 'mux' Function

```

Library IEEE;
use IEEE.std_logic_1164.all;
use work.genmux.all;

entity muxtest is
port (
  signal a,b,c: in std_logic;
  signal s_a: in std_logic_vector(1 downto 0);
  signal y: out std_logic;
  signal j,k,l: in std_logic_vector(3 downto 0);
  signal s_b: in std_logic_vector(1 downto 0);
  signal z: out std_logic_vector(3 downto 0)
);
end muxtest;

architecture behavior of muxtest is


begin

  y <= mux (a,b,c,s_a);
  z <= mux (j,k,l,s_b);

end behavior;

```

 The mux operator is overloaded; the correct mux function is chosen by doing template matching on the parameter lists.



BlackJack Dealer

⇒ This example will be a BlackJack Dealer circuit (example taken from *The Art of Digital Design*, Prosser & Winkel, Prentice–Hall).

⇒ One VHDL model will be written for the control and one for the datapath. A schematic will be used to tie these two blocks together.

→ Later, a VHDL structural model will be used to connect the blocks.

⇒ Control:

→ Four States:

Get — get a card

Add — add current card to score

Use — use an ACE card as 11

Test — see if we should stand or if we are broke

⇒ Datapath:

→ 5-bit register for loading score; needs a synchronous clear.


→ Mux for choosing between card value, plus 10 and minus 10.

→ Adder for adding card with current score.


→ ACE card detect (an ACE card has value '0001')

→ Comparator logic for checking is score is greater than 16 or greater than 21.


BlackJack Dealer Control

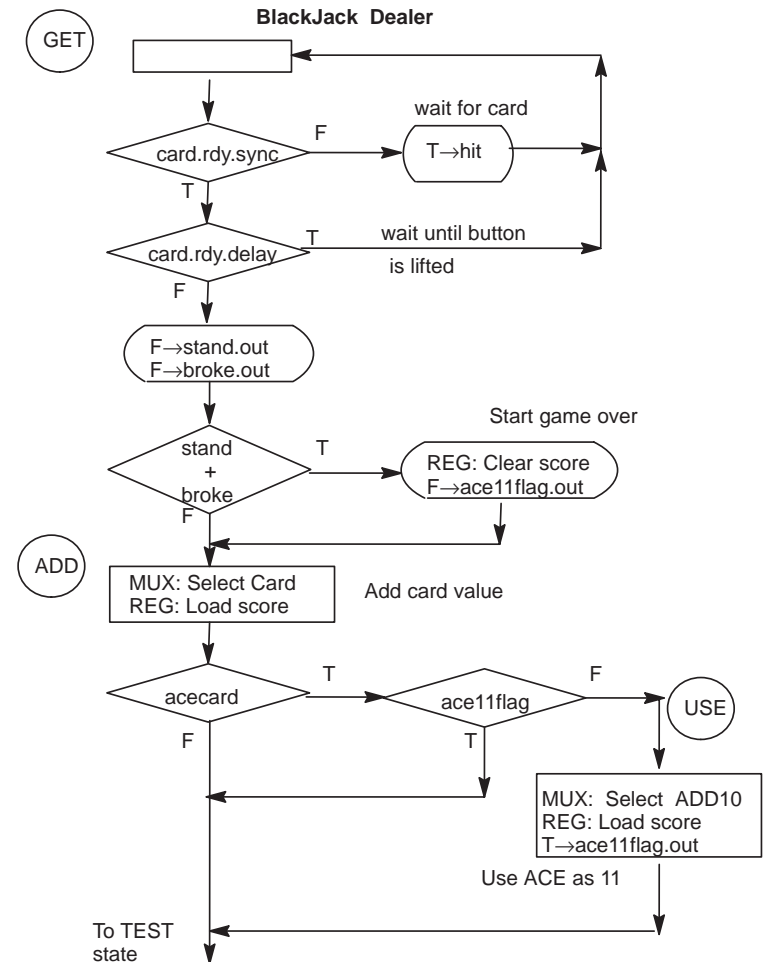

BlackJack Dealer Control (cont)

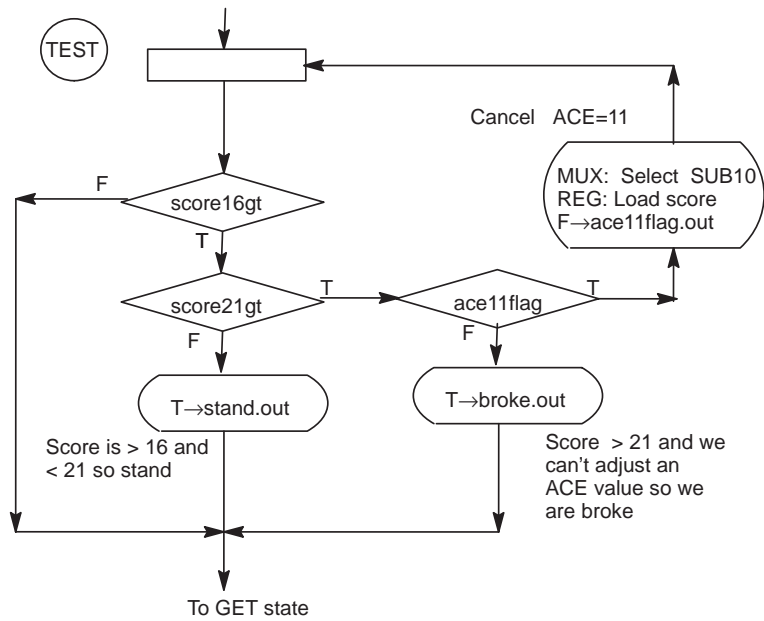

BlackJack Datapath

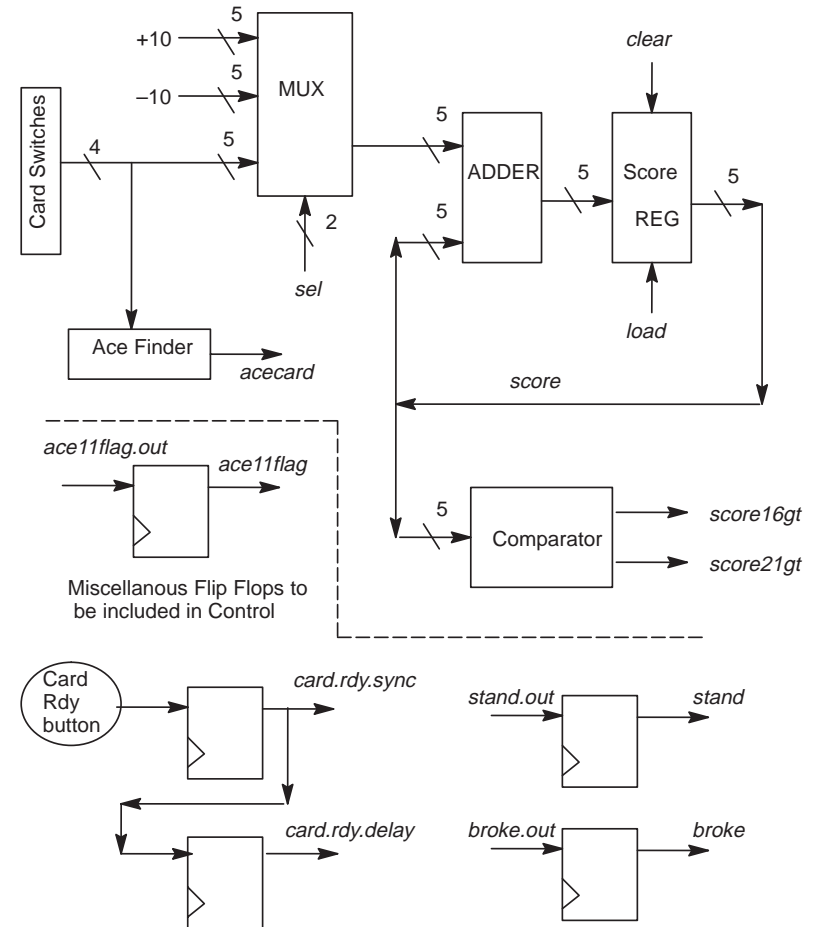

VHDL File for BlackJack Datapath

```
entity bjdpath is port (
  signal clk,reset_b, load, clear_b:      in std_logic;
  signal sel:                             in std_logic_vector(1 downto 0);
  signal card:                            in std_logic_vector(3 downto 0);
  signal acecard,score16gt,score21gt:    out std_logic;
  signal score:                           out std_logic_vector(4 downto 0)
);end bjdpath;
```

architecture behavior of bjdpath is

```
signal adder_out, score_in: std_logic_vector(4 downto 0)
mux_out, score_out : std_logic_vector(4 downto 0);
— temporary signal for carries
signal c: std_logic_vector (5 downto 0);
```

```
begin
score_state: process(clk, reset_b)
begin
if (reset_b = '0') then score_out <= "00000";
elsif (clk'event and clk = '1') THEN
  score_out <= score_in;
  END IF;
end process score_state;
```

```
— combinational logic for score register
score_in <= "00000" when (clear_b = '0') else
  adder_out when (load = '1') else
  score_out;
```

State process for
score register flip-
flops.

Combinational logic
for Score Register

VHDL File for BlackJack Datapath (cont.)

```
— adder process
— adder_out <= score_out + mux_out
adder:process (score_out, mux_out)
begin
  c(0) <= '0';
  for i in score_out'range loop
    adder_out(i) <= score_out(i) xor mux_out(i) xor c(i);
    c(i+1) <= (score_out(i) and mux_out(i)) or
      (c(i) and (score_out(i) or mux_out(i)));
  end loop;
end process adder;
mux_out <= "01010" when (sel = B"00") else
  "10110" when (sel = B"10") else
  '0' & card;
acecard <= '1' when (card = B"0001") else '0';
score <= score_out;
score16gt <= '1' when (score_out > B"10000") else '0';
score21gt <= '1' when (score_out > B"10101") else '0';

end behavior;
```

ADDER process

MUX for
card, plus 10,
minus 10.

Ace Finder

Comparators

VHDL File for BlackJack Control

```
entity bjcontrol is port (
  signal clk, reset_b, card_rdy, acecard: in std_logic;
  signal score16gt, score21gt: in std_logic;
  signal hit, broke, stand: out std_logic;
  signal sel: out std_logic_vector(1 downto 0);
  signal score_clear_b, score_load: out std_logic
); end bjcontrol;

architecture behavior of bjcontrol is
  

Entity declaration  
and State Assignments


  — declare internal signals here
  signal n_state, p_state : std_logic_vector(1 downto 0);
  signal ace11flag_pstate, ace11flag_nstate: std_logic;
  signal broke_pstate, broke_nstate: std_logic;
  signal stand_pstate, stand_nstate: std_logic;
  signal card_rdy_dly, card_rdy_sync: std_logic;

  — state assignments are as follows
  constant get_state: std_logic_vector(1 downto 0) := B"00";
  constant add_state: std_logic_vector(1 downto 0) := B"01";
  constant test_state: std_logic_vector(1 downto 0) := B"10";
  constant use_state: std_logic_vector(1 downto 0) := B"11";

  constant add_10_plus: std_logic_vector(1 downto 0) := B"00";
  constant add_card: std_logic_vector(1 downto 0) := B"01";
  constant add_10_minus: std_logic_vector(1 downto 0) := B"10";
```

VHDL File for BlackJack Control (cont.)

```
begin

  — state process to implement flag flip-flops and FSM state
  state: process(clk, reset_b)
  begin
    if (reset_b = '0') then p_state <= "00";
    elsif (clk'event and clk = '1') THEN
      p_state <= n_state;
      ace11flag_pstate <= ace11flag_nstate;
      broke_pstate <= broke_nstate;
      stand_pstate <= stand_nstate;
      card_rdy_dly <= card_rdy_sync;
      card_rdy_sync <= card_rdy;
    END IF;
  end process state;

  broke <= broke_pstate;
  stand <= stand_pstate;
```

State process to define flip-flops for various flags and finite state machine .

VHDL File for BlackJack Control (cont.)

```
comb: process (p_state, ace11flag_pstate, broke_pstate, stand_pstate,
acecard, card_rdy_dly, card_rdy_sync, score16gt, score21gt)
```

```
begin
sel <= B"00";
score_load <= '0'; score_clear_b <= '1';
hit <= '0'; n_state <= p_state;
ace11flag_nstate <= ace11flag_pstate;
stand_nstate <= stand_pstate; broke_nstate <= broke_pstate;
```

```
case p_state is
```

```
when get_state =>
```

```
    if (card_rdy_sync = '0') then hit <= '1';
    elsif (card_rdy_dly = '0') then
        stand_nstate <= '0'; broke_nstate <= '0';
        if (stand_pstate = '1' or broke_pstate = '1') then
            score_clear_b <= '0';
            ace11flag_nstate <= '0';
        end if;
        n_state <= add_state;
    end if;
```

*'get' and 'add'
states*

```
when add_state =>
```

```
    sel <= add_card; score_load <= '1';
    if (acecard = '1' and ace11flag_pstate = '0') then
        n_state <= use_state;
    else n_state <= test_state;
    end if;
```

VHDL File for BlackJack Control (cont.)

```
when use_state =>
```

```
    sel <= add_10_plus;
    score_load <= '1';
    ace11flag_nstate <= '1';
    n_state <= test_state;
```

```
when test_state =>
```


```
    if (score16gt = '0') then
        n_state <= get_state;
    elsif (score21gt = '0') then
        stand_nstate <= '1';
        n_state <= get_state;
    elsif (ace11flag_pstate = '0') then
        broke_nstate <= '1';
        n_state <= get_state;
    else
        sel <= add_10_minus;
        score_load <= '1';
        ace11flag_nstate <= '0';
    end if;
```

*'use' and
'test' states*


```
when OTHERS => n_state <= p_state;
```

```
end case;
end process comb;
end behavior;
```

Top Level Schematic for Dealer

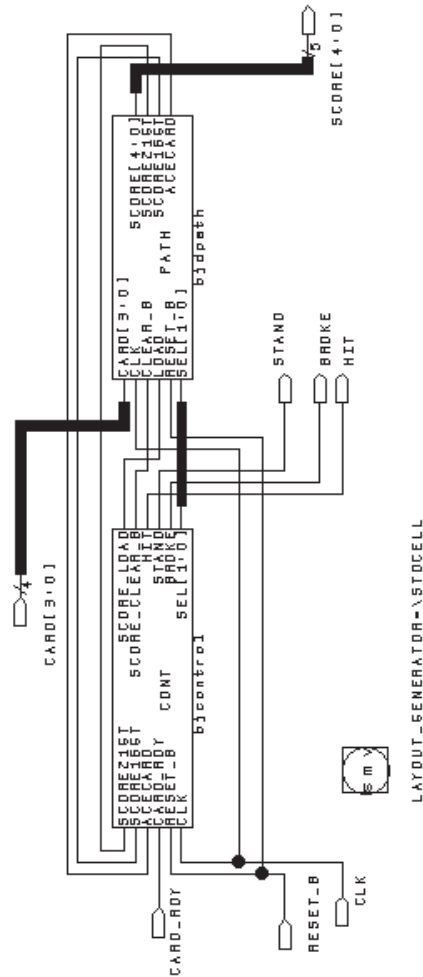

Blackjack Dealer Simulation

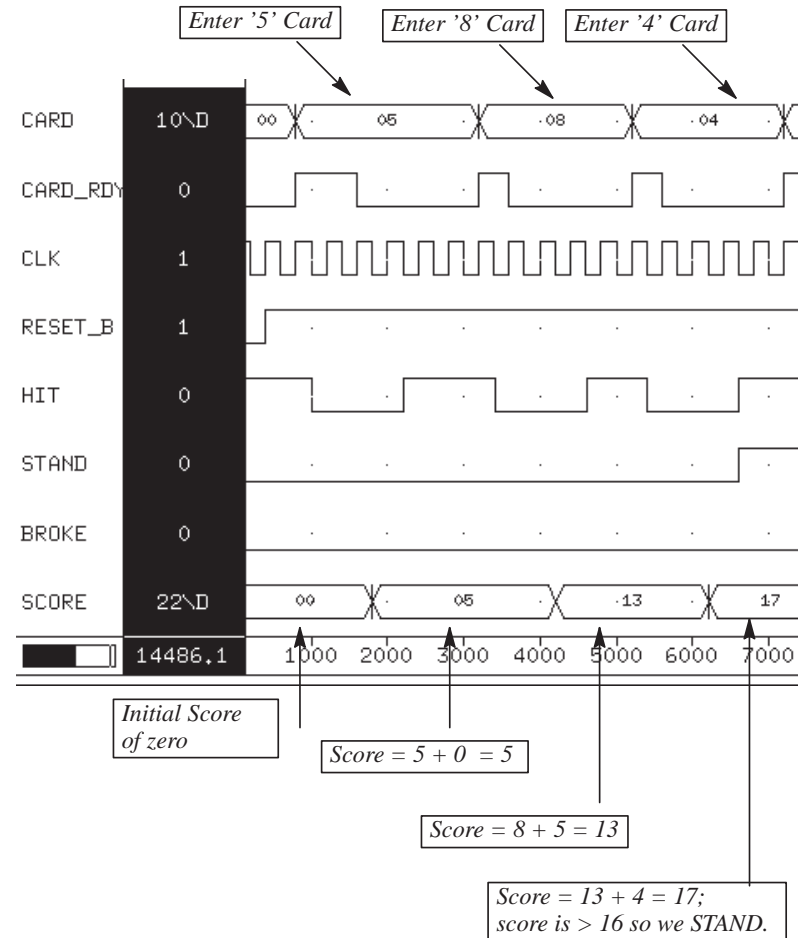

Structural VHDL for BlackJack Player

```
entity bj_struct is port (
  signal reset_b, clk, card_rdy :    in std_logic;
  signal card:                      in std_logic_vector(3 downto 0);
  signal stand, broke, hit:         out std_logic;
  signal score: out                  std_logic_vector(4 downto 0) );
end bj_struct;
```

← *Normal entity declaration.*

```
architecture structure of bj_struct is
  component bjcontrol port (
    signal clk, reset_b:           in std_logic;
    signal card_rdy, acecard:      in std_logic;
    signal score16gt, score21gt:   in std_logic;
    signal hit, broke, stand:      out std_logic;
    signal sel:                   out std_logic_vector(1 downto 0);
    signal score_clear_b:         out std_logic;
    signal score_load:            out std_logic );
  end component;
```

← *Need a component declaration for each different type of component used in the schematic*

```
component bjpath
  port (
    signal clk, reset_b:           in std_logic;
    signal load, clear_b:         in std_logic;
    signal sel:                   in std_logic_vector(1 downto 0);
    signal card:                  in std_logic_vector(3 downto 0);
    signal acecard, score16gt:    out std_logic;
    signal score21gt:            out std_logic;
    signal score:                 out std_logic_vector(4 downto 0) );
  end component;
```

Structural VHDL for BlackJack Player (cont)

```
signal load_net, clear_net, acecard_net : std_logic;
signal sel_net : std_logic_vector (1 downto 0);
signal s21gt_net, s16gt_net: std_logic;
```

← *Internal signal declaration for those nets not connected to external ports.*

```
begin
  c1: bjcontrol
  port map (
    clk => clk,
    reset_b => reset_b,
    card_rdy => card_rdy,
    acecard => acecard_net,
    score16gt => s16gt_net,
    score21gt => s21gt_net,
    hit => hit, broke => broke, stand => stand,
    sel => sel_net,
    score_clear_b => clear_net,
    score_load => load_net);
```

← *Each component used in the design is given along with its port map.*

'c1' is the component label, 'bjcontrol' gives the component type.

```
c2: bjpath
  port map (
    clk => clk,
    reset_b => reset_b,
    load => load_net,
    clear_b => clear_net,
    sel => sel_net,
    card => card,
    acecard => acecard_net,
    score16gt => s16gt_net,
    score21gt => s21gt_net,
    score => score );
```

← *Only two components in this design.*

```
end structure;
```

Results of *bj_struct* Synthesis

