

Due by online submission **Monday** 4/11/2015 (Tuesday 9am)

- [illegible]

- a. Calculate and tabulate:
 - i. the overdrive voltage and current in all devices. For this step you may assume that $\lambda=0$. The simplest order may be Mb1 through Mb6, then M1 through M5.
 - ii. Calculate the bias voltages on all nodes, assuming $V_{I,CM}=1V$. Specifically: tail, G2, G3, G5, G6, S3B, S4AB, and out.
 - iii. the g_m and r_o parameters for M1 through M5
 - b. Calculate G_m , R_o , and A_v
 - c. Calculate the input common mode range and output swing.
 - d. What is the minimum voltage that could be used on the gates of M3AB to still keep M2AB in saturation? If you used that voltage, what is the new input common mode range and output swing?
 - e. If the load capacitance is 1pF (roughly the same as the input capacitance),
 - i. what are the pole and unity gain frequencies?
 - ii. What is the phase margin?
 - iii. What are the frequencies of the pole/zero doublets from the current mirror?
3. In Figure 2 of this Analog Devices discussion on voltage regulators
<http://www.analog.com/en/design-center/landing-pages/001/fundamentals-of-ldo-design-and-applications.html>
- a. Estimate the low-frequency loop gain T in terms of the op-amp voltage gain A_o , g_m of the pass transistor, and load resistance R_L (not shown in the figure).

- b. Why does the SENSE value connect to the positive input of the op-amp? Is this positive feedback?
4. For the circuit in figure 6.9 in the book
 - a. what ratios of C_2 to C_1 are needed to make a variable gain amplifier with gain equal to any integer between 1 and 8?
 - b. for a given open-loop op-amp gain A , which of the closed-loop gains above has the worst gain error? (you may assume that $C_p=0$)
 - c. if the desired closed-loop gain accuracy is 0.4% regardless of gain setting, what is the minimum open-loop gain necessary for the op-amp?
 - d. if the amplifier must settle to within 0.4% of the correct value within 10us, what is the minimum unity gain bandwidth of the op-amp?
5. In the TI document on SAR ADCs,
<http://www.ti.com.cn/cn/lit/an/slyt176/slyt176.pdf>
 - a. does the comparator compare at ground or the top rail?
 - b. Assuming a single-sided supply ($V_{DDA}, 0$) does the voltage on the inputs to the comparator stay between the supply rails?
6. [ee240A] For the amplifier in problem 2, how does performance change
 - a. if the bias current drops to 1uA and all devices are biased at roughly $V_{gs}=V_t$?
 - b. if the bias current remains 100uA, but the length of all devices is changed to 14nm, and the widths vary from 200nm to 400nm as appropriate for a current density of 0.5mA/um? Use your answers to problem 4 homework 2. Assume that the load capacitance is comparable to the input capacitance (which is?).