

Midterm Friday in class + 30 min 1:10-2:30


1 page, 2 sides notes

Extra OH today after class

Tues 4:30-5:30

RHP zero


Biasing

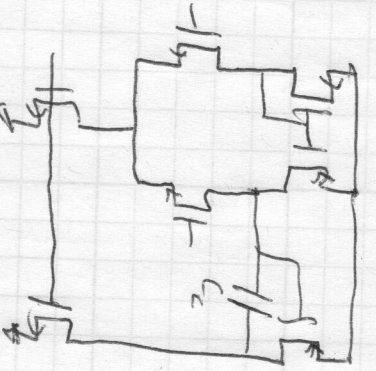

$$\omega_z = -\frac{g_{m2}}{C_c}$$

$$\omega_u = \frac{g_{m1}}{C_c}$$
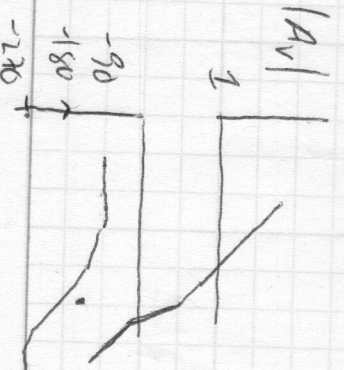
$$\omega_{p2} \approx \frac{g_{m2}}{C_1 + C_2 + \frac{C_1 C_2}{C_c}}$$




RHP zero complicates design

make $G_{m2} \gg G_{m1}$ costs power

make $C_c \gg C_2$ costs BW

RHP zero

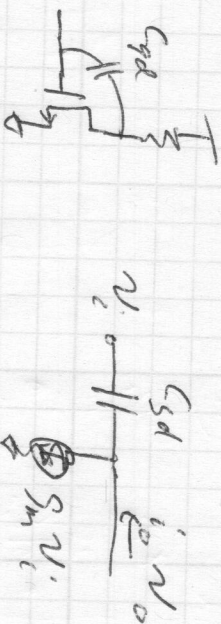


$$G_m: i_o = g_m v_i + s C_{gd} (v_o - v_i)$$

$$= g_m \left(1 - \frac{s C_{gd}}{g_m}\right) v_i$$

$$G_m = g_m \left(1 + \frac{s}{\omega_z}\right) \quad \omega_z = -\frac{g_m}{C_{gd}}$$

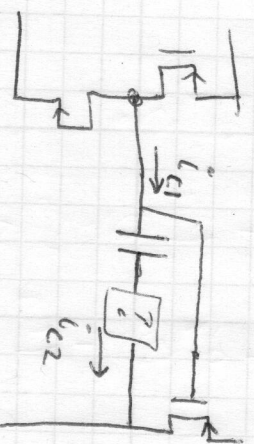
→ need C_c to split poles, compensate op-amp.
→ want to get rid of feedforward current that causes RHP zero.




$i_{c1} = s C_c (v_{o1} - v_{o2}) = s C_c (1 - A_{v2}) v_{o1}$ "good current"
 i_{c2} fights g_{m4} "bad current" (feedforward)

Simplest: $R_2 = \frac{1}{g_{m4}}$ and $|i_{c2}|$ is always $< g_{m2} v_i$ in G_m calc.

Supply-independent Biasing

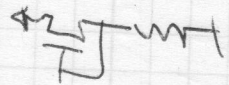

Simple
Varies a lot w/ PVT

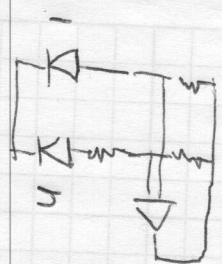

Bandgap voltage ~ constant
Few mV over Temp
What biases the bandgap?

If $I_1 = I_2$ then $V_{ov1}^2 = K(V_{ov1} - I_2 R)^2$


$K = 4$
 $I_2 R = V_{ov1}$

$V_{ov1} = \sqrt{K} (V_{ov1} - I_2 R)$


$(1 - \frac{1}{\sqrt{K}}) V_{ov1} = I_2 R$

e.g. $K = 4$ $I_2 R = \frac{1}{2} V_{ov1}$


$V_{ov2} = \frac{1}{2} V_{ov1}$

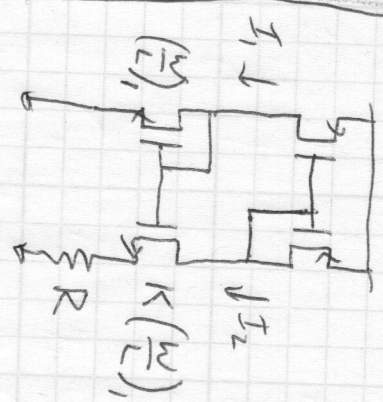

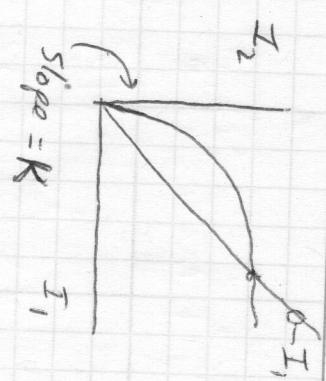$I_1 = \frac{\mu_n C_{ox}}{2} (\frac{W}{L})_1 (V_{ov1})^2$
 $I_2 = \frac{\mu_n C_{ox}}{2} K (\frac{W}{L})_1 (V_{ov1} - I_2 R)^2$




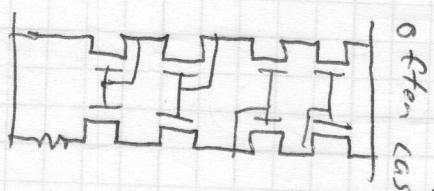$g_{m1} = \frac{2 I_1}{V_{ov1}} = \frac{2 I_2}{2 I_2 R} = \frac{1}{R}$ nice!



Often cascaded to get better mirror performance (supply rejection)

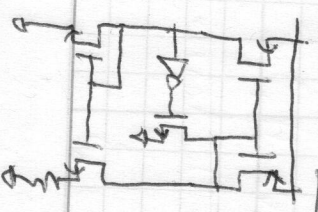Startup issues: $I_1 = I_2 = 0$ is an equilibrium. Should be unstable b/c



necessary? cost?