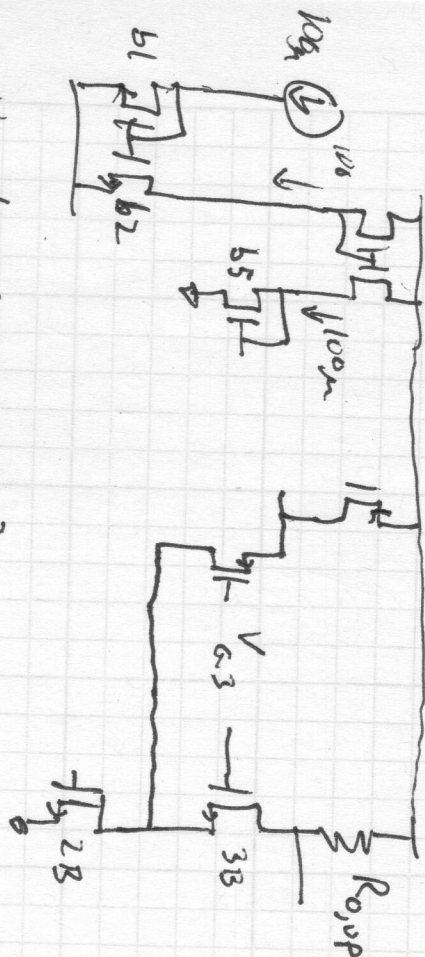




How to size M65?

What is $V_{G3,min}$?

Theoretically: $\left(\frac{W}{L}\right)_{b5} = \frac{1}{4} \left(\frac{W}{L}\right)_{b1}$

$\Rightarrow V_{ovb5} = 2 V_{ovb1}$

better to play it safe and use at least 5:1

If not quadratic

- choose based on appropriate model
- verify w/ simulation

$V_{D2B,min} = V_{ov2}$
 $V_{G3,min} = V_{ov2} + V_{th} + V_{ov3} = V_{th} + 2V_{ov}$

Assuming $I_{D55} = I_{D51}$ then
 $\left(\frac{W}{L}\right)_{b5} V_{ovb5}^2 = \left(\frac{W}{L}\right)_{b1} V_{ovb1}^2$

$V_{ovb5} = \sqrt{\frac{(W/L)_{b1}}{(W/L)_{b5}}} V_{ovb1}$

Poles of sources: most are low impedance $\sim \frac{1}{g_m}$

so high freq $\frac{1}{2C_{gs}}$

source of M_{B3} that is high impedance at low freq.

Pole of S_{B3} : when impedance of

capacitance $\approx \frac{1}{\omega 2C_{gs3}}$

is equal to the impedance "looking up"

