
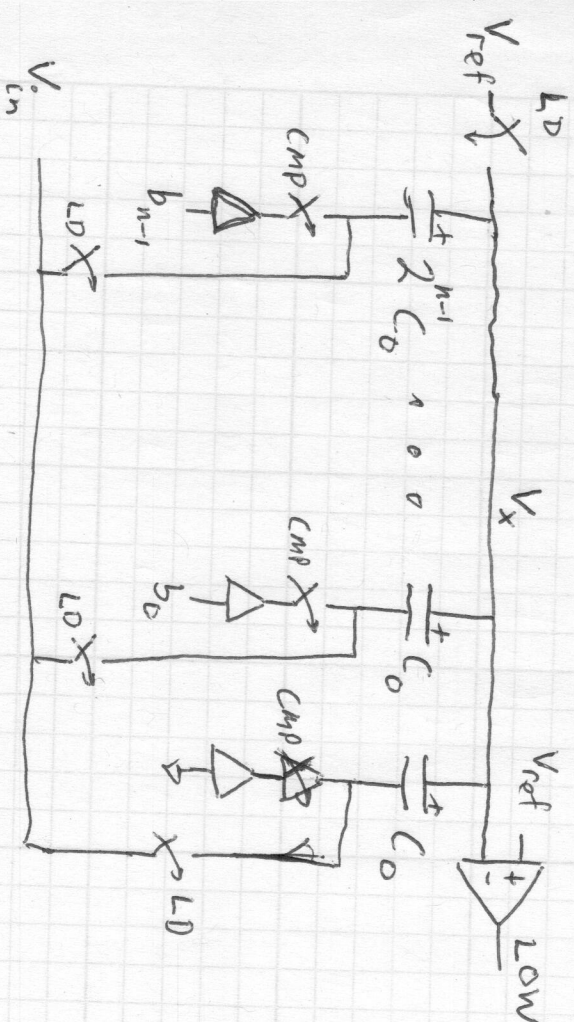


ADC
PGA
Switches

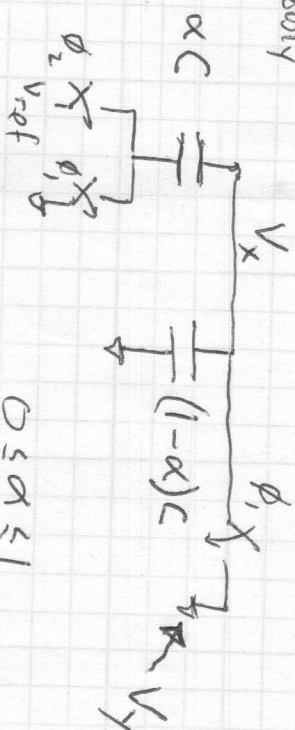

Previously




$$\phi_2: V_x = \alpha V_{ref}$$

use binary array to create α

if $V_y \neq 0$ then

$$\phi_2: V_x = \alpha V_{ref} + V_y$$


LD phase:

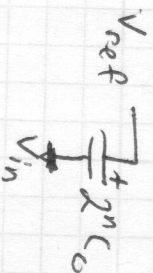

$$Q_x = (V_{ref} - V_{in}) 2^n C_0$$

once LD goes low, Q_x fixed

CMP phase:

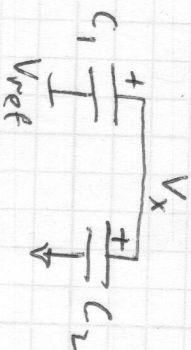


$$\begin{aligned} Q_{x+} &= Q_{x+} + Q_{z+} \\ &= C_1 (V_x - V_{ref}) + C_2 V_{ref} \\ &= (C_1 + C_2) V_x - C_1 V_{ref} \end{aligned}$$

Must be same charge as above $(V_{ref} - V_{in}) 2^n C_0$



$$Q_{x,LD} = Q_{x,comp} \Rightarrow (V_{ref} - V_{in}) \frac{C_1 + C_2}{2C_0} = (C_1 + C_2) V_x - C_1 V_{ref}$$

$$V_{ref} - V_{in} = V_x - \frac{C_1}{C_1 + C_2} V_{ref}$$
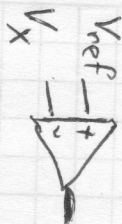
$$V_x = V_{ref} + \frac{C_1}{C_1 + C_2} V_{ref} - V_{in}$$


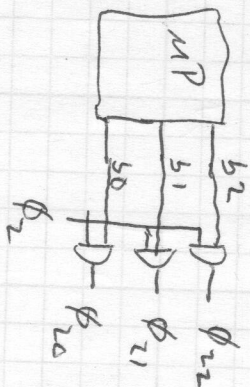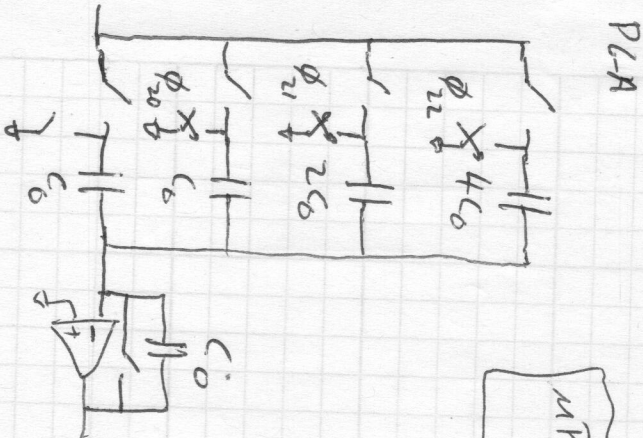
$$V_{id} = V_{ref} - V_x = V_{in} - \frac{C_1}{C_1 + C_2} V_{ref} = V_{in} - \frac{B}{2^n} V_{ref}$$



note that V_x can go above V_{ref} .

Worst case: $V_{in} = 0$ 1st SAR guess is 10000...D

$$\Rightarrow V_x = V_{ref} + \frac{1}{2} V_{ref}$$

possibly challenging for design of / switch

$$V_{ref} \xrightarrow{LD} 1.5 V_{ref}$$

switches



modelled as a resistor $\approx$ const current

$$V_c(t) = V_0 e^{-t/\tau} \quad \frac{dV_c}{dt} = \frac{-I}{C} = \text{const}$$

