

Project

ADC clock edges

Sighs this week
Roll week


electronic turn-in

Extra OH

High-swing cascode has

DRUG-
speed vs. L

Compare to NMOS biasing

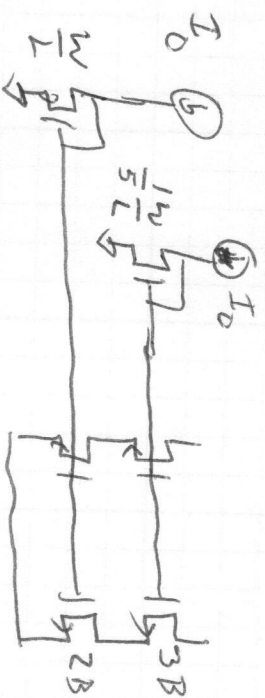


the source of M3B is just over
 V_{ov2B} above ground.

Much better swing.

High swing cascode biasing

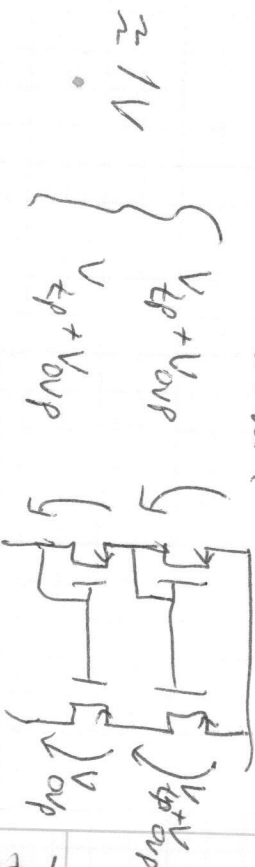
Problem: diode connected cascodes cause
headroom headache



the source of M4A is stuck at
 $V_{tp} + V_{ovp}$ away from V_{DD}

Can we do the same w/ ~~PMOS~~ mirrors?

Consider

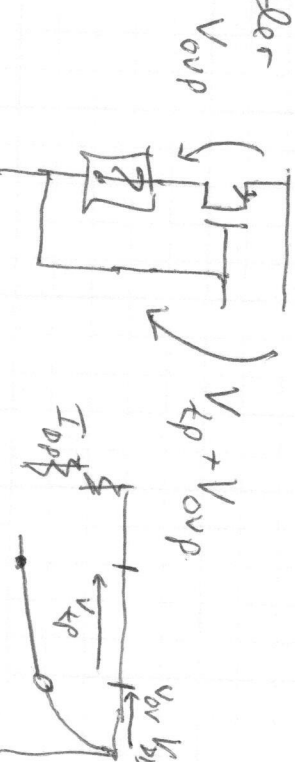

what could go in the box?

Resistor

Battery


Diode

Anything that lets current down
with less than V_{tp} voltage drop

140

165p


W14L

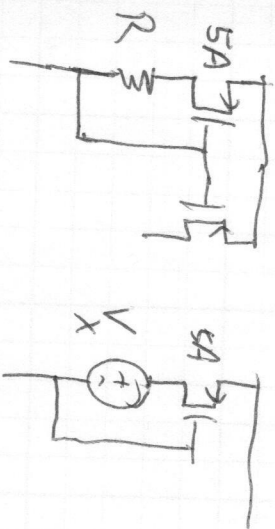


Q: How big can R or V_x be and still have $5A$ in saturation?

A: $I_{D5A} R < V_{tp}$ $V_x < |V_{tp}|$

Differential AEC

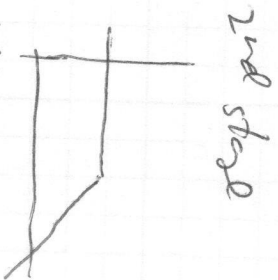

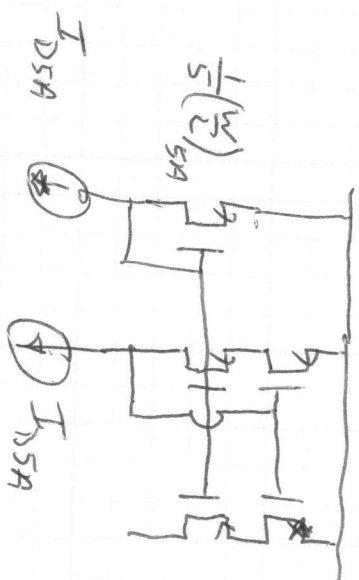need either
op-amp phase considerations
→ $V_{p2} A_{v1} A_{v2}$
→ $V_{p2} A_{v1} A_{v2}$
or put op-amp pole at very low freq, some pole splitting



Speed

$$V_i + \sqrt{2} V_o + \sqrt{2} V_i$$

unity gain frequency for ω transit during a way of itself.

$$A_v = g_m r_o$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov}$$

$$\omega_p = \frac{1}{r_o C_{gs}}$$

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

$$\omega_u = \frac{g_m}{C_{gs}}$$

$$\omega_u = \frac{3 \mu_n}{2} \frac{V_{ov}}{L^2} = \frac{3}{2} \mu_n \frac{V_{ov}}{L} \frac{1}{L}$$

$$\approx \frac{1}{\tau}$$

$$\tau = \text{transit time} = \frac{L}{\text{velocity}}$$

$$\omega_u = \frac{E}{\hbar} \frac{1}{\text{velocity}}$$

In scattering limited case

$$I_D = \mu C_{ox} V_{sc} W$$

$$g_m = \mu C_{ox} V_{sc}$$

$$\omega_n = \frac{g_m}{C_{gs}} = \frac{\mu C_{ox} V_{sc}}{\frac{2}{3} \mu L C_{ox}} = \frac{3}{2} \frac{V_{sc}}{L}$$

ω_T = transit frequency