

Midterm next Friday

1 page notes, 2 sides
no calculators, cell phones, ...

HM3 V_L-fixed

CMOS inverter

$$A_{vo}, \omega_p, \omega_L \Leftrightarrow G_m, R_o, C_L \Leftrightarrow g_m, r_o, C_{gs}, C_{gd}$$



last time

$$\frac{\omega_L}{\omega_p} = \frac{4\mu}{1\mu} \quad \text{vs.} \quad \frac{\omega_L}{\omega_p} = \frac{400\mu}{1\mu}$$

$$V_{ov} = 1V \quad \xrightarrow{\text{smaller } V_{ov} \text{ @ const current}} \quad V_{ov} = 0.1V$$

smaller V_{ov}
@ const current
→
higher gain
wider BW

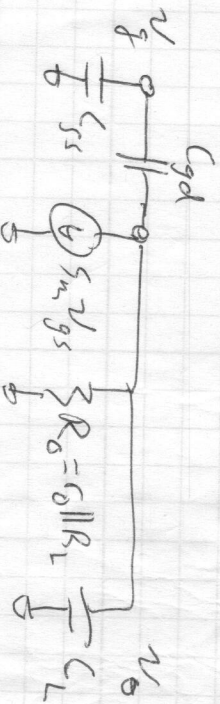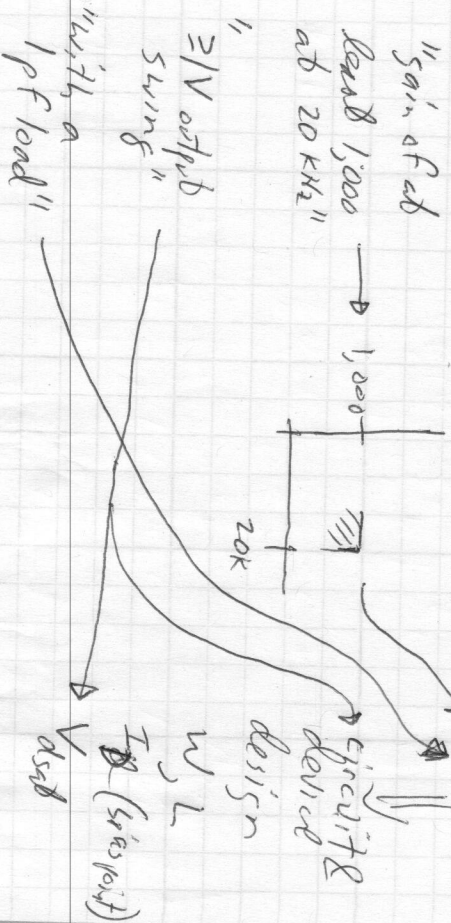Specifications $\Rightarrow$ freq response $\Rightarrow$ amp parameters




low freq: driving R_o : $-g_m R_L$




high freq: driving C_L : $-\frac{g_m}{j\omega C_L}$

highest freq: C_{gd} driving C_L : $\frac{C_{gd}}{C_{gd} + C_{gs}}$

linearize

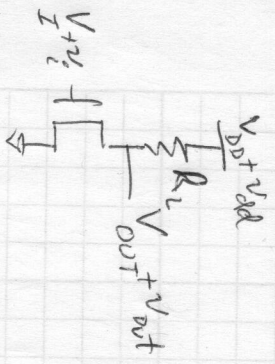

bias point

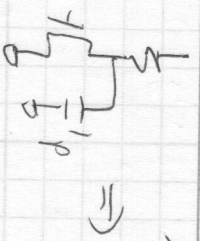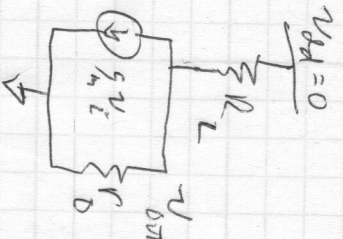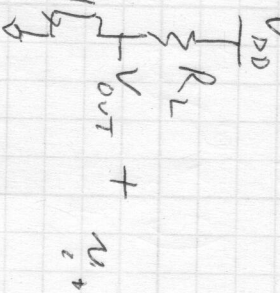

$$KCL @ v_0 \quad g_m v_i + \frac{1}{R_L} v_0 + s C_L v_0 = 0$$

$$\Rightarrow \frac{v_0}{v_i} = \frac{-g_m R_L}{1 + s R_L C_L} = \frac{A_{vo}}{1 + s/\omega_p}$$

$$|A_{vo}| = g_m R_L$$


$$\omega_p = \frac{1}{R_L C_L}$$

$$\omega_u \approx \frac{g_m}{C_L}$$

effect of

increasing R_L

$A_{vo} \uparrow$ $\omega_p \downarrow$

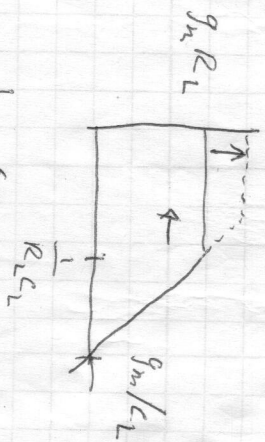


increasing C_L

$\omega_p \downarrow$ $\omega_u \downarrow$




increasing g_m


$A_{vo} \uparrow$ $\omega_u \uparrow$

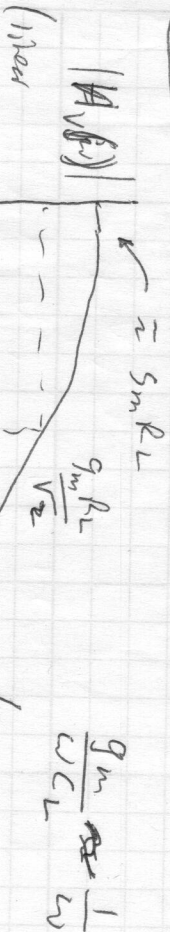

linear scales not so useful

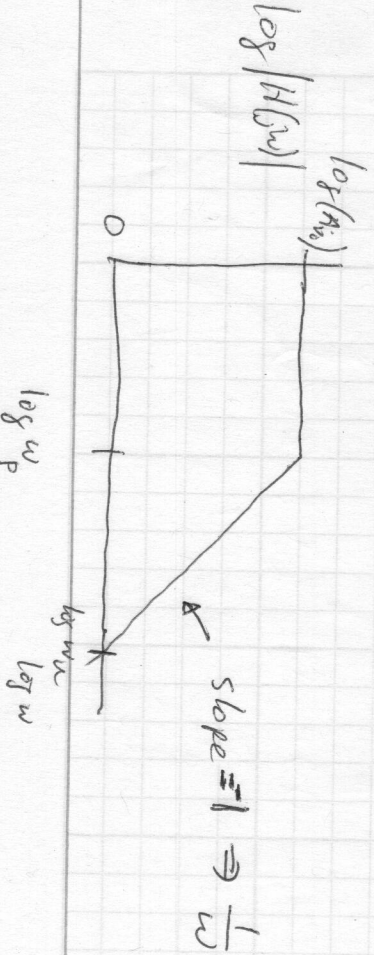

bias point

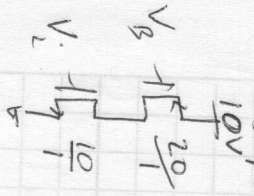


$$\mu_n C_{ox} = 50 \frac{\mu A}{V^2}$$

$$\lambda = 0.05 V^{-1}$$

$$|V_T| = 2V$$

$$\mu_p C_{ox} = 25 \frac{\mu A}{V^2}$$

$$V_{DD} = 10V$$

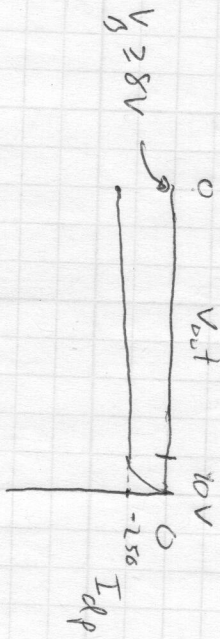


$$V_B = 7V \quad -I_{dp} = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L} \right)_p \left(V_{gs} - V_{tp} \right)^2 \left(1 + \lambda V_{ds} \right)$$

What V_I do we need if $V_B = 6V$?

$$I_{DN} = \frac{\mu_n C_{ox}}{2} V_{ov}^2 \left(1 + \lambda V_{Ds} \right) = \frac{250 \mu A}{V^2} V_{ov}^2 \left(1 + \frac{V_{Ds}}{20V} \right)$$


Pick $V_{ov} = 2V \Rightarrow V_{gs} = 4V$
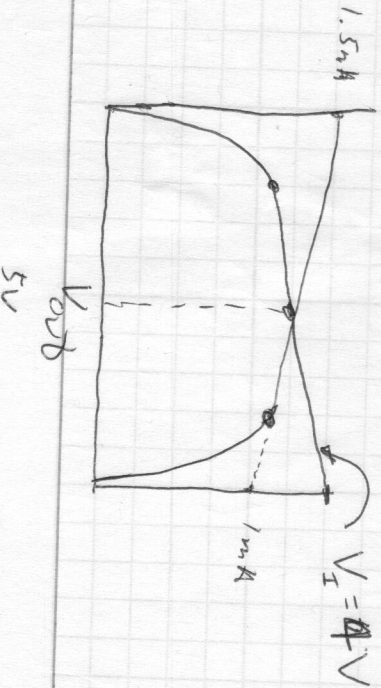
$$I_{DN} = 1mA \left(1 + \frac{V_{Ds}}{20V} \right)$$



$$|I_{Dp}| = \left(250 \frac{\mu A}{V^2} \right) (-1V)^2 \left(1 + 0.05 \frac{1}{V} (V_{ovt} - 10V) \right)$$

$$= 250 \mu A \left(1 + \frac{|V_{Dsl}|}{20} \right)$$

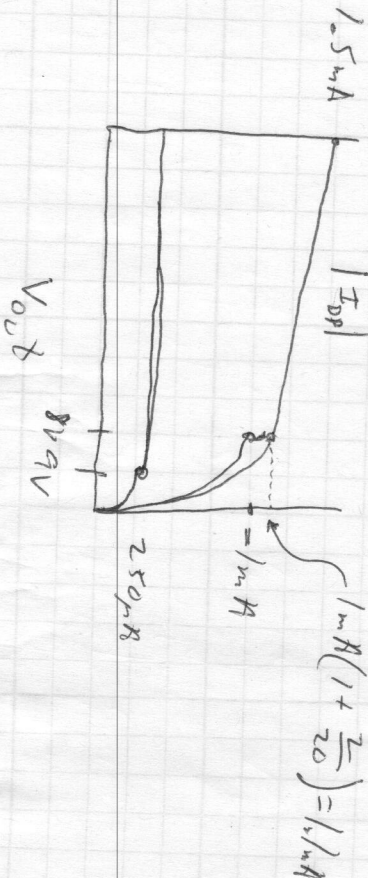

Upper limit of bias adjustment

$$I_{DN} = 1mA \left(1 + \frac{V_{Ds}}{20V} \right) \quad I_{Dp} = 1mA$$

$$= 250 \frac{\mu A}{V^2} V_{ovn}^2 \left(1 + \frac{8V}{20V} \right) = 1.01mA \approx I_{Dp}$$

$$V_{ov} = \sqrt{\frac{1.01mA}{0.25 \frac{\mu A}{V^2} (1.24)}} \approx 1.77V, V_I = 3.77V$$

Lower limit

$$I_{DN} = 250 \frac{\mu A}{V^2} V_{ovD}^2 \left(1 + \frac{2V}{20V} \right) = 1mA \left(1 + \frac{8V}{20V} \right)$$

$$V_{ov} = \sqrt{\frac{1.4mA}{0.25 \frac{\mu A}{V^2} (1.1)}} = 2.26V, V_I = 4.26V$$

$$A_V = \frac{A_{V_{ovt}}}{A_{V_{In}}} = \frac{8-2V}{3.77-4.26} = -12$$