

Lab 3


HW 6

2 stage

source/sink current

(part 1: later we'll see how C_c plays)

poles have under feedback

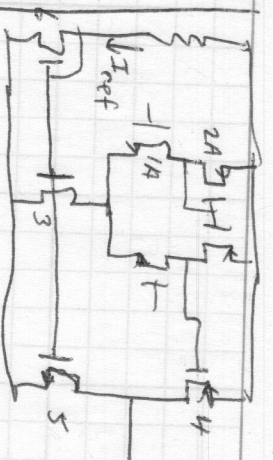

last time: input cm rgt, output swing

Specs on these translate to V_{ov} constraints

output current

$$\text{Sink: } \left(\frac{W}{L}\right)_5 I_{ref} \left(\frac{W}{L}\right)_6$$

Max source current?

$$|I_{d4}| - I_{D5}$$

constant

depends on output of 1st stage (swing)

How big to make M_4 ?

$$\text{Bias point: } V_{G4} = V_{G2A} = V_{DD} - |V_{tp}| - |V_{ov2}|$$

$$\text{Choose } V_{ov4} = V_{ov2}$$

$$|I_{D2A}| = \frac{1}{2} I_{tail}$$

$$|I_{D4}| = |I_{D5}| = |I_{tail}| \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3} 2 I_{D2A}$$

$$\text{SO } \left(\frac{W}{L}\right)_4 = 2 \left(\frac{W}{L}\right)_{2A} \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3}$$

Feedback

- improves linearity, gain accuracy, output resistance, input impedance, ...
- but can cause instability



$$V_o = A(V_i - V_f) = A(V_i - FV_o)$$

$$(1 + AF)V_o = AV_i$$

$$\frac{V_o}{V_i} = \frac{A}{1 + AF} \approx \frac{1}{F} \text{ if } AF \gg 1$$



Poles move under feedback:

can be good (e.g. increased bandwidth)
or bad (instability)


EX: single pole amplifiers

$$A = \frac{A_o}{1 + s/\omega_p}$$

$\rightarrow$ $\frac{1}{1 + s/\omega_p}$

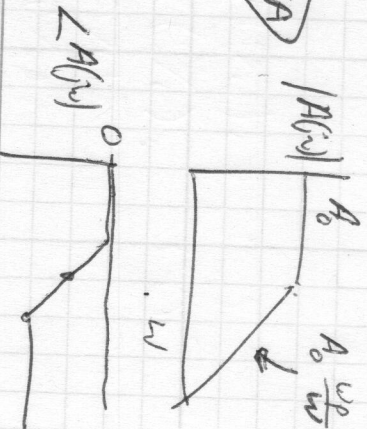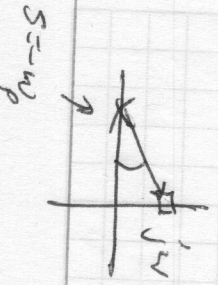

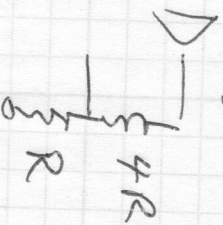F usually comes from a ratio of passives, which can be quite accurate



"R" might vary w/ temperature, process
but $\frac{R}{R + 4R} = \frac{1}{5}$ is quite accurate ~ 0.1% error


in feedback

$$A_{CL} = \frac{A}{1 + AF} = \frac{\frac{A_o \omega_p}{s + \omega_p}}{1 + \frac{A_o F \omega_p}{s + \omega_p}} = \frac{A_o \omega_p}{s + \omega_p + A_o F \omega_p}$$

$$= \frac{A_o \omega_p}{(A_o F \omega_p + \omega_p) \left(1 + \frac{s}{\omega_{pCL}}\right)} = \frac{A_o \omega_p}{s + \omega_p (1 + A_o F)}$$

$$\omega_{pCL} = (1 + A_o F) \omega_p$$
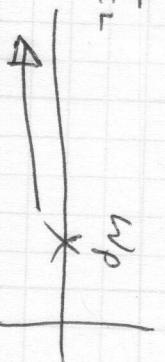
$$= \frac{A_o}{1 + A_o F} \cdot \frac{1}{1 + \frac{s}{\omega_{pCL}}}$$



$$A_{cl}(j\omega) = \begin{cases} \frac{A_0}{1 + A_0 f} \approx \frac{1}{f} & \omega \ll \omega_{pCL} \\ \frac{1}{f} \frac{1}{1 + j} & \omega = \omega_{pCL} \\ \frac{A_0 \omega_p}{j\omega} & \omega \gg \omega_{pCL} \end{cases}$$

Same as open-loop
above ω_p !