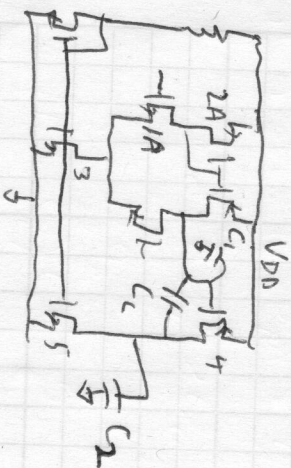


Compensation pole splitting

Midterm Friday April 1 10:10 - 2:30



$$A_{vo} = G_{m1} R_{o1} G_{m2} R_{o2}$$

with $C_c \neq 0$, both poles move

from 9.31 in book
magic!
 ω_{p1} goes down, ω_{p2} goes up!

if $C_c = 0$

$$\omega_{p1} = \frac{1}{R_{o1} C_1}$$

$$\omega_{p2} = \frac{1}{R_{o2} C_2}$$

uncompensated

$$\omega_{p1c} \approx \frac{1}{R_{o1}(G_{m2} R_{o2} C_c)}$$

$$\omega_{p2c} \approx \frac{G_{m2}}{C_1 + C_2 + \frac{C_1 C_2}{C_c}}$$

$$\approx \omega_{u2}$$

Compensation

change circuit to move poles of open loop amplifier so that closed loop system will have desired properties.

typically: add C_c across a gain stage


(K2-u, LM324, 1a53)

to set a phase margin $\geq 45^\circ$


need at least $\omega_{p2} > \omega_{uc}$

$$\text{so } \omega_{uc} = A_v \omega_{p1c}$$


$$= \frac{G_{m1}}{C_c}$$

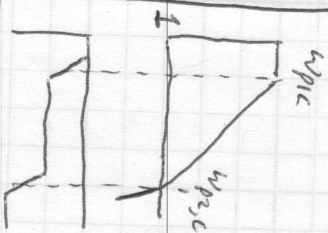


from last time

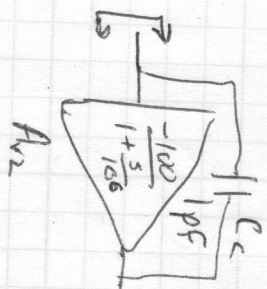

C_{Miller}

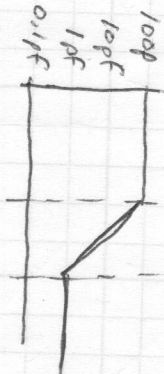

$|Z_{\text{Miller}}|$

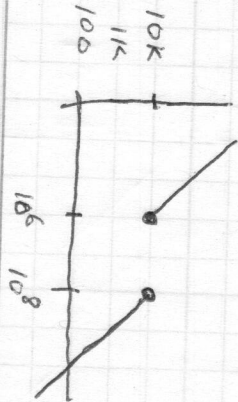

1650



140



$$G_m v_{i2} + \frac{1}{R_{o2}} v_{o2} + s C_c v_{o2} = 0$$

$$\begin{aligned} \frac{v_{o2}}{v_{i2}} &= \frac{-G_m}{\frac{1}{R_{o2}} + s C_c} \\ &= \frac{-G_m R_{o2}}{1 + s R_{o2} C_c} \end{aligned}$$
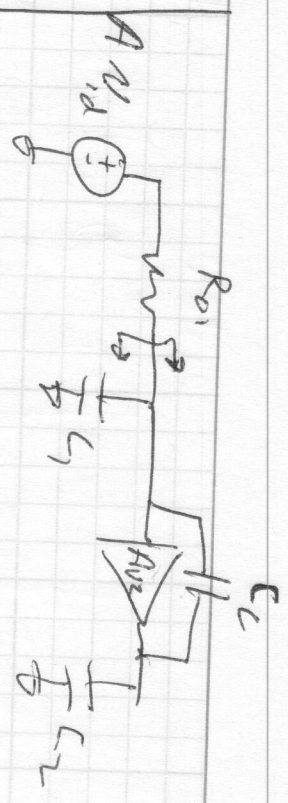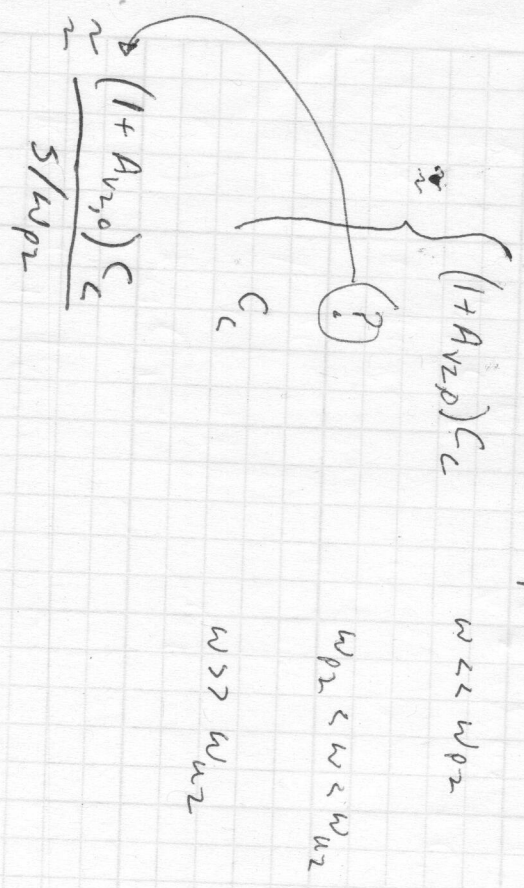
$$C_{\text{miller}} = (1 + A_{v2}) \frac{1 + \frac{s}{(1 + A_{v2}) \omega_{p2}}}{1 + s / \omega_{p2}} C_c$$



$$C_{\text{miller}} = C_c + (1 - A_{v2}) C_c$$


$$C_{\text{miller}} = \left(1 - \frac{-G_m v_{o2}}{1 + s / \omega_{p2}} \right) C_c$$


$$= \frac{1 + s / \omega_{p2} + A_{v2}}{1 + s / \omega_{p2}} C_c$$

$$Z_{\text{miller}} = \frac{1}{j\omega C_{\text{miller}}} = \frac{1}{j\omega \left(\frac{1 + A_{v2,0} C_c \omega_{p2}}{j\omega} \right)}$$

$$Z_{\text{miller}} = \frac{1}{j\omega (1 + A_{v2,0}) C_c \omega_{p2}}$$

constant, real!

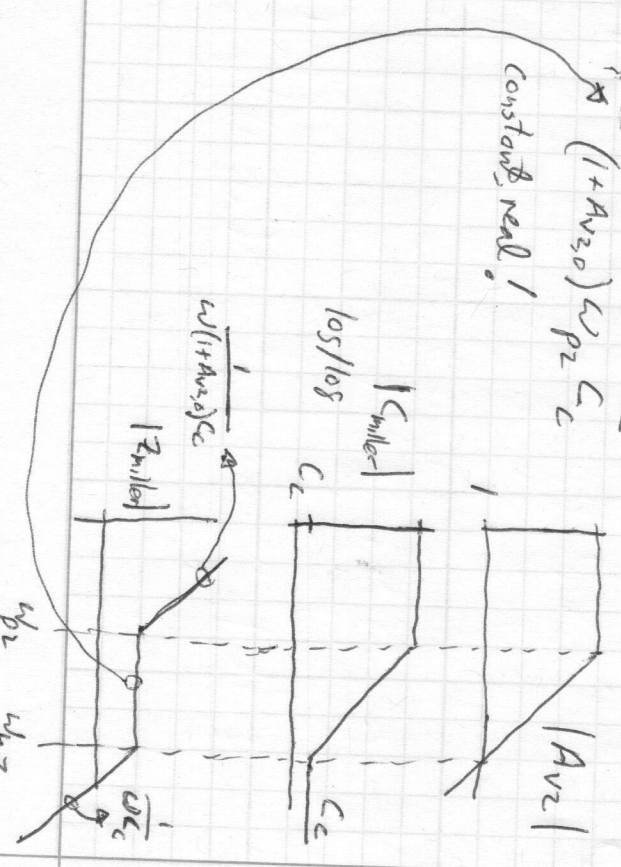

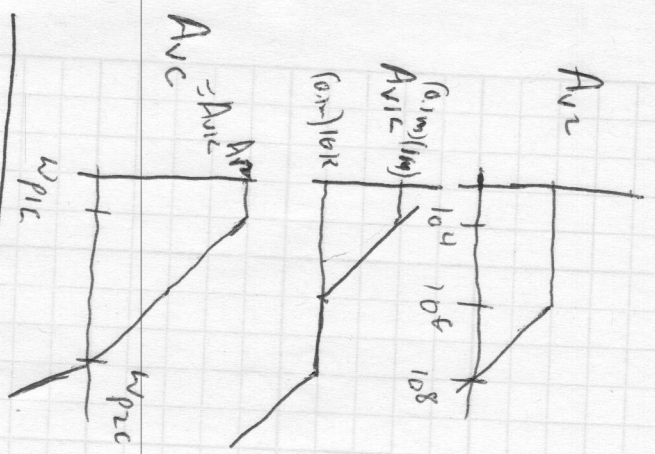

$w_{p1} \rightarrow w_{p1c}$

w_{p2} cancelled by w_{d2} , w_{d1}