

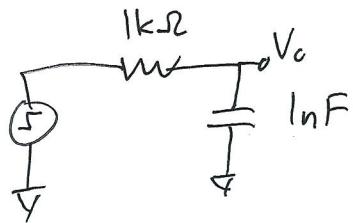
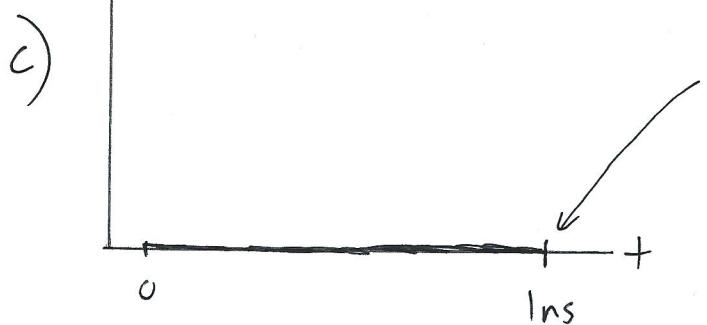


(1)

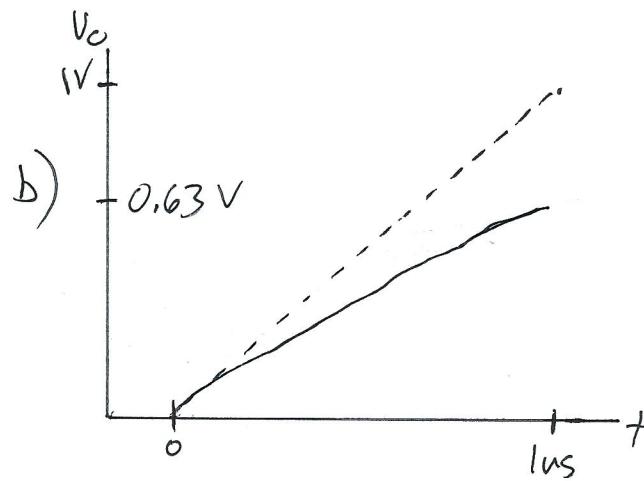

$$\tau = 1 \mu s$$


$$V_o = 1 - \exp(-t/\tau)$$

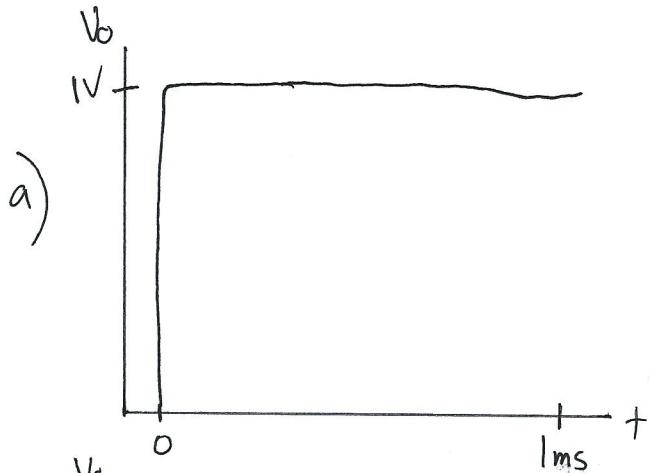

$$\text{After } 1ns \quad V_o = 0.001V$$

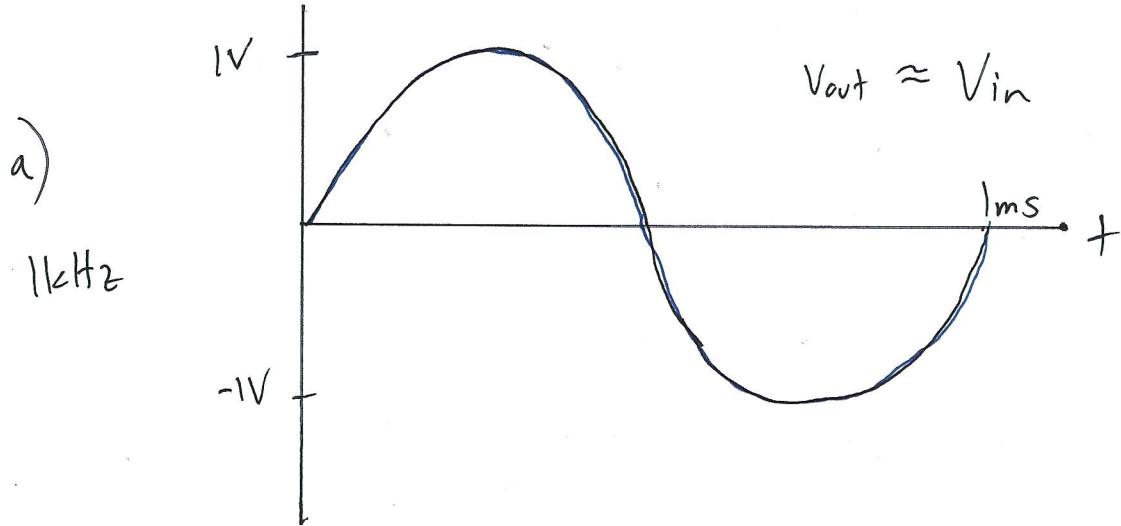
(2) Rough sketches by hand, no calculator

$$3dB \text{ frequency} = 1M\text{rad/s} \div 2\pi \approx 165 \text{ kHz}$$



b)

100kHz

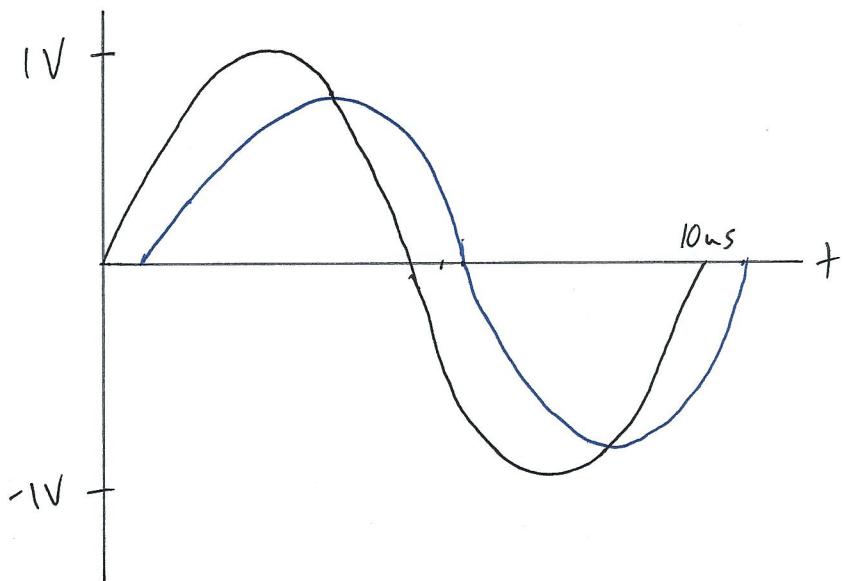


Slightly below cutoff,  
so amplitude slightly  
bigger than 0.5 and  
phase  $< 45^\circ$

(Actual answer  
 $0.85 \angle -32^\circ$ )

c)

1MHz

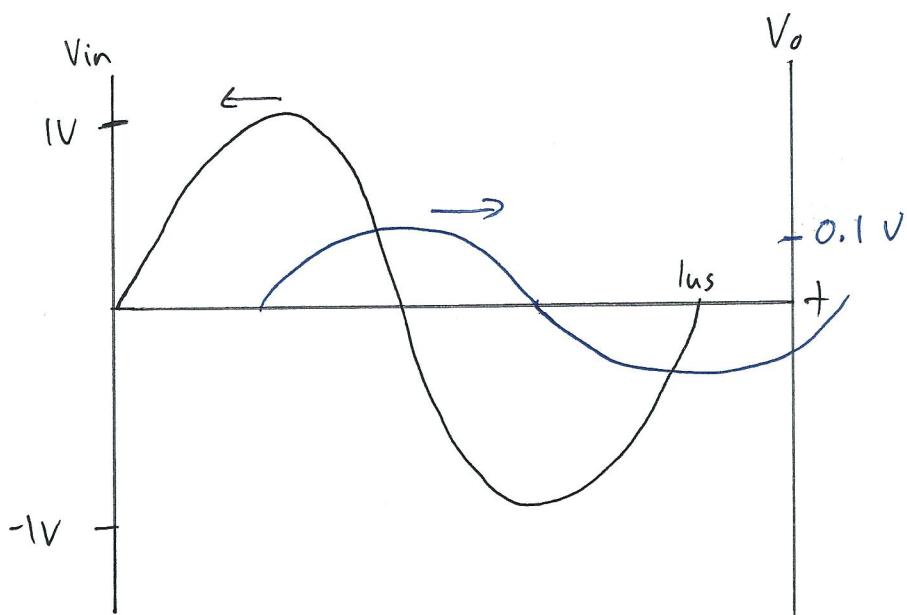


$\approx \frac{1}{10}$  amplitude

+  $90^\circ$  phase  
shift

d)


16Hz

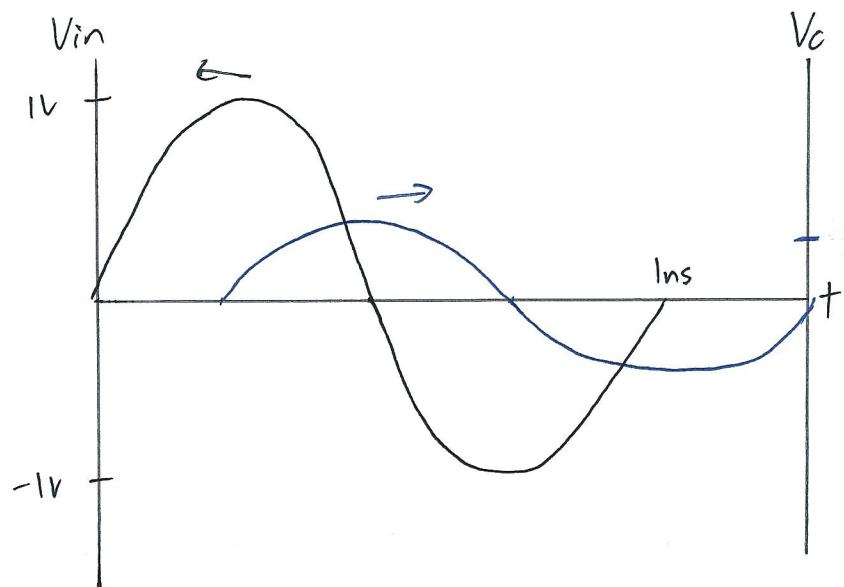

$\approx \frac{1}{10^4}$  amplitude

$10^{-4}$  V +  $90^\circ$  phase  
shift

(3)

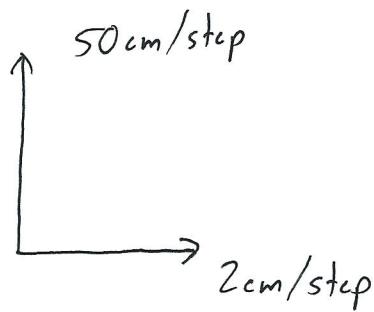


10 steps north is 500 cm higher elevation

To return to original altitude, must then walk

$$\frac{500 \text{ cm}}{2 \text{ cm/step}} = 250 \text{ steps west}$$

(4)

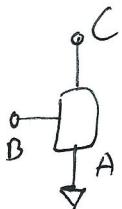

$$I_c = f(V_{ba}, V_{ca})$$

a)  $I_c + i_c = f(V_{BA} + v_{ba}, V_{CA} + v_{ca})$

b) 2D Taylor:

$$f(x + \Delta x, y + \Delta y) = f(x, y) + f'_x(x, y) \Delta x + f'_y(x, y) \Delta y + \dots$$

$$I_c + i_c = f(V_{BA}, V_{CA}) + \underbrace{\left. \frac{\partial f}{\partial V_{BA}} \right|_{V_{BA}, V_{CA}}}_{\text{This is } I_c} \cdot v_b + \underbrace{\left. \frac{\partial f}{\partial V_{CA}} \right|_{V_{BA}, V_{CA}}}_{\text{call } g_b} \cdot v_c$$

$\underbrace{\hspace{10em}}$  call  $g_c$

$$i_c = g_b v_b + g_c v_c$$

$$c) i_c = 0 \quad O = g_b V_b + g_c V_c$$

$$V_c = -\frac{g_b}{g_c} V_b$$


d) Call north the "b" direction and east "c" direction,

$V_b$  is then # of steps north,  $V_b$  is # steps east,

$g_b$  is altitude per step north,  $g_c$  is altitude/step east,

$$V_c = -\frac{g_b}{g_c} V_b = -\frac{50}{2} \cdot 10 = -250 \text{ steps east}$$

(-east = west)

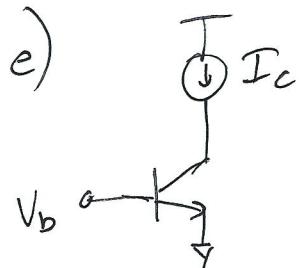

$$I_c = I_s \left( 1 + \frac{V_{CE}}{V_A} \right) \exp \left( \frac{V_{BE}}{V_t} \right)$$

$$I_{c,\text{taylor}} = I_c + \left. \frac{\partial I_c}{\partial V_{BE}} \right|_{V_{BE}, V_{CE}} \cdot V_{bc} + \left. \frac{\partial I_c}{\partial V_{CE}} \right. \cdot V_{cc} + \cancel{\dots}$$

$$I_{c,\text{taylor}} = I_c + \left[ \frac{I_s}{V_t} \exp \left( \frac{V_{BE}}{V_t} \right) + \frac{I_s}{V_t} \frac{V_{CE}}{V_A} \exp \left( \frac{V_{BE}}{V_t} \right) \cdot V_{bc} + \frac{I_s}{V_A} \exp \left( \frac{V_{BE}}{V_t} \right) \cdot V_{ce} \right]$$


$$I_c + i_c = I_c + \frac{I_c}{V_t} V_{bc} + \frac{I_c}{V_A} V_{cc}$$

$$i_c = 0 \quad V_{ce} = \frac{-\frac{I_c}{V_t} V_{be}}{\frac{I_c}{V_A}}$$


$$V_{ce} = -\frac{V_A}{V_t} V_{bc}$$

(5)


a)

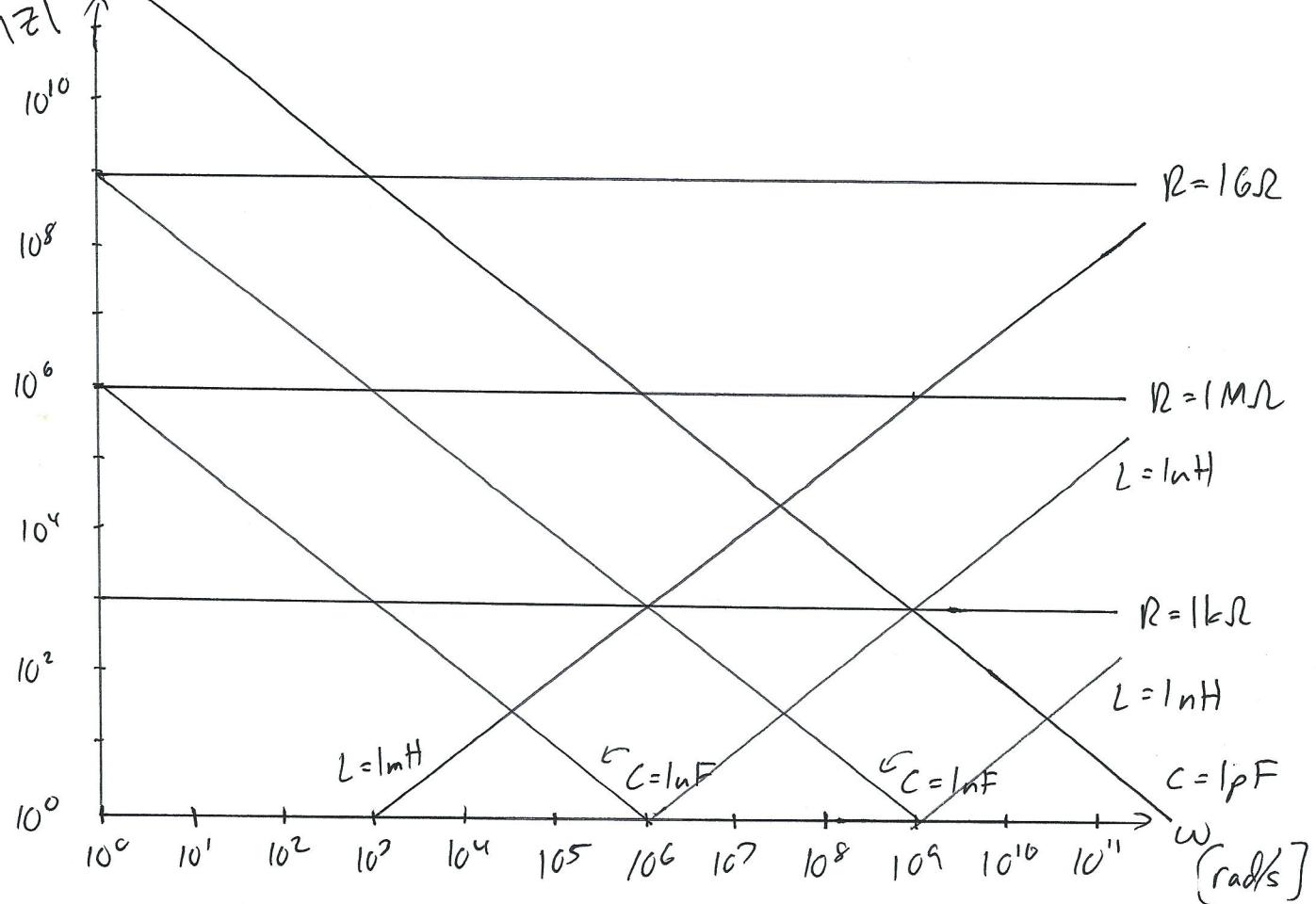


b)  
c)

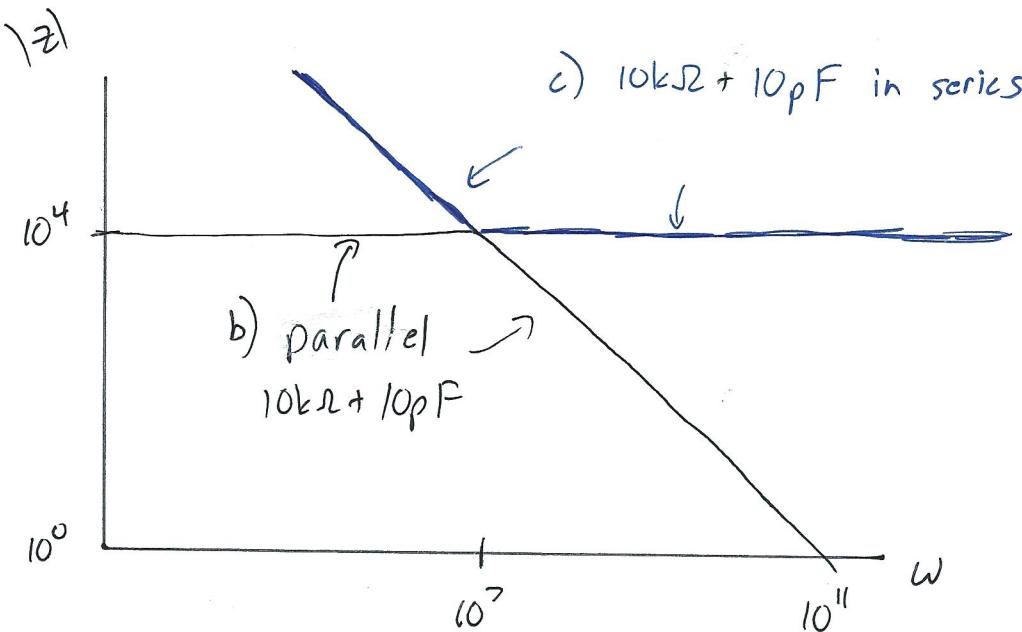


d)

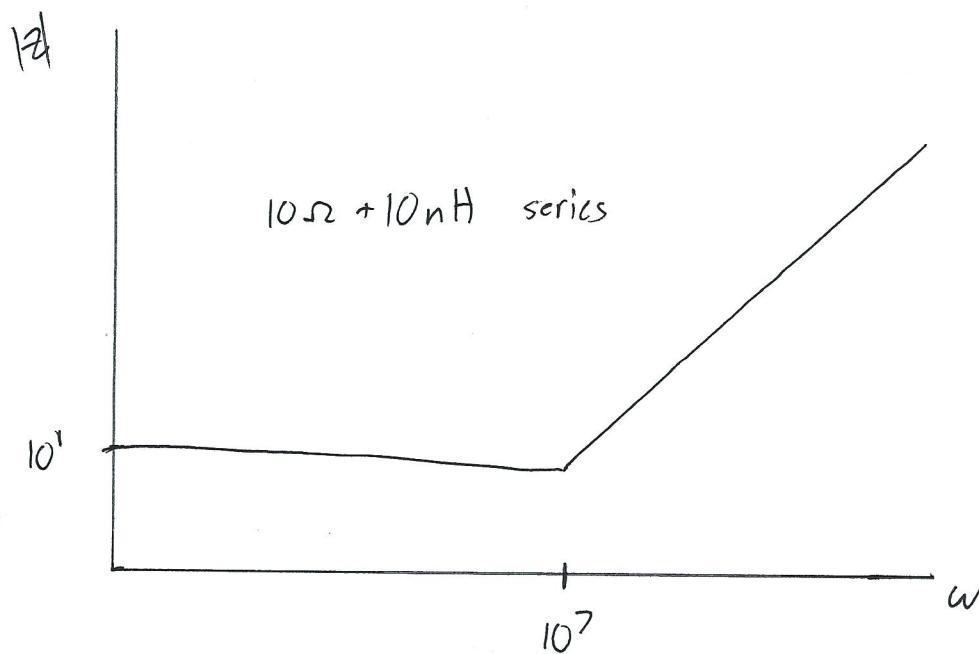

e)

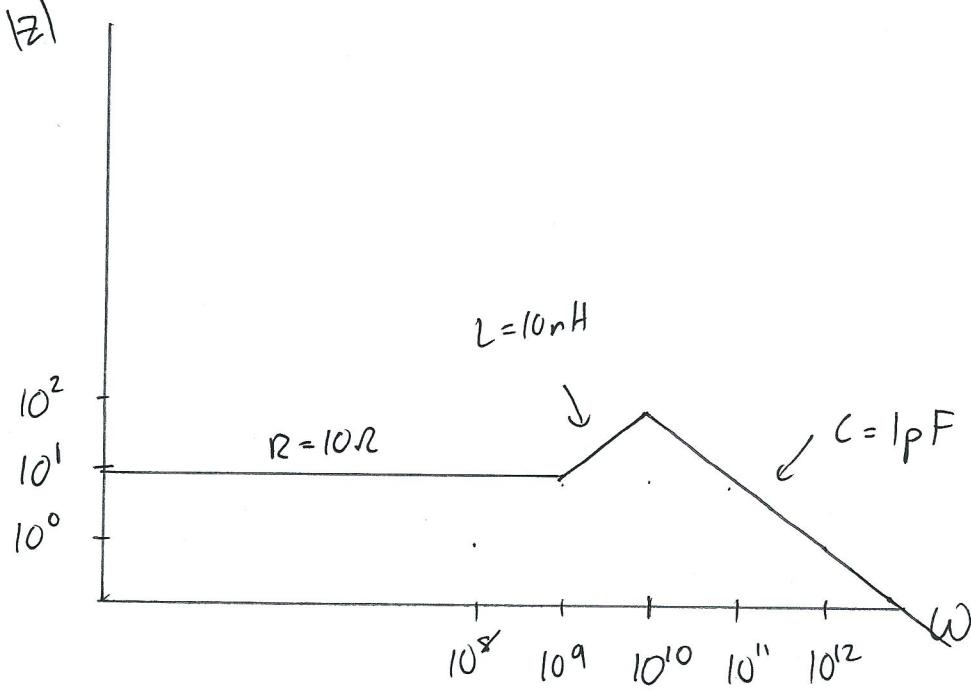

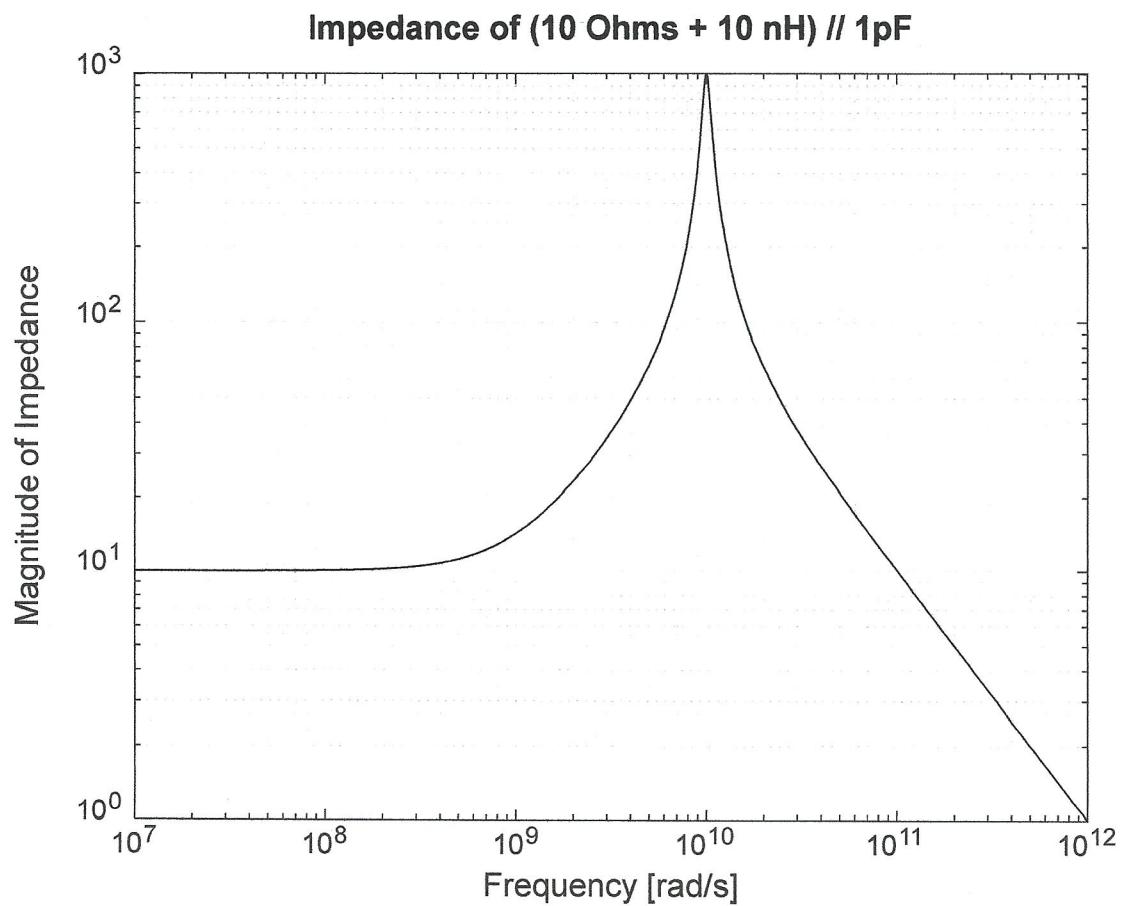
Note that our straight line approximation ignores the "peaking" in this second order response. See following plot for what it actually looks like.



$$Q = \frac{\omega_o * L}{R} = 10$$

Note that the impedance peaks to a value Q times higher than that predicted by our straight line impedance approximation.

(6)

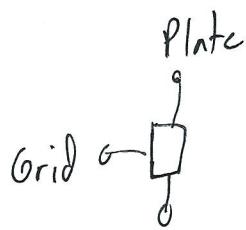

$$g_m = \frac{\Delta I_{plate}}{\Delta V_{grid}}$$

Cathode

$$r_o = \frac{\Delta V_{plate}}{\Delta I_{plate}}$$

$$g_m = \frac{100mA - 200mA}{-75V + 52V} = 4.35 \text{ mS}$$

$$r_o = \frac{3500V - 750V}{100mA - 50mA} = 55 k\Omega$$

$$A_v = -g_m r_o = -239.3 \text{ V/V}$$

Could also estimate from the slope of grid vs plate voltage curve at bias point.

$$A_v \approx \frac{\Delta V_{plate}}{\Delta V_{grid}} \approx -\frac{1000}{4} = -250 \text{ V/V}$$

HW1 Rubric

---

1) 6 pts

-- 2 pts per plot

2) 12 pts total

-- 3 pts per plot, 1 pt for correct amplitude, 1 pt for correct phase shift, 1 pt for labeling axis

3) 4 pts

-- half for attempt, +4 for correct answer

4) 10 pts

-- 2 pts for each item

5) 17 pts

-- a) 1 pt for each component

-- b) through e) 2 pts each

6) 6 pts

-- 2 pts each for gm,ro,Av

---

55 pts total