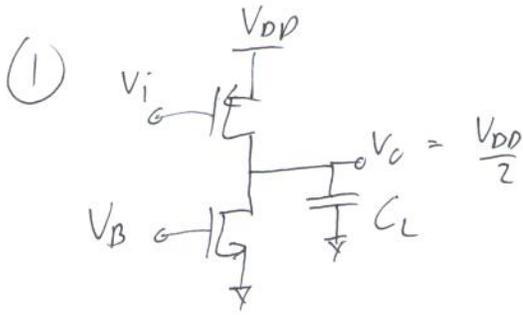


# EE 140 HW 4



24 pts  
+1 per entry



Change	$I_D$	$g_m$	$r_o$	$A_v$	$\omega_p$	$\omega_n$	$C_{in}$	swing
$2 \times W$	$2 \times$	$2 \times$	$\frac{1}{2} \times$	$1 \times$	$2 \times$	$2 \times$	$2 \times$	$1 \times$
$2 \times W, 2 \times L$	$1 \times$	$1 \times$	$2 \times$	$2 \times$	$\frac{1}{2} \times$	$1 \times$	$4 \times^{(1)}$	$1 \times$
$2 \times V_{ov}$	$4 \times$	$2 \times$	$\frac{1}{4} \times$	$\frac{1}{2} \times$	$4 \times$	$2 \times$	$\frac{1}{2} \times - 1 \times^{(2)}$	$\frac{1}{2} \times$

(1) If  $C_{gs}$  dominates,  $C_{gs} = \frac{2}{3} (2W)(2L) C_{ox} \rightarrow 4 \times$  increase

If  $C_{gd}$  dominates,  $C_{gd} = C_{o1} W \cdot 2 \rightarrow 2 \times$  increase, but gain also went up  $2 \times$  so still  $4 \times$  increase,


(2)  $C_{gs}$  doesn't change but Miller-multiplied  $C_{gd}$  drops to  $\frac{1}{2} \times$ .

(2) Problem 5 from FOA midterm 1

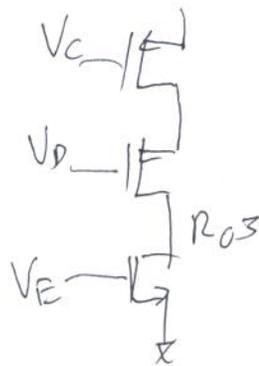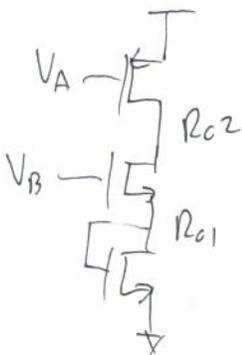

(2)

b) low freq cap into  $V_B$  ?

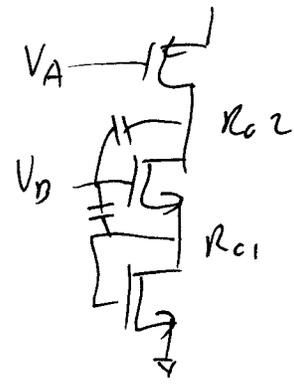

$$A_{VB \rightarrow 1} = G_m R_c$$

$$G_m = \frac{g_m}{1 + g_m \frac{1}{g_m}} = \frac{g_m}{2}$$

from a) know  $R_{c1} \approx \frac{2}{3} \frac{1}{g_m}$

$$A_{VB \rightarrow 1} = \frac{g_m}{2} \frac{2}{3} \frac{1}{g_m} = \frac{1}{3}$$

$A_{VB \rightarrow 2}$  :

$$G_m = \frac{g_m}{1 + g_m \frac{1}{g_m}} = \frac{g_m}{2}$$

$$R_{c2} = \frac{2}{3} r_o \quad (\text{from (a)})$$

$$A_{VB \rightarrow 2} = -\frac{g_m}{2} \frac{2}{3} r_o = -\frac{g_m r_o}{3}$$

$$C_{in} = (1 - A_{VB \rightarrow 1}) C_{gs} + (1 - A_{VB \rightarrow 2}) C_{gd}$$

$$C_{in} = \frac{2}{3} C_{gs} + \left(1 + \frac{g_m r_o}{3}\right) C_{gd}$$

(b) 4 pts total

+2 for finding both Miller gains

+2 for getting correct  $C_{in}$  expression

(a) 8 pts total  
 +1 each for ro\_up, ro\_down, and ro\_total  
 +1 setting up equations for Cin  
 +1 for finding correct Cin

$$R_{o1, up} = \frac{r_o + r_o}{1 + g_m r_o} \approx \frac{2}{g_m}$$

$$R_{o1, down} = \frac{1}{g_m}$$

$$R_{o1} = \frac{2}{g_m} \parallel \frac{1}{g_m} = \frac{2}{3g_m}$$

$$R_{o2, up} = r_o$$

$$R_{o2, down} = r_o + (1 + g_m r_o) \frac{1}{g_m} \approx 2r_o$$

$$R_{o2} = r_o \parallel 2r_o = \frac{2}{3} r_o$$

$$R_{o3, up} = g_m r_o^2$$

$$R_{o3} = r_o$$


$$R_{o3, down} = r_o$$

③  $|A_v| = 50 \text{ V/V}$

$$\omega_u = 2\pi \cdot 1.6 \text{ G}$$

$$C_L = 200 \text{ fF}$$

$$\text{swing} = 1 \text{ V}$$

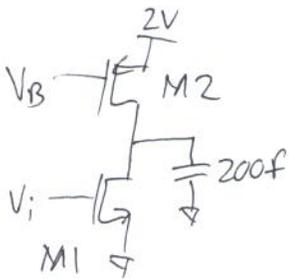

$$\omega_u = \frac{g_m}{C_L}$$

$$g_m = (2\pi \cdot 1.6 \cdot 10^9) (2 \cdot 10^{-13}) \approx 2 \text{ mS}$$

$$A_v = \frac{1}{\lambda V_{ov}}$$

Choose  $V_{ov} = 200 \text{ mV}$  (for both NMOS + PMOS)

then need

$$\lambda \leq 0.1 \text{ V}^{-1}$$

$$\lambda = \frac{0.1 \mu\text{m}}{L} \frac{1}{\text{V}} \quad \text{so}$$

$$L = 1 \mu\text{m}$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$I_D = \frac{g_m V_{ov}}{2} = 200 \mu\text{A}$$

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} V_{ov}^2$$

$$W = \frac{2 I_D L}{\mu C_{ox} V_{ov}^2}$$

$$W_n = 100 \mu\text{m}$$

$$W_p = 200 \mu\text{m}$$

17 pts

+1 per entry in M1/M2 design table

+1 per entry in  $A_v, w_p, w_u, C_{in}, \text{swing}$  table

	W	L	$I_D$	$V_{ov}$	$g_m$	$r_o$
M1	100 $\mu\text{m}$	1 $\mu\text{m}$	200 $\mu\text{A}$	0.2V	2 mS	50 k $\Omega$
M2	200 $\mu\text{m}$	1 $\mu\text{m}$	200 $\mu\text{A}$	0.2V	2 mS	50 k $\Omega$

$A_{vo}$	$w_p$	$w_u$	$C_{in}$	swing
50 %	24 MHz	1.2 GHz <sup>(1)</sup>	1.35 pF	1.6 V


$$C_{in} = C_{gs} + (1 + A_v) C_{gd} = \frac{2}{3} W L C_{ox} + 51 C_{ol} \cdot W$$

(1) Note that we don't meet the bandwidth spec because

$C_{gd} \approx 60 \text{ fF}$  in total (NMOS + PMOS) at the output node which is significant compared to 200 fF,

The only way to get the bandwidth with a common source would be to make the devices so large that  $C_{gd} \gg C_L$  which is impractical,

P4) a)

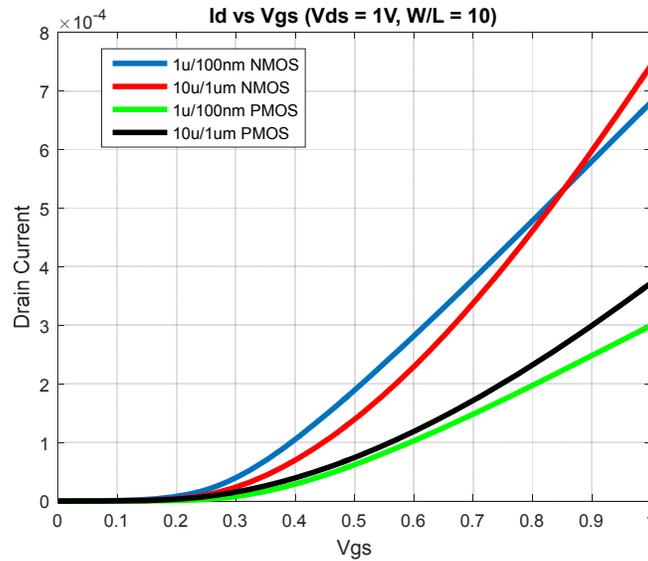

4a) 4 pts. Full credit for noting that the short channel devices look mostly velocity saturated, and that the long channel devices look quadratic over some range.

Short channel devices do look linear as expected in velocity saturated devices. The long channel devices look mostly quadratic. They look like they start to turn linear near the higher values of  $V_{gs}$  (~0.8V).

b) We can find  $V_t$  by choosing two ( $V_{gs}, I_D$ ) pairs on the curve and dividing them.

For the NMOS:

$$\frac{I_{D1}}{I_{D2}} = \frac{(V_{gs1} - V_t)}{(V_{gs2} - V_t)} = \frac{378\mu A}{580\mu A} = \frac{0.7V - V_t}{0.9V - V_t}$$

Which results in  $V_{tn} = 325$  mV.

For the PMOS:

$$\frac{I_{D1}}{I_{D2}} = \frac{(V_{gs1} - V_t)}{(V_{gs2} - V_t)} = \frac{149\mu A}{248\mu A} = \frac{0.7V - V_t}{0.9V - V_t}$$

Which results in  $V_{tp} = 400$  mV.

We can find  $C_{ox} * V_{scl}$  for the NMOS by:


$$C_{ox} * V_{scl} = \frac{I_D}{W(V_{gs} - V_t)} = \frac{429\mu A}{1\mu m(0.75V - 0.325V)} = 1000 \frac{A}{\mu m V}$$

For the PMOS:

$$C_{ox} * V_{scl} = \frac{I_D}{W(V_{gs} - V_t)} = \frac{173\mu A}{1\mu m(0.75V - 0.400V)} = 500 \frac{A}{\mu m V}$$

4b) 4 pts. Full credit for attempt at estimating  $V_t$  and  $C_{ox}V_{scl}$  from slope

c)

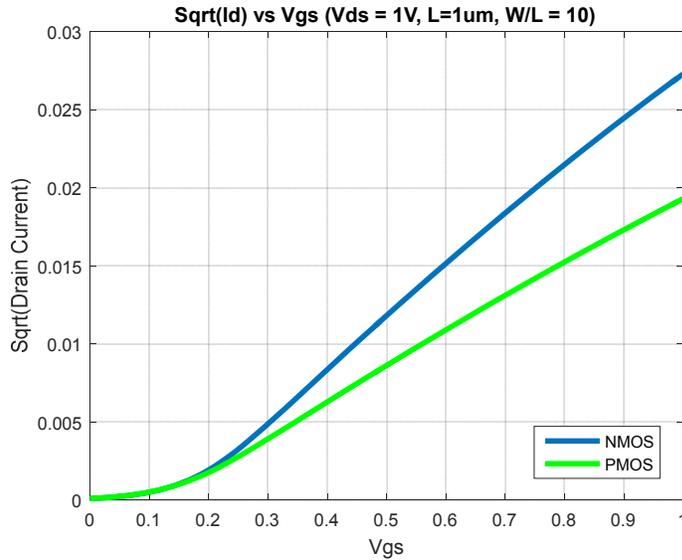

Using the same approach as (b) and choosing points on the straight portion of the curve:

For the NMOS:

$$\frac{\sqrt{I_{D1}}}{\sqrt{I_{D2}}} = \frac{(V_{gs1} - V_t)}{(V_{gs2} - V_t)} = \frac{0.0101}{0.03149} = \frac{0.45V - V_t}{0.55V - V_t}$$

Which results in **V<sub>tn</sub> = 400 mV**.



For the PMOS:

$$\frac{\sqrt{I_{D1}}}{\sqrt{I_{D2}}} = \frac{(V_{gs1} - V_t)}{(V_{gs2} - V_t)} = \frac{0.007461}{0.00977} = \frac{0.45V - V_t}{0.55V - V_t}$$

Which results in **V<sub>tp</sub> = 114 mV**. (note that this seems too low)

4c) 4 pts. Full credit for the right approach (slope of curve)

d)

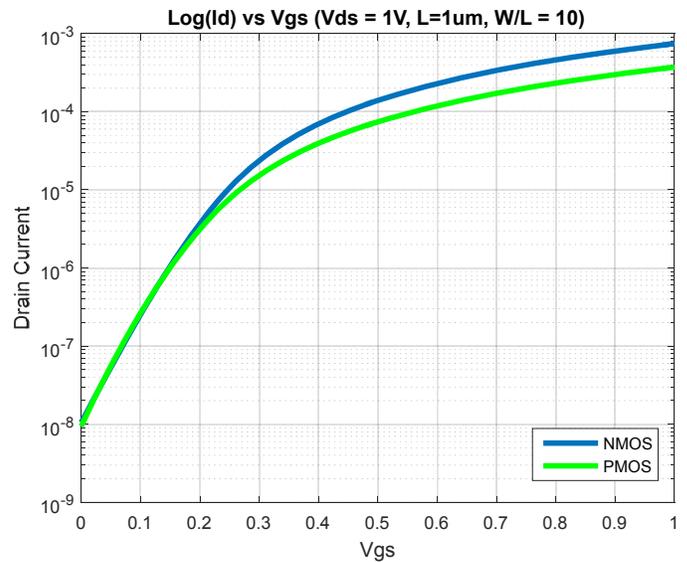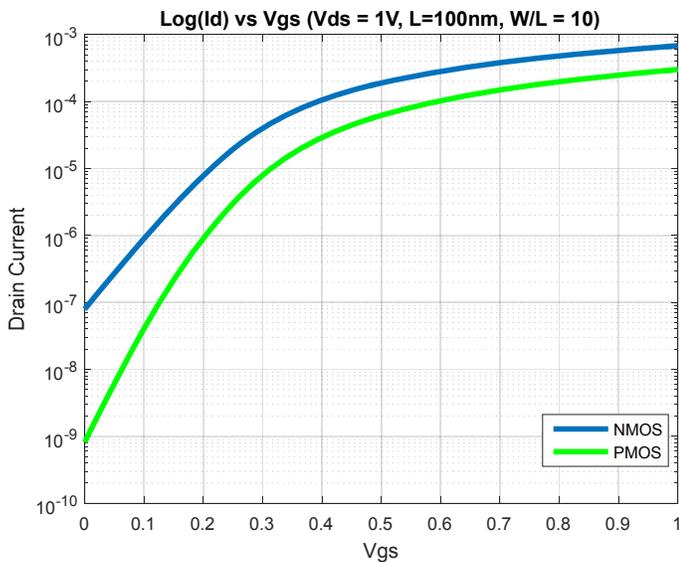

For the short channel devices (left plot),

The NMOS slope is:

$$\frac{0.105V - 10mV}{decade} = 95mV/dec$$

Which yields  $n=95/60 = 1.58$  for the short channel NMOS.

4d) 2 pts. Full credit for right approach (  $n \cdot 60mV/decade = 1/(\text{slope of curves})$  )

The PMOS slope is:



$$\frac{0.065V - 5mV}{decade} = 60mV/dec$$

Which yields  $n=60/60 = 1$  for the short channel PMOS. Note that this model shows that the PMOS is as good as a BJT; it can't get any better than this.

For the long channel devices (right plot), they both have nearly the same slope of 70mV/decade.

Which yields  $n=70/60 = 1.2$  for the long channel NMOS and PMOS.

e)

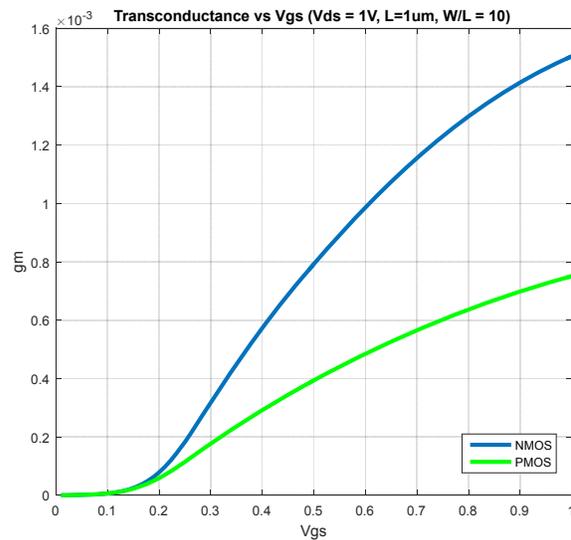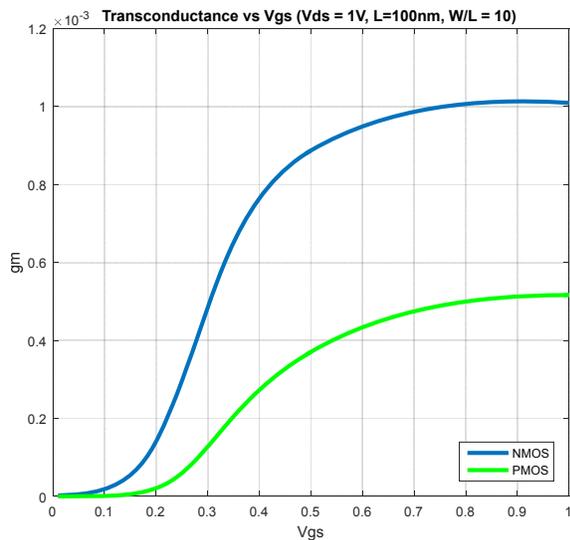



For short channel devices (left) we expect to see that  $g_m$  becomes constant when velocity saturation is reached, which appears to begin happening somewhere around  $V_{gs}$  of 0.4V (which is a higher field than the expected 1V/ $\mu m$ ).

For long channel devices (right)  $g_m$  should linearly increase with  $V_{gs}$  which appears to be mostly the case here until we begin reaching higher values of  $V_{gs}$ . Our 1V/ $\mu m$  model says the long channel devices should saturate at  $V_{gs}=1V$ .

4e) 4 pts.

--> 1 pt each for saying that short channel (vel. sat model ) should be constant, long channel (quadratic model) should be linear in  $V_{ov}$   
 --> 1 pt each for giving a reasonable range for short and long.  
 --> 2 pts for saying something related to field to explain why.


f)

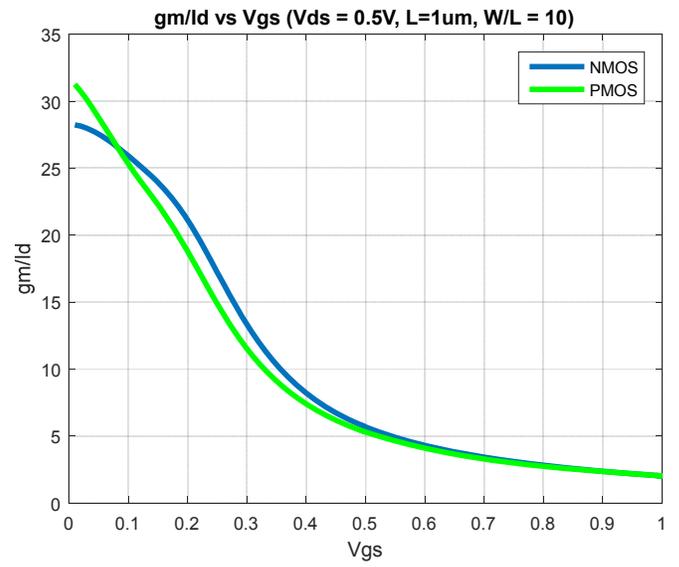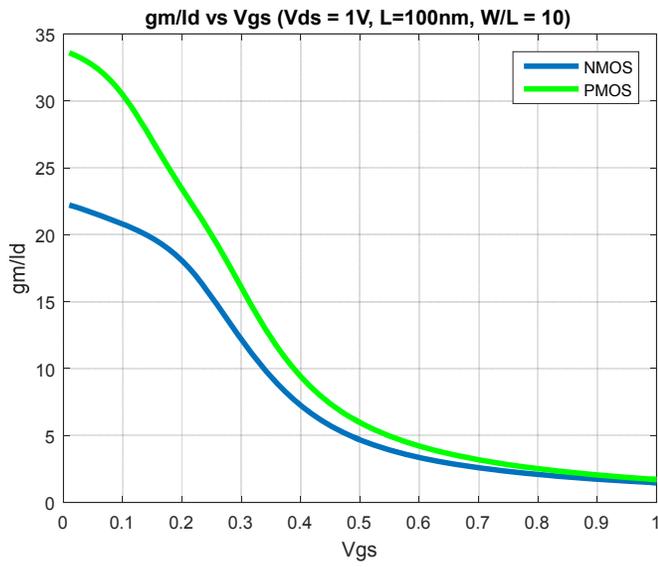

The short channel PMOS in subthreshold appears to be the best, closely followed by both of the long channel devices, also in subthreshold.

4f) 2 pts. Full credit for plots and choosing highest gm/Id

P5)

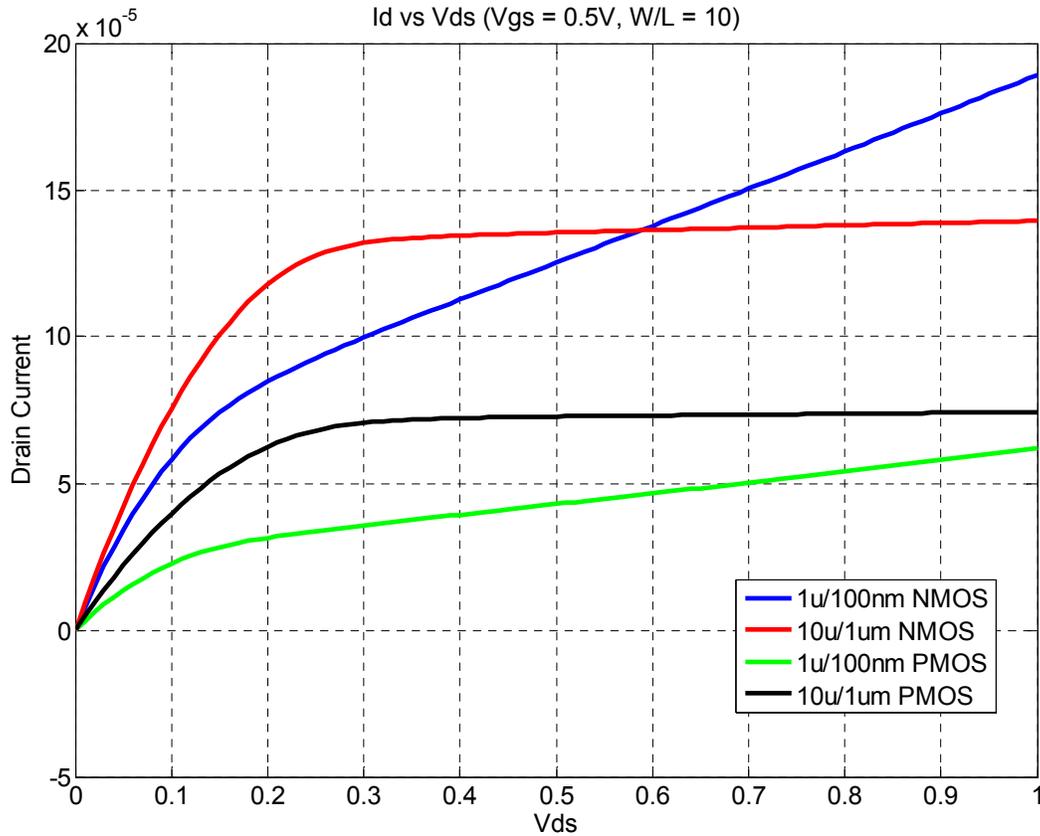

There appear to be visible transitions from saturation to triode for all devices. For the short channel devices  $v_{dsat}$  appears to be about 0.2 V while the long channel devices have  $v_{dsat} \sim 0.3V$ .



Extrapolating linear region to intersect with the x-axis yields:



Device	VA
NMOS 1um/100nm	0.5 V
NMOS 10um/1um	16 V
PMOS 1um/100nm	0.7 V
PMOS 10um/1um	21 V

8 pts for part (a)  
 +2 for plot,  
 +2 for some discussion of triode/saturation for long vs short channel,  
 +1 (4pts total) for each of the four VA values within reasonable range

b)

4 pts +1 per plot

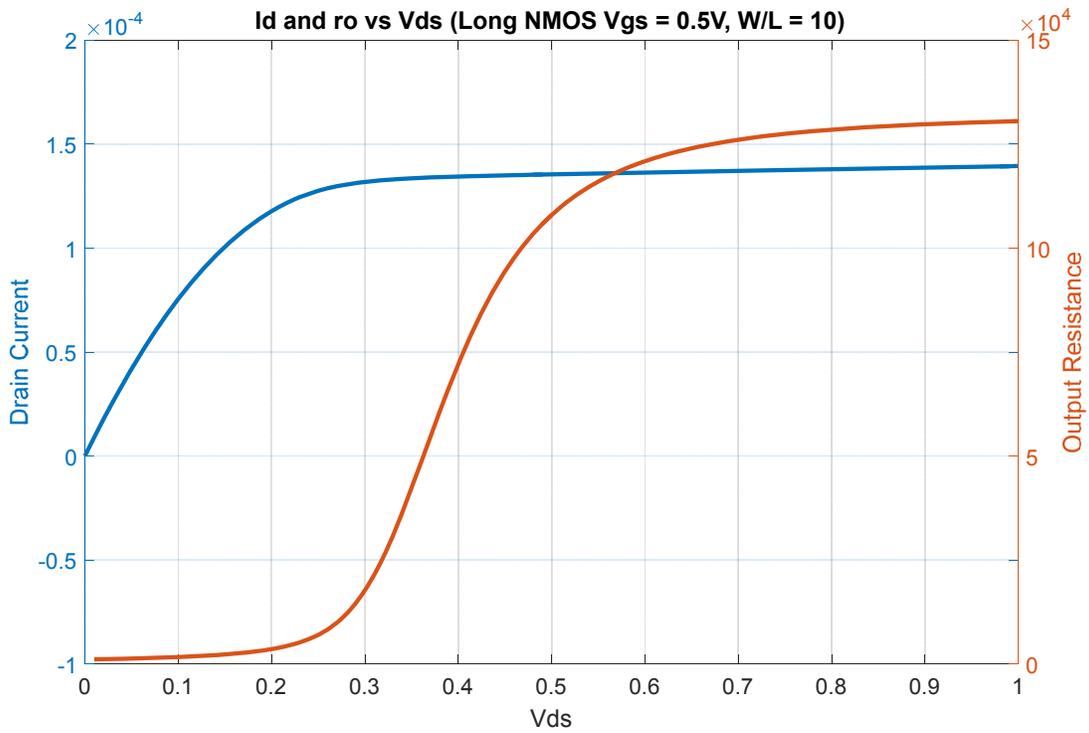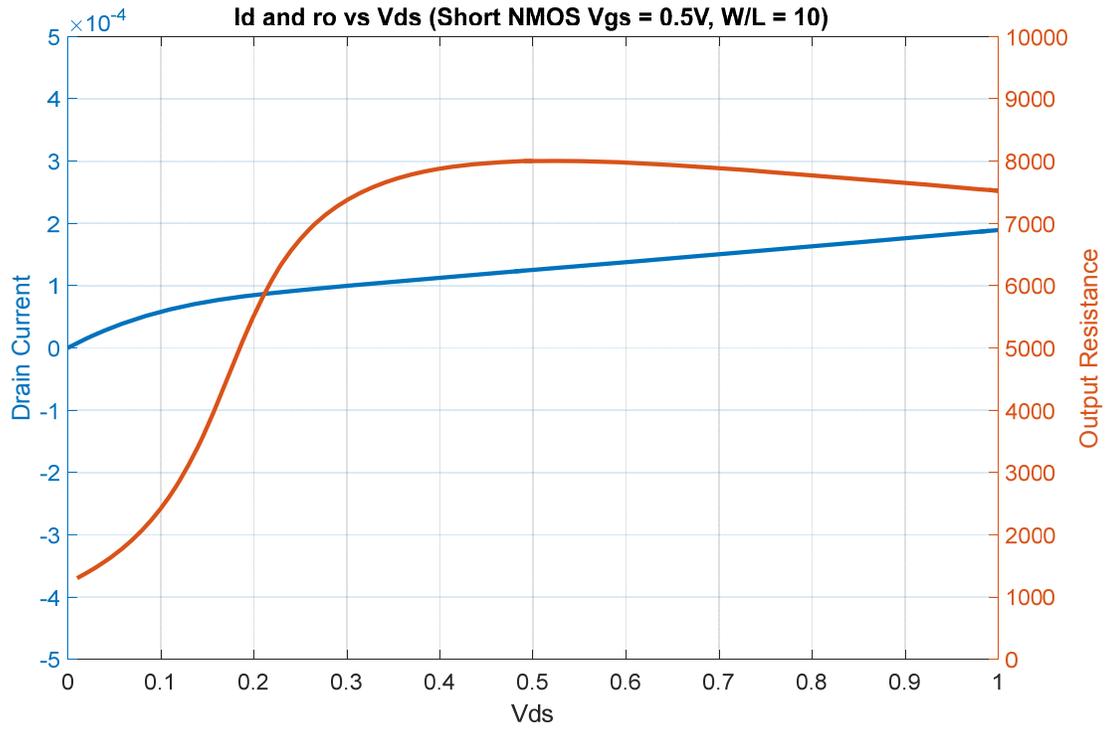

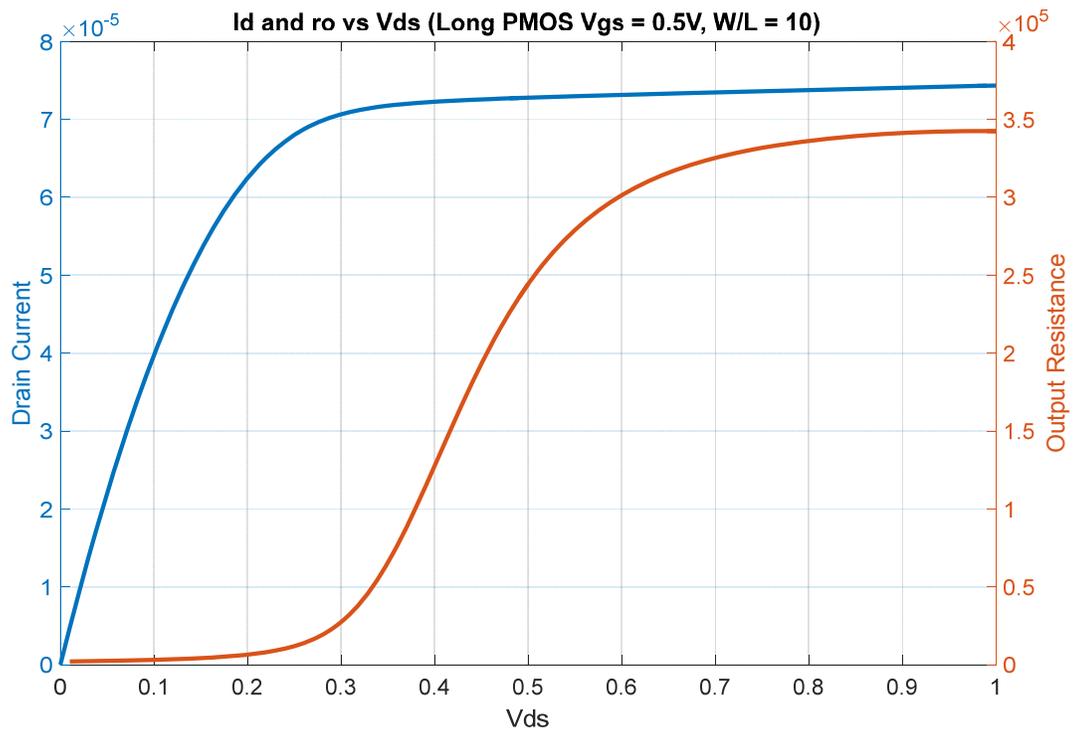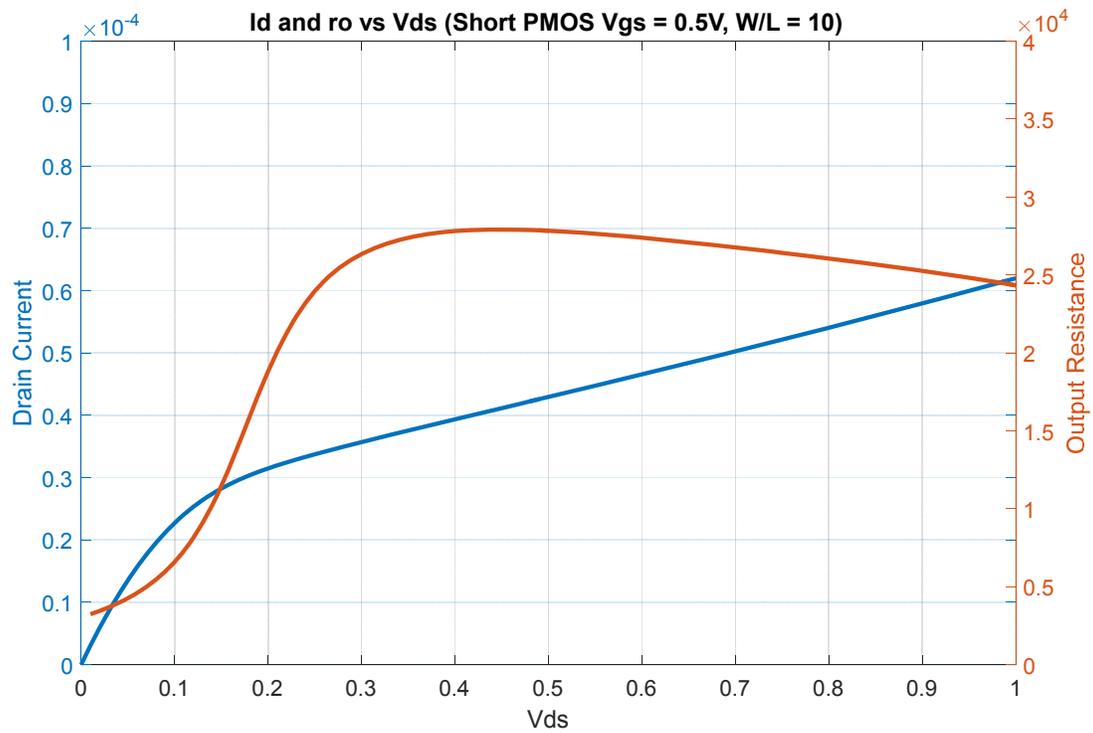

8 pts. +1/2 for each max ro and vds range  
Reasonably close values are fine

c)

Device	Max ro [Ohms]	Vds Range for >Ro/2
NMOS 1um/100nm	8k	>160mV
NMOS 10um/1um	130k	>390mV
PMOS 1um/100nm	28k	>170mV
PMOS 10um/1um	340k	>440mV

d)

Using  $r_o = \frac{1+\lambda V_{DS}}{\lambda I_D}$  with  $\lambda = 1/V_A$  yields the following results.

Device	Ro @ Vds = 1 V
NMOS 1um/100nm	7.9k
NMOS 10um/1um	120k
PMOS 1um/100nm	27k
PMOS 10um/1um	300k

They match relatively well for the short channel devices and are within 10% or so for the long channel devices.

The long channel matching becomes much worse below  $V_{ds} \sim 0.5V$ , while the short channel matches relatively well down to a lower  $V_{ds}$  of 0.2 V - 0.3 V.

4 pts. Full credit for any answer showing some thought.

## HW4 grading rubric

1) 24 pts total. 1 pt each for each value in each part.

2) 10 pts total

2a) 8pts

1 pt each for  $r_{o\_up}$ ,  $r_{o\_down}$ ,  $r_{o\_total}$  (6pts total)

1 pt for  $C_{in}$  equation

1 pt for correct  $C_{in}$

2b) 2pt for setting up equations, 2 pt for correct  $C_{in}$

3) 23 pts total.

17 pts for design process. 1 pt for each value in transistor table and 1 pt for each in spec table ( $A_v, w_p, w_u, etc$ )

3a) 2 pts. Full credit for any discussion of channel field

3b) 2 pts. Full credit for some discussion of design choices that affect power

3c) 2 pts. Full credit for some discussion of design choices that affect capacitance

4) 20 pts total

4a) 4 pts. Full credit for noting that the short channel devices look mostly velocity saturated, and that the long channel devices look quadratic over some range.

4b) 4 pts. Full credit for attempt at estimating  $V_t$  and  $C_{ox}V_{scl}$  from slope

4c) 4 pts. Full credit for the right approach (slope of curve)

4d) 2 pts. Full credit for right approach ( $n \cdot 60mV/decade = 1/(\text{slope of curves})$ )

4e) 4 pts.

--> 1 pt each for saying that short channel (vel. sat model) should be constant, long channel (quadratic model) should be linear in  $V_{ov}$

--> 1 pt each for giving a reasonable range for short and long.

--> 2 pts for saying something related to field to explain why.

4f) 2 pts. Full credit for plots and choosing highest  $g_m/I_d$

5) 20 pts total.

5a) 8 pts

+2 for plot,

+2 for some discussion of triode/saturation for long vs short channel,

+1 (4pts total) for each of the four  $V_A$  values within reasonable range

5b) 4 pts. +1 per plot

5c) 4 pts. +1/2 for each max  $r_o$  and  $v_{ds}$  range

5d) 4 pts. Full credit for any answer showing some thought.

240A only

P6) 10 pts

Half for coming up with a model.

Half for evaluating its accuracy.