

EE140 HW Solutions

$$\textcircled{1} \quad \frac{A_o}{1+A_o f} - \frac{1}{f} = \frac{A_o f - (1+A_o f)}{f(1+A_o f)} = \frac{-1}{f(1+A_o f)}$$

$$\frac{\frac{-1}{f(1+A_o f)}}{\frac{1}{f}} = \frac{-1}{1+A_o f} \approx \frac{-1}{A_o f} \quad \begin{array}{l} \text{Reasonable approximation} \\ \text{for large } A_o. \end{array}$$

#1) 2 pts

$$\textcircled{2} \quad A_o = 10^4 \quad \omega_p = 10^6 \text{ rad/s} \quad f = 0.1$$

$$\text{a) } \frac{A_o}{1+A_o f} = \frac{10^4}{1+10^4 10^{-1}} = 9.99 \text{ V/V}$$

#2) 8 pts total
2 pts for each part

$$\text{b) } \frac{1}{f} = 10 \text{ V/V}$$


$$\text{c) } \frac{-1}{A_o f} = \frac{-1}{10^4 10^{-1}} = -0.001$$

$$\text{d) } @ 10\omega_p \text{ gain decreases } 10\times, \text{ so } \frac{-1}{A f} = -0.01$$

$$@ 100\omega_p \text{ gain decreased } 100\times, \text{ so } \frac{-1}{A f} = -0.1$$

(3)

a, b

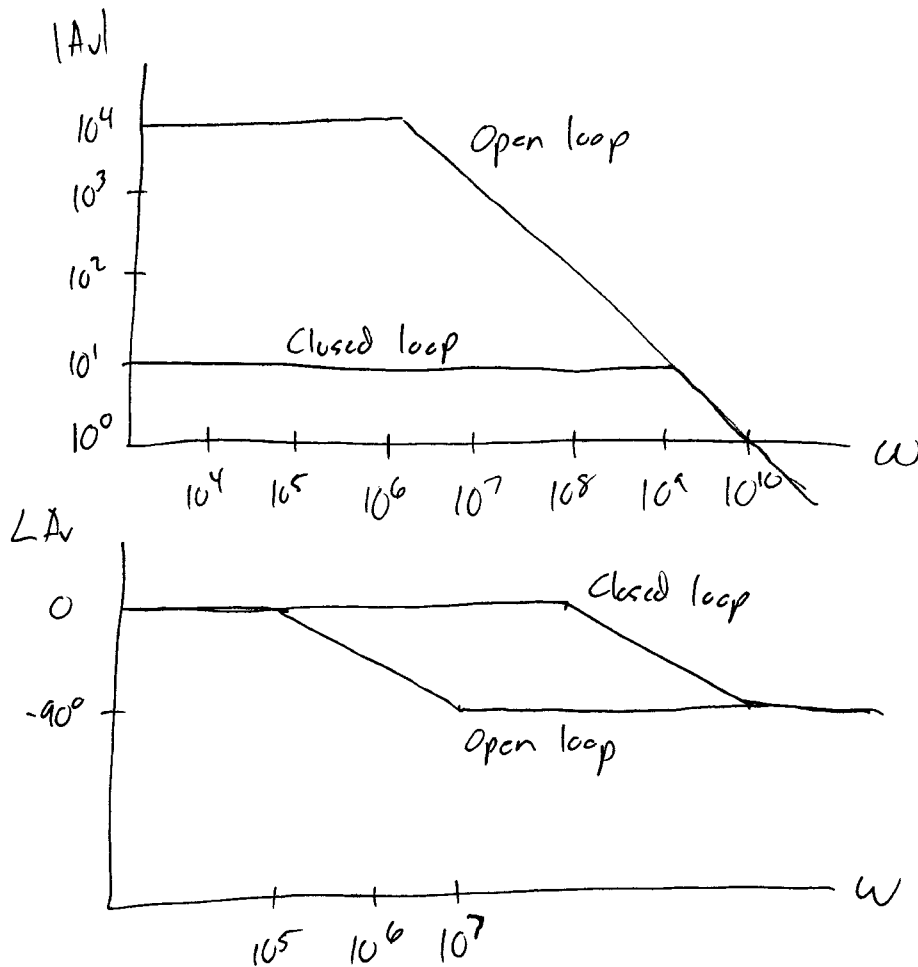

#3) 12 pts total

a) 3 pts: 1 each for magnitude, pole frequency, -45 degrees at pole frequency

b) 3 pts: same as (a)

c) 2 pts

d) 2 pts

e) 2 pts

c) Open loop unity gain = 10^{10} rad/s


Closed loop unity gain is also 10^{10} rad/s

d) Open loop pole is 10^6 rad/s


closed loop pole is 10^9 rad/s

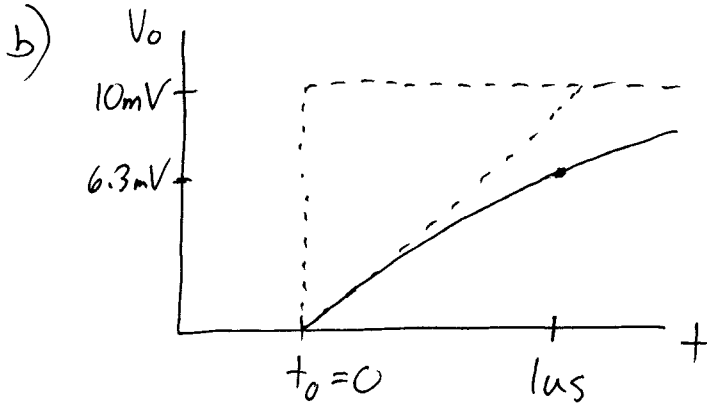e) Gain Bandwidth product is 10^{10} rad/s in both open and closed loop.

④ a) $\tau = 1\mu s$ for open loop $\left(\frac{1}{10^6}\right)$



c) $\tau = 1ns$ for closed loop

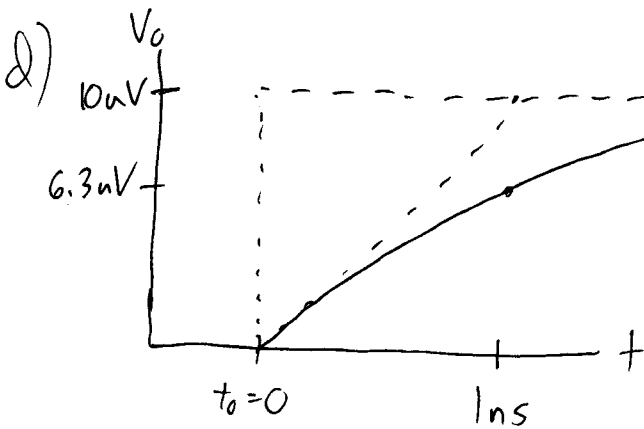

e) Part (d) would look like a straight vertical line on the axis used for part (b). And it only goes up to $10\mu V$ instead of $10mV$.

#4) 8 pts total

a) 1 pt


b) 2 pts, must show exponential and correct final value

c) 1 pt

d) 2 pts, same as (b)

e) 2 pts, much steeper, different final value

5) a) see attached plot

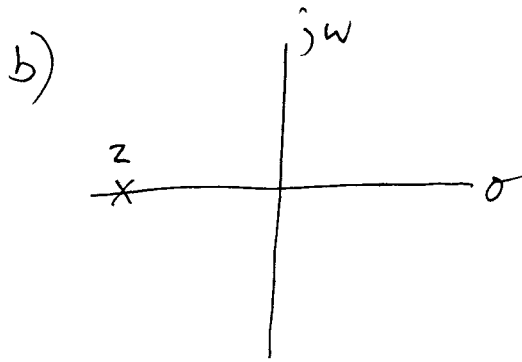

Both poles are on the negative real axis at 10^6 rad/s,


#5) 10 pts total
a) 4 pts, 1 each for magnitude, pole frequency, $1/w^2$ rolloff, -90 deg at poles
b) 2 pts
c) 2 pts
d) 2 pts

c) $f=1$ gives a phase margin of 0°

d) No, it will technically not oscillate with only two poles, but in reality it will due to other high frequency poles,

#6) 21 pts total
a) 2 pts, 1 each for magnitude, pole frequency
b) 4 pts: low frequency capacitance, high frequency capacitance, pole+zero frequencies
c) 4 pts: 1 for each region
d) 2 pts: getting the low frequency gain right; shape should be the same as 6c
e) 3 pts: low freq gain, 1st pole, 2nd pole
f) 2 pts
g) 2 pts
h) 2 pts

6) (a) - (e) See attached plots


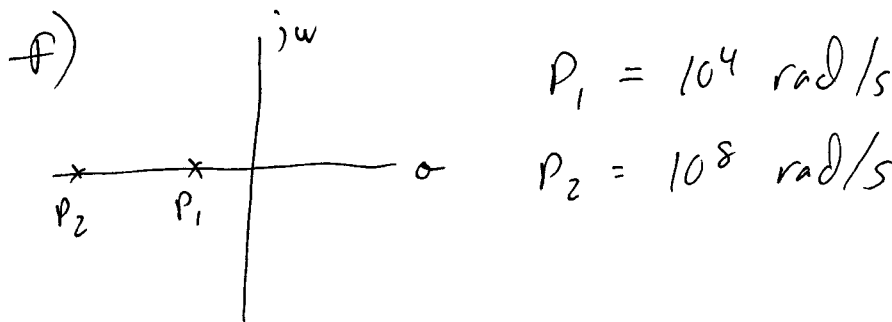


g) ω_u is $\sqrt{10} \approx 3 \times$ past $\omega_{p2} \approx 3 \cdot 10^8$ rad/s

$$PM = 180^\circ - 90^\circ - \tan^{-1}(\sqrt{10}) \approx 18^\circ$$


h) It is stable, but this is a pretty low phase margin,

Bode plot for problem 5a) and 6e)

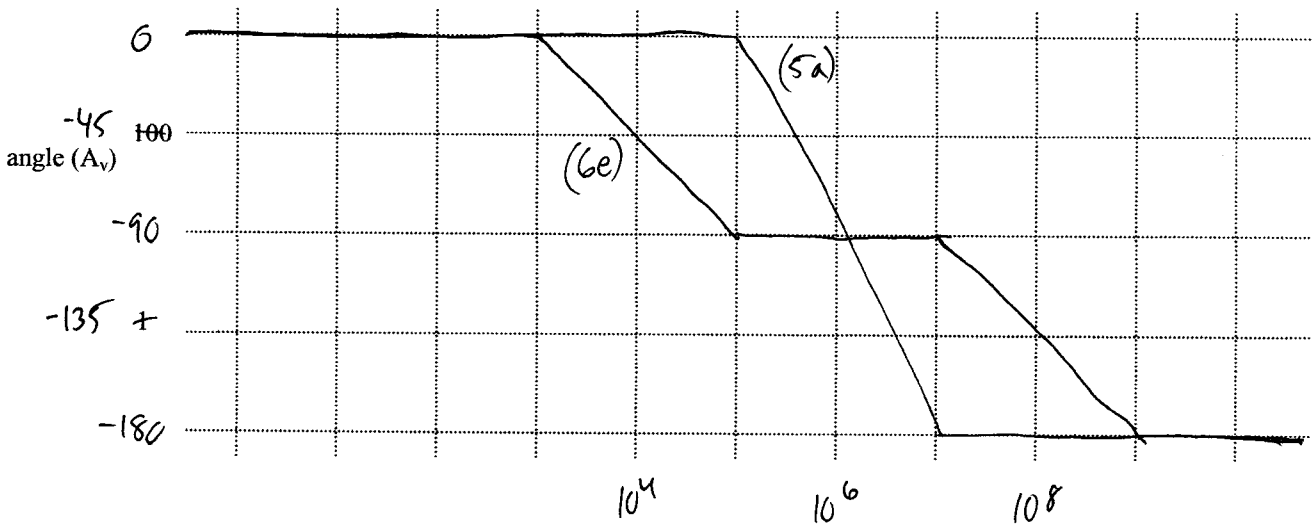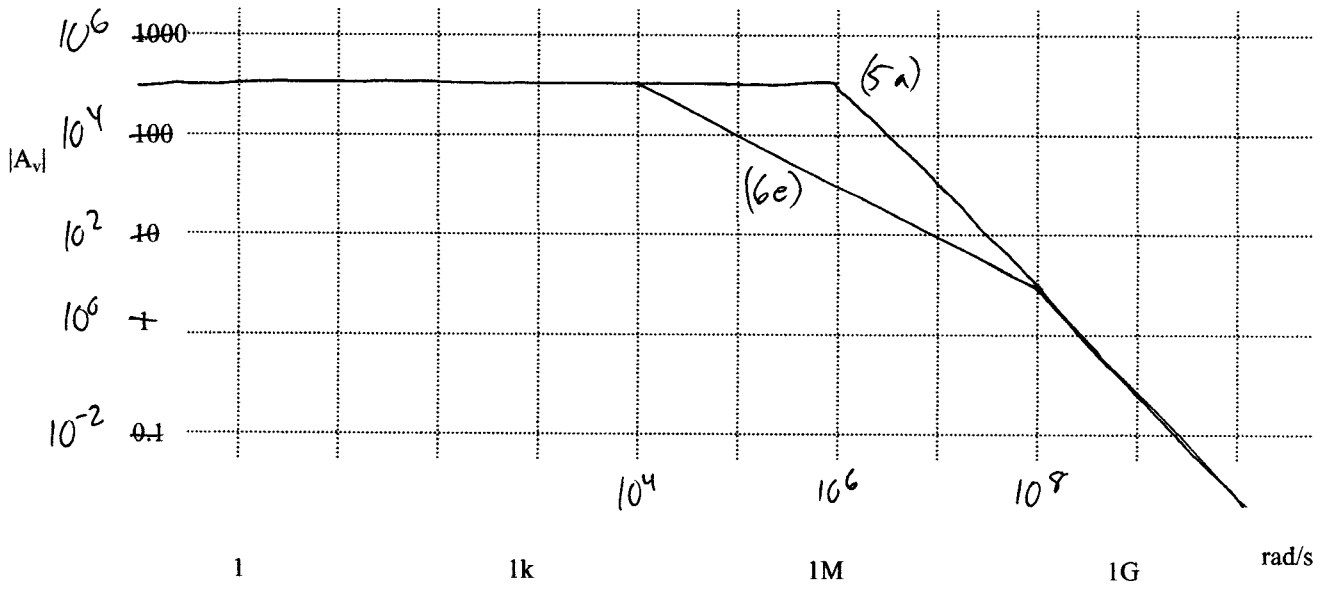


- #7) 8 pts total (EE240 only)
- +2 pts Expected gain error from f
 - +2 pts Does it depend on f
 - +2 pts Temp difference for same error
 - +2 pts Minimum gain necessary

Problem 6, part a) Second stage gain - $|A_{v2,0}|$; part d) $|A_{v1,c}|$

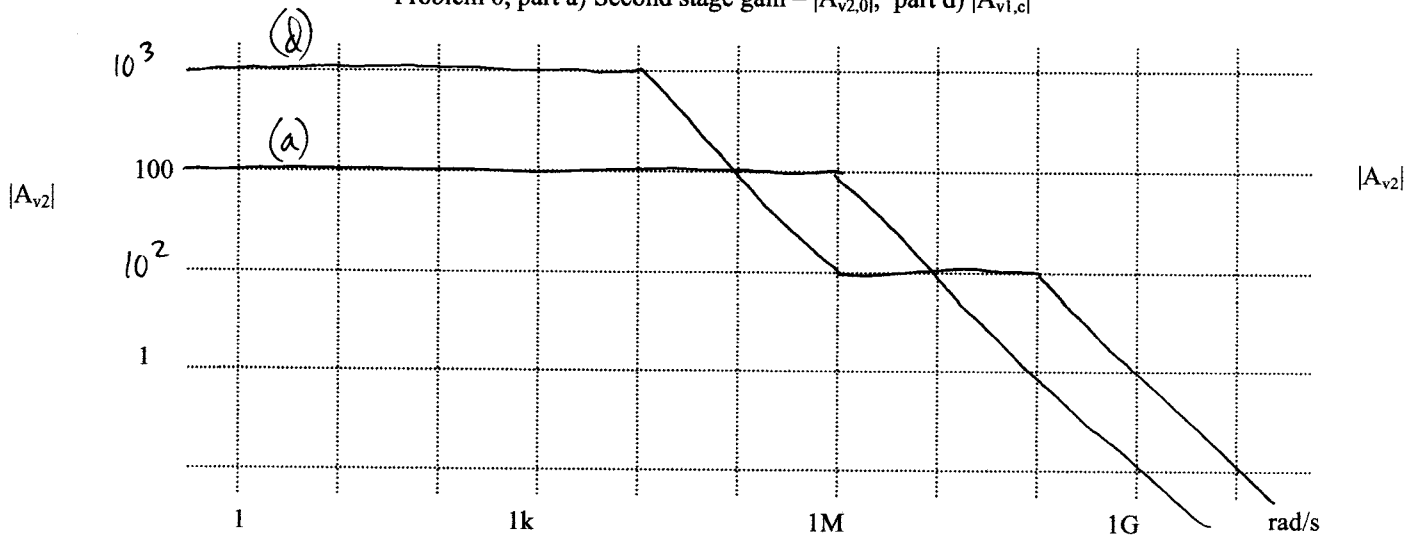

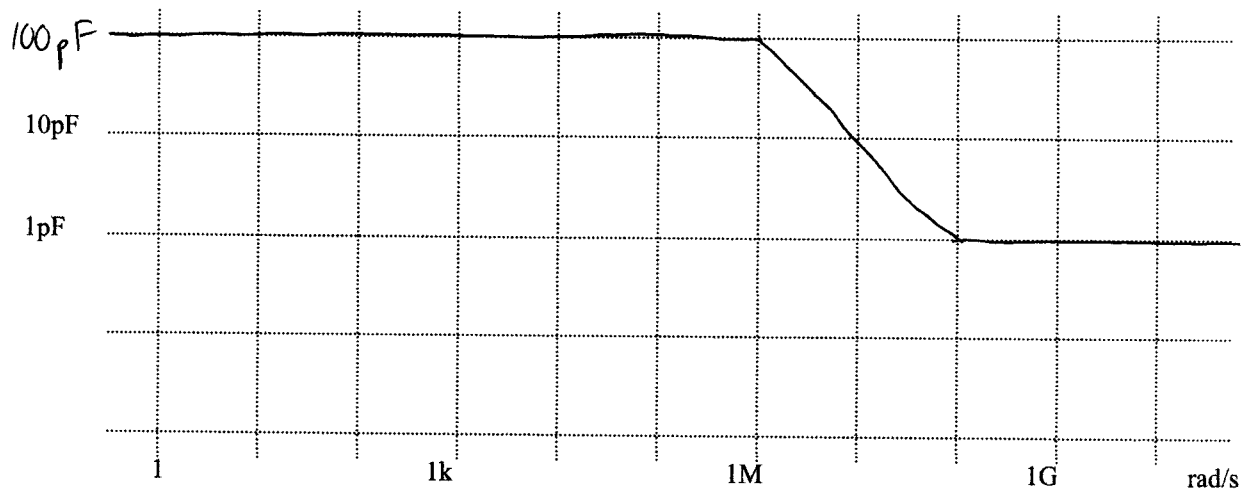problem 6, part b) magnitude of second stage input (Miller) capacitance



problem 6, part c) second stage input impedance, and R_{o1}

