

EE140 HW8

$$(1) I_S = 10^{-15} \text{ A} \quad I_D = 10^{-5} \text{ A}$$

$$n = 144$$

$$a) V_{D1} = \frac{kT}{q} \ln\left(\frac{I_D}{I_S}\right) = \frac{kT}{q} \ln(10^{10}) \approx 600 \text{ mV}$$

$$b) V_{D2} = \frac{kT}{q} \ln\left(\frac{I_D}{nI_S}\right) = \frac{kT}{q} (\ln(10^{10}) - \ln(144)) \approx 470 \text{ mV}$$

$$c) \Delta V_D = \frac{kT}{q} \cdot \ln(n) \approx \frac{5kT}{q}$$

T	ΔV_D
200K	86 mV
300K	130 mV
400K	170 mV

#1) 10 pts

a) 1 pt

b) 1 pt

c) 3 pts - 1 per temperature

d) 1 pt

e) 3 pts - 1 for each curve (-1 for unlabeled axis)

f) 1 pt for curves shift up, but difference does not change

d)

$$V_{D2} = V_{D1} - \Delta V_D$$

$$\begin{array}{ccc} \uparrow & & \uparrow \\ -1.5 \text{ mV/K} & & \ln(n) \cdot \frac{k}{q} \approx .43 \text{ mV/K} \end{array}$$

so tempco of V_{D2} is $-1.5 \text{ mV/K} - .43 \text{ mV/K}$

$$\approx -1.93 \text{ mV/K}$$

$$\textcircled{2} \text{ a) } \frac{\Delta V_D}{R_1} = 10 \mu\text{A}$$

$$R_1 = \frac{\Delta V_D}{10 \mu\text{A}} = \frac{130 \text{mV}}{10 \mu\text{A}} = 13 \text{ k}\Omega$$

T	ΔV_D	I
200K	86mV	6.6 μA
400K	170mV	13 μA

$$\text{c) } V_{R2} = 2\Delta V_D$$

T	V_{R2}
200K	172mV
300K	260mV
400K	340mV

#2) 10 pts

a) 1 pt

b) 2 pts, 1 for values at each temperature

c) 3 pts - 1 for V_{R2} at each temperature

d) 2 pts for adding line to plot from #1

e) 2 pts - 1 for temp coefficient, one for giving a fix


$$\text{d) } V_{\text{ref}} = V_{D1} + \frac{R_2}{R_1} \ln(n) V_T$$

T	V_{ref}	(see prev page)	slope = $-\frac{.64 \text{mV}}{\text{K}}$
200K	923mV		
300K	859mV		
400K	795mV		

e) Fix it by increasing R_2/R_1 to 3.

Tempo is $-0.64 \frac{\text{mV}}{\text{K}}$ (Need to add $1.5 \times .43 \text{mV/K}$)


Problem 1e & 2d

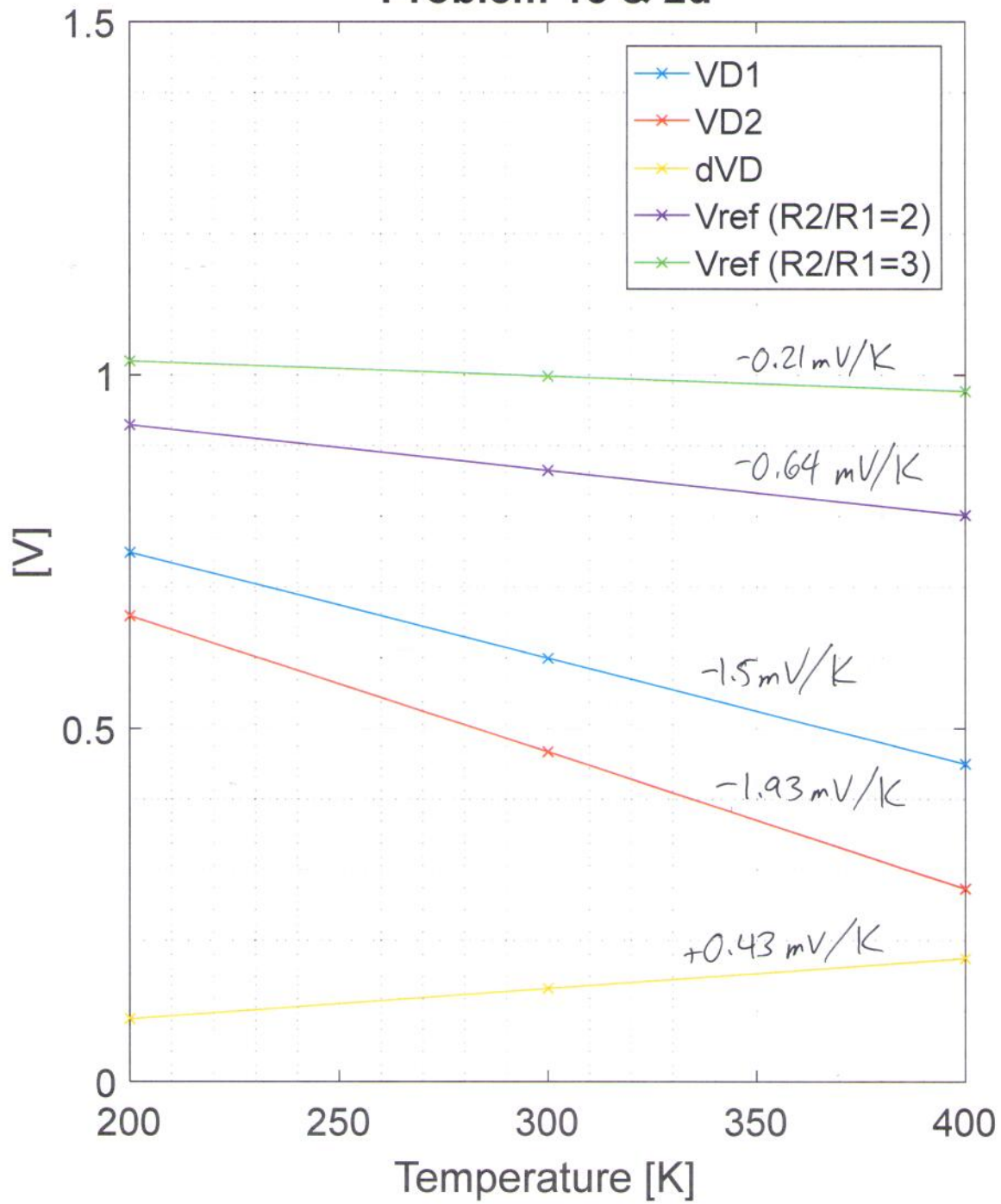

f) If I_d goes up by 2x, both V_{d1} and V_{d2} shift up by $V_T \cdot \ln(2)$

The difference between V_{d1} and V_{d2} DOES NOT CHANGE! It is constant regardless of the current.

(3)

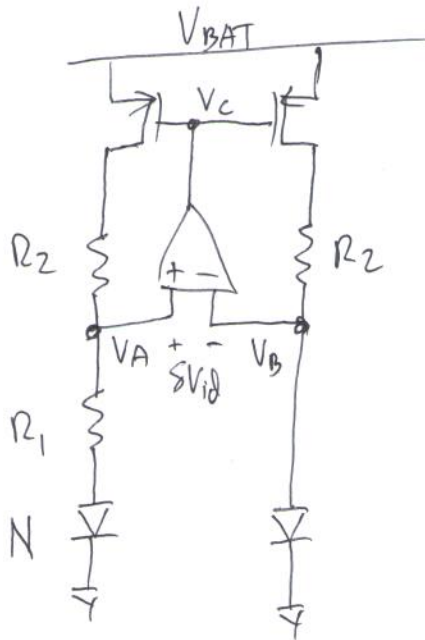

#3) 8 pts

a) 3 pts for writing an expression for differential gain

b) 3 pts - 1 each for estimating pole locations at A,B,C

c) 2 pts for some discussion of stability and compensation

(240 only)

#4) 4 pts for some discussion of stability

a) Apply sV_{id}

$$sV_A = A_v \cdot sV_{id} \cdot g_m \cdot (R_1 + R_D) \quad \left(R_D = \frac{V_{th}}{I} \right)$$

$$sV_B = A_v \cdot sV_{id} \cdot g_m \cdot R_D$$

Assuming in both cases that $R_2 + r_o$ is very large.

The differential output is $sV_A - sV_B$:

$$\frac{sV_A - sV_B}{sV_{id}} = A_v \cdot g_m \cdot R_1$$

but we know $I \cdot R_1 = \Delta V_{BE} = \ln(n) V_{th}$

$$\text{so } R_1 = \frac{\ln(n) V_{th}}{I} = \frac{\ln(n) \cdot 2 V_{th}}{g_m \cdot V_{ov}} \quad \left(g_m = \frac{2I_D}{V_{ov}} \right)$$

$$\frac{\delta V_A - \delta V_B}{\delta V_{id}} = A_v \cdot g_m \cdot \frac{\ln(n) \cdot 2V_{th}}{g_m \cdot V_{ov}} = A_v \cdot \frac{2 \ln(n) \cdot V_{th}}{V_{ov}}$$

b) Poles :

@ V_C $\frac{1}{R_{out, amp} \cdot (2C_{gs} + A_{v, PMOS} \cdot C_{gd} \cdot 2)}$ $A_{v, PMOS} = (g_m \times r_o // R_2 + R_D)$

@ V_A $\frac{1}{(R_2 + r_o) // (R_1 + R_D) \cdot C_{in, amp}}$

@ V_B $\frac{1}{(R_2 + r_o) // (R_1 + R_D) \cdot C_{in, amp}}$

Zeros : $\frac{g_m, PMOS}{C_{gd, PMOS}}$ (Also there is the diff pair current mirror pole/zero doublet)

c) Yes, depending on the pole/zero locations and resulting phase margin.

Can compensate by adding cap at node C_1 , or across nodes A and C_1 .