

b) $G_m = g_{m1} = 250 \mu S$

Ro: If $\lambda_n = \lambda_p$ and $I_{tail} = I_{d2}$, then $R_o = \frac{1}{4} (g_m r_o)$ $r_o = \frac{1}{4} (200) 800k = 40 M\Omega$

$A_v = G_m * R_o = 10,000 V/V$

c) Input common mode range

$Max = V_{dd} - V_{ov6} - V_{ov1} - V_{tp} = (1.2 - 0.1 - 0.1 - 0.2) = 0.8 V$

$Min = V_{g3} - V_{ov3} - V_{tn} - V_{tp} = (0.32 + 0.2) - 0.1 - 0.2 - 0.2 = 20 mV$ (approximately ground)

Output swing

$Max = V_{dd} - V_{ov5} - V_{tp} - V_{ov4} = (1.2 - 0.1 - 0.2 - 0.1) = 0.8 V$

$Min = V_{g3} - V_{ov2} - V_{tn} + V_{ov3} = (0.32 + 0.2 - 0.1 - 0.2 + 0.1) = 0.32 V$

d) $V_{g3_min} = V_{ov2} + V_{ov3} + V_{tn} = 400 mV$

New input common mode range

$Max = V_{dd} - V_{ov6} - V_{ov1} - V_{tp} = (1.2 - 0.1 - 0.1 - 0.2) = 0.8 V$ (unchanged)

$Min = V_{g3} - V_{ov3} - V_{tn} - V_{tp} = 0.4 - 0.1 - 0.2 - 0.2 = -0.1 V$

New output swing

$Max = V_{dd} - V_{ov5} - V_{tp} - V_{ov4} = (1.2 - 0.1 - 0.2 - 0.1) = 0.8 V$ (unchanged)

$Min = V_{g3} - V_{ov2} - V_{tn} + V_{ov3} = (0.4 - 0.1 - 0.2 + 0.1) = 0.2 V$

e) $CL = 1 pF$

i) Dominant pole at output = $1/(R_o * CL) = 25,000 rad/s$

ii) $C_{gs5} = (2/3) W * L * C_{ox} + C_{ol} * W \approx 80 fF$

$\omega_{p,mirror} = g_{m5} / (2 * C_{gs5}) = 250 \mu S / (160 fF) \approx 1.6 Grad/s$

$\omega_{z,mirror} = g_{m5} / (C_{gs5}) = 250 \mu S / (80 fF) \approx 3.2 Grad/s$

iii) $C_{gs5} = (2/3) W * L * C_{ox} + C_{ol} * W \approx 40 fF$

$\omega_{p,cascode} = g_{m3} / C_{gs3} = 250 \mu S / (40 fF) \approx 6.3 Grad/s$

iv) $\omega_u = g_{m1} / CL = 250 \mu S / (1 pF) = 250 Mrad/s$

v) $PM = 180 - \text{atan}\left(\frac{\omega_u}{\omega_{P1}}\right) - \text{atan}\left(\frac{\omega_u}{\omega_{p,mirror}}\right) + \text{atan}\left(\frac{\omega_u}{\omega_{z,mirror}}\right) - \text{atan}\left(\frac{\omega_u}{\omega_{p,cascode}}\right)$

$PM = 180 - 90 - 9 + 4 - 2 = 83 \text{ degrees}$

Close enough to approximate as a one pole amplifier.

Rubric for Problem 1:

#1) 31 pts

a) i) 5 pts for correctly filled out table

a) ii) 4 pts - 1/2 pt each for the 8 voltages listed

a) iii) 4 pts for correctly filled out table

b) 3 pts, 1 each for G_m, R_o, A_v

c) 4 pts, 1 each for input max/min, and output max/min

d) 5 pts, 1 for V_{g3_min} and 1 each for input max/min, and output max/min

e) i) 1 pt


e) ii) 2 pts, 1 for pole, 1 for zero

e) iii) 1 pt


e) iv) 1 pt

e) v) 1 pt for PM approximately 90

(2) a)

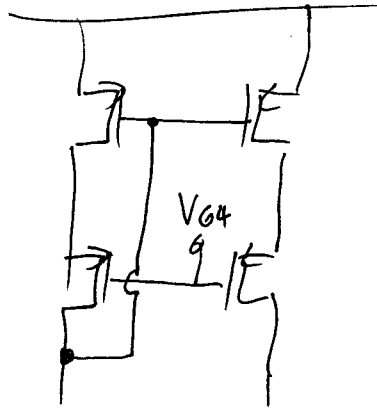

b)

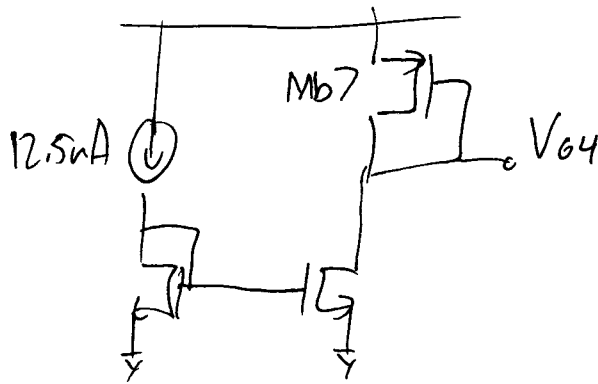

Use the existing 12.5uA source to mirror a current over to Mb7

Want $V_{S4} = V_{DD} - V_{ov5}$ so $V_{G4} = V_{DD} - V_{ov5} - V_{tp} - V_{ov4}$

To get $2 \times V_{ov}$ for Mb7, size it to be

$\frac{1}{4} \left(\frac{W}{L} \right)_4$ and leave the others the same size.

#2) 6 pts

a) 2 pts for correctly redrawing

b)

2 pts for drawing bias circuit

1 pt for what gate voltage to bias it with

1 pt for dimensions and why

③ a) The second stage gain is inverting so this is still negative feedback,

$$b) f = \frac{R_2}{R_1 + R_2}$$

$$V_{out} = \frac{A}{1 + Af} V_{in} \approx \frac{R_1 + R_2}{R_2} V_{in} \text{ for large } A$$

$$c) A = A_o g_m (R_L // r_o // (R_1 + R_2))$$

$$T = Af = A_o g_m \frac{(R_L // r_o) \cdot R_2}{R_1 + R_2 + R_L // r_o}$$

#3) 5 pts

a) 1 pt for second stage is inverting; negative feedback

b) 2 pts; 1 pt for f, 1 for V_{out}

c) 2 pts for writing an expression for loop gain

(4) a) Gain is $\frac{C_1}{C_2}$ so integer ratios from 1-8

b) $A_v = 8$ because it has the smallest feedback factor ($f = 1/a$) and gain error is $\frac{-1}{Af}$

c) $\frac{1}{Af} = 0.4\%$ $A \geq \frac{1}{(\frac{1}{9})(0.004)}$ $A \geq 2250 \text{ V/V}$

d) Need about 6τ to get to $< 0.4\%$

$6\tau = 10 \mu\text{s}$ $\tau = 5/3 \mu\text{s}$

#4) 4 pts
a) 1 pt for ratios of 1-8
b) 1 pt for identifying gain of 8 as $f=1/9$
c) 1 pt for calculating A_0
d) 1 pt for calculating bandwidth

Amp will be the slowest at highest gain settings

$GB = \frac{1}{f} \cdot \frac{1}{\tau} = \frac{9}{5/3 \mu\text{s}}$ $GB = 5.4 \cdot 10^6 \text{ rad/s}$

(5) a) compares at ground

b) No. If $V_{in} > V_{ref}/2$ then V^+ swings below ground.

#5) 2 pts
a) 1 pt for bottom rail
b) 1 pt for it swings below bottom rail

(240A only) #6) 6 pts
a) 2 pts
b) 4 pts