

Specification	Requirement
V_{DD}	1.2 V
Settling Accuracy (f=8)	< 0.4 %
Settling Time (f=8)	< 5 μ s
C_L	400 fF
Input Common Mode Range	Includes ground
Temperature	-40 C < T < +85 C

Recommended Design Strategy

- 1) Calculate the requirements for open loop gain and unity gain bandwidth.
- 2) Choose device lengths ($L = 1 \mu\text{m}$ is a good place to start) and overdrive voltages.
- 3) Calculate the transconductance required for the bandwidth and the current given your choice of overdrive voltage.
- 4) Calculate widths for all transistors. Start with the current mirror for the input diff pair and work your way toward the output. The table below should give you a reasonable place to start with hand calculations using the quadratic model.

	V_{th}	λ (@ $L=1\mu\text{m}$)	μC_{ox}
nmos1v	0.18 V	0.08 1/V	250 $\mu\text{A}/\text{V}^2$
pmos1v	0.16 V	0.05 1/V	125 $\mu\text{A}/\text{V}^2$

5) After sizing all transistors run a DC sim and check all the voltages and currents (Don't forget to apply a DC bias at the input). If the simulated values are very far off from what your hand calculations predicted, STOP! Go back through systematically and look for the discrepancy. If your DC bias is wrong, your amplifier is never going to work as expected.

6) Once your DC bias is working, use the test bench (see below) to check the AC small signal frequency response of your amplifier. If you fail to meet your gain or bandwidth specs, think about what you need to change in order to increase the gain or bandwidth and make those

changes. Keep track of what changes you make and what their effects were (making copies of your schematics with revision numbers is recommended). Continue this strategy until you have met all specs.

7) You'll likely find that one temperature condition is more difficult to meet than the others. It is easiest to focus on getting your amplifier working under this most difficult constraint, then the other temperatures should achieve the specs with ease.

Test Bench

We often use components from analogLib to test our circuits (things like voltage sources, etc) but we want our schematics to only include real devices that we can fabricate (this becomes important for layout). The solution is to create a test wrapper which turns our schematic with real devices into a component with input and output pins. We can then create a new schematic, instantiate the symbol of our circuit, and attach analogLib parts to the pins for testing.


Since we will use test benches to evaluate your final project performance, you will get familiar with the process in this lab. The test bench has already been created for you as an example. The overview of the steps to use the test bench are outlined below, and then explained in detail:

- 1) Copy over the test bench files to your directory
- 2) Add the test bench to your library path
- 3) Copy your schematic to the test bench library
- 4) Load saved state and run simulation

The Detailed Steps:

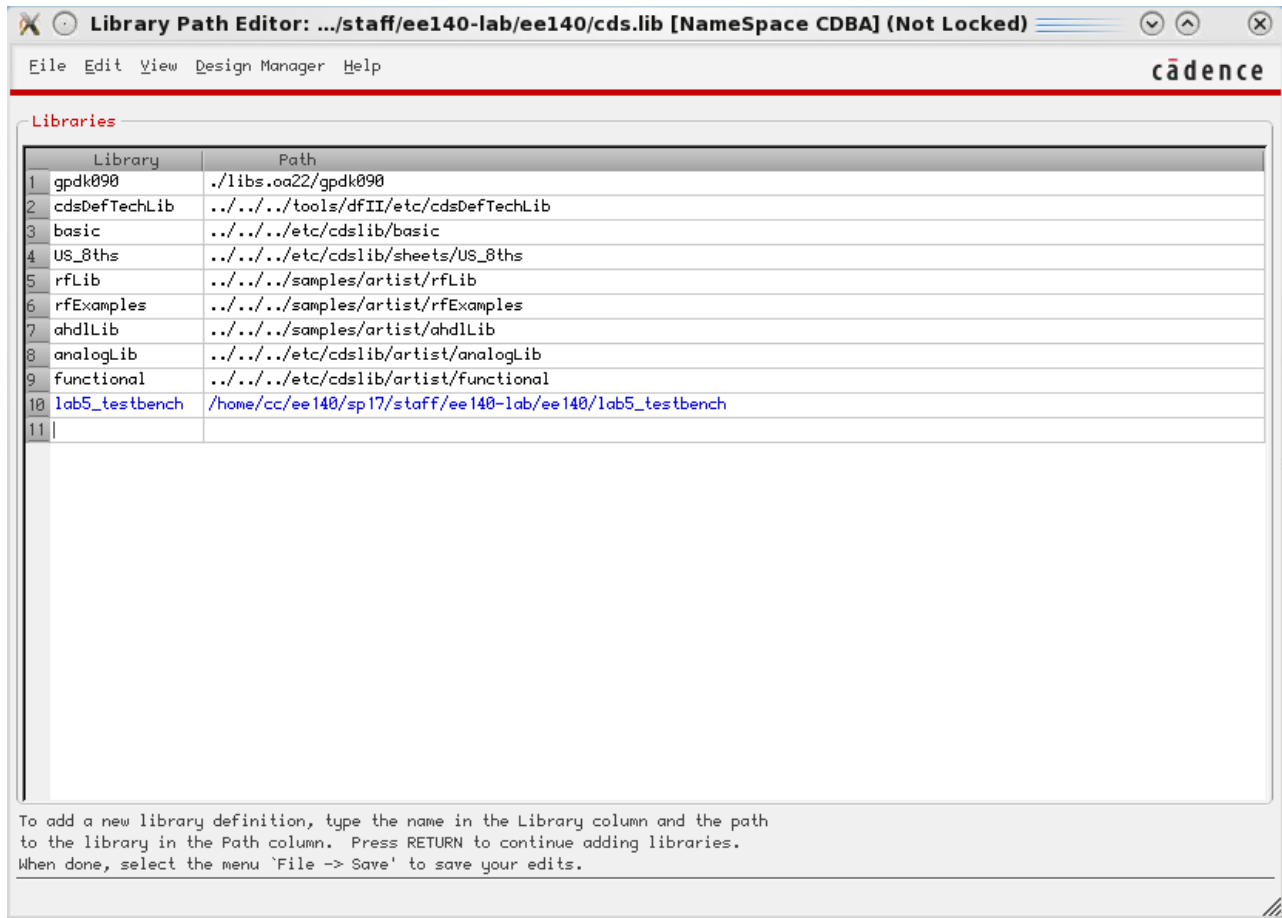- 1) Copy over the test bench files to your directory
 - From within your ee140 folder (or wherever you launch cadence from) run:

```
cp -R /scratch/ee140/lab5_testbench ./lab5_testbench
```
- 2) Add the test bench to your library path
 - In Library Manager, go to Edit > Library Path
 - At the bottom, add "lab5_testbench" and the path to where you copied the files (see example screenshot).
 - Save the changes to your library path and you should now have the test bench in your list of libraries.



3) Copy your schematic to the test bench library

- Inside “lab5_testbench” you will two cells:
 - “amplifier” contains the symbol view only. You should copy your schematic view into this location by right clicking your schematic, choosing copy, and filling out the form as shown below.
 - Your schematic needs to have the same pin names and types (inputOutput) as the symbol.
 - If you get warnings about data.dm, they are safe to ignore and overwrite.



5) Load saved state and run simulation

- The other cell inside lab5_testbench has two views. One is the test bench schematic which instantiates your amplifier symbol along with analogLib parts for testing. The other is a saved ADE state called “saved state”. Saved states allow you to save a particular simulation configuration so that you can easily run it again later.
- Double click on “saved state”. This will open ADE with DC and AC simulations already set up. There are also variables for VDD and the common mode input voltage which default to 1.2 V and 0 V respectively. Click run. If you have set everything up correctly a plot should open showing the magnitude and phase response of your amplifier.

Debugging

It's a good idea to build things in pieces and test as you go. You could start with the bias network, building up the circuit one leg at a time and verifying that you get the expected gate bias voltages, and then adding in the transistors in the signal path. Or you could build the signal path first, with ideal sources to set biases, and verify that it operates the way that you expect before adding in the bias network.

“Test as you go” means “do a hand analysis to estimate bias point voltages and currents, small-signal model parameters, gain, BW, etc., and then check with simulation to make sure that is what your circuit is doing”. If SPICE and hand analysis don't match, stop! Go back and figure out if your analysis is wrong, or you built the circuit wrong, or what. A DC plot of V_{out} vs. V_+ will tell you gain and output swing (take a derivative and see how close you can get to the rails before the gain drops off). That same plot with several different values for V_- will give you an idea of what your input common mode range is, and how gain and swing vary with input common mode. Estimate phase margin, and then put the amplifier in unity gain feedback and see if the response to a step input looks like you expect.

Deliverables (via PowerPoint)

- Show how you calculated gain and bandwidth requirements.
- Schematic of opamp and bias generation with sizes and currents annotated.
- Bode plot of amplifier frequency response (mag and phase)
- The following table:

Temperature	DC Gain	Unity Gain Bandwidth	Phase Margin
-40 C			
25 C			
85 C			

And a reminder....

A Note on Plots in Cadence

- The default plotting options in Cadence are garbage for presentations.
- The pro-level thing to do is export the data and plot with MATLAB, Excel, etc.
- Cadence plots are only acceptable for submission if at a minimum the following steps have been performed:
 - Graph > Properties > Set background to white > OK
 - Graph > Properties > Graph Options > Font > Fixed [Sony] > Size 18
 - Right click on traces > Width > Extra Thick
- Even with these adjustments, the plots are still not great for presentation. You can experiment with other settings, but they will never look as good as if you had exported.

A Note on Schematics in Cadence

- Like with default plots, schematics in Cadence are poor.
- Drawing your circuits neatly goes a long way in making them understandable.
- If you want really nice schematics, use Adobe Illustrator.
- Otherwise to get decent schematics from Cadence, follow these steps:
- File > Export Image
 - > Background > White
 - > Foreground > Black
 - Bi-color
 - Selected Area > Select > Draw a box around your circuit (It is not click'n'drag)
 - Choose a name, then Save to File
- Annotate sizes and nodes onto schematics by adding labels in post-processing.