

Mittern

Lab 5

HW

Project

Cascade op-amp

telescopic


folded

2 stage = increase gain


decouple in/out CM/swing

drive resistive loads (moderate)

problem: stability

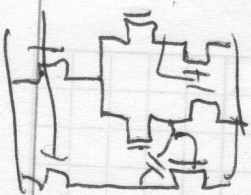

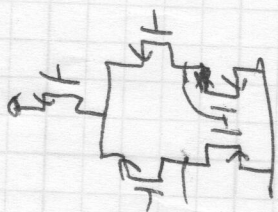Seen several op-amps now. All get used in
very common
and die



good: simple!

easy sizing

single pole, $PM \sim 90^\circ$

if we don't need resistive loads (i.e. just capacitive)

there are other topologies that are

- single stage

- high gain

- good in/out CM/swing

limits
- input common mode


- output swing

- low gain

- high impedance loads only

17SP WILL


148/240A

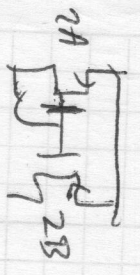

Add { 1BC } to increase

output resistance, gain


(doesn't work w/ resistive load)

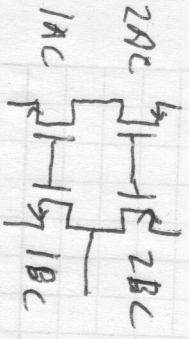

Add { 1AC } for symmetry

and to improve/biasing

telescopic cascode

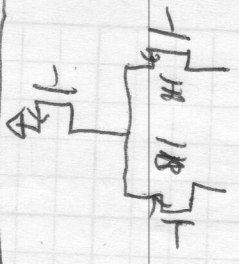




good: high gain

single pole \Rightarrow stable

not so good: in/out $< m/s/w/s$

So... very popular solution: folded cascode

"folding"

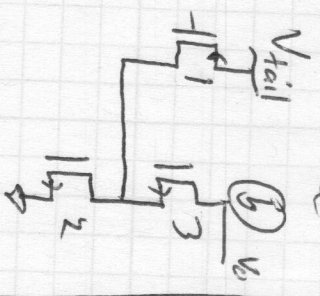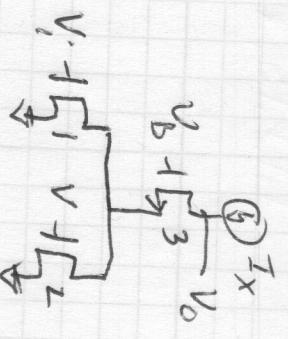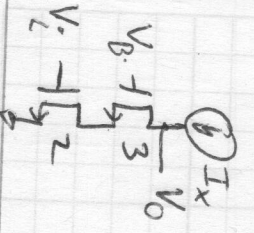

$g_{m2}(g_{m3}r_{o3}r_{o1}) - g_{m1}(g_{m3}r_{o3})(r_{o1}r_{o2}) \Rightarrow$ same!


Simple load

easy, but restricts output swing

better: use b_n, b_p

size b_n st.


$V_{GSb_n} \approx V_t + 2V_{ov1}$

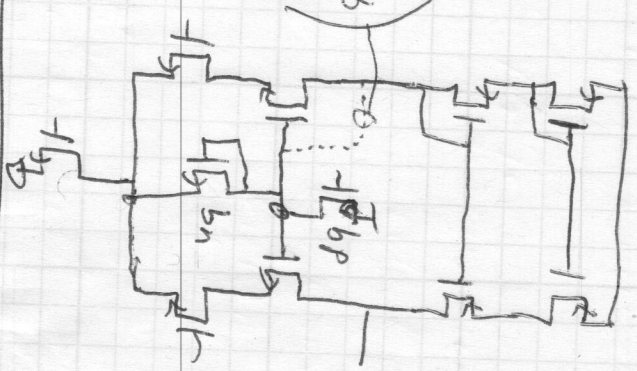

9.08

fig 9.12

$G_m = -\frac{1}{2}g_{m1}$
 $R_o = ?$

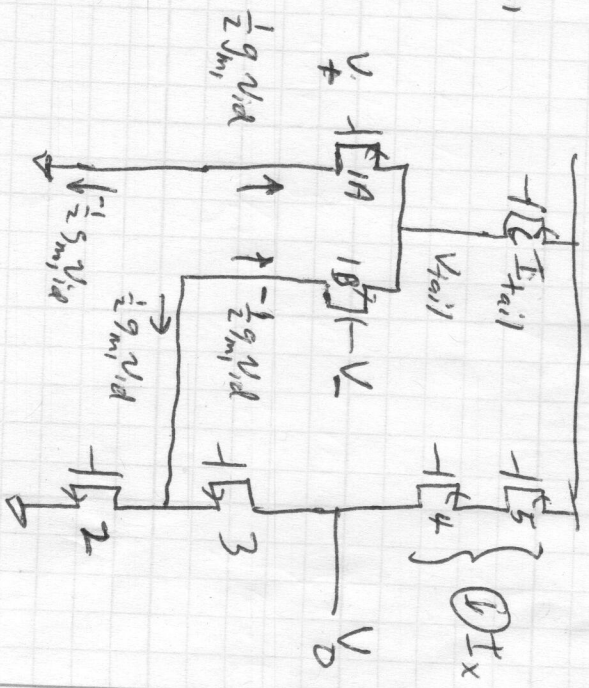

$I_{DL} = I_X + \frac{1}{2}I_{tail}$

$$R_o = R_{sup} \parallel R_{DN}$$

$$R_{up} \approx g_{m4} r_{o4} r_{o5}$$

$$R_{DN} = g_{m3} r_{o3} (r_{o2} \parallel r_{o1B})$$

Typically

$$I_{D3,4,5} \approx I_{D1A,2B}$$

if so $I_{D2} = I_{D3} + I_{D1B} = 2 I_{D1B}$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} \quad r_{o1B} = \frac{1}{\lambda_1 I_{D1B}}$$

output swing

$$V_{o,min} = V_{G3} - V_{\epsilon n} \geq V_{ov2} + V_{ov3}$$

depends on how you bias V_{G3}

$$V_{o,max} = V_{G4} + |V_{ZP}| \leq V_{D6} - |V_{ov4}| - |V_{ov5}|$$

if $\lambda_n = \lambda_p$ then $r_{o2} \approx \frac{1}{2} r_{o1B}$

$$r_{o2} \parallel r_{o1B} = \frac{1}{3} r_{o1B} = \frac{1}{3} r_{o3,4,5}$$

$$R_{DN} = g_{m3} r_{o3} \left(\frac{1}{3} r_{o3,4,5} \right)$$

$$R_{up} \parallel R_{DN} \approx \frac{1}{4} g_{m4} r_{o4}^2$$

$$A_v = -g_{m4} R_v = + \frac{1}{8} (g_{m4} r_{o4})^2$$

Input common mode

$$V_{i,cm,max} = V_{D0} - |V_{ov6}| - |V_{ZP}| - |V_{ov1}|$$

$$V_{i,cm,min} = V_{S3} - |V_{ZP}|$$

$$V_{S3} = V_{G3} - V_{\epsilon n} - V_{ov3} \geq V_{ov2}$$

lowest possible

$$V_{i,cm,min} = V_{ov2} - |V_{ZP}| < 0$$

input common mode below ground!