

Lab 5
HW 9

Folded cascode



circuits, sizes, gain
freq response
biasing

with PMOS diff pair

- common-mode input extends below 0
(if $|V_{tp}| > V_{s3} = V_{D2}$)
- mostly single-pole response
dominant pole = $\frac{1}{R_D C_L} = \frac{2}{g_m r_o^2 C_L}$
- bias for $M4, M5, M3$?
- recover other half of g_{m1} ?

Last tile

- cascodes give sig R_D
- V_{G3} sets V_{S3} bias point
 $V_{S3} = V_{G3} - (V_{tn} + V_{ov3})$
- can hang many different things off of V_{S3}

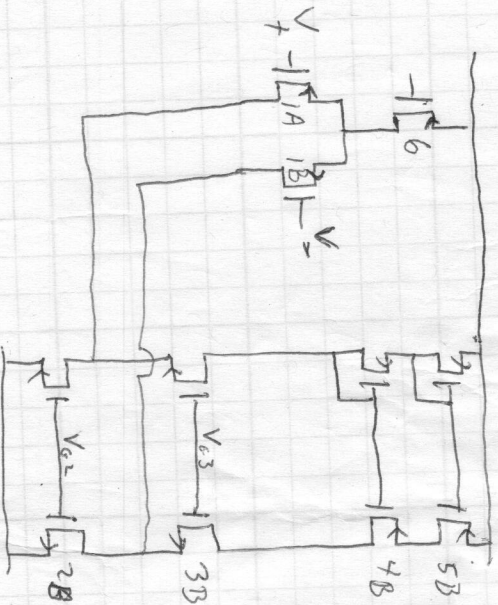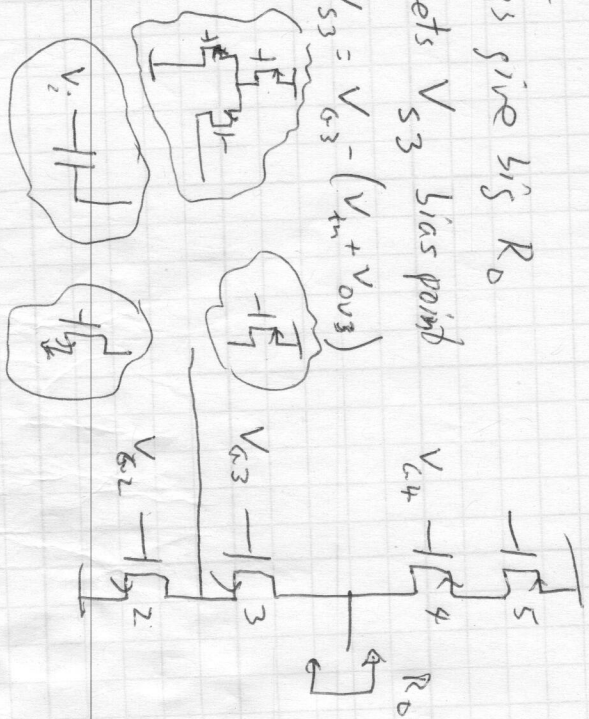

Lab 5
HW 9


Usually current in 1, 3, 4, 5 are the same (signal path)

if so, then $I_{D3A} = I_{D1A} + I_{D3A} = 2 I_{b1} = I_{tail} = I_{b6}$

$(\frac{V_c}{L})_1 = (\frac{V_c}{L})_4 = (\frac{V_c}{L})_5$

$(\frac{V_c}{L})_6 = 2 (\frac{V_c}{L})_1$

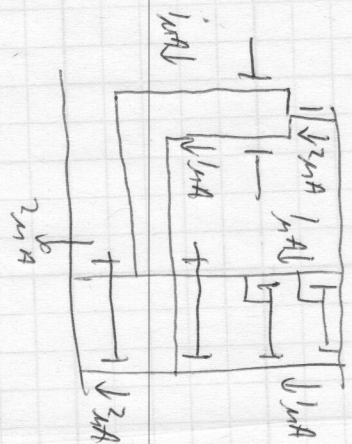$(\frac{V_c}{L})_2 = 2 (\frac{V_c}{L})_3$



What frequency response? Mirrors

Dominate pole

$\frac{1}{R_o C_L} \Rightarrow \omega_u = \frac{g_m R_o}{R_o C_L} = \frac{g_m}{C_L}$

mirrors (2) $\omega_{pms} = \frac{g_{ms}}{2 C_{gs}}$

$\omega_{zms} = 2 \omega_{pms}$

$2 \omega_{zms}$ or $2 \omega_{pms}$?


R_o unchanged from $\omega_{pms} \approx \frac{1}{2} (g_m r_o) r_o$

$G_m = -\frac{1}{2} g_m + \frac{1}{2} g_m$

$2 I_B$ $2 I_A$ mirror

$G_m = -g_{m1}$

$A_v = \frac{1}{4} (g_m r_o)^2$

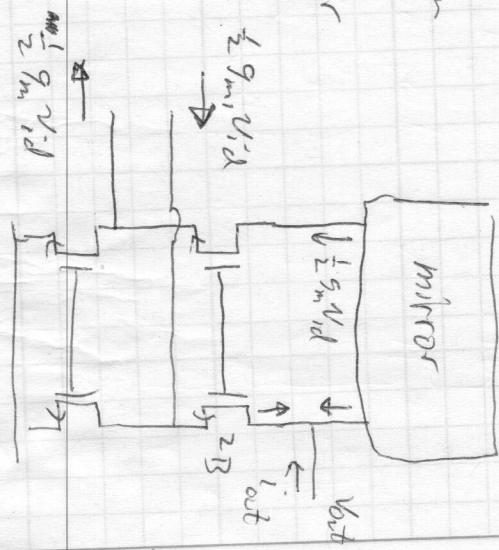

single cascade

$i_i = g_m v_{gs} + \frac{1}{r_o} v_{ds} + s C_{gs} (-v_s)$


$= (g_m + \frac{1}{r_o} + s C_{gs}) (-v_s)$


$v_{gs} = \frac{-i_i}{g_m (1 + \frac{1}{g_m r_o} + \frac{s C_{gs}}{g_m})}$

$i_o = g_m v_{gs} = g_m (-v_s)$

$= \frac{+i_i}{1 + \frac{1}{g_m r_o} + \frac{s}{\omega_{pc}}}$

$\omega_{pc} = \frac{g_m}{C_{gs}}$

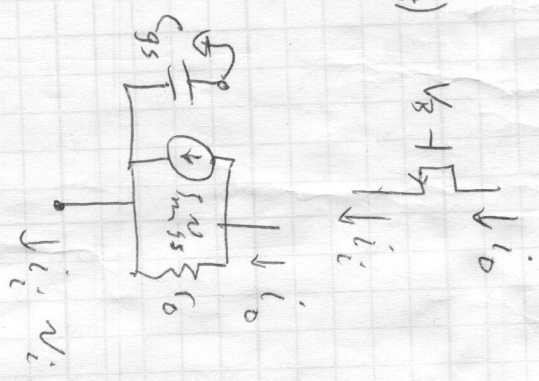

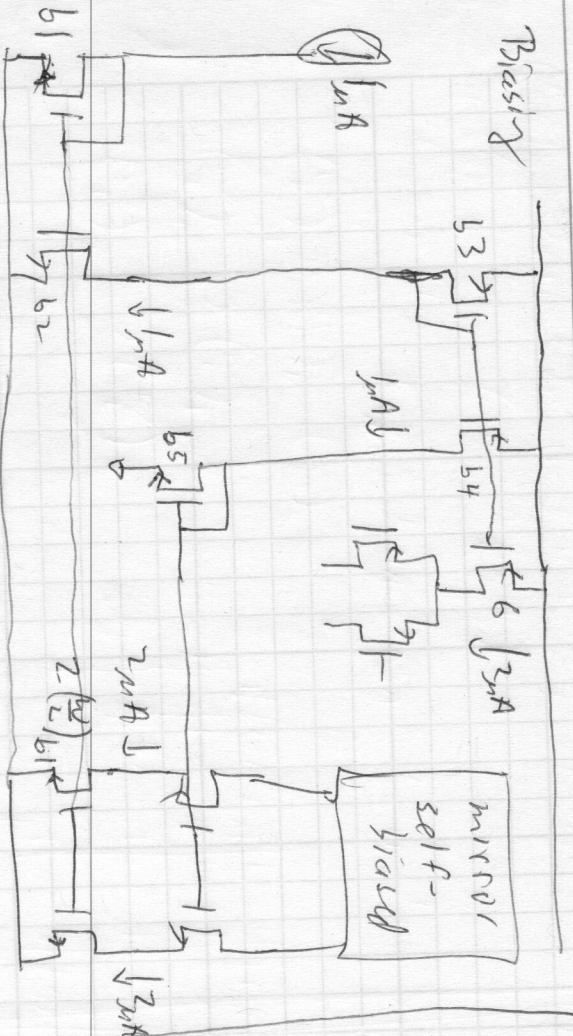

Size b1 to get the right V_{ovn}

$$\left(\frac{W}{L}\right)_{2A} = 2 \left(\frac{W}{L}\right)_{b1}$$


$n = 2, 3$

Size b3 to get the right V_{ovp}

$$\left(\frac{W}{L}\right)_6 = 2 \left(\frac{W}{L}\right)_{b3}$$

How to size b5 to get desired V_{G3} ?

One way:

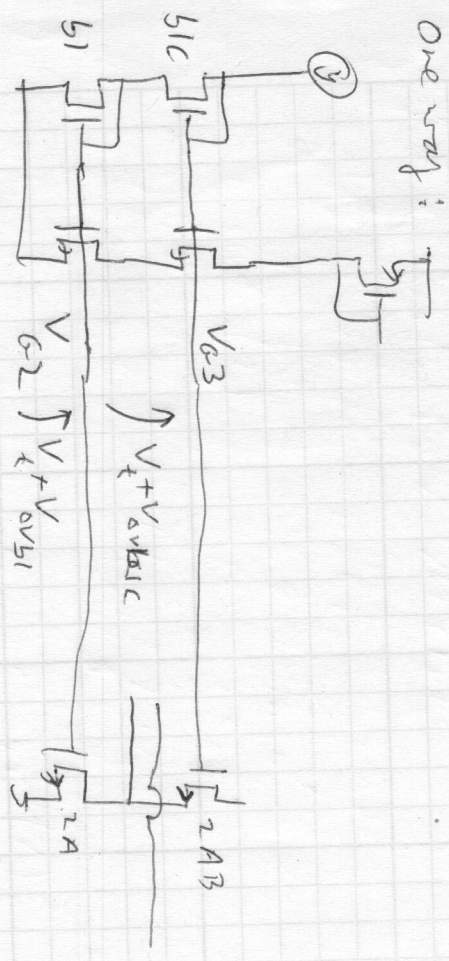

$$V_{G3} = 2V_t + 2V_{ov} \Rightarrow V_{D,min} = V_t + 2V_{ov}$$

$$\text{and } V_{D,min} = V_{G3} - |V_{tp}| = V_{tn} + V_{ovD} - |V_{tp}| > 0$$