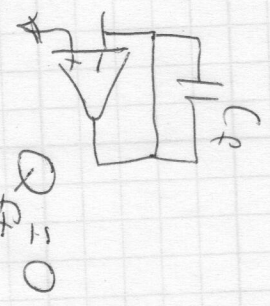


$\phi_1 = \frac{V_1}{1 + C_1}$


$Q_{1+} = V_1 C_1$



$Q_{F+} = 0$

Must have op-amp stable in unity gain!  
 Must be able to pull output to ground

how fast?

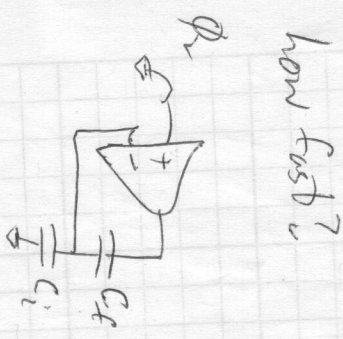

$F = \frac{C_f}{C_1 + C_i} \left( \neq \frac{1}{C_i/C_1} \right)$

if  $C_i = 8C_f$

$A_v = 8$

$F = \frac{1}{9}$


$n = 7 \Rightarrow 0.1\%$

$\omega_{pdc} = f_w \omega_n$

$\tau = \frac{1}{f_w \omega_n}$

need  $n\tau < T_2$

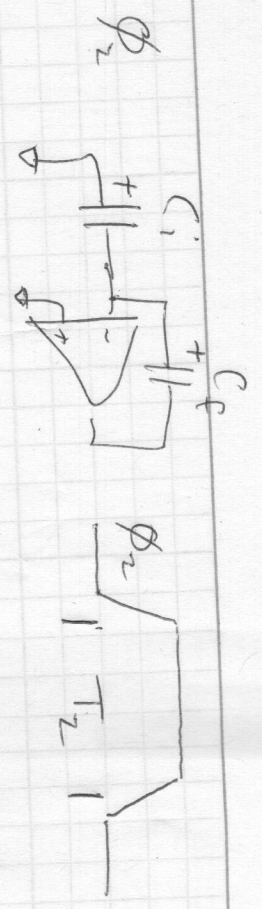$\frac{n}{f_w \omega_n} < T_2 \Rightarrow \omega_n > \frac{n}{f T_2}$



after settling



$V = 0 \Rightarrow Q_{1+} = Q_{2+} = 0$

$Q_{F+2} = Q_{1+2} = -V_i C_i$



$V_{out} = V_i - V_{CF} = 0 - \frac{Q_{F+2}}{C_f} = + \frac{C_i}{C_f} V_i$



Programmable gain

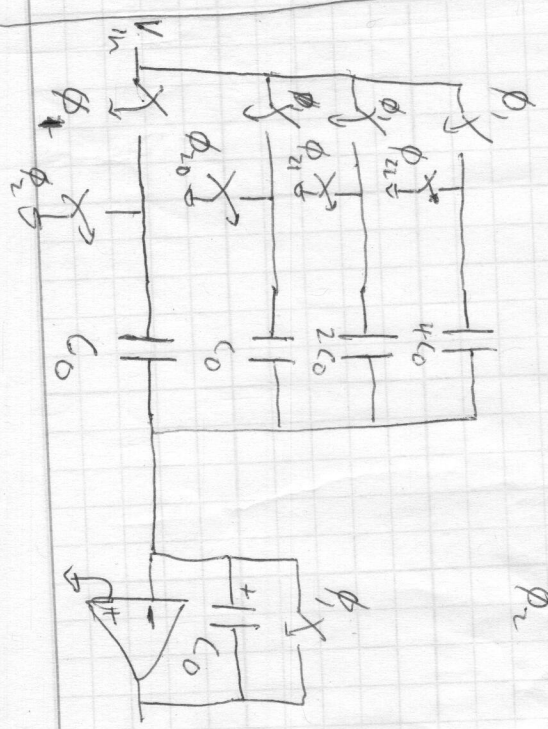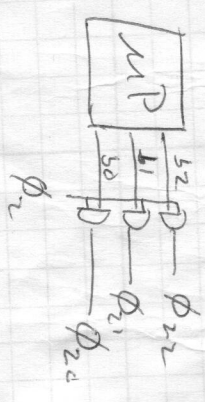

Cap DAC

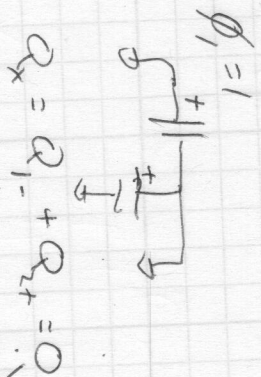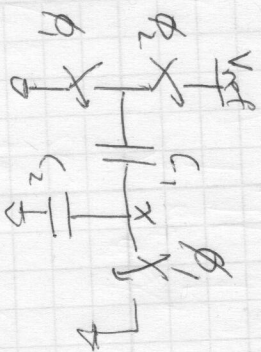

$\phi_1=0, \phi_2=1$

$\phi_2=1$




$Q_x = Q_{1-} + Q_{2+} = 0$

$= -C_1(V_{ref} - V_x) + C_2 V_x$

$(C_1 + C_2)V_x = C_1 V_{ref}$

$V_x = \frac{C_1}{C_1 + C_2} V_{ref}$


$Q_x \text{ still } 0$

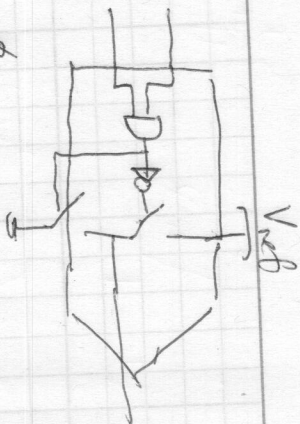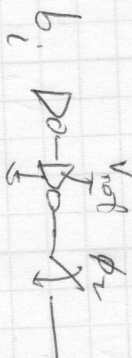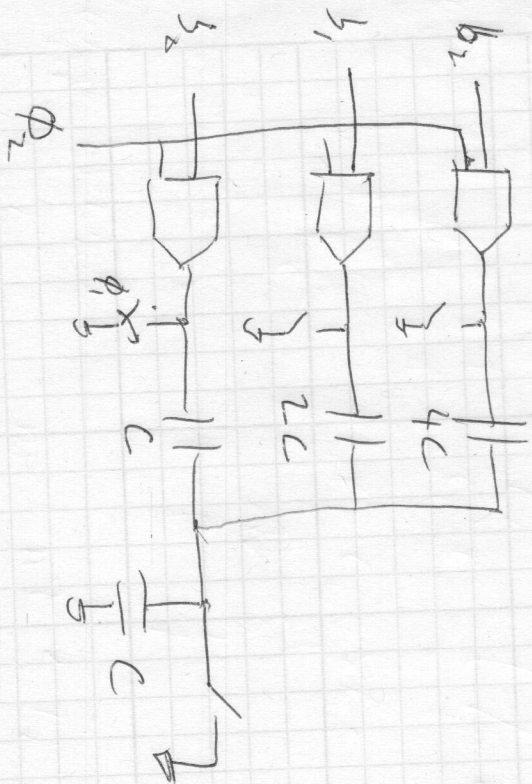

$V_o = \begin{cases} 2 & \phi_1=0 \\ 1 & \phi_1=1 \end{cases}$

$B = [b_1 b_2]$	$C_1$	$C_2$	$V_{out}$
$0 [00]$	$0$	$8C$	$0$
$1 [01]$	$C$	$7C$	$\frac{1}{8} V_{ref}$
$2 [10]$	$2C$	$6C$	$\frac{2}{8} V_{ref}$
$3 [11]$	$7C$	$1C$	$\frac{7}{8} V_{ref}$

Single ADC

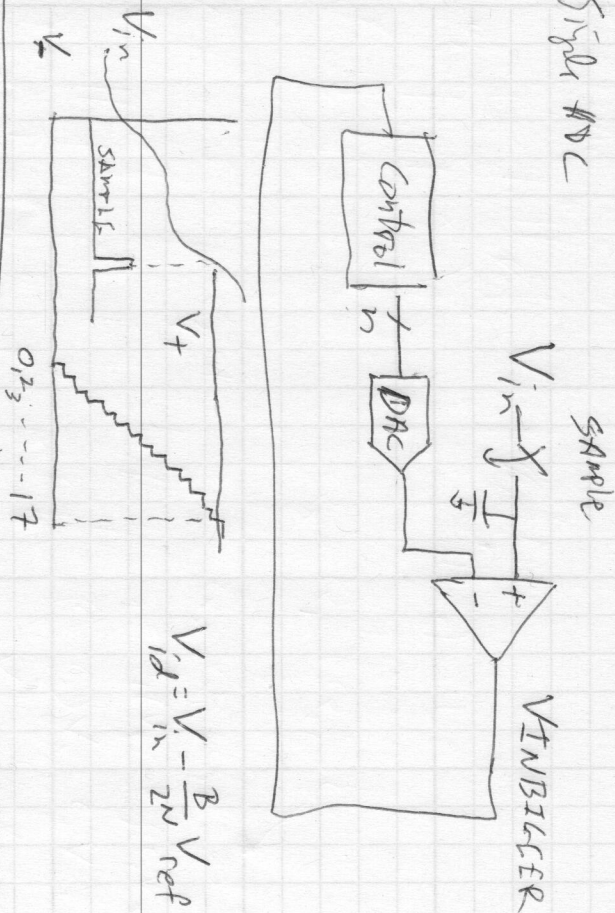

problems: slow - binary search

variable input offset

