


Corrections $< 1\mu A \Rightarrow$ wrong. Often higher.

You don't know enough to design \Rightarrow true in general!
 But you do know enough to meet the project specs


Test harness

Charge injection regulators

Test harness

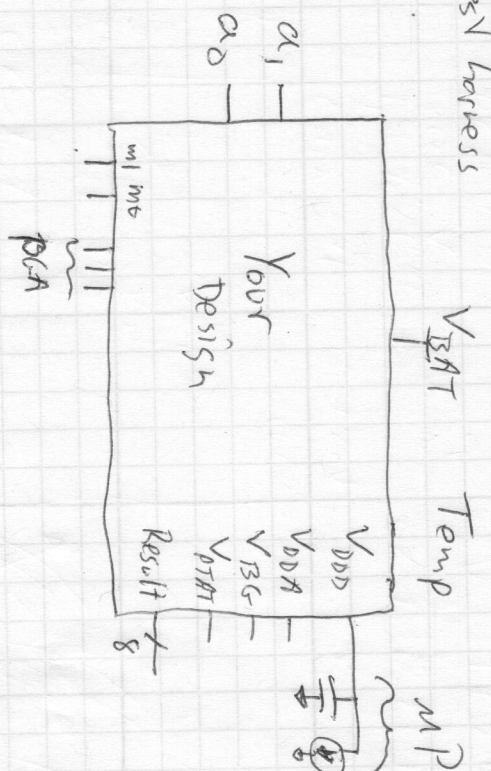

Regulators

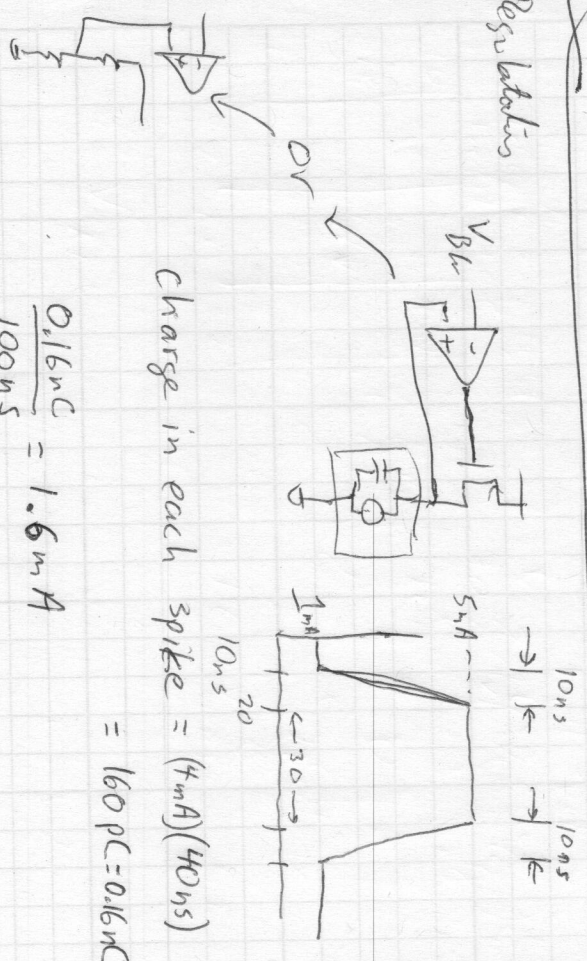


Charge in each spike = $(4\mu A)(40ns) = 160pC = 0.16nC$

$\frac{0.16nC}{100ns} = 1.6\mu A$

average current = $2.6\mu A$

$\frac{260\mu A}{MHz} \approx$ typical $32bit\mu P$

What if

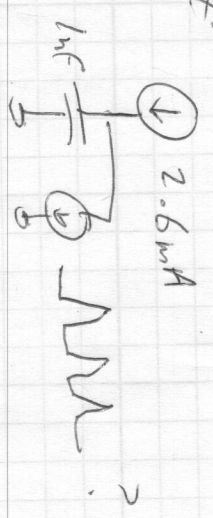

$\Delta Q = 0.16nC$ $\Delta V = \frac{\Delta Q}{C} = \frac{0.16nC}{1nF} = 160mV$

If you center the 10MHz dips, it meets the spec!



Debugging

Presently results

- make it clear what you are talking about
 what circuit - ADC w/ ideal input voltage and supply
 what test conditions - 25C, $V_{DD} = 1.2V$
 what expected result - $V_{ref} = 1.0V$
 Should see 5_7
 5_6
 5_7 so long as V_{ref} instead

Explain what it means
 "because there is charge leaking"


PGA ideal supply hardware

T_{amp}	70		
25		1mV	70mV
0			
V_{BAT}	1.6	2.4	3.2

Full system LSP error temp conversion


T_{amp}	70		
25	3	0	7
0		42	
V_{BAT}	1.6	2.4	3.2

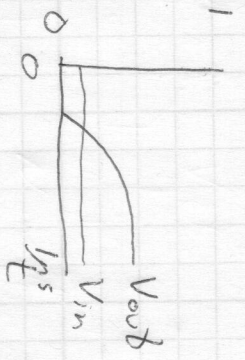PGA
 20C, $V_{BAT} = 3.6V$
 1pF load
 GAIN = 4



OK, but




can't see the error. 4mV? 10mV?

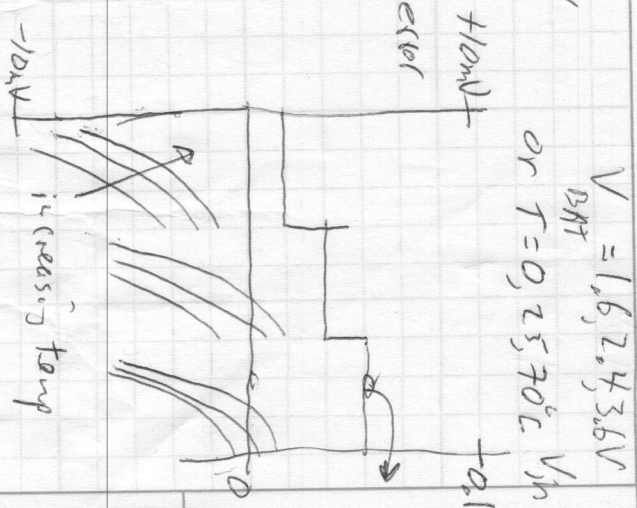

$V_{BAT} = 1.6, 2.4, 3.6V$
 or $T = 0, 25, 70C$


Comparators

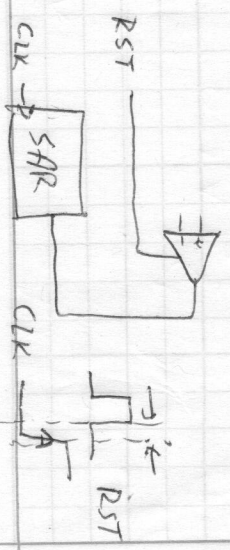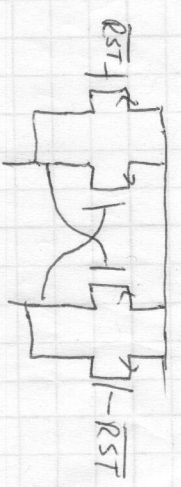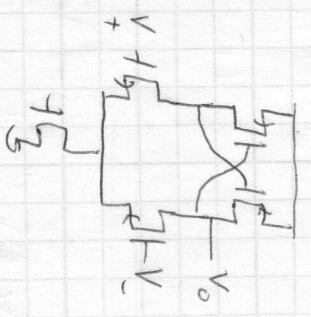- 1) use thick ox ($4 \times 2 V_T$) input devices
- 2) use carbon w/ strongarm




1.2 -
1.04 - does not need spec


1.03 -
1.14 - does not need spec

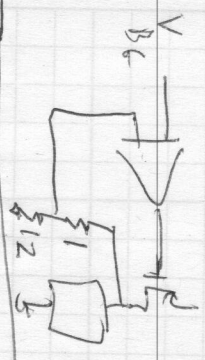


In feedback

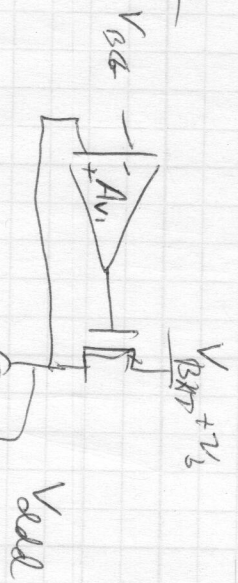

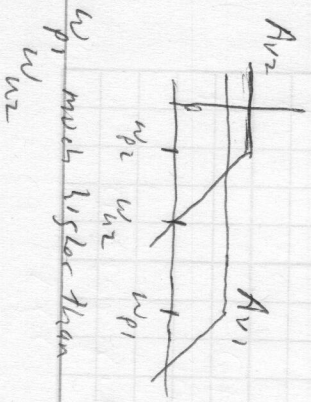For stability need poles separated, either



or

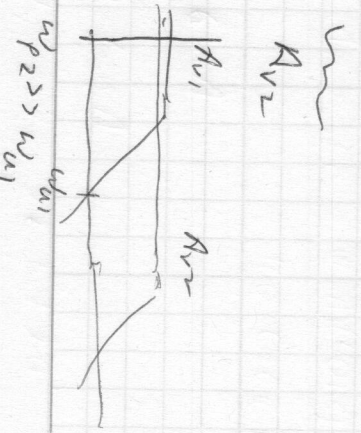


What about supply variation?

DC, AC

First, consider:

$$\textcircled{b} \frac{V_o}{V_i} = -g_m R_o$$

$$\frac{V_o}{V_x} = +g_m R_o$$

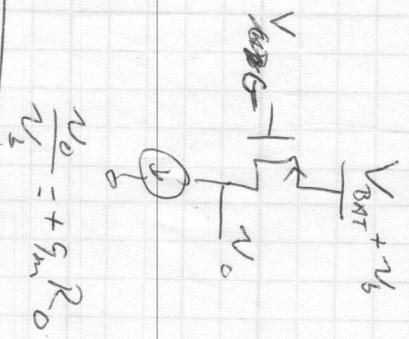

For distal neg, pretty clear. Output cap is huge, make w_p dominant, make 1st stage very low gain and fast. (short channels)

For analog regulators, if $w_p \ll w_{p1}$ then at 10 MHz, $V_\phi \approx 0$



$$\frac{V_{dcl}}{V_s} = +g_m R_o \quad \text{load}$$

$$\textcircled{c} \int \frac{1}{s} ds \Rightarrow V_s = 8mV$$