

EE140 / 240A Analog/Linear ICs

↳ more HW
↳ more project specs

Who am I? UCSD, UCSB, UCLA, UCS, DUST, UCB

TAs: Brad Wheeler
David Burnett

HW: generally due late Friday (9 AM sat)
this week: Monday
self-graded

Labs: Bipolar op-amps, ~~bits~~ ≈ 5 weeks?
any lab OK

What is analog?

- anything not digital

- many things that are digital: DRAM, SRAM, flash

digital communication - anything with speed
ethernet, HDMI, USB, RF


- interfaces to the real world. E.g. cell phone

inputs/sensors: XL, gyro, magnetometer, phones
camera, fingerprint sensor

outputs: speakers, displays, buzzer, backlight, flash

LEDs, humidity, barometric pressure
↳ sensors

Project: ~~all~~ most of the analog from an embedded MP

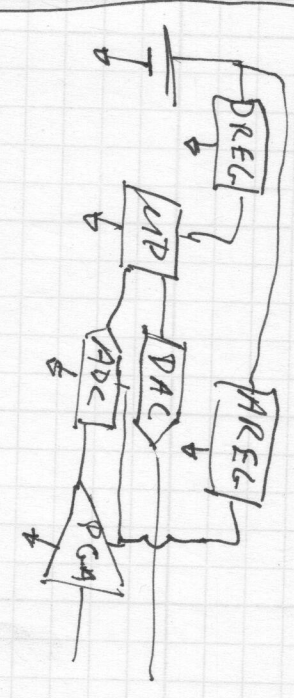

ee144
tapeout!

What is 1V? How do you know?

Bandgap reference (and temp sensor)

All of these contain an opamp.
All use feedback

battery charger

DC-DC converters

power-on reset

Who designs this stuff?

~~ADI~~ Apple, Broadcom

Apple, Samsung, Qualcomm, ...

Marvell, Intel, ...

>> \$25B

\$8B

Mkt 2015

- TI
- Infineon
- Skynworks
- ADI
- ST
- Maxim
- NXP
- LT
- ON

\$1.3B

\$25B

140/240A

1750


W/L

Key concepts

- Gain, BW, power
- noise, power
- feedback, stability
- Process, voltage, temp variation

Tools - hand analysis
 cadence, SPICE, layout+extract
 Same software as used in industry

carry op-amps, red op-amps

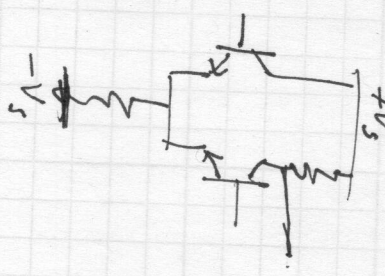

Are they good enough?
 How do we know?
 Hand analysis of all "concepts"
 SPICE simulation
 - verify hand analysis

What's an op-amp?

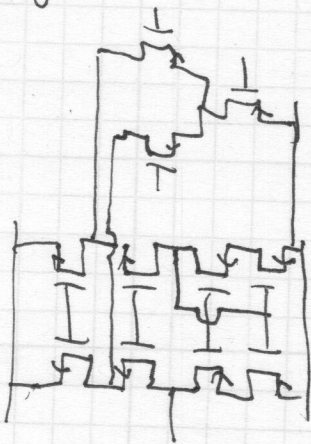


Fig 9.15

Gain	∞	100
BW	∞	1GHz
R_{in}	∞	10pF
R_{out}	0	1m Ω
CMRR	∞	60dB
input offset	0	10mV
Stability	uncond	OK?






What were you supposed to learn

- 160B, 105?
- frequency response, Bode plots
- device physics \rightarrow large signal model
- linearization: small signal model
- single transistor amplifiers: CS/CE
- diff pair? CG/CB CD/CC


inductors & capacitors are just freq. dependent resistors

$$Z = \frac{1}{j\omega C} \quad |Z| = \frac{1}{\omega C}$$

$$Z = j\omega L \quad |Z| = \omega L$$

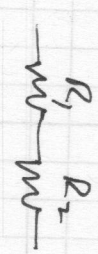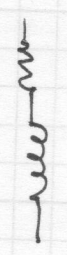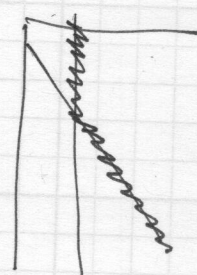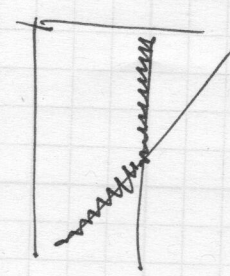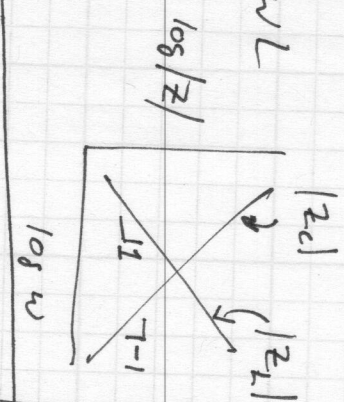

$\max(R_1, R_2)$

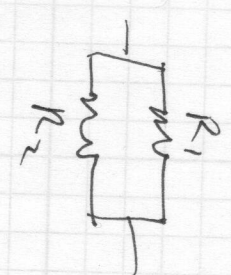

$\min(R_1, R_2)$

worst case error: $2^{\pm 1}$ with $R_1 < R_2$ or $R_2 < R_1$: $2^{\pm \frac{1}{2}}, \pm 450$

Device physics

Vacuum tubes

