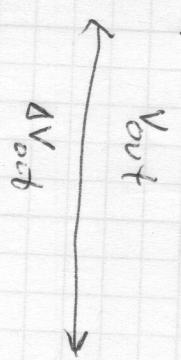


HW, Lab

OH for now Tues 11-12
F 4-5

large signal
 $A_v = -g_m R_o$
small signal




$A_v = \frac{\Delta v_{out}}{\Delta v_{in}}$

Device Models

lots of things look like

where V_{cont} has big impact on I_{out}


V_{out} has a small impact on I_{out}

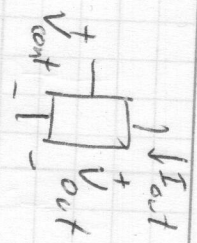

Vacuum tube - triode (pentode) 1907



B5T 1947

NFET 1927!
JFET

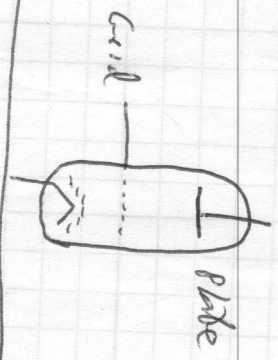

Large signal Models

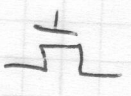
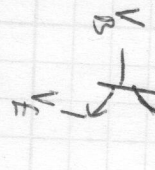
$I_c = I_s (e^{V_{BE}/V_T} - 1) (1 + \frac{V_{CE}}{V_A})$




$I_D = \begin{cases} 0 & V_{GS} < V_{th} \\ \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) & V_{GS} \geq V_{th} \end{cases}$

1/40/2408 17 SP W1L2




large signal behavior - follower

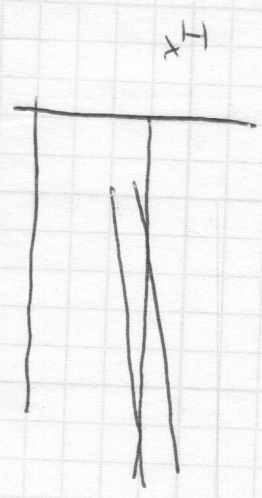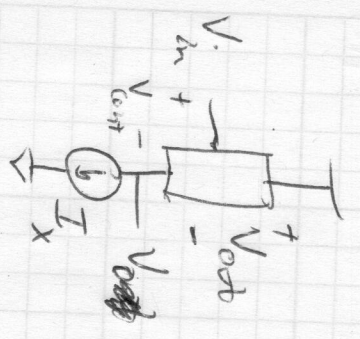

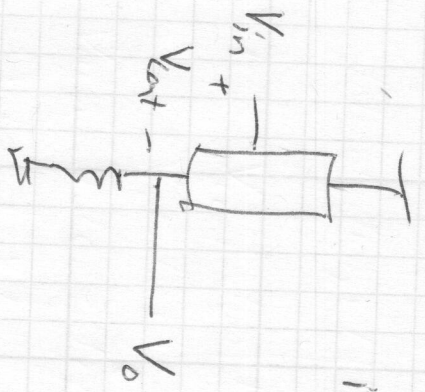Vout will not change much
Vo must follow Vin



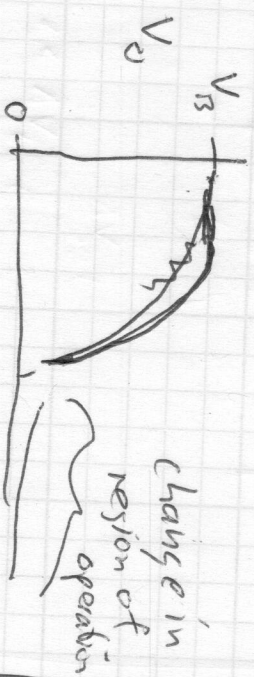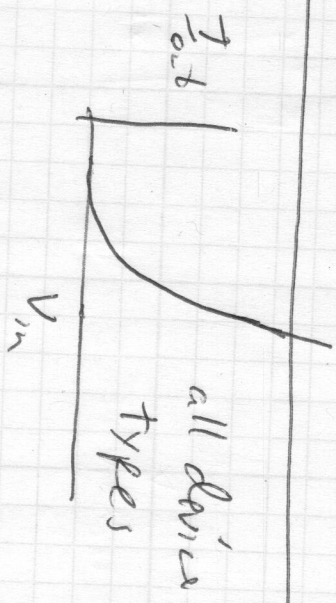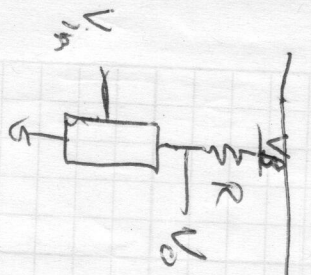if Vo changes 10X
Iout changes 10X
how much does
Vout change?



what is the gain?

what happens
in 2 line?

How to get gain?

1) solve non-linear equations


$$V_o = V_{cc} - I_c R_L$$

$$= V_{cc} - I_s e^{V_{be}/V_T - 1} (1 + \frac{V_o}{V_A})$$

Painful w/ 1 device

~ impossible w/ 2



here then 2

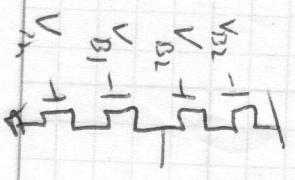

2) Find a bias point

operating point
 known useful set of
 voltages & currents
 => still solving nonlinear equations
 but just for one pt, not for
 the whole curve

2B) linearize at that point

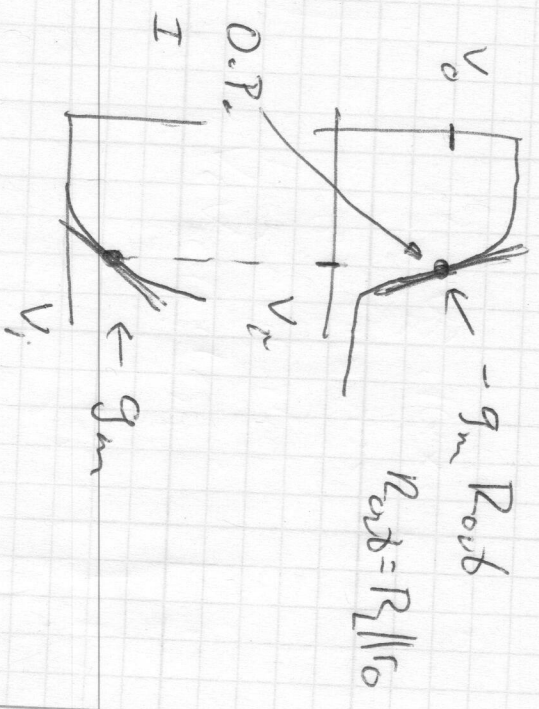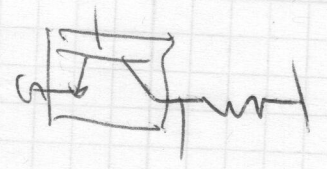


(Full nonlinear dynamic) = (single point solution) + (small signal model) + h.o.t

DC and freq response!
 Heaviside

non linear o.p.
 Taylor
 linearization error

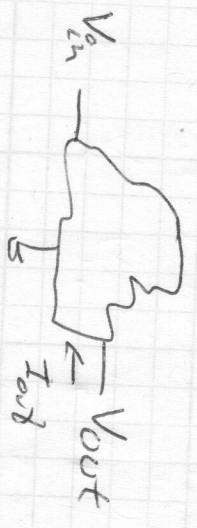where does $A_v = -g_m R_{out}$ come from?



f exists st. $I_{out} = f(V_{in}, V_{out})$ is some
 used w/ calc derivative,

find a point (V_{in}, V_{out}) st. $I_{out}(V_{in}, V_{out}) = 0$
 That's an O.P.

near that point $I_{out}(V_{in} + \delta V_{in}, V_{out} + \delta V_{out}) =$