


S model

I_{th} gain

I_m vs V_{GS}-V_{TH}

SV3 - threshold cond.

velocity scatter's limit

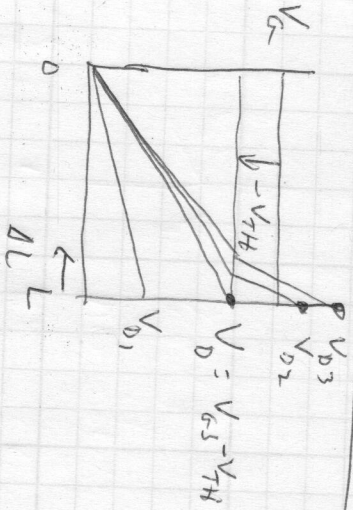


$$I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (2.27)$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2 I_D}{V_{GS} - V_{TH}}$$

$$r_{oD} = \frac{\lambda I_D}{1 + \lambda V_{DS}}$$

$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D} \approx \frac{1}{\lambda I_D}$$

Last line

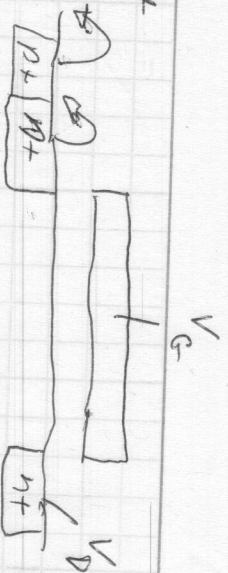

$$I_D = \left[\mu_n \cdot \text{charge density per length} \right] \left[\text{velocity} \right]$$

$$= \begin{cases} 0 & V_{GS} \leq V_{TH} \\ C_{ox} (V_{GS} - V_{TH} - \lambda V_{DS}) W \left[\mu \frac{V_{DS}}{L} \right] & V_{GS} > V_{TH} \\ C_{ox} \left(\frac{V_{GS} - V_{TH}}{2} \right) (W) \left[\mu \frac{V_{GS} - V_{TH}}{L} \right] & V_{GS} > V_{TH} \text{ and } V_{DS} > V_{GS} - V_{TH} \end{cases}$$

for most cases worse than V_A


$$\frac{1}{\lambda} = 10V \rightarrow 1V \text{ or less}$$

$$V_A = 10-100V \text{ typ.}$$

intrinsic gain

$$A_v = -g_m r_{oD} = \left(\frac{2 I_D}{V_{GS} - V_{TH}} \right) \left(\frac{1 + \lambda V_{DS}}{\lambda I_D} \right) = \frac{2(1 + \lambda V_{DS})}{(V_{GS} - V_{TH}) \lambda}$$

140/240A 17 SP W2L3

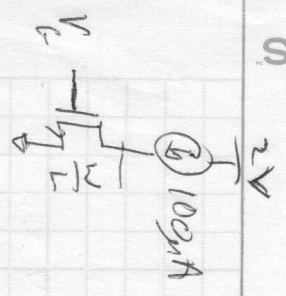


$V_{TH} = 0.5V$
 $\lambda = 0.2$
 $M_n C_{ox} = \frac{200\mu A}{V^2}$

$\frac{W}{L} = \frac{I_{DQ}}{C_{ox} V_{GS}^2}$ Find V_{GS}

st. device is in saturation

Find output swing

Find intrinsic gain

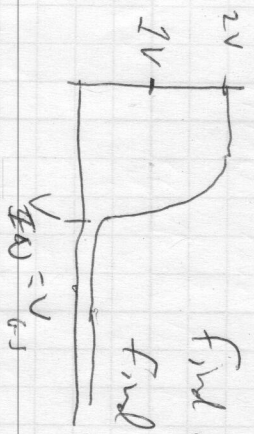

$100\mu A = \frac{K_n C_{ox}}{2} \left(\frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \right)$

What is $\frac{W}{L} = \frac{100\mu A}{0.2\mu m}$? $V_{GS} = 40mV + V_{TH}$

I_{DQ} sure
 $g_m = \frac{200\mu A}{40mV} = 5mS$ $A_v = -250$

What if $\frac{W}{L} = \frac{10,000\mu m}{0.2\mu m}$? $V_{GS} - V_{TH} = 4mV$

$g_m = \frac{200\mu A}{4mV} = 50mS$ $A_v = -2,500$

is that good?

Sub-threshold conduction

$100\mu A = 100\mu A (5) \left(\frac{W}{L} (V_{GS} - V_{TH})^2 (1 + 0.2(2V)) \right)$
 pick


$\frac{1}{2} V^2 = (V_{GS} - V_{TH})^2$

$V_{GS} = V_{TH} \approx 0.4V$

$V_{GS} \approx 0.9V$




$g_m = \frac{200\mu A}{0.4V} = 0.5mS$ $A_v \approx -25$

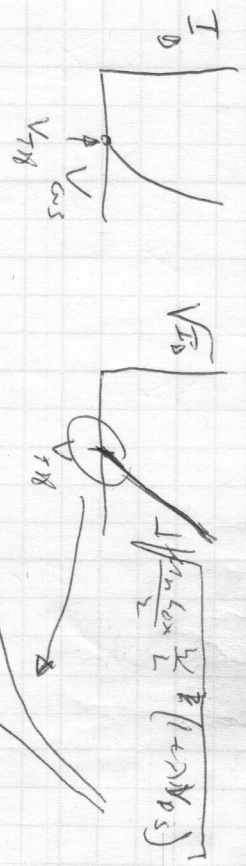
$r_o \approx \frac{1}{(0.2)(100\mu A)} = 50k\Omega$ $sway \approx 0.4-2$



Why?

Consider a capacitor

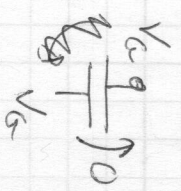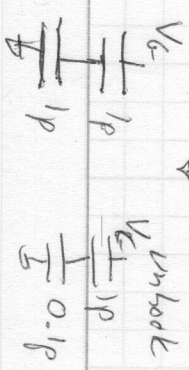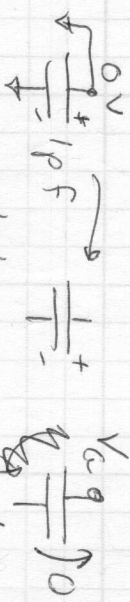

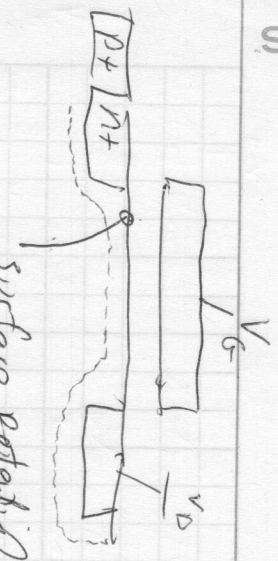

surface potential $\phi_s \approx V_{GS} \frac{C_{ox}}{C_{ox} + C_{dep}}$

V_{GS} increasing

$\Rightarrow \phi_s$ increasing (slower)


\Rightarrow barrier to source majority carriers decreasing

\Rightarrow current $\sim e^{q\phi_s/kT} = e^{qV_{GS}/kT}$

$n = \frac{C_{ox} + C_{dep}}{C_{ox}} \approx 1 - 2$ 1.5 common

velocity saturation $10^5 \frac{m}{s}$

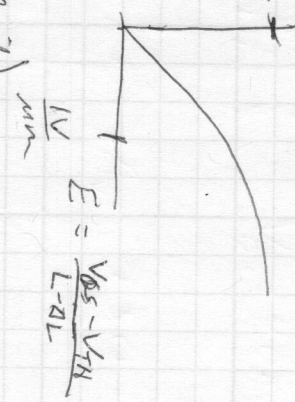compare to $c = 3 \times 10^8 \frac{m}{s}$








$I_D = (\text{avg. charge density}) (\text{velocity})$

$\sim (V_{GS} - V_{TH}) \sim (V_{GS} - V_{TH})$ **quadratic**

$\sim (V_{GS} - V_{TH})$ **velocity sat.**

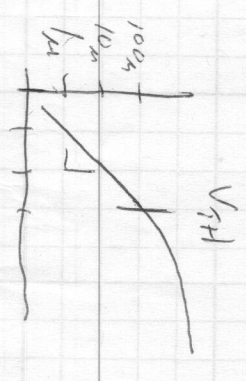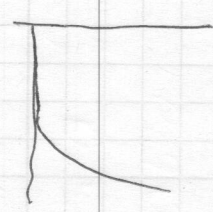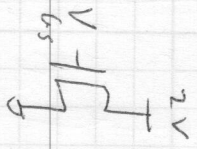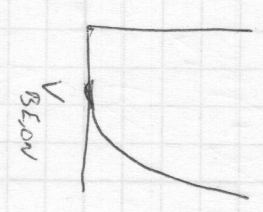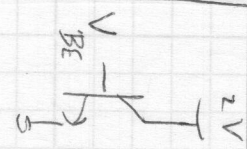$I_D = \mu C_{ox} (V_{GS} - V_{TH})^2$ **velocity sat.**




quadratic
-relatively flat

-quadratic ($V_{GS} - V_{TH}$)

dependence

- steep
- evenly spaced

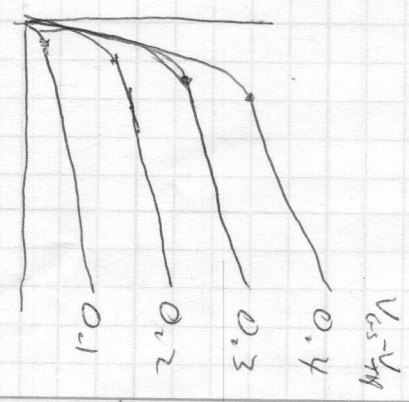

scattering