

What is design?

SS model

single pole amplification

What specs?

"I need an amplifier"

What gain/freq response? v_{out}/v_{in}

What output impedance? What is it driving? resistive load, capacitive, ...

What does the source look like? resistive, capacitive, ...

How accurate does the gain need to be?

⇒ Feedback control

⇒ Stability

Power constraints

output swing

Done w/ device models, on to circuits

Design: from specs to devices/circuits

Analysis: Find operating point

(by solving nonlinear eqs.)

Find linear model

$\Rightarrow g_m, r_o, C_{gs}, C_{gd}, \dots$

Linear analysis



- gain, gain vs. freq (Bode)

- time domain response

nonlinear effects

output swing

Design

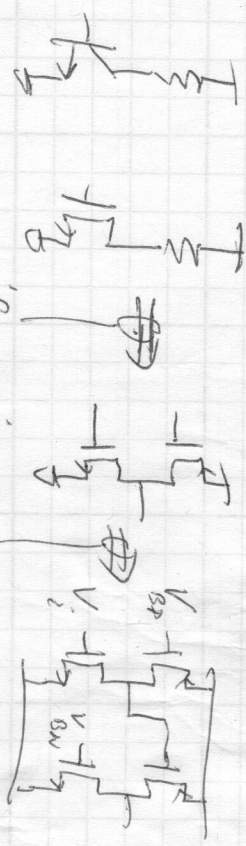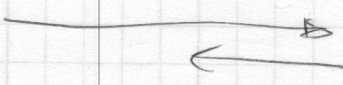


uniform-gain freq resp

wave wave

freq response stability in feedback

input capacitance

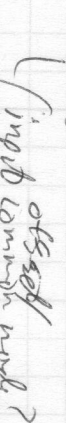

Feedback?

1/4/2014

1750 W3L2

MOS 11 example Fig 2.39


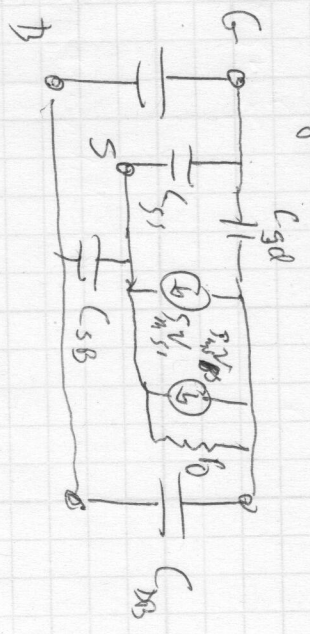
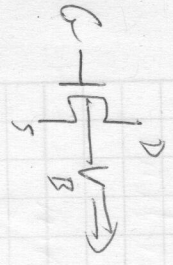


Fig 2.37

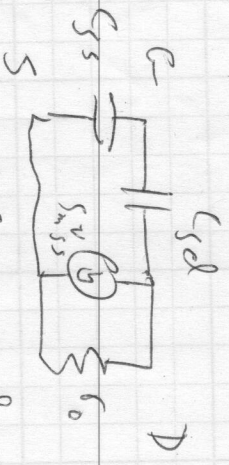

almost the same for bipolar, JFET, tubes, ...

Same model for MOS & bipo


$$I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

Process (may have small # of discrete choices)

$$q_n = \frac{2 I_D}{V_{OV}} = \mu_n C_{ox} \frac{W}{L} \frac{V_{OV}}{V_{OV}}$$

In general choose I_D , $\frac{W}{L}$, V_{OV} (maybe L) to satisfy specs pick any 2

operating point


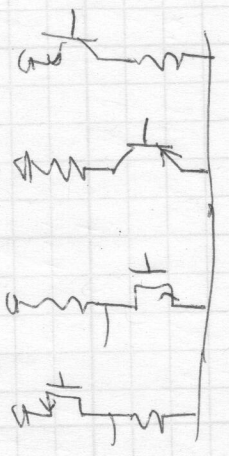


Current depends on V_{out} & R_L

Varies a lot

q_n, r_o depends on current only for bipolar
current + geometry for MOS

Small signal model

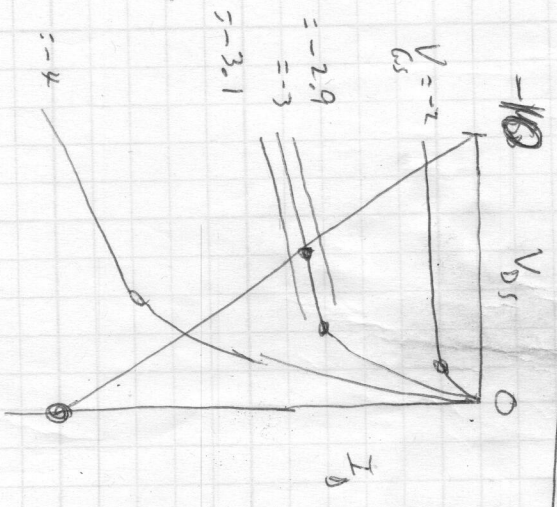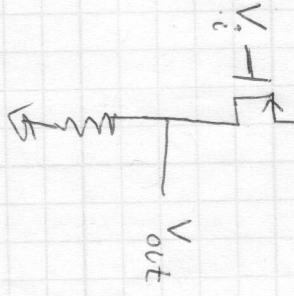

Pick $V_i = V_I = 3V$ operates with

$\Rightarrow V_{OUT} = 5V$



$g_m = \frac{\partial I_{OUT}}{\partial V_i}$

$V_{out} = V_{out}$
 $V_{in} = V_{IN}$




$= \frac{\Delta I}{\Delta V} = \frac{-9mA - (-10mA)}{3V - (-3V)}$

$= 10mS$ positive!

What's the SS model for a supply?

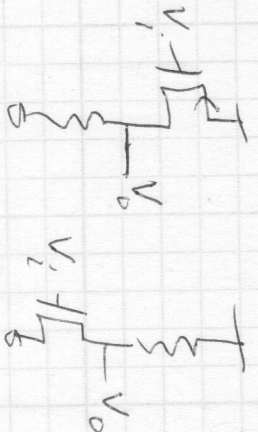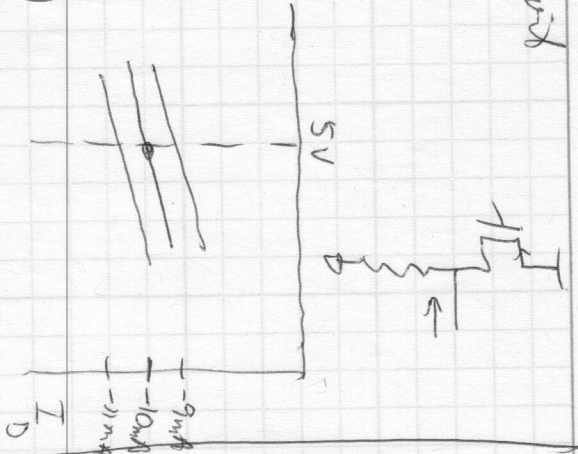

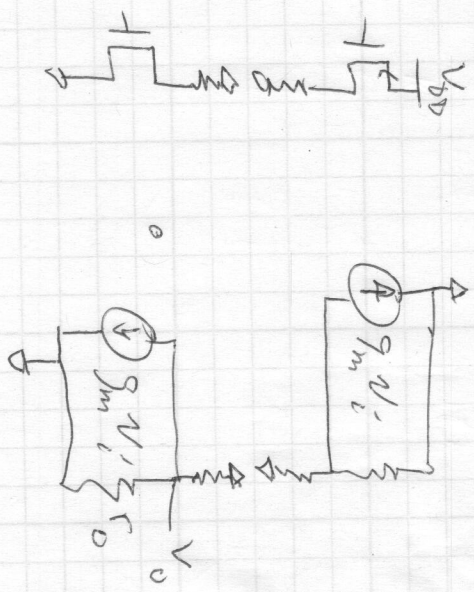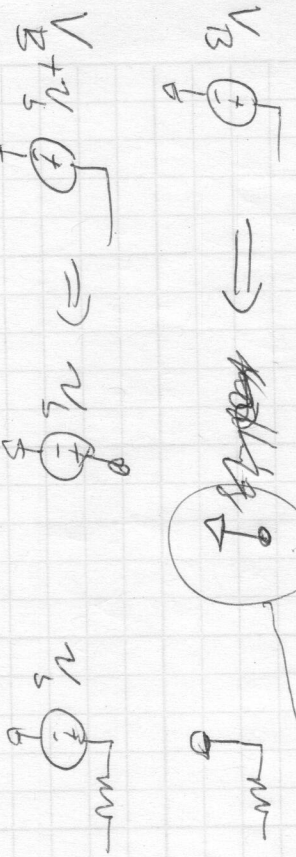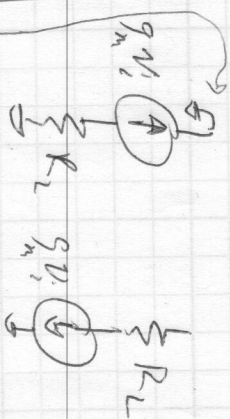raise V_i w/ V_o const
pulls ~~more~~ current out
of the output
decreases the voltage
on the node
i.e. capacitor or resistor



$V_o = -g_m v_i (R_D || R_L)$

