

Middle / in class F wk 5 3:10 - 4:00

Middle 2 in class F wk 10 3:10 - 4:30

1 page, 2 sides notes

C S amp design

Design an amplifier w/ low freq gain of >100
up to at least 1 MHz w/ $C_2 = 1\mu F$
swing $\pm C_{in} <$

in a technology where $\mu_{nox} = 200 \frac{A}{V^2}$ $\mu_{pox} = 100 \frac{A}{V^2}$

$$|V_{th}| = 0.5V$$

$$\lambda = \frac{1}{2V} \left(\frac{0.1\mu m}{L_{min}} \right)$$

$$V_D = 2V$$

$$C_{ox} = 5 \frac{fF}{\mu m^2}, C_{de}' = 0.1 \frac{fF}{\mu m}$$

$$A_{vo} = 100 \quad w_p > 2\pi / 10^6 \approx 10^3 \text{ rad/s}$$

$$w_u = A_{vo} w_p = 10^9 \text{ rad/s}$$

$$w_u = \frac{g_m}{c_L} \quad g_m > w_u c_L = 10^9 \frac{\text{rad}}{\text{s}} \cdot 10^{-12} \text{ F} = 10^{-3} \text{ s}$$

$$g_m = \frac{2I_o}{V_{ov}}$$

$$\text{pick } V_{ov} = 100mV$$


(roughly lower limit on quadratic model)
(lowest current)
(will re-examine this choice)

$$I_o = \frac{V_{ov}}{2} g_m = \left(\frac{100mV}{2} \right) (1 \text{ mA}) = 50 \mu A$$

$$\Rightarrow L_n = 0.25 \mu m$$

$$\hookrightarrow R_{in} = R_o = 100k = \frac{1}{I_n I_D} = \left(2V \frac{1}{0.1\mu m} \right) \frac{1}{50 \mu A} = 40k\Omega \cdot \left(\frac{L}{0.1\mu m} \right)$$
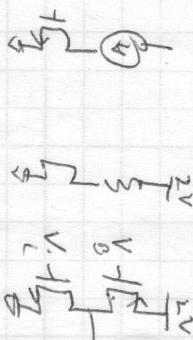
$$A_{vo} = g_m R_o \geq \frac{A_{vo}}{g_m} = \frac{100}{1 \text{ mA}} = 100k$$



resistive load: ① make $R_L \gg r_o$

say $1\text{M}\Omega$ (vs. 100K)

with $50\mu\text{A}$ flowing, need

$$V_{DD} > (50\mu\text{A})(1\text{M}\Omega) = 50\text{V}$$

No too big

② make $r_o \gg R_L$, let $R_L = 100\text{k}$

$$\Rightarrow \text{need } V_{DD} = (50\mu\text{A})(100\text{k}) = 5\text{V}$$

No V_D too big

$$50\mu\text{A} = \left(\frac{100\text{k}}{r_o}\right) \left(\frac{V_D}{2}\right) (0.1\text{V})^2$$

$$\frac{W}{L} = 50 \quad W_n = 2.5\text{um} \quad L_p = 0.5\text{um}$$

$$W_p = 50\text{um} \quad L_p = 0.5\text{um}$$

\Rightarrow if V_{in} decreases, I_{Dn} increases

need I_{Dn} to decrease 20% from $V_{DD} = 0.1\text{V}$

$$\text{to hit } V_{out,max} = V_{DD} - |V_{DSDP}| = 1.9\text{V}$$

$$I_D \sim V_{ov}^2$$

$$(V_{ov} + \Delta V) \approx V_{ov}^2 + 2V_{ov} \Delta V$$

$$\approx V_{ov}^2 \left(1 + 2\frac{\Delta V}{V_{ov}}\right)$$

so 20% decrease in current

$\Rightarrow -10\%$ decrease in $V_{ov} = 10\text{mV}$


must use mos (pmos load)

$$R_o = 100\text{k} = r_{on} \| r_{op} \quad r_{on} = r_{op}$$

$$r_{on} = r_{op} = 200\text{k} \Rightarrow \lambda = 0.1 \frac{1}{V} \Rightarrow L_n = L_p = 0.5\text{um}$$

$$I_D = \frac{V_{DD}}{2} \left(\frac{V_D}{L_n}\right) V_{ov}^2 (1 + \lambda V_{DS})$$

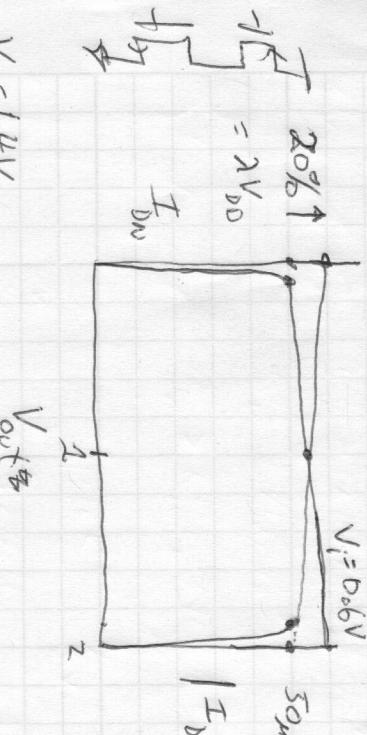\Rightarrow ignoring here because we is needed in to calc.



$$V_{BP} = 1.4\text{V}$$

$$\rightarrow V_{BSN}$$

$$\leftarrow V_{BSP}$$

$$\text{or } \Delta V_{out} = A_{vo} \Delta V_{in} \Rightarrow \Delta V = \frac{C_{ov}}{C_{ov} + C_{in}} \Delta V = g_m V$$

$1mV$ step response

$$\text{Initially } (t=0) \quad V_o = 0$$

$$I = \frac{V_i - V_o}{R} = C \frac{dV}{dt}$$


$$\text{points to destination in}$$

$$\frac{dV}{dt} = \frac{V_i - V_o}{RC} = \frac{V_i - V_o}{1 \text{ nA}}$$

$$\tau = (100k)(10^{-12}) = 10^{-7} \text{ s}$$

$$Q = \frac{C_o V_o}{R_o} = \frac{C_o V_o}{R_o} e^{\frac{-t}{\tau}}$$

Norton Thevenin

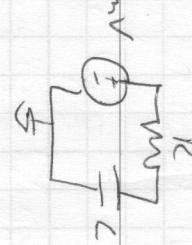

single pole step response


$$\text{error} \sim e^{-t/\tau}$$

$$\text{progress} \sim 1 - e^{-t/\tau}$$

	$\frac{1}{\tau}$	Percent error
1	63%	37%
3	95%	5%
5	99%	1%
7	99.9%	0.1%

$$G_{fs} = \frac{2WL}{3} C_{ox} + C_{od}' W$$

$$C_{od} = 600 \text{ fF}$$

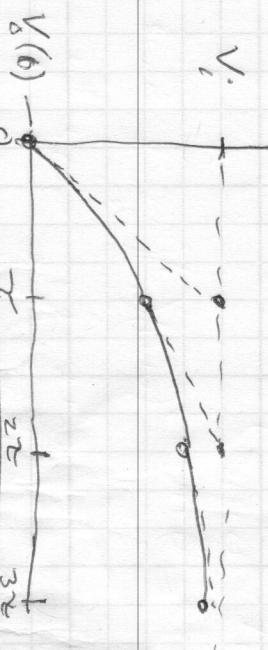

"must settle to within 1% in X seconds,"
 $\Rightarrow 5\tau < X$

"switched cap gain ~~overshoot~~ < 0.1%"

amp adds 7.5 fF to output
~~negligible~~

initially ($t=0$) $V_o = 0$
 $\text{slope always points to destination in}$
 $\frac{dV}{dt} = \frac{V_i - V_o}{RC} = \frac{V_i - V_o}{1 \text{ nA}}$

$$C_{sdn} = (0.1 \frac{\text{fF}}{\text{nm}}) 25 \text{ nm} = 2.5 \text{ fF}$$

$$C_{sdp} = (0.1 \frac{\text{fF}}{\text{nm}}) 50 \text{ nm} = 5 \text{ fF}$$

and adds 7.5 fF to output