

Midterm 1 in class F 2/17 1pg 2 slides notes
no silicon!

Section W4-5 here if possible

HW4 due Wed next week

Lab week 5: no lab 7h 10-11 OH
2-3+ Review
F 11-12 OH

My OH W 11-12 F 4-5 normally
WK 5: W 11-12, 7h 3-4
Read OH 7h 11-12 F 10-11

HW4

CS tradeoffs

Last time: CS amp $A_{vo} = 100$, $\omega_p = 10^7$, $\omega_n = 10^9$, $C_L = 1pF$

Dick $V_{ovn} = V_{ovp} = 100mV$ $\Delta r_{ov} = r_{ovp}$

calculate $L = 0.5 \mu m$ ($\frac{W}{L} = 10$) $50 \mu m$ $W_n = 2.5 \mu m$
 $W_{pp} = 50 \mu m$

$I_D = 50 \mu A$ $g_m = 1mS$ $R_o = 100K$


Step response



t/τ	% v_o/v_i	% error
1	63%	37%
3	95%	5%
5	99%	1%
7	99.9%	0.1%

$v_o = -5m R_o (1 - e^{-t/\tau}) v_i$

Lab 3

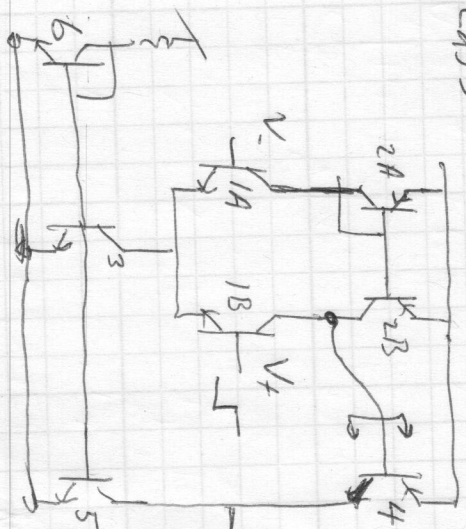

$r_{\pi 4} = \frac{\beta}{g_m}$

$f = \frac{R_2}{R_1 + R_2}$

$R_{o1} = r_{o1B} \parallel r_{o2B} \parallel r_{\pi 4}$ $A_{v1} = g_{m1} R_{o1}$ $A_{v2} = g_{m4} R_{o2}$

$R_{o2} = r_{o1} \parallel r_{o2} \parallel R_{out}$

is C_L the right capacitance? what about C_{gd} & C_{db} ?

$C_{gd} = W C_{ox}$

$C_{db} = (2.5 \mu m) (0.1 fF/\mu m) = 2.5 fF$


$C_{db} = 50 \mu m (0.1 fF/\mu m) = 5 pF$

should add C_{dsn} , C_{dsp} } $\approx 10 fF$

Fine

What about input? Say the source resistor is $1M\Omega$ (another analyzer say)

like $\tau_i = R_{in} C_{in} < 10^{-7}$

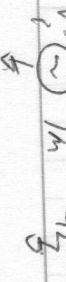

$\Rightarrow C_{in} < 10^{-13} F = 100 fF$

140/240h

17 SP



W4L2

input capacitance

$$C_{gs} = (25 \mu\text{m}) (0.5 \mu\text{m}) (0.5 \text{ fF}) + 2.5 \text{ fF}$$

$$= 6.01 + 2.5 = 8.6 \text{ fF}$$

What about C_{gd} ? Miller

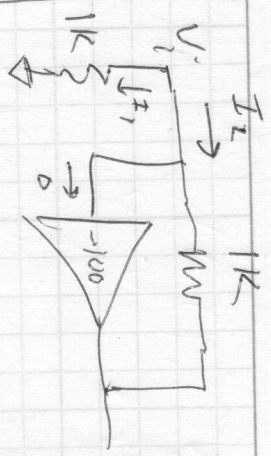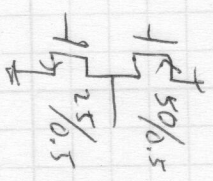

if $V_i = 1\text{V}$ $I_1 = 1\text{mA}$

$I_2 = 101\text{mA}$

Negative gain works to decrease impedance of something strapped across it.

more voltage \Rightarrow more current \Rightarrow lower impedance

too high! How do we drop it?

Reduce A_{vo} - can't, it's a spec.

Reduce C_{gd} \Rightarrow reduce W_n


Constrained by $g_m = \frac{2I_D}{V_{ov}}$

$= \mu_n C_{ox} \frac{W}{L} V_{ov}$

$= \sqrt{2\mu_n C_{ox} W I_D}$

$W_n \searrow 5x \Rightarrow V_{ov} \nearrow 5x \quad I_D \nearrow 5x$

- 2.18
- .19
- .20

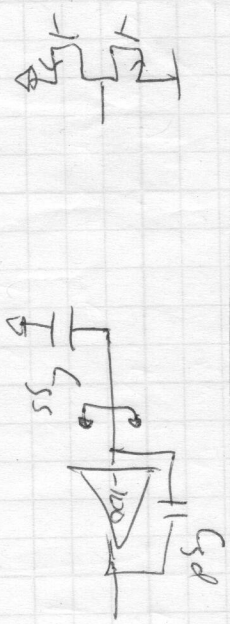

$$Q_{in} = V_i C_{gs} + C_{gd} (V_i - 100V_i) =$$

$$V_i [C_{gs} + (1-100)C_{gd}]$$

C_{total} C_{Miller}

$$C_{in} = 8.6 \text{ fF} + 101(2.5 \text{ fF}) = 260 \text{ fF}$$

$W_n = 5 \mu m$ $V_{ov} = 500 mV$ $I_D = 250 \mu A$
 pick $W_p = 10 \mu m$ $V_{ovp} = 500 mV$ } affects output swing & cap.
 $W_p = 250 \mu m$ $V_{ovp} = 100 mV$

$$C_{in} = C_{gsn} + C_{gsn}(1 - A_{vo})$$


$$= (45 \mu m^2)(0.5 \frac{FF}{\mu m^2}) + (5 \mu m)(0.1 \frac{FF}{\mu m})(101)$$

$$= 12.5 FF + 101 FF = 113.5 FF < 100 FF$$

$W_{pin} > W_{p,out}$
 details of w_{pin} are for after mid 1

	double $W_{n,p}$	double V_{ov}	double L
I_D	2	4	1
g_m	2	2	1
$r_{o,s}$	1/2	1/4	2
A_v	1	1/2	2
w_p	2	4	1/2
w_n	2	2	1
C_{in}	2	$\approx 1/2$	≈ 2
cost	2	1	4 2

parasitic assumes \rightarrow cost of C_L | swing g_o

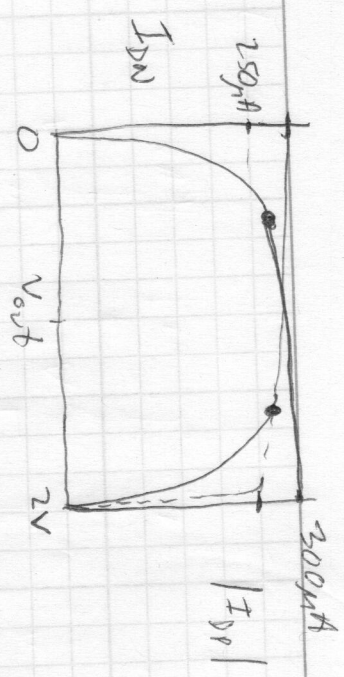

take a given CS amp

what happens if you?
 double W_n, W_p ? (2 parallel caps)
 double $L_{n,p}$?
 double V_{ov} ?
 what effect on $I_D, g_m, r_o, A_v, w_p, w_n, C_{in}$?

what if I need high gain (small V_{ov} , long L)
 but low input cap? (for output)

- multiple stages
- cascade - higher output impedance } good
 lower input capacitance }
 lower swing }
 harder to bias } bad

