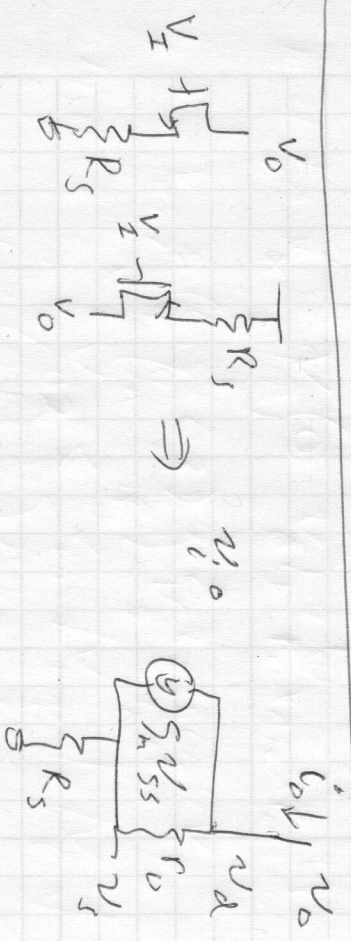



Midterm Friday closed book 1pg 2 sides notes
 HW 1-4 no silicon
 Ch 1-3, 6.1, 6.2 egn 6.21, 6.22
 Cascode



① RCL @ v_o
 $i_o = g_m v_{gs} + \frac{1}{r_o} v_{ds}$
 $v_{gs} = i_o R_S$
 for R_o calc.
 $v_{ds} = v_o - i_o R_S$
 some people write $g_o v_{ds}$

$v_{gs} = i_o R_S$
 $v_{ds} = v_o - i_o R_S$

CS w/ cascode

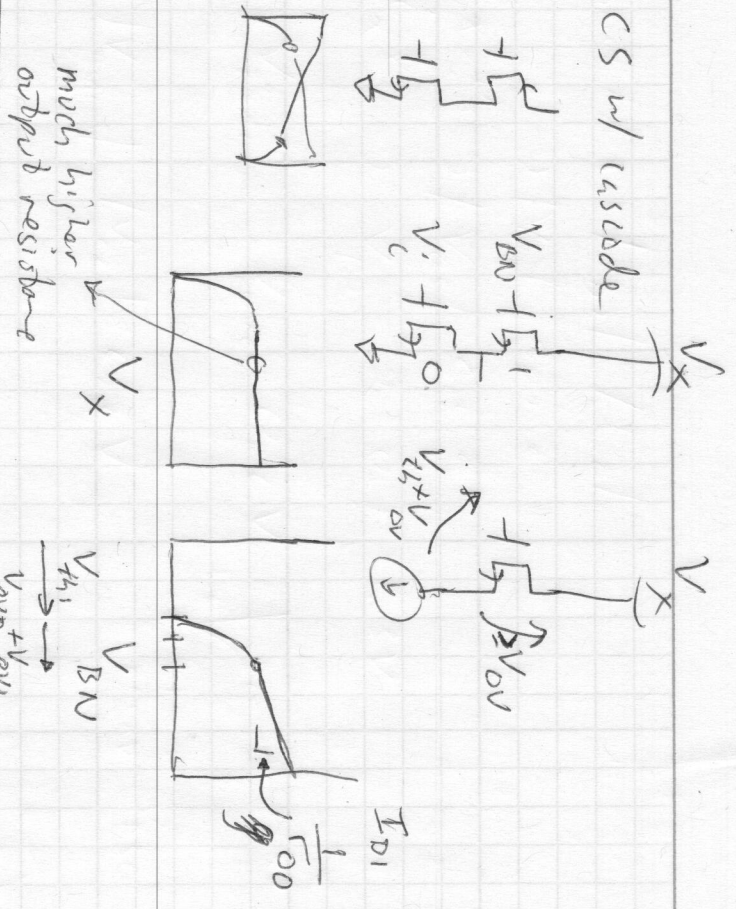

much higher output resistance

Notes: in a sum all terms must have the same units! check that!

①+②
 $i_o = g_m (v_i - i_o R_S) + \frac{1}{r_o} (v_o - i_o R_S)$

for R_o calc: $v_i = 0$
 $R_o = \frac{v_o}{i_o}$

for g_m calc: $v_o = 0$
 $g_m = \frac{i_o}{v_i}$

expect when $R_S = 0 \Rightarrow g_m, r_o$
 when $R_S = \infty \Rightarrow 0, \infty$




when $g_m = 0 \Rightarrow ? g_m, R_S + R_S$
 check

② w/ $v_i = 0$
 $i_o + g_m R_s i_b + i_o \frac{R_s}{r_o} = \frac{1}{r_o} v_o$

$$R_o = \frac{v_o}{i_o} = r_o \left[1 + g_m R_s + \frac{R_s}{r_o} \right]$$

$$= r_o + R_s + g_m r_o R_s$$

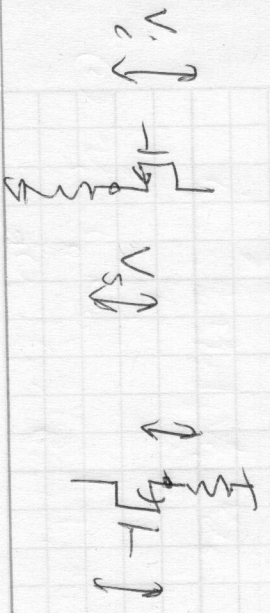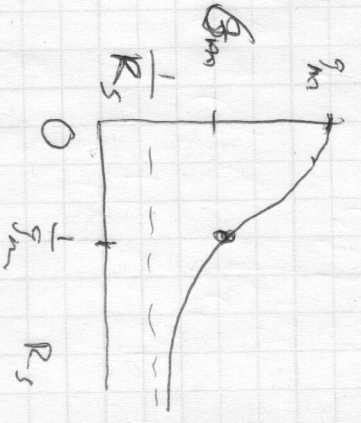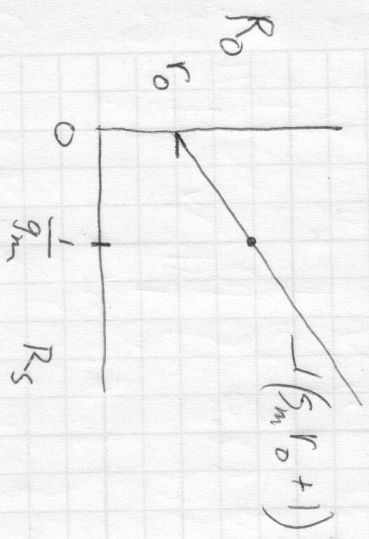or $\left. \begin{matrix} \frac{1}{g_m} V_B \\ -\frac{1}{g_m} V_B \end{matrix} \right\} \Rightarrow R_o = r_o + R_s + (g_m r_o R_s)$




$A_v = \frac{-R_D}{R_S} \cdot \frac{1}{1 + g_m R_S} \approx \frac{1}{g_m R_S}$


③ w/ $v_o = 0$
 $i_o = g_m v_i - g_m R_s i_b - i_o \frac{R_s}{r_o}$

$$G_m = \frac{i_o}{v_i} = \frac{g_m}{1 + g_m R_s + \frac{R_s}{r_o}}$$

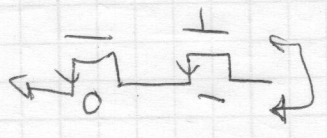
w/ body effect $\Rightarrow g_m + g_{mb}$



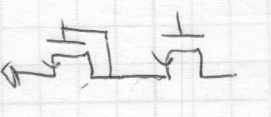$R_o = r_o + (1 + g_m r_o) r_{o0} \approx g_m r_o^2$
 10, 100, ... ?



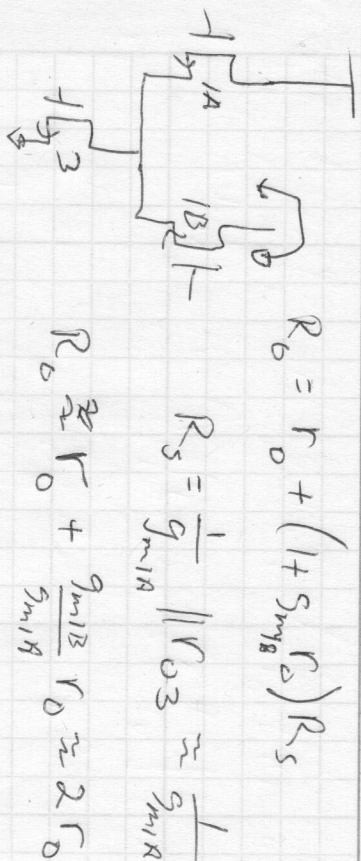
$R_o = r_{o1} + (1 + g_m r_{o1}) \frac{1}{g_{m0}}$
 $\approx r_{o1} \left(1 + \frac{g_m}{g_{m0}} \right)$



$$R_o = r_o + (1 + \beta R_E) R_C$$

$$R_S = \frac{1}{g_{m1A}} \parallel r_{o3} \approx \frac{1}{g_{m1A}}$$

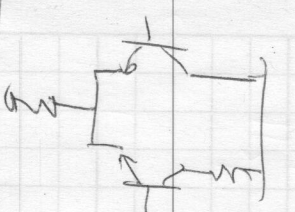
$$R_o \approx r_o + \frac{g_{m1B}}{g_{m1A}} r_o \approx 2 r_o$$




Q: What small signal current flows in i_{d1A} if v_{d1B} increases?

$$A: i_{d1A} \approx -i_{d1B} = \frac{v_{d1B}}{2 r_{o1B}}$$

$$R_o = \frac{v_o}{i_o} \Big|_{v_i=0} = r_o$$

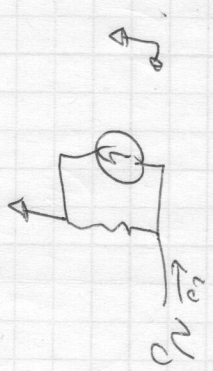


$$R_i = \frac{v_i}{i_i}$$

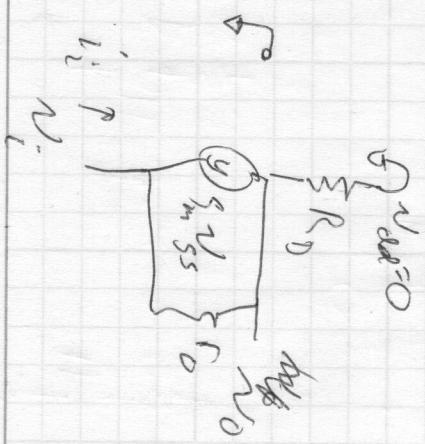

$$v_o = i_i R_o$$


Common gate

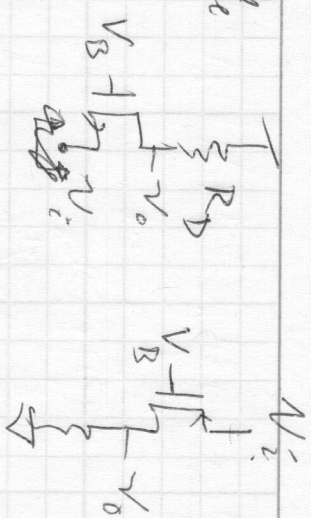

$$G_m, R_o, R_i$$

$$G_m = \frac{i_o}{v_i} \Big|_{v_o=0} = -\left(g_m \left(+ \beta r_o \right) + \frac{1}{r_o} \right)$$

$$v_i = 0$$

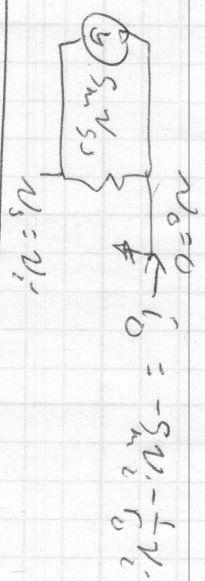

$$KCL @ v_i \quad i_i + \beta v_i + \frac{1}{r_o} (v_o - v_i) = 0$$

$$i_i + g_m (-v_i) + \frac{1}{r_o} (i_i R_o - v_i) = 0$$

$$i_i \left(1 + \frac{R_D}{r_o} \right) = \left(g_m + \frac{1}{r_o} \right) v_i$$

$$R_i = \frac{v_i}{i_i} = \frac{1 + R_D/r_o}{g_m \left(1 + \frac{1}{g_m r_o} \right)} \approx \frac{1}{g_m} \left(1 + \frac{R_D}{r_o} \right)$$

$$= \frac{R_D}{g_m r_o} \quad \text{if } R_D \gg r_o$$