

Feedback


tough to get stable gain w/ e.g. CS  
 easy w/ feedback & ratio of passives

but stability!

pole locations and step response

sub really  $r_o$  varies all over the map

compare to

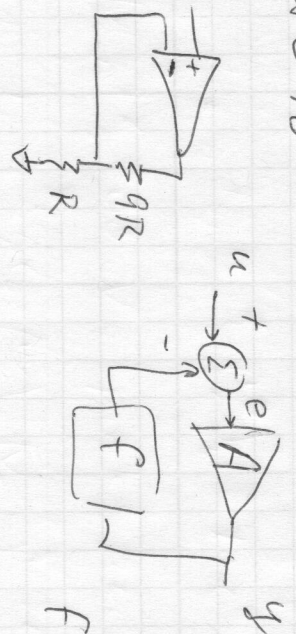

$$F = \frac{R}{10R} \approx \frac{1}{10}$$

$$y = Ae = A(u - fy)$$


$$(1 + AF)y = Au$$

$$H(s) = \frac{y}{u} = \frac{A}{1 + AF} \approx \frac{1}{F}$$

Feedback

consider gain accuracy of amps we've looked at.  
 goal: gain of 10 (or -10)

$$A_v = -g_{mD} R_D$$

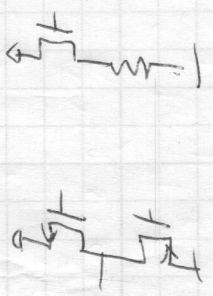

Best case  
 $I_D$  varies,  $V_{ov}$  varies  
 $A_v$  varies  
 $A$  is not really const.  
 $PVT$  have sig effect

2 sources of error

- mismatch in R, 9R  
 with careful layout  $\approx 0.1\%$

$$-\frac{A}{1 + AF} \neq \frac{1}{F}$$

$$\frac{A}{1 + AF} = \frac{A}{AF} \frac{1}{1 + \frac{1}{AF}} = \frac{1}{F} \frac{1}{1 + \frac{1}{AF}}$$

$$\frac{1}{1 + \frac{1}{AF}}$$

make A sig enough so that  $\frac{1}{1 + \frac{1}{AF}}$  is as small as you need, over all input, PVT variation  $< 1$

feedback is good for a lot of things

- stable gain (can set linearly) & always
- improved input/output resistance
- wider bandwidth

but there's a risk of instability

unity gain buffer



$$F = 1 \quad \frac{A}{1+AF} = 1$$

latch



poles move in feedback

say A is a single pole sys,  $A = \frac{A_0}{1+s/w_{po}}$

$$\frac{A}{1+AF} = \frac{A_0}{1+s/w_{po}} \cdot \frac{1}{1+\frac{A_0 F}{1+s/w_{po}}} = \frac{A_0}{1+A_0 F + s/w_{po}}$$

$$= \frac{A_0}{(1+A_0 F)(1 + \frac{s}{w_{pCL}})}$$

where  $w_{pCL} = (1+A_0 F)w_{po}$

instability occurs when feedback

becomes positive at some frequency


$$| \text{magnitude} | \geq 1$$

in that case  $\Rightarrow$  oscillations

for this picture,  $\text{arg} = 0$

once you have oscillations, other nonlinearities

can make weird things happen

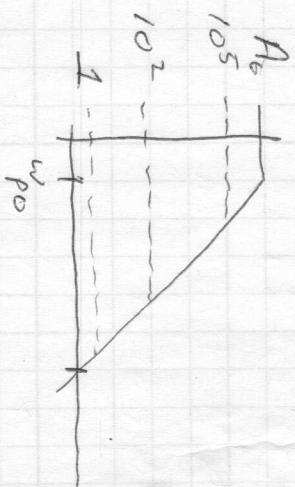

$A_0 = 10^6$   
 $w_{po} = 10 \text{ rad/s}$

$$F = 0.000001 = 10^{-5}$$

$1/f \approx 10^5 \quad w_{pCL} \approx 10^4 w_{po}$





$$F = 0.01 = 10^{-2}$$

$1/f = 10^2 \quad w_{pCL} = 10^4 w_{po}$


$$F = 1$$

$1/f = 1 \quad w_{pCL} = 10^6 w_{po}$

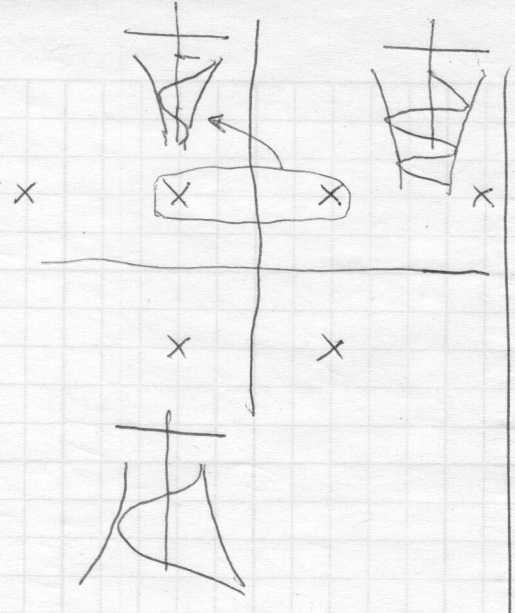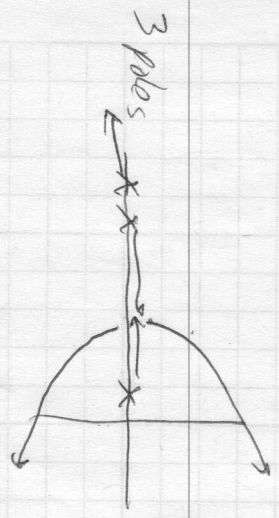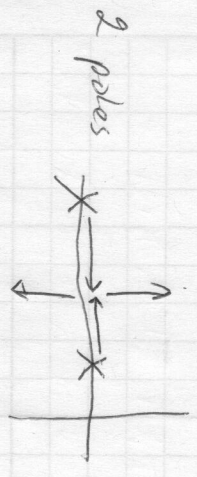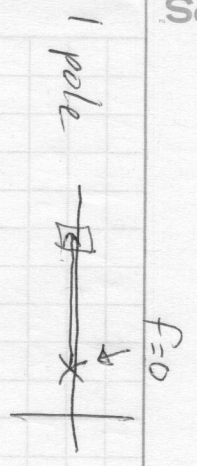$F \rightarrow 1 \quad A_{CL} \downarrow \quad w_{pCL} \rightarrow$



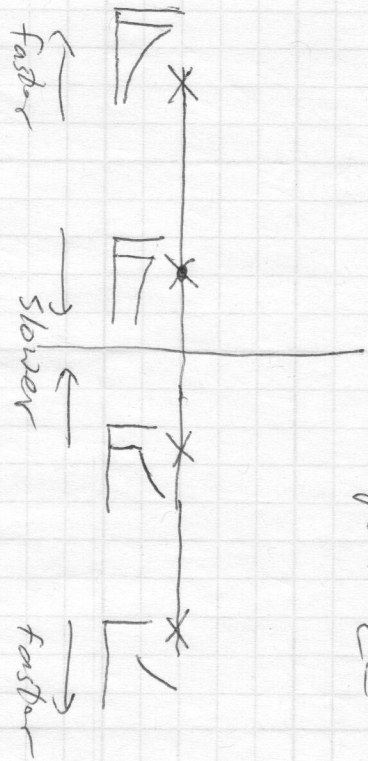Time  $y(t)$   
~~Frequency~~ response & pole location  $P_i$   
 $y(t) \sim \sum e^{P_i t}$



$P_i = \sigma \pm j\omega \Rightarrow e^{\sigma t} e^{j\omega t}$   
 $e^{\sigma t} (\cos \omega t)$