


freq response rates

Miller figures

slow rate

nearside, pole & zero

$$\frac{dv_o}{dt} = \frac{i_o}{C_2}$$

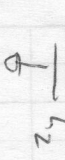



What are limits on i_o ?

N_{o1} , M4 turns off




$$i_o = -I_B$$

N_{o1} M4 conducts a lot more current

output can increase faster then decrease

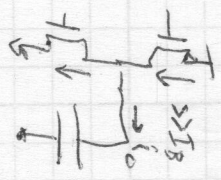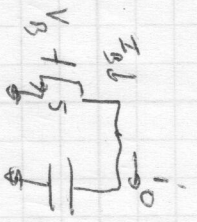


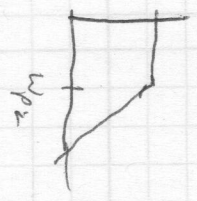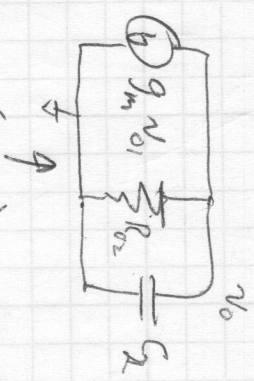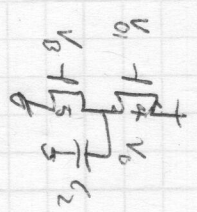slow rate - non-linear (current limit) behavior




For linear system (model)

response gain is indep of amplitude

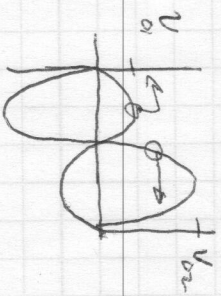

$$v_{o2} = A_v(\omega) v_{o1}$$

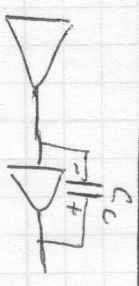(at least) 2 input non-linearities
- voltage supply limit (ROI)
- current limit



$$v_o = -G_m R_{o1} v_{o1}$$

$$v_o = v_{o1} + V_c$$

$$\frac{dv_o}{dt} = \frac{dv_{o1}}{dt} + \frac{dv_c}{dt}$$

Small relative to $\frac{dv_o}{dt} \left(\frac{1}{A} \right)$

v_o can not change any faster than V_c !

$$\frac{dv_c}{dt} = \frac{I_c}{C_c}$$

usually limited by I_{tail}

Heaviside transfer function

$$V_o = \frac{mT}{T} V_i$$

$$\frac{dV_o}{dt} = \frac{i_c}{L} \quad i_c = \frac{V_i - V_o}{R}$$

$$RC \frac{dV_o}{dt} = V_i - V_o$$

$$RC \frac{dV_o}{dt} + V_o = V_i$$

(more generally)

$$a_n \frac{d^n y}{dt^n} + a_{n-1} \frac{d^{n-1} y}{dt^{n-1}} + \dots + a_1 y = b_0 \frac{d^m u}{dt^m} + \dots + b_m u$$

Linear ODE

$$\{ \cos \omega t \text{ terms} \} + \{ \sin \omega t \text{ terms} \} = V_I \sin \omega t$$

0

$$\{ \cos(\omega t) \} + \{ \sin \omega t \} = V_I \sin \omega t$$

always works about that way, even in the general case.

let $V_i = V_I \sin(\omega t)$

assume $V_o = V_o \sin(\omega t + \theta) = V_{os} \sin \omega t + V_{oc} \cos(\omega t)$

$$RC \frac{d}{dt} [V_o \sin(\omega t + \theta)] + V_o \sin(\omega t + \theta) = V_I \sin(\omega t)$$


$$RC V_o \omega \cos(\omega t + \theta) + V_o \sin(\omega t + \theta) = V_I \sin(\omega t)$$

$$RC V_{os} \omega \cos(\omega t) + RC V_{oc} (-\omega) \sin(\omega t) + V_o \sin(\omega t) = V_I \sin(\omega t)$$

must be true $\forall t$

So find ω matches $\sin(\omega t)$ and $\cos(\omega t)$

find coefficients

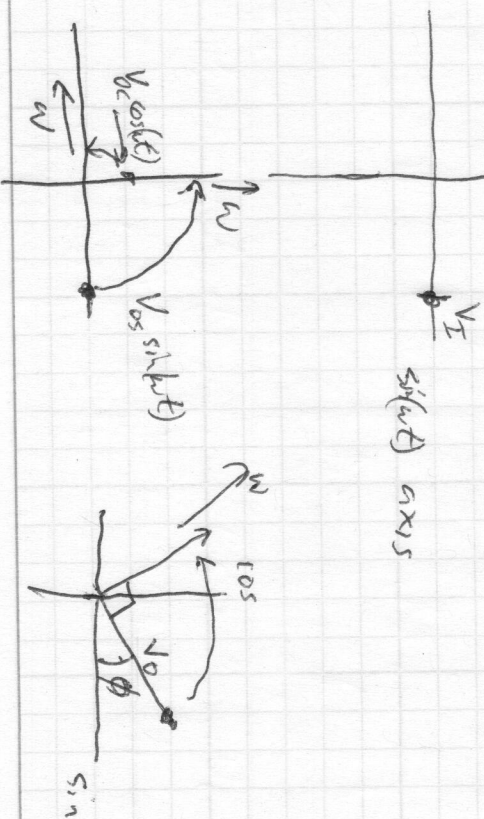

Heaviside: complex #s to the rescue,

derivative: rotate 90° CCW

scale by ω

deriv root \sin, \cos axes, grad use complex #s!


rotate 90° CCW: multiply by j

scale by ω : multiply by ω

derivatives: multiply by $j\omega$


$$(RCs + 1)V_0 = \sqrt{R^2 C^2 \omega^2 \cos^2(\phi) + \sin^2(\phi)} V_0$$

$$RC \omega \cos(\phi)$$

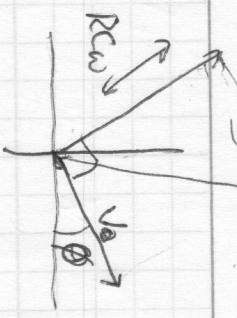


input sine wave
output sine wave
derivatives in wave
scaled deriv sine wave

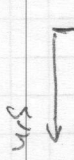one all just ~~scalars~~ dots
these are in
sines space




$$sD (RC \frac{d}{dt} + 1) V_0 \sin(\omega t + \phi) = V_I \sin \omega t$$

turns into geometry search for V_0, ϕ

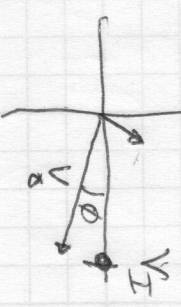


$\omega RC < 1$

Parameterize by ω
Solutions

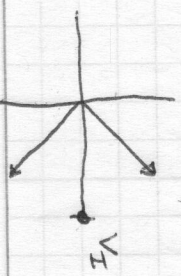


$\omega RC = 1$

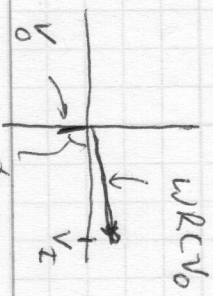

$\omega RC > 1$

$\phi \approx 90$

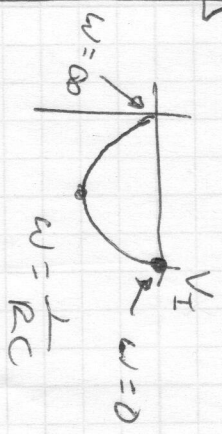

$|V_0|$ goes from V_I to 0

ϕ goes from 0 to -90

-45 when $V_0 = \frac{1}{\sqrt{2}} V_I$

so $(RC \frac{d}{dt} + 1) v_o = v_i$

turns into $(RCj\omega + 1) v_o = v_i$

$$\frac{v_o}{v_i} = \frac{1}{1 + RCj\omega} = H(j\omega)$$

Heaviside!

convenient to look at this

function in the complex plane $H(s)$ and

don't forget why we evaluate at $j\omega$

Pole locations compared to unforced solutions

to the original ODE

$y_i(t) = e^{p_i t}$ Real poles, LHP $p_i < 0$
RHP $p_i > 0$

Complex poles $p = \sigma \pm j\omega$

- LHP $\sigma < 0$
- RHP $\sigma > 0$

$\sigma \pm j\omega \Rightarrow e^{\sigma t} \sin(\omega t + \phi)$




$$H(s) = \frac{\sum_{i=0}^m b_i s^{m-i}}{\sum_{k=0}^n a_k s^{n-k}} = \frac{b(s)}{a(s)} = \frac{\prod (s - z_i)}{\prod (s - p_i)}$$

poles are places where $a(s) = 0$, $H(s) = \infty$

Zeros are places where $b(s) = 0$, $H(s) = 0$

Zeros come from having 2 paths to the output
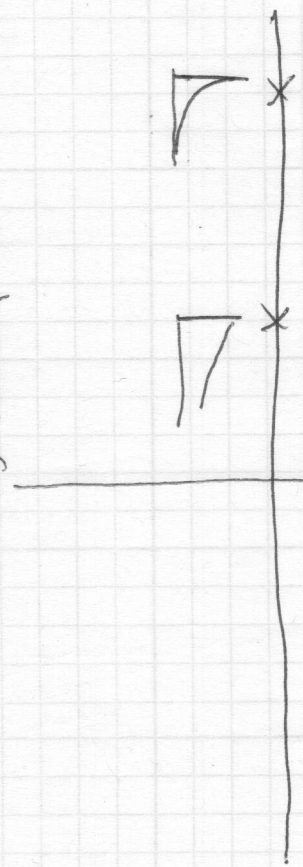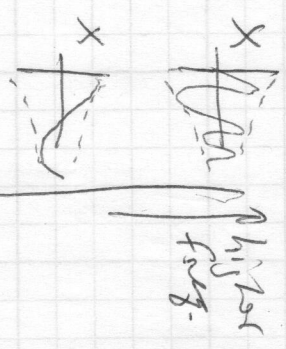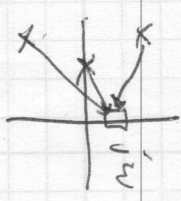
$$H(j\omega) = \frac{\prod_{i=0}^m (j\omega - z_i)}{\prod_{i=0}^n (j\omega - p_i)}$$



all have same sign!