

LTI ODE


Steady state
transients

Zeros

1, 2, 3 poles in feedback

externally compensated op-amps

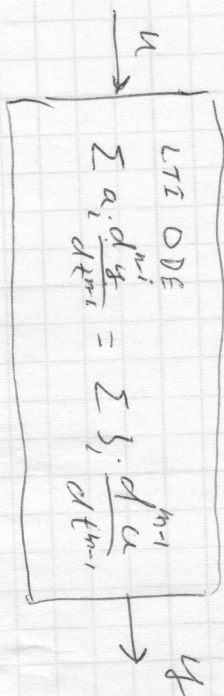Linear Time Invariant Ordinary Differential Equations
(circuits, physiology, economics, ...)




$$u(t) = \sum A_i \sin(\omega_i t) \rightarrow y(t) = \sum A_i |H(j\omega_i)| \sin(\omega_i t + \angle H(j\omega_i))$$



Steady state response

Poles are the natural response $P_i = \sigma + j\omega$
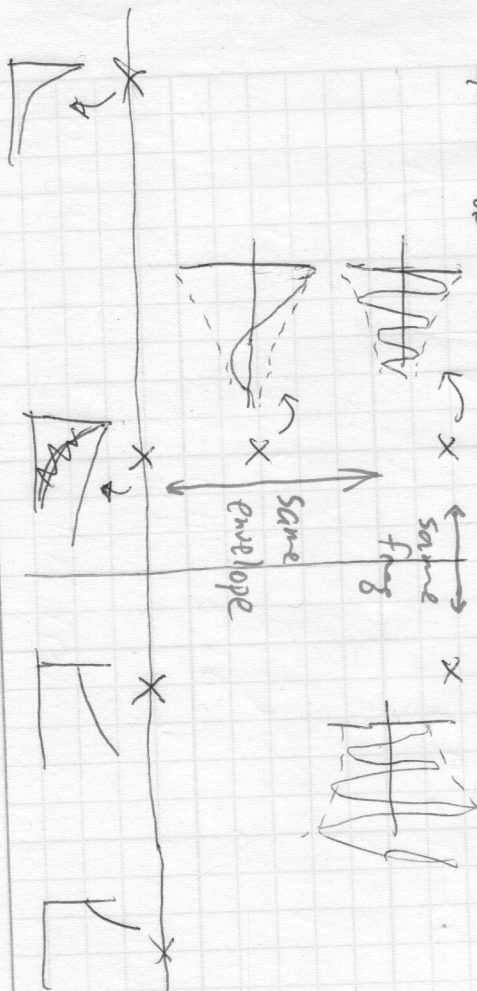
$$y(t) \propto \sum e^{P_i t} \quad P_{i+1} = \sigma \pm j\omega$$



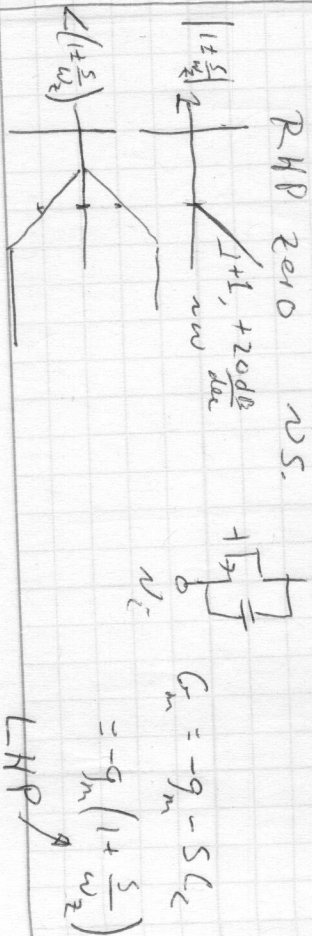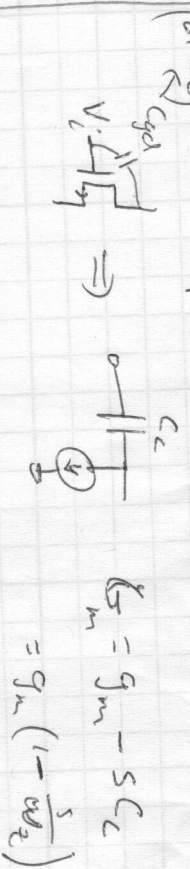Zeros: - at least 1 derivative of input in ODE
- 2 poles ~~to~~ from input to output




$$\sum_{i=1}^{n-1} \frac{dy}{dx} = u + a \frac{du}{dt}$$



tends to speed up response




what about RHP?

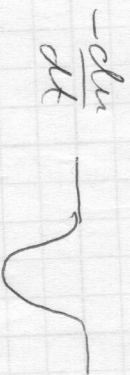

can start response in opposite direction!

Poles move in feedback



1 pole

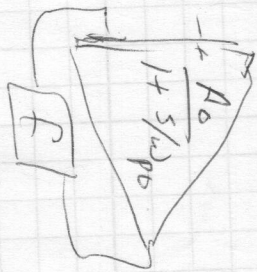

closed loop $A_{cl} = \frac{A_c}{1+A_0 F}$

$$\omega_{pcl} = (1+A_0 F) \omega_p$$

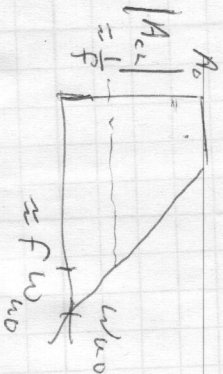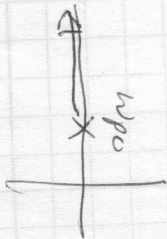
$$\omega_{u,cl} = A_{cl} \omega_{p,cl} = A_0 \omega_p = \omega_u$$



faster, lower gain

3 poles (0-located)


$$\frac{A_0}{(1+s/w_p)^3}$$

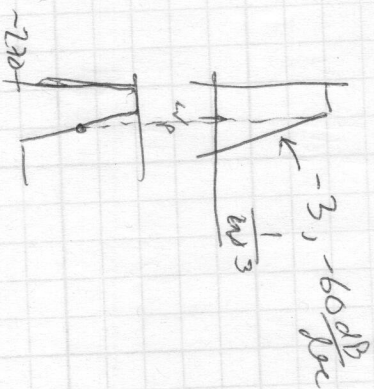

closed loop


$$\frac{A_0}{1+A_0 F} = \frac{A_0}{(1+s/w_p)^3 + A_0 F}$$

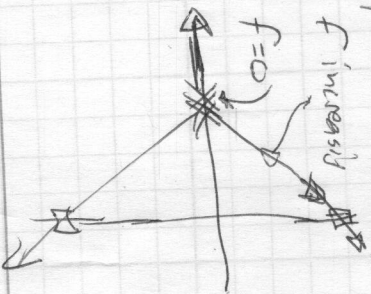poles: $s = -\omega_p \pm j\sqrt{3}\omega_p$ and $s = -\omega_p$



2 poles (0-located)



$$\frac{A_0}{(1+s/w_p)^2}$$

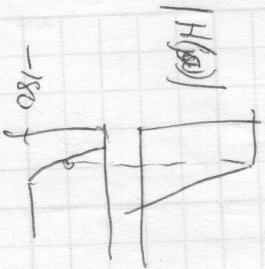


poles: $-\omega_p \pm j\omega_p \sqrt{3}$




F increasing

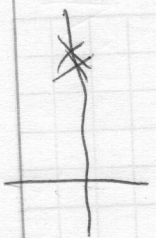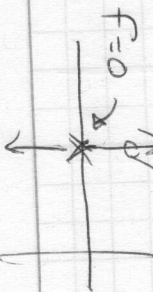

Uncompensated

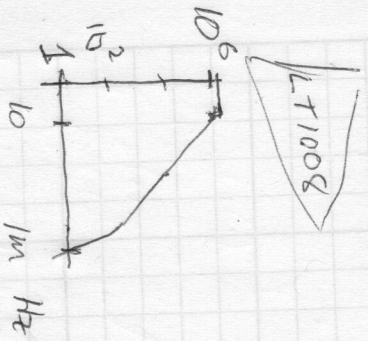


Compensation

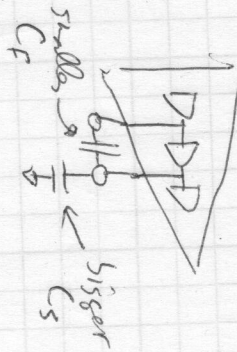

Uncompensated, $F = 10^{-3} \Rightarrow A_{VCL} \approx \frac{1}{F} = 10^3$

$BW \approx 10^4 \text{ Hz}$

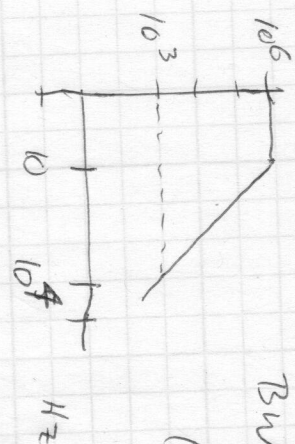$(\text{Gain})(BW) = 10^3 \cdot 10^4 = 10^7$



Compensated $C_F = 30 \text{ pF}$ $F = 1$

$A_{VCL} \approx \frac{1}{F} = 1$

$BW = 1 \text{ MHz}$

$(\text{Gain})(BW) = (1)(10^6) = 10^6 \text{ MHz}$

