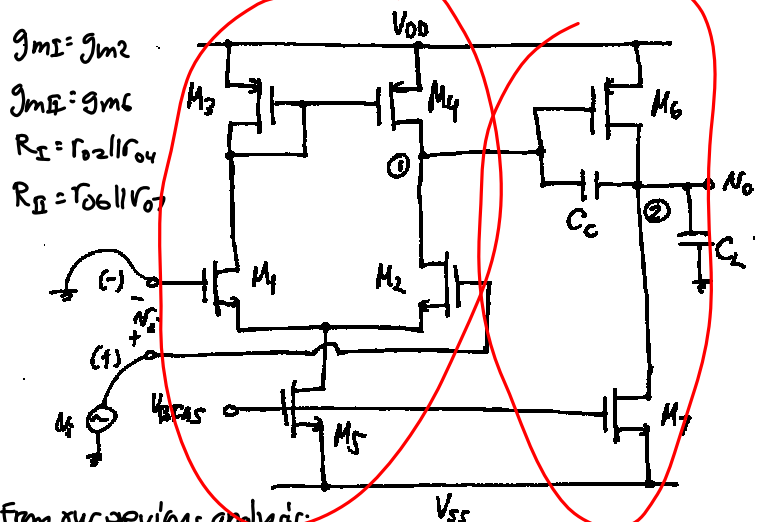


Lecture X: RHP Zero

- Announcements:
- Yep, I'm a substitute teacher
- Lecture Topics:
 - ↳ Nulling the RHP Zero
-
- Not sure, but I'm told that you've already derived the poles and zero of a two-stage CMOS amp
- And you understand how to compensate by

CMOS 2-Stage OpAmp Compensation (Summary)



From our previous analysis:

$$P_1 = -\frac{1}{g_{mII} R_I R_{II} C_C} \quad [C_C \gg C_I \text{ or } C_{II}] \quad [C_L \gg C_I]$$

$$P_2 = -\frac{g_{mII} C_C}{C_I C_{II} + C_C(C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{m6}}{C_L}$$


$$z = +\frac{g_{mII}}{C_C} \leftarrow \text{RHP zero (this will cause problems)}$$

Remarks:

- ① Note that as $C_C \uparrow \rightarrow |p_1| \downarrow$
- ② As $C_C \uparrow \rightarrow |p_2| \uparrow \rightarrow |p_2| = \frac{g_{mII}}{C_I + C_{II}}$ } pole-splitting
- ③ With $C_C = 0$ (i.e., before compensation)

$$P_1 = -\frac{1}{R_I C_I}, \quad P_2 = -\frac{1}{R_{II} C_{II}}$$



- ④ On a pole/zero diagram:

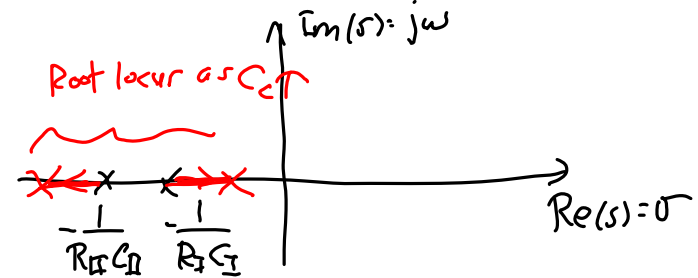

Great! → But what about the RHP zero!

- Now, go through the handouts:
 - ↳ Review of Pole/Zero Plots
 - ↳ RHP Zero
- These give a general picture of how a RHP zero can hurt stability (but a LHP plane zero can really help)

Where Does the RHP Zero Come From?

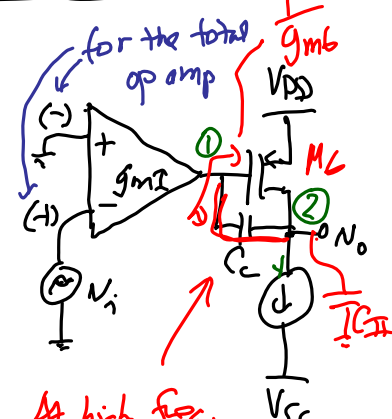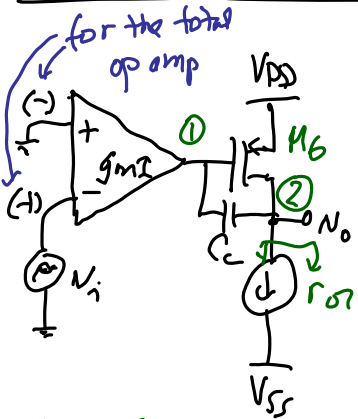

At low freq.:


$$\frac{v_O}{v_i} = -g_{m6}(r_{o6} || r_{O2})$$

$$\text{total gain} = \frac{v_O}{v_i} \cdot \frac{v_i}{v_O} = (+)$$

At high freq.,
this shorts → get a
feed-forward path

$$\frac{v_O}{v_i} = -\frac{g_{m1}}{g_{m6}} = (-)$$

g goes up!

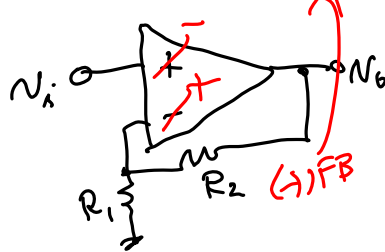


Observation:

Miller effect compensation requires FB path.


↓ BUT: The feedforward path (that creates the zero) is not needed!

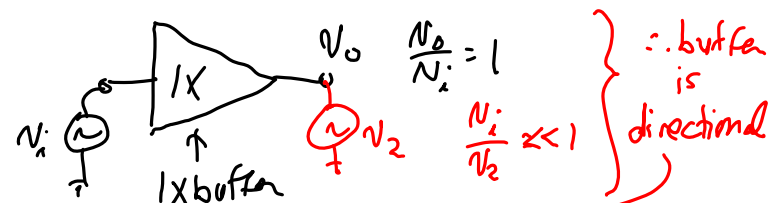Solution: ① Kill the feedforward path.
② keep the feedback path.



Solution: Put a 1x buffer in series w/ C_E to prevent the feedforward path, but allow FB!

The Ckt.

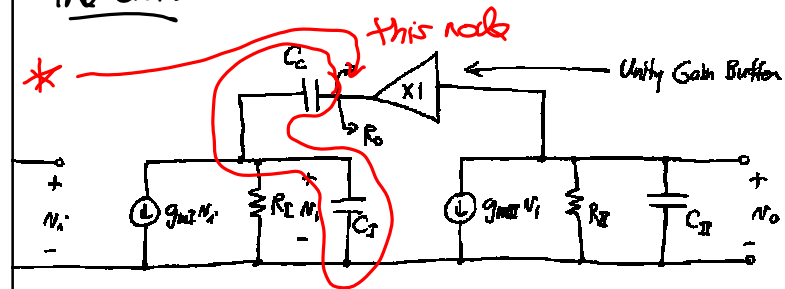

Apply KCL:

$$p_1 \approx -\frac{1}{g_{mII} R_I R_{II} C_c} \quad (\text{same as before})$$

$$p_2 \approx -\frac{g_{mII} C_c}{C_{II}(C_I + C_c)} \approx -\frac{g_{mII}}{C_{II}} \quad [C_c \gg C_I]$$

$$p_3 \approx -\frac{1}{R_o(C_I C_c / (C_I + C_c))} \approx -\frac{1}{R_o C_I}$$

series comb. of C_I & C_c * ← comes from


$$z \approx -\frac{1}{R_o C_c} \leftarrow \text{LHP zero!}$$

Great!

Remarks:

- ① An additional pole $p_3 = -\frac{1}{R_o C_I}$ has been created! But since R_o is small (for a buffer) and C_I is small, p_3 is at a very high freq. \rightarrow contributes very little phase @ ω_{ulg} , where $|T(j\omega)| = 1$.
- ② A LHP zero now emerges, $z_I = -\frac{1}{R_o C_c}$.
 This helps stability as discussed before.
 (by contributing (+) phase shift \rightarrow PMM)

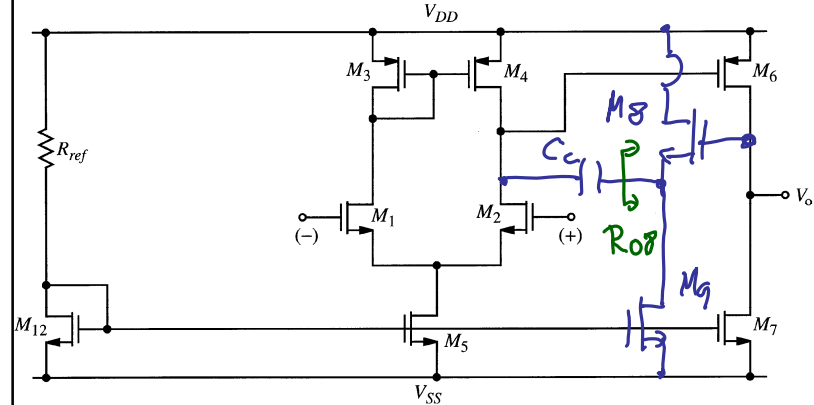Actual Implementation of Buffer-Based Zero Cancellation



$$R_{o8} = \frac{1}{g_{m8}} = \frac{1}{\sqrt{2} \mu_n C_{ox} (\frac{W}{L})_8 I_{D8}}$$

\rightarrow Want this sufficiently small to drive $1/p_3 \uparrow$

increase I_{D8} or increase $(\frac{W}{L})_8$

Problems: more power \times more area \times cost!

Solution: Better technique!

\downarrow over

