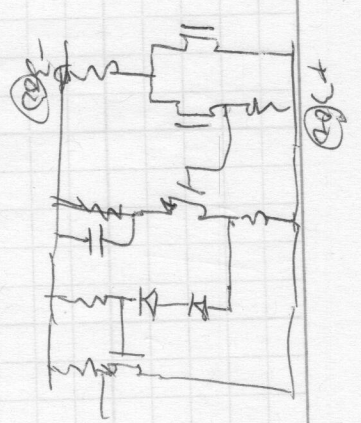




K2-W  
RHP zero  
pole/zero doublet  
2nd stage pole w/  $C_c$




HWF op-amp specs: swing, input common mode  
determining  $V_{ov}$  is  
Tail given  
 $I_S$  is given



expect negative gain here

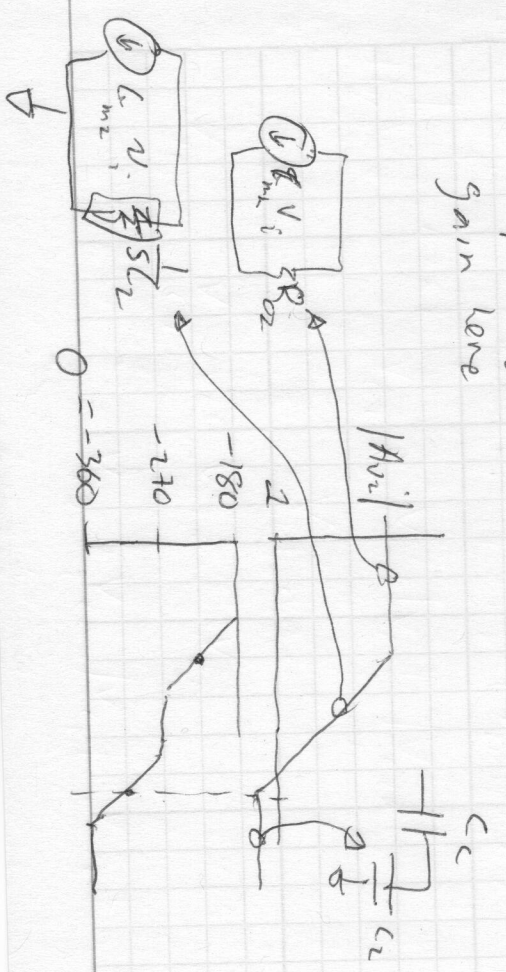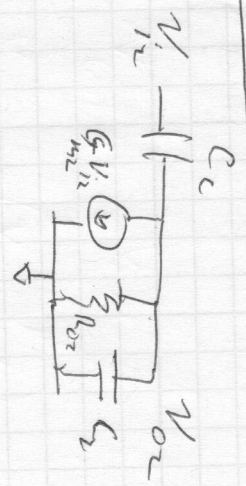

RHP zero

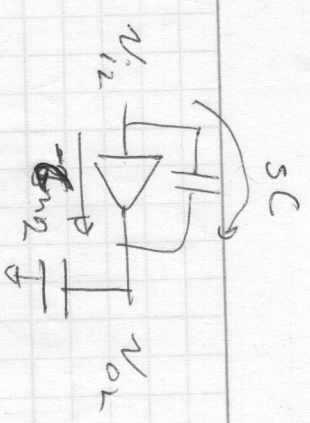

current that we want:  
effect of  $v_{o2}$  on  $v_{o1}$  (Miller)  
current that we don't want:  
effect of  $v_{o1}$  on  $v_{o2}$

If you have  $v_{i2}$  <sup>up</sup> fast enough, then  $v_{o2}$  initially has positive response,  $\frac{C_c}{C_{t1}}$  then settles to negative  $-G_{m2}R_{o2}$

How fast is "fast enough"?

when  $5C_c$  is bigger than  $C_{t2}$  (more correct in  $\beta$  than in transistors capacitor)

that defines  $\omega_z$   $j\omega_z C_c = G_{m2}$


2nd stage pole is general not easy to write a simple expression, but

assuming that Miller is used to split the poles for apud, then

$$\omega_{p2} \approx \frac{g_{m2}}{C_1 + C_2 + \frac{C_1 C_2}{C_c}}$$

$$\approx \frac{g_{m2}}{C_1 + C_2} \quad \text{if } C_c \gg C_1 \text{ or } C_2$$

One way to look at it =

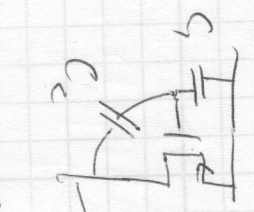


What is output resistance at high freq?  $V_o$  controls gate via cap divides  $V_g = \frac{C_c}{C_1 + C_c} V_o$

$R_{oz}$  reduced by AP!

high freq  $R_{oz} \approx \frac{1}{g_{m2} \frac{C_c}{C_1 + C_c}} = \frac{C_1 + C_c}{g_{m2} C_c}$

$$C_{oz} = C_2 + \frac{C_c C_1}{C_1 + C_c} \Rightarrow \omega_{p2} \text{ same result!}$$

Mirror pole

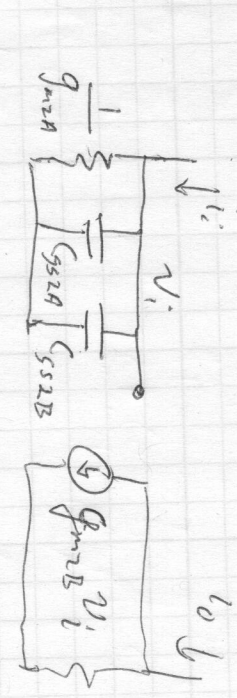


$$i_i = g_{m2A} v_i + 2 s C_{gs2} v_i$$

$$\frac{v_o}{v_i} = g_{m2A} \left( 1 + \frac{s}{g_{m2} C_{gs}} \right)$$

$$\frac{i_o}{i_i} = \frac{g_{m2B}}{g_{m2A}} \frac{1}{1 + s/\omega_{pm}}$$
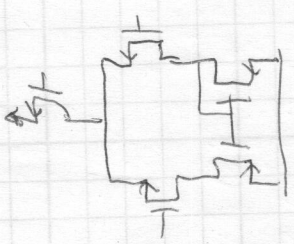
$$\omega_{pm} = \frac{g_{m2A}}{2 C_{gs}}$$




$$G_r = \frac{1}{2} g_{m1B} + \frac{1}{2} g_{m1A} \quad (\text{mirror})$$

$$= g_{m1} \left( 1 + \frac{1}{1 + s/\omega_{pm}} \right)$$

$$= \frac{g_{m1}}{2} \left( \frac{2 + s/\omega_{pm}}{1 + s/\omega_{pm}} \right)$$

$$= \frac{g_{m1}}{2} (2) \frac{(1 + \frac{s}{2\omega_{pm}})}{1 + s/\omega_{pm}}$$
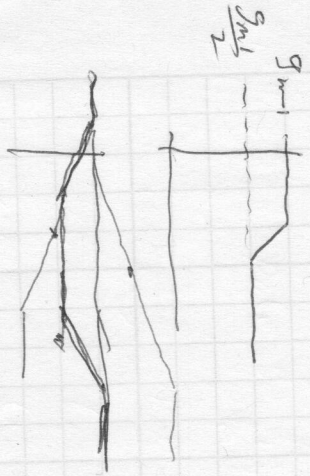
$$= g_{m1} \frac{1 + s/2\omega_{pm}}{1 + s/\omega_{pm}}$$



-3 degrees @  $\frac{w_p}{10}$   
 and @  $10 w_p$   
 -22 degrees @  $\sqrt{2} w_p$

in feedback,  $w_{PIE} \approx f_{Wuc}$   $w_{up} = Wuc$

	uncompensated	(Miller) compensated
$w_{p1}$	$\frac{1}{R_{o1} C_1}$	$\frac{1}{R_{o1} C_{m2} R_{o2} C_c}$
$w_{p2}$	$\frac{1}{R_{o2} C_2}$	$\frac{g_{m2}}{C_1 + C_2 + \frac{C_c}{2}}$
zeros	$w_{pm} = \frac{g_{m2}}{2 C_{c32}}$	same
doublet	$w_{zm} = 2 w_{pm}$	
unity gain	?	$\frac{g_{m1}}{C_c}$ (assuming 1) 2) 3)