

Lab 4

P8Z wired up

Supply indep

current

voltage.

Midterm Friday 3/24 3:10 - 4:30

See me if that's a problem

What about the reverse current? and voltage? (Lab 4)

like to have supply-indep.

current voltage } separately

current: to set device performance.

Voltage: to know what "1V" means.

Challenge: Process V_t, μ_{ox}, λ

Variations in Voltage $V_{th} = n \times \{1.6 \rightarrow 0.8\}$




Temperature 0-70C consumer

-40 to 85C industrial

-55 - 125C mil

1750 W9L2 / 140/240R

2 stage

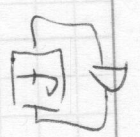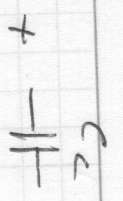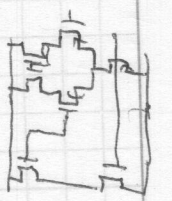

Uncompensated

Compensated

Feedback

$$\omega_{p1} = \frac{1}{R_0 C_1}$$

$$\omega_{p2} = \frac{1}{R_{o2} C_2}$$

minor doublet

$$\omega_{pm} = \frac{g_m}{2C_{SS}}$$

$$\omega_{zn} = 2\omega_{pm}$$

$$\omega_n = ?$$

$$\omega_{p1c} = \frac{1}{R_1 C_1 R_2 C_2}$$

$$\omega_{p2c} = \frac{g_m}{C_1 + C_2 + \frac{C_1 C_2}{g_m}}$$

doublet: same

RHP zero: $\frac{g_m}{C_c}$

zeros x, y, z,

$$\omega_n = \frac{g_m}{C_c}$$

$\omega_n \approx$ same

$$\omega_{PIF5} \approx \omega_n$$

Incl varies $\sim V_{BNT}, R(T), V_{th}(T), V_{to}?$

V_{ref} varies $V_T + V_{ov}$

Sensitivity of y to x $S_x^y = \lim_{\Delta x \rightarrow 0} \frac{\Delta y/y}{\Delta x/x} = \frac{x}{y} \frac{dy}{dx}$

$$e.g. I_{ref} = \frac{V_{BNT} - V_{th} - V_{ov}}{R}$$


$$S_{I_{ref}}^{I_{ref}} = \frac{V_{BNT}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{BNT}}$$

$$= \frac{V_{BNT}}{V_{BNT} - V_{th} - V_{ov}} \frac{1}{R}$$

$$= \frac{V_{BNT}}{V_{BNT} - V_{th} - V_{ov}} \approx 21$$

Can we do better?

I_1, I_2

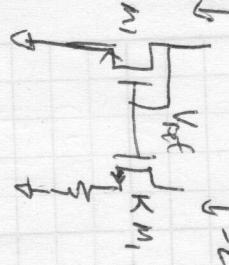

assume both in saturation

$$I_1 = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 V_{ov1}^2$$


$$I_2 = \frac{\mu_n C_{ox}}{2} K \left(\frac{W}{L}\right)_1 (V_{ov1} - I_2 R)^2$$

$$I_2 = K I_1 \text{ if } I_2 R \ll V_{ov1}$$

as I_1 increases, $I_2 R$ increases, V_{ov} increases

but V_{ov} increases more slowly

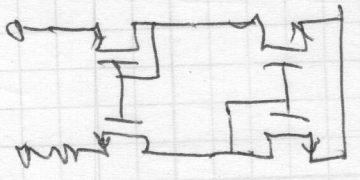enforce that $I_2 = I_1$. How? current mirror



when $I_1 = I_2$

$$V_{ov1}^2 = K (V_{ov1} - I_2 R)^2$$


$$V_{ov1} = \sqrt{K} (V_{ov1} - I_2 R)$$

$$\frac{V_{ov1}}{\sqrt{K}} = V_{ov1} - I_2 R$$

$$I_2 R = \left(1 - \frac{1}{\sqrt{K}}\right) V_{ov1}$$

$$K=4 \Rightarrow I_2 R = \frac{1}{2} V_{ov1} = V_{ov2}$$

Fig 12.3
(11.3 1st ed.)

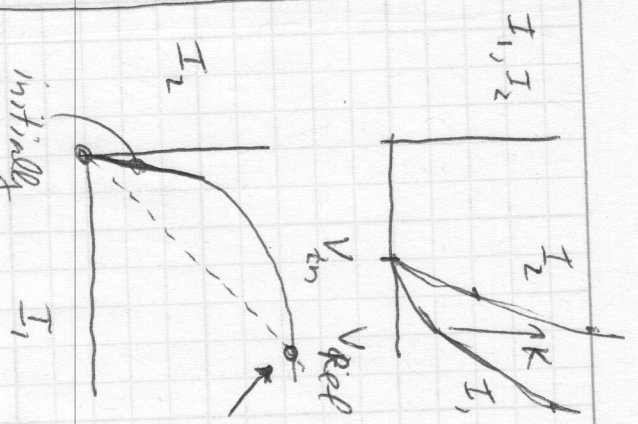

equal in 2 planes

if $K=4$

$$g_{m1} = \frac{2 I_{D1}}{V_{ov1}} = \frac{2 I_2}{2 I_2 R} = \frac{1}{R} \text{ nice!}$$

"constant g_m biasing"

→ generally use long channel devices

→ put resistor on pmos side to avoid body effect in n-well process

→ Startup: tie gates together w/ low


current paths to avoid $I_1 = I_2 = 0$

Temperature sensors,
Temp independent bias voltage

In week 2 we saw that

$$nI_x V_D = \ln(n) V_{TH} = \ln(n) \frac{k_B T}{q}$$




PTAT (12.16)

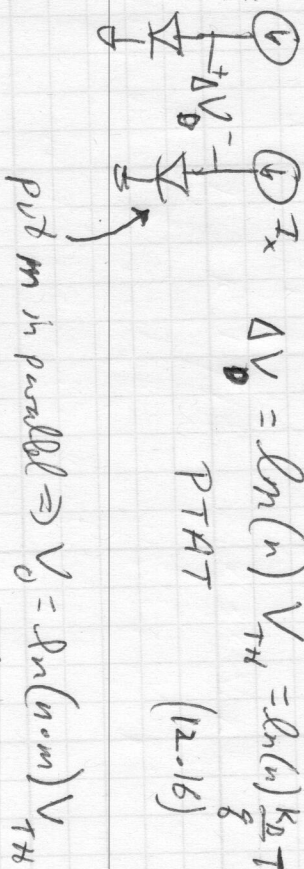

$$V_D(T) \approx V_D(300K) + \alpha \Delta T$$

$$\alpha = (-1.5 \text{ to } -2) \text{ mV/K}$$

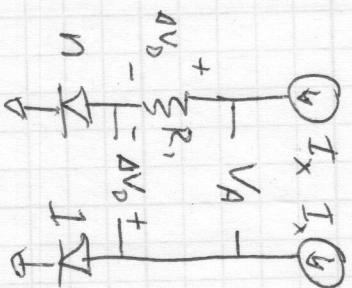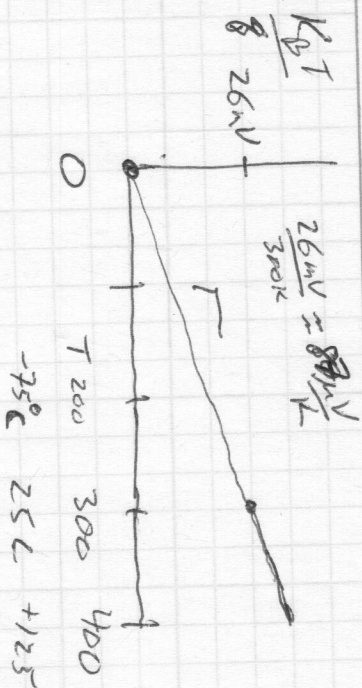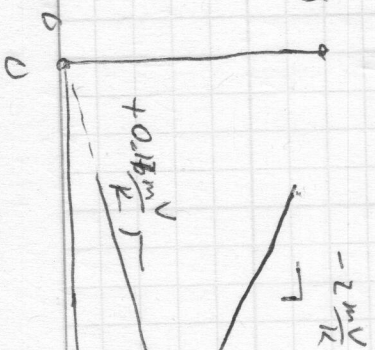
goals: $V_D(T) + \frac{\alpha}{\ln(n)} \frac{k_B}{q} \Delta V_D$



increase I_x until $V_A = 0$

$$I_x R_1 = \ln n V_{TH}$$

PTAT!

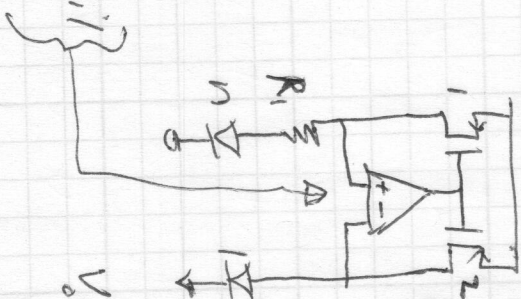

$$V_D = V_D + I_x R_3$$

$$= V_D(T) + \frac{R_3}{R_1} \ln n V_{TH}$$

Choose R_3/R_1 right \Rightarrow no temp CO

