

Midterm Friday 3:10 - 4:30

- previous examples online


$$G_{m2} = \frac{g_{m2}}{2} \quad \text{if } k=4$$

$$\frac{i_o}{v_{dd}} = \frac{1}{r_{o4}} \left[\frac{2g_{m1}}{g_{m2}} - \frac{g_{m4}}{g_{m3}} \right]^{-1}$$

$$= \frac{1}{r_{o4} (2k-1)}$$



make $L_{3,4}$ long or if you have room (at least the top cascode)

lost time

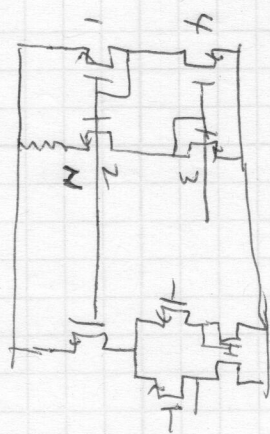

$$I_{D2} = \frac{2}{\mu_n \text{ Cox } (\frac{W}{L})_1} \frac{1}{R_s} \left(1 - \frac{1}{\sqrt{R}}\right)^2$$

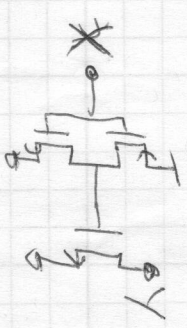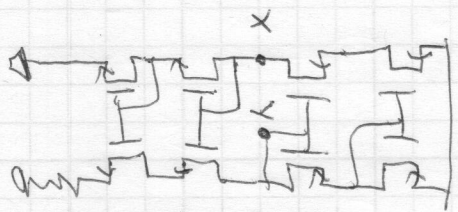
$$\frac{\partial I_{D2}}{\partial v_{DD}} = \frac{i_o}{v_{DD}} = \frac{1}{r_{o4}} \left[\frac{1}{G_{m2} (r_{o4} \parallel \frac{1}{g_{m1}})} - \frac{g_{m4}}{g_{m3}} \right]^{-1}$$



Startup: if $X=0$ pull y low else let y go

make sure that the inverter N and P are sized so that it turns the pull down off when the reference is operating normally

Buckley

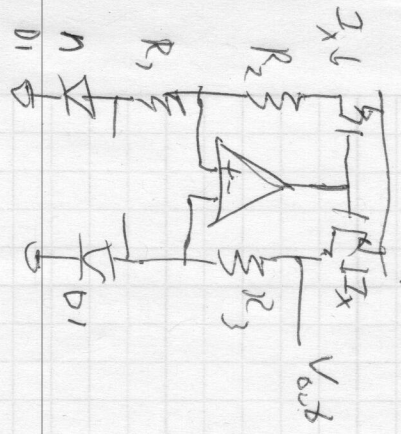

say $n=10$

Feedback circuit

polarity

stability

If $I_{D1} = I_{D2}$ then $V_{D1} > V_{D2}$

in fact $V_{D1} = V_{D2} + \ln(n) V_{Th}$

$$V_{D1} - V_{D2} = \ln(n) \frac{k_B}{q} T$$

if $n=10$

$$0.2 \frac{mV}{K} = \frac{60mV}{300K}$$

True at any current $I_X = 1 \mu A, 1 mA$

$$I_X = 1 mA$$

Let $I_{S1} = 10^{-13} A$ for D1

$$I_{D1} = I_{S1} (e^{V_{D1}/V_{Th}} - 1)$$


@ 25°C $\frac{60mV}{\text{decade}}$

product 600mV

$$V_{D1} = \ln\left(\frac{I_{D1}}{I_{S1}}\right) V_{Th} = 600mV$$

$$V_{D2} = \ln\left(\frac{I_{D2}}{I_{S1}}\right) V_{Th} = 600mV - 60mV$$
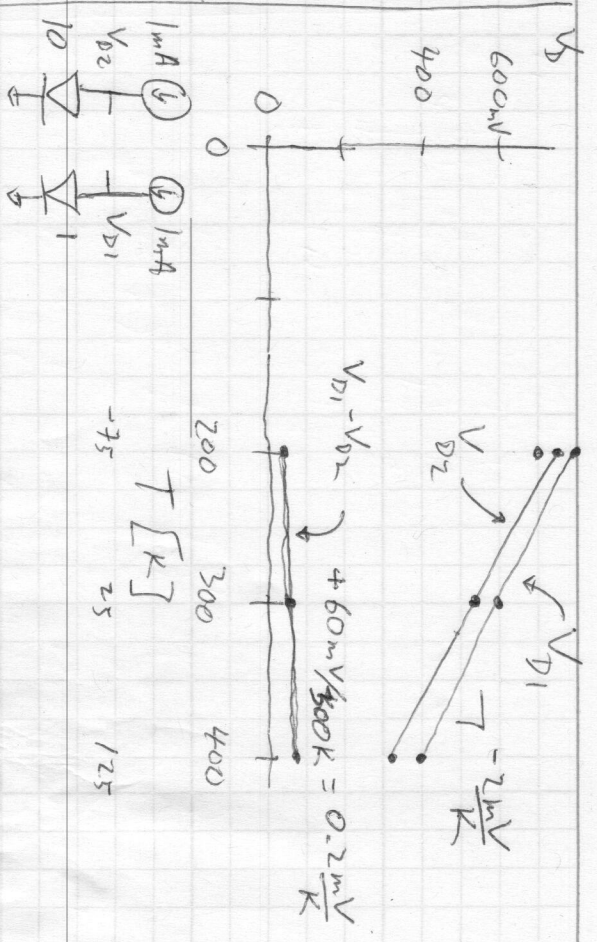
$$= \left[\ln\left(\frac{1}{n}\right) + \ln\left(\frac{I_{D2}}{I_{S1}}\right) \right] V_{Th}$$



Let $R_1 = 60 \Omega$

If $I_X = 1 mA$ $V_{R1} = (1mA)(60\Omega) = 60mV$

@ 25°C, now $V_+ = V_-$

What if I_X is 2mA? $V_+ > V_-$

V_{D2} increases, V_{D1} increases, I_X decreases

until $V_+ = V_-$