

EECS140 Midterm 1  
Spring 2017


Name \_\_\_\_\_

SID \_\_\_\_\_

Page	Score
1	/12
2	/10
3	/20
4	/18
Total	/60

- [4] A single-pole amplifier has a low frequency gain magnitude of 500 and a gain magnitude of 5 at 1 GHz. What are the pole and unity gain frequencies?
  
- [8] You have made a new NMOS transistor. You measure the drain current as a function of the gate-to-source and drain-to-source voltage, and find that it is  $I_d = \alpha(V_{gs} - 1V)^{1.5}(V_{ds})$  when  $1V < V_{gs} < 10V$  and  $0 < V_{ds} < 10$ , where  $\alpha$  is a positive constant with appropriate units.
  - Write an expression for the transconductance in terms of just voltages, and in terms of  $I_d$  and some voltages.
  
  - Write an expression for the output resistance in terms of  $I_d$
  
  - Write an expression for the intrinsic gain in terms of the bias point
  
  - To maximize the gain, where would you bias this device (what voltages)?

 3. [5] A voltage source with a  $1\text{M}\Omega$  output impedance drives an amplifier with a  $1\text{nF}$  input capacitance. At  $t=0$ , the voltage source jumps from 0 to 1V (a step input). Carefully sketch by hand the voltage seen at the input to the amplifier on three different time scales:
- 0 to  $1\ \mu\text{s}$
  - 0 to  $1\ \text{ms}$
  - 0 to  $1\ \text{s}$



4. [5] By hand, sketch the response of the RC filter above to an input sine wave with a 1V amplitude and a frequency of  $1,000\ \text{rad/s}$ . Draw the input for reference, and then the output. Label both axes. Label the input and output sine waves.




5. [8] You have an NMOS-input common source amplifier with a PMOS load and a large load capacitance. Both transistors are biased in saturation, and the quadratic model is appropriate. The magnitude of the gain is large ( $>100$ ). You try two independent changes to the circuit. Case 1: doubling the width of both devices. Case 2: doubling both the width and the length of both transistors without changing anything else. How do these changes affect the operating point and performance of the amplifier?

Process specs  $\mu_n C_{ox}=200\mu A/V^2$ ,  $\mu_p C_{ox}=100\mu A/V^2$ ,  $\lambda=1/(10V)(L_{min}/L)$ ,  $-V_{tp}=V_{tn}=1V$ ,  $V_{DD}=5V$ ,  $L_{min}=1\mu m$ ,  $C_{ox}=5fF/\mu m^2$ ,  $C'_{ol}=0.5 fF/\mu m$ .

	$I_D$	$V_{ov}$	$g_m$	$R_o$	$A_v$	$\omega_p$	$\omega_u$	$C_{in}$
Case 1								
Case 2								

 6. [12] In the same process described above, you have made a similar amplifier with  $(W/L)_N=10\mu/1\mu$ ,  $(W/L)_P=20\mu/1\mu$ . You choose  $V_{GSN}=1.2V$ .
- [4] Carefully sketch  $I_{DN}$  vs.  $V_{out}$ . Put a dot at the transition between triode and saturation. Get the slope right in saturation.
  - [2] What input voltage  $V_{Pmid}$  will result in an output voltage of 2.5V?
  - [2] Sketch the magnitude of the PMOS current vs.  $V_{out}$  if the input is held at  $V_{Pmid}$ .
  - [4] What is the output swing?



7. [12] Fill in the following table for a single-pole amplifier. Each row is a different amplifier.

$g_m$	$R_o$	$C_L$	$A_{v0}$	$\omega_p$	$\omega_u$
		1 $\mu$ F	1000		10 M rad/s
		1nF	$10^6$	10 rad/s	

8. [6] Here's a power MOSFET made at Virginia Tech. The vertical axis is in Amps, from 0 to 12. The horizontal axis is in Volts, from 0 to 12.

- What is a rough guess at the threshold voltage?
- Roughly what is  $g_m$  when  $V_{GS}=V_{DS}=7V$ ?
- Roughly what is  $r_o$  when  $V_{GS}=V_{DS}=7V$ ?

