

EECS140 Midterm 1  
Spring 2017

Name Rubric

SID \_\_\_\_\_

Page	Score
1	/12
2	/10
3	/20
4	/18
Total	/60

1. [4] A single-pole amplifier has a low frequency gain magnitude of 500 and a gain magnitude of 5 at 1 GHz. What are the pole and unity gain frequencies?

$$f_u = 5 \text{ GHz} \quad +2$$

$$f_p = 10 \text{ MHz} \quad +2$$

2. [8] You have made a new NMOS transistor. You measure the drain current as a function of the gate-to-source and drain-to-source voltage, and find that it is  $I_d = \alpha(V_{gs} - 1V)^{1.5}(V_{ds})$  when  $1V < V_{gs} < 10V$  and  $0 < V_{ds} < 10$ , where  $\alpha$  is a positive constant with appropriate units.

- a. Write an expression for the transconductance in terms of just voltages, and in terms of  $I_d$  and some voltages.

$$g_m = \frac{\partial I_d}{\partial V_{gs}} = \frac{1.5 I_D}{V_{GS} - 1V}$$

- b. Write an expression for the output resistance in terms of  $I_d$

$$\frac{1}{r_o} = \frac{\partial I_D}{\partial V_{ds}} = \frac{I_D}{V_{ds}}$$

- c. Write an expression for the intrinsic gain in terms of the bias point

$$A_v = g_m r_o = \frac{1.5 V_{ds}}{V_{GS} - 1V}$$

- d. To maximize the gain, where would you bias this device (what voltages)?


$$V_{GS} = 1V$$

$$V_{DS} = 10V$$


3. [5] A voltage source with a  $1\text{M}\Omega$  output impedance drives an amplifier with a  $1\text{nF}$  input capacitance. At  $t=0$ , the voltage source jumps from 0 to 1V (a step input). Carefully sketch by hand the voltage seen at the input to the amplifier on three different time scales:

- 0 to  $1\ \mu\text{s}$
- 0 to  $1\ \text{ms}$
- 0 to  $1\ \text{s}$

initial slope 1  
0.63 1

 

 4. [5] By hand, sketch the response of the RC filter above to an input sine wave with a 1V amplitude and a frequency of  $1,000\ \text{rad/s}$ . Draw the input for reference, and then the output. Label both axes. Label the input and output sine waves.



axis labels 1  
phase shift 1  
amplitude 1

5. [8] You have an NMOS-input common source amplifier with a PMOS load and a large load capacitance. Both transistors are biased in saturation, and the quadratic model is appropriate. The magnitude of the gain is large ( $>100$ ). You try two independent changes to the circuit. Case 1: doubling the width of both devices. Case 2: doubling both the width and the length of both transistors without changing anything else. How do these changes affect the operating point and performance of the amplifier?

Process specs  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $\mu_p C_{ox} = 100 \mu A/V^2$ ,  $\lambda = 1/(10V)(L_{min}/L)$ ,  $-V_{tp} = V_{tn} = 1V$ ,  $V_{DD} = 5V$ ,  $L_{min} = 1 \mu m$ ,  $C_{ox} = 5 fF/\mu m^2$ ,  $C'_{ol} = 0.5 fF/\mu m$ .

	$I_D$	$V_{ov}$	$g_m$	$R_o$	$A_v$	$\omega_p$	$\omega_u$	$C_{in}$
Case 1	2	1	2	$1/2$	1	2	2	2
Case 2	1	1	1	2	2	$1/2$	1	4

6. [12] In the same process described above, you have made a similar amplifier with  $(W/L)_N = 10 \mu/1 \mu$ ,  $(W/L)_P = 20 \mu/1 \mu$ . You choose  $V_{GSN} = 1.2V$ .


- [4] Carefully sketch  $I_{DN}$  vs.  $V_{out}$ . Put a dot at the transition between triode and saturation. Get the slope right in saturation.
- [2] What input voltage  $V_{Pmid}$  will result in an output voltage of 2.5V? *axis label*
- [2] Sketch the magnitude of the PMOS current vs.  $V_{out}$  if the input is held at  $V_{Pmid}$ .
- [4] What is the output swing?

$0.2$  to  $4.8$

$$\frac{\mu_n C_{ox} W}{2 L} V_{ov}^2 = \left( \frac{100 \mu A}{V^2} \right) (10) (0.64 V^2)$$

$$= 40 \mu A$$
 
$$1 + \lambda V_{DD} = 1 + 0.1(5) = 1.5$$



7. [12] Fill in the following table for a single-pole amplifier. Each row is a different amplifier.

$g_m$	$R_o$	$C_L$	$A_{v0}$	$\omega_p$	$\omega_u$
10	100	1 $\mu$ F	1000	$10^4$	10 M rad/s
$10^{-2}$	$10^8$	1 nF	$10^6$	10 rad/s	$10^7$

2 pts per Partial for having equations

8. [6] Here's a power MOSFET made at Virginia Tech. The vertical axis is in Amps, from 0 to 12. The horizontal axis is in Volts, from 0 to 12.

a. What is a rough guess at the threshold voltage?

$3V < V_T < 5V$  +2 +1 for  $V_{Dsat}$  eqn if wrong

b. Roughly what is  $g_m$  when  $V_{GS} = V_{DS} = 7V$ ?

$2/3 < g_m < 2$  +1 for correct approach

c. Roughly what is  $r_o$  when  $V_{GS} = V_{DS} = 7V$ ?

$7\Omega < r_o < 15\Omega$

+1 for approach

