

Name _____

SID _____

Page	Score
1	/12
2	/10
3	/23
4	/17
Total	/62

1. [2] The LM741 op-amp looks like a single-pole amplifier with a low frequency gain magnitude of about one million and a gain magnitude of 1,000 at 1 kHz. What are the pole and unity gain frequencies?

2. [6] You have made a new NMOS transistor. You measure the drain current as a function of the gate-to-source and drain-to-source voltage, and find that it is $I_d = \alpha(V_{gs} - 1V)^3 V_{ds}^2$ when $1V < V_{gs} < 2V$ and $1 < V_{ds} < 2$, where α is a positive constant with appropriate units.
 - a. Write an expression for the transconductance in terms of just voltages, and in terms of I_d and some voltages.

 - b. Write an expression for the output resistance in terms of I_d

 - c. Write an expression for the intrinsic gain in terms of the bias point

 - d. To maximize the gain, where would you bias this device (what voltages)?

3. [4] You have a diode with $N_D = 10^{15}/\text{cm}^3$, $N_A = 10^{20}/\text{cm}^3$. You calculate that the depletion width is about a micron.
 - a. Is the depletion region mostly in the P side or the N side?


 - b. Estimate the built-in potential at room temperature

 - c. If you increase the N_D doping by a factor of 10,
 - i. how much does the built in potential change?

 - ii. roughly how much does the depletion width change? (e.g. increase by 10x, decrease by $\sqrt{10}$, slight increase, no change, etc.)

4. [4] You have 10 identical diodes. You apply 1mA to one diode and measure 0.7V across it.
 - a. What current do you measure if you apply 0.76V across a single diode?
 - b. What voltage do you measure if you apply 1mA to 10 diodes in series?
 - c. What voltage do you measure if you apply 1mA to 10 diodes in parallel?
 - d. What voltage do you measure if you apply 2.7mA to a single diode?

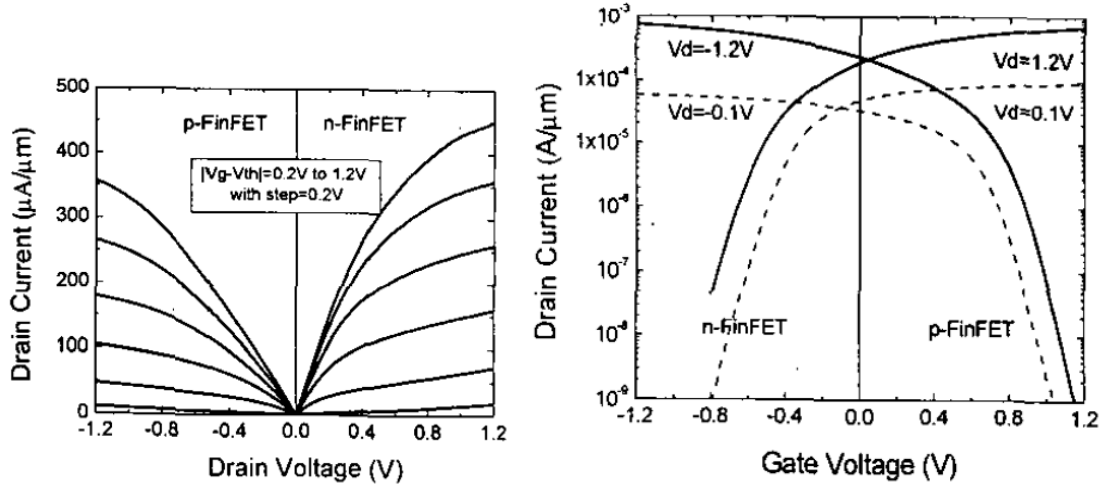5. [6] The graphs below are from an AMD paper from 2002 describing preliminary results from 10nm FinFETs. You can ignore the weird threshold voltages.



- a. [4] Estimate I_d , g_m , and r_o for a $1\mu\text{m}$ wide NMOS biased at $V_{ds} = V_{gs} = 0.8\text{V}$. What is the intrinsic gain of this device?

Fig. 5 Subthreshold I_d - V_g behavior of 10nm gate length CMOS FinFET transistors.
- b. [2] Estimate the NMOS subthreshold slope in mV per decade, and the parameter “n”.

6. [14] You have an NMOS-input common source amplifier with a PMOS load and a large load capacitance. Both transistors are biased in saturation, and the quadratic model is appropriate. The magnitude of the gain is large (~ 100).

Process specs $\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 100 \mu A/V^2$, $\lambda = 1/(10V)(L_{min}/L)$, $-V_{tp} = V_{tn} = 1V$, $V_{DD} = 5V$, $L_{min} = 1 \mu m$, $C_{ox} = 5 fF/\mu m^2$, $C'_{ol} = 0.5 fF/\mu m$.

You change the bias point so that you double V_{ov} . How do the following change?

	I_D	V_{ov}	g_m	R_o	A_v	ω_p	ω_u	C_{in}
double V_{ov} in quadratic		2						

At a different and higher bias point, you enter into the scattering-limited velocity saturation region of operation. If you double V_{ov} again at this operating point, what do you expect to happen

	I_D	V_{ov}	g_m	R_o	A_v	ω_p	ω_u	C_{in}
Double V_{ov} in velocity saturation		2						

7. [9] In the same process described above, you have made a similar amplifier with $(W/L)_N = 40 \mu/1 \mu$, $(W/L)_P = 80 \mu/1 \mu$. You choose $V_{GSN} = 2V$. Assume that the quadratic model is appropriate.


- [3] Carefully sketch I_{DN} vs. V_{out} . Put a dot at the transition between triode and saturation. Get the slope right in saturation.
- [1] What PMOS gate bias voltage will result in an output voltage of 2.5V?

$V_{GP} =$

- [3] Sketch the magnitude of the PMOS current vs. V_{out} with the PMOS gate biased at V_{BP} .
- [2] What is the output swing?

$\{V_{out,min} V_{out,max}\} =$


Label this axis!

 

8. [6] Fill in the following table for a single-pole amplifier. Each row is a different amplifier.

g_m	R_o	C_L	A_{v0}	ω_p	ω_u
1m	1M	1uF			
		1pF	10		100Grad/s

 9. [11] For the circuit below, assume that $\mu_n C_{ox}(W/L)_n = \mu_p C_{ox}(W/L)_p$ and $\lambda_n = \lambda_p$ for all devices, and $V_{tn} = -V_{tp} = 0.5V$. You may assume that all devices are biased in saturation, and the quadratic model is appropriate. You may assume that $g_m r_o \gg 1$ for all combinations (so simplify).



a. In terms of g_{m1} , r_{o2} , r_{o4} , etc., what is the impedance seen looking up from VS2

$R_{S2up} =$

b. ...and looking down from VS2?

$R_{S2down} =$

c. What is the simplified impedance seen at VS2 and Vout, assuming that all " g_m "s are equal and all " r_o "s are equal?

$R_{S2} =$

$R_{out} =$

d. What is the appropriate DC bias on the gate of M1?

$V_{IN} =$

e. What is the minimum voltage for the gate of M3 such that M4 stays in saturation?

$V_{BN,min} =$

f. What is the maximum voltage for the gate of M2 such that M1 stays in saturation?

$V_{BP,max} =$

g. If the gates of M2 and M3 are biased according to your answers above, what is the output swing?

$\{V_{out,min} V_{out,max}\} =$

h. If $V_{BP} = V_{BN} = 5V$ do all devices remain in saturation? If so, what is the output swing

$\{V_{out,min} V_{out,max}\} =$