

University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science

EECS 150
Fall 2005

R. H. Katz

Student Background Questionnaire and Diagnostic Quiz

Name: _____

Student ID: _____ Card Key # (for lab access): _____

Circle one: Freshman Sophomore Junior Senior Graduate

Have you taken CS 61C? Yes No When? Semester/Year: _____

Have you taken EE 40? Yes No When? Semester/Year: _____

What is your most ambitious software project (not limited to course projects)?

What is your most ambitious hardware project (not limited to course projects)?

How would you describe your skills and interests (circle one per line)?

Mathematical/Analytical

Engineering/Building Things

Hardware

Software

Electrical Engineering

Computer Science

Components

Architecture

Systems

Applications


Technology

Business

The following are diagnostic questions to test your retention of basic knowledge from CS 61c. If they are mysterious, then you probably are not ready to take CS 150.

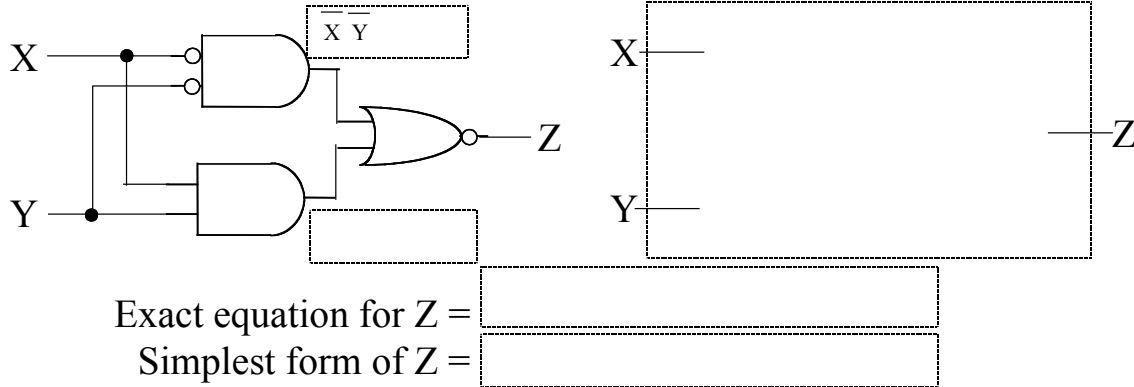
1. Logic Gates and Boolean Equations

The following implements a logic function $Z(X, Y)$. Write a Boolean equation that corresponds exactly to the schematic and a second equivalent equation with the fewest possible Boolean operations and operands. You may use any kind of Boolean operation in your solution to the second part of this question. Write the schematic for this simplest form in the box at the right.



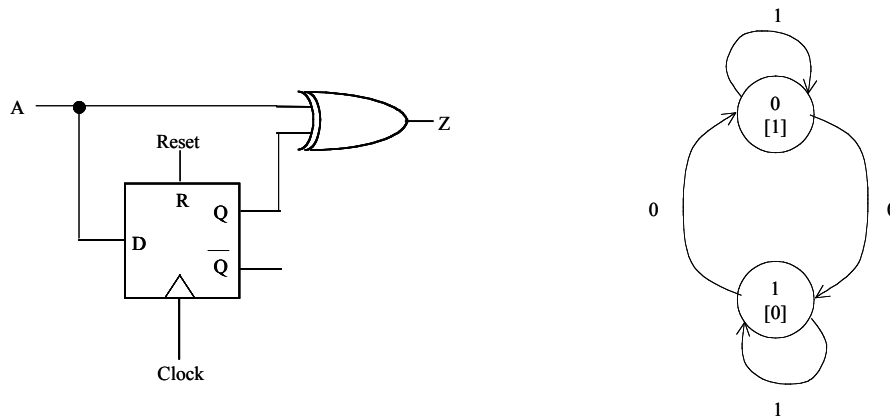2. Flip-flops and State Diagrams

The state diagram on the right purportedly represents the sequential circuit at the left. It has many mistakes, sometimes repeated more than once. Give THREE unique things that are GENERICALLY wrong this diagram:



1. _____
2. _____
3. _____