# NEM Relay Design for Compact, Ultra-Low-Power Digital Logic Circuits

T.-J. K. Liu<sup>1</sup>, N. Xu<sup>1</sup>, I.-R. Chen<sup>1</sup>, C. Qian<sup>1</sup>, J. Fujiki<sup>2</sup>

<sup>1</sup>Dept. of Electrical Engineering and Computer Sciences University of California, Berkeley, CA USA <sup>2</sup>Toshiba Corporation, Tokyo, Japan

**December 16, 2014** 

#### Acknowledgement

**Center for Energy Efficient Electronics Science (NSF Award 0939514)** 

### A Vision of the Future Internet of Things $\rightarrow$ ultra-low-power required!



### **CMOS Energy-Efficiency Limit**



### **CMOS Energy-Efficiency Limit**



#### Why Nano-Electro-Mechanical Relays?

- Zero off-state leakage → Zero static power
- Abrupt switching  $\rightarrow$  Low  $V_{DD}$  (low dynamic power)

**Basic Electro-Mechanical Switch** 







 Relay endurance > 10<sup>15</sup> cycles for hot-switching below 1 Volt

H. Kam et al., 2010 IEDM

#### **Outline of Presentation**

- Overcoming Surface Adhesion Energy Limit
- Compact BEOL Relay Design
- Zero Crowbar Current Relay-Based Circuits
- Conclusion

## **Normally-OFF Switch Design**

#### **OFF State (as fabricated)**

**ON State** 





• Turn OFF by spring force  $\rightarrow F_{spring} > F_{adh}$ 

- Turn ON by electrostatic force  $\rightarrow F_{elec} > F_{spring} > F_{adh}$
- Minimum operating energy is limited by adhesion

   Limits actuation area and/or voltage scaling

## **Normally-ON Switch Design**

#### **ON State (as fabricated)**

**OFF State** 



• Spring force counteracts adhesive force

• Turn OFF by electrostatic force  $\rightarrow F_{elec} < F_{adh}$ 

Operating energy can be smaller than E<sub>adhesion</sub>
 <u>Challenge</u>: Ultra-small (~1 nm) contact gap required

I-R. Chen et al. (UC Berkeley), to be published



- Electrostatic force is applied to switch between states
- Contacting state is non-volatile if F<sub>adh</sub> > F<sub>spring</sub>

#### **Outline of Presentation**

- Overcoming Surface Adhesion Energy Limit
- Compact BEOL Relay Design
- Zero Crowbar Current Relay-Based Circuits
- Conclusion



#### **3-D Integration with CMOS**

 Advanced back-end-of-line (BEOL) processes have multiple metal layers and air gaps

 -> can be adapted for fabrication of NEM relays!

#### **Scanning Electron Micrographs**



D. C. Edelstein (IBM), 214th ECS Meeting, Abstract #2073, 2008



S. Natarajan *et al.* (Intel), Paper 3.7, *2014 IEDM* 

#### **BEOL SPDT NEM Switch**



courtesy of Dr. Kimihiko Kato (UC Berkeley)

- 5-terminal SPDT switch implemented using 4 interconnect layers
  - Vias are used for electrical connection and as torsional elements for lower k<sub>eff</sub>
- Fixed actuation electrodes on opposite sides of movable structure
   → 2 stable states (contacting D<sub>0</sub> or D<sub>1</sub>)

## **BEOL NEM Switch Operating Voltage**

N. Xu et al., (UC Berkeley), Paper 28.8, IEDM 2014

 Low-voltage (<1 V) operation can be achieved with a small device footprint (< 0.1 μm<sup>2</sup>).



#### **BEOL Design Parameters**

Material	Al
Pitch	<b>42 nm</b>
Width	<b>21 nm</b>
Aspect Ratio	1.9

#### **NVM Technology Comparison**

• A bi-stable NEM switch operates with much lower energy and delay than other NVM devices.



#### **Outline of Presentation**

- Overcoming Surface Adhesion Energy Limit
- Compact BEOL Relay Design
- Zero Crowbar Current Relay-Based Circuits
- Conclusion

### 6-Terminal (6-T) SPDT NEM Relay



If a common output electrode is used insulated from the input then the relay functions as a 2:1 multiplexer (MUX)  $OUT = \overline{IN} \cdot D_0 + IN \cdot D_1$ 



#### **Basic 6-T Relay Logic Gates**



- OUT terminals each are connected to a D terminal
  - → one mechanical delay, i.e. single-stage operation

Measured Voltage Waveforms



#### **Multiple-Input AND and OR Gates**

- Any combinational logic function can be implemented with 2:1 MUX relays using binary decision diagram techniques
  - D. Lee et al. (Stanford), IEEE T-CADICS, Vol. 32, pp. 653-666, 2013



J. Fujiki et al. (UC Berkeley), IEEE T-ED, Vol. 61, pp. 3296-3302, 2014

#### 4:1 Multiplexer ...

A 2N:1 multiplexer is implemented with N(N+1)/2 switches



• An N-bit decoder is implemented using 2<sup>N+1</sup>-2 switches

#### **Full Adder**

for carry-lookahead adder



#### **Device Count Comparison**

• Relay-based implementation results in lower device count:

FUNCTION	CMOS	6-T NEM RELAY
BUF	4	1
NOT	2	1
NAND	4	2
XOR	6	2
2:1 MUX	8	1
Full adder	24	8

• Note that each of the relay-based circuits are single-stage (1 mechanical delay).

#### **Outline of Presentation**

- Overcoming Surface Adhesion Energy Limit
- Compact BEOL Relay Design
- Zero Crowbar Current Relay-Based Circuits
- Conclusion

#### Conclusion

- Surface adhesion does not set a fundamental limit for NEM relay operating energy if adhesion force is used to switch ON a relay
- An advanced CMOS BEOL technology can be leveraged to fabricate vertical NEM relays
   Footprint < 0.1 μm<sup>2</sup>; switching voltage < 1 V See Paper 28.8 (12 noon tomorrow!)
- A complementary (SPDT) relay design ensures zero crowbar current (as well as zero leakage) and provides for substantial reduction in device count