

EE105 Lab Experiments

Report 10: Differential Amplifiers

Solutions

3.2.2 Measure I_{C1} , I_{C2} , I_{C3} , and $V_{OUT,DC}$. How do they compare with hand calculations?

$$I_{C1} = 1.741 \text{ mA}$$

$$I_{C2} = 2.076 \text{ mA}$$

$$I_{C3} = 1.035 \text{ mA}$$

$$V_{OUT,DC} = 3.860 \text{ V}$$

I_{C1} matches very well with hand calculations (0.6 % error). I_{C2} is much larger than what we'd expect assuming $V_A = \infty$, meaning V_{CE2} must be quite high (which makes sense given the biasing). I_{C3} , correspondingly, is larger than expected, making $V_{out,DC}$ smaller than expected.

3.2.3 Sketch the waveforms at v_{in+} and v_{out+} .

3.2.4 Measure the peak-to-peak voltages of v_{in+} and v_{out+}

$$v_{in+,p-p} = 56.25 \text{ mV}$$

$$v_{out+,p-p} = 4.875 \text{ V}$$

3.2.5 Qualitatively describe how v_{out+} and v_{out-} are related. Is this what you'd expect?

They're inverses of each other. Given that this is a differential amplifier, this is expected.

3.2.6 Measure the peak-to-peak voltage of $v_{out+} - v_{out-}$ and calculate the differential gain of the circuit. Does this match the gain you calculated in the prelab?

$$v_{out,p-p} = 9.688 \text{ V}$$

$$A_{DM} = 172.2$$

This exceeds the gain computed in the prelab by about 9.5 %. This is a result of I_{C3} , and therefore g_{m3} , being larger than expected.

3.2.7 What do you see at the output? Why?

There should be no output signal. This is because the common-mode gain is extremely small.

3.2.8 Measure the gain. Does it match your prelab calculations? Does it match your result from 3.2.6?

$$A_{DM} = \boxed{160.0}$$

It is a bit more than the gain in the prelab and a bit less than the gain from 3.2.6. It's within 10 % of both.

3.3.2 Sketch the output waveform. Why isn't it sinusoidal?

The gain is too large. The output is swinging to the rail, creating a square-like wave.

3.3.4 Calculate the differential gain of the amplifier with the added load.

$$R_{out} = 5 \text{ k} \parallel r_{o4} \parallel r_{o6} = 3.876 \text{ k}\Omega$$

$$A_{DM} = \boxed{129.1}$$

3.3.5 Sketch v_{out} . What is the measured differential gain of the circuit? How does it compare to your hand calculations? Does it match the gain you observed in step 3.2.6? Should it?

$$A_{DM} = \boxed{158.1}$$

The gain is about 22.5 % higher than expected. This means that the output resistance didn't drop as much as expected, which means that r_{o4} and r_{o6} aren't as low as calculated by hand. It's within 10 % of the gain measured in 3.2.6. They should be roughly the same, assuming that the 5 k Ω load dominates R_{out} .

3.4.1 Attach your netlist on a separate sheet.

* EE105 Lab 10 - Differential Amplifiers with Active Load

.inc '2N3904.mod'

.inc '2N3906.mod'

* +/- 9V supply

vcc vcc gnd 9V

vee gnd vee 9V

```

* Current mirror
r1 vcc vb1 10k
q1 vb1 vb1 vee QN3904

* Tail transistor
q2 vc2 vb1 vee QN3904

* Input transistors
q3 vop vip vc2 QN3904
q4 von vin vc2 QN3904

* Load resistors
r2 vop vcc 5k
r3 von vcc 5k

* Differential input
vdiff vdiff gnd SIN(0 30mV 1k 0s 0 0)
eip vip gnd vdiff gnd 0.5
ein vin gnd vdiff gnd -0.5

.op
.tran 0.001ms 5ms
.option post=2 nomod
.end

```

3.4.2 Use SPICE to find I_{C1} , I_{C2} , I_{C3} , and $V_{out,DC}$. Compare these values with your calculations from the prelab and measurements in lab.

$$I_{C1} = 1.7083 \text{ mA}$$

$$I_{C2} = 1.8852 \text{ mA}$$

$$I_{C3} = 935.9 \text{ } \mu\text{A}$$

$$V_{OUT,DC} = 4.321 \text{ V}$$

These values are comparable to both the hand-calculated values and the values measured in lab. They match more closely to the hand-calculated values than the measured values.

3.4.3 Attach your plot on a separate sheet. What is the gain as measured from the plot? Does it match your hand calculations? Does it match your measurements?

$$A_{DM} = 155$$

This gain is comparable to both the hand-calculated gain and the measured gain of this circuit. It lies within 10 % of both values.