

EE105 Lab Experiments

## Report 3: Bipolar Junction Transistor Characterization

### Solutions

3.1 & 3.2 For each measurement of  $V_{BE}$ ,  $V_{BC}$ ,  $I_B$ , and  $I_C$ , fill in the corresponding entry in Table 1 and compute the resulting  $\beta$  and  $\alpha$ .

Parameters	Forward Active	Saturation	Cutoff	Reverse Active
$V_{BE}$	0.6 V	0.596 V	-2.68 V	-4.55 V
$V_{BC}$	-1.72 V	0.473 V	-7.33 V	0.492 V
$I_B$	2.2 nA	3.2 nA	0 A	3.5 nA
$I_C$	0.5 mA	0.363 mA	0 A	-0.0126 mA
$\beta$	227.27	N/A	N/A	-3.6
$\alpha$	0.9956	N/A	N/A	0.7826

**Table 1:** Regions of operations and measurements

3.1.2 Measure  $V_{BE}$  and  $V_{BC}$ . What is the region of operation?

Forward active

$$V_{BE} = 0.6 \text{ V}$$

$$V_{BC} = -1.72 \text{ V}$$

3.1.3 Measure  $I_B$  and compute  $\beta$ .

$$\beta = \frac{I_C}{I_B} = \frac{0.5 \text{ mA}}{2.2 \text{ nA}} = 227.27$$

$$I_B = 2.2 \text{ nA}$$

$$\beta = 227.27$$

3.1.4 Calculate  $I_E$  using  $\alpha$  and measure  $I_E$ . Do the results agree?

$$\alpha = \frac{\beta}{1 + \beta} = \frac{227.27}{1 + 227.27} = 0.9956$$

$$\text{(Calculated) } I_E = \frac{I_C}{\alpha} = 0.50221 \text{ mA}$$

$$\alpha = 0.9956$$

$$\text{(Calculated) } I_E = 0.50221 \text{ mA}$$

$$\text{(Measured) } I_E = 0.5022 \text{ mA}$$

3.1.5 Measure  $I_B$  and  $I_C$  with your fingers around the BJT. How do the values compare to the values without heating the BJT?

$I_C$  increases, but  $I_B$  stays the same.

$$I_B = 2.2 \text{ nA}$$

$$I_C = 0.5045 \text{ mA}$$

3.1.6 Explain, using the equation you know for collector current, how you'd expect  $I_C$  to vary with temperature. Does this agree with your experimental results? If not, explain why this might be the case. *Hint:  $I_S$  depends on the intrinsic carrier concentration  $n_i$  and the diffusion coefficients  $D_n$  and  $D_p$ . Intuitively, how would  $n_i$ ,  $D_n$ , and  $D_p$  change with temperature? How would  $I_S$  change with temperature as a result?*

If you consider  $I_S$  a constant, as we have often done in this class, you may think it obvious that the collector current should decrease if  $T$  increases, since  $I_C = I_S (e^{qV_{BE}/kT} - 1)$ . However,  $I_S$  in fact depends on  $n_i$ ,  $D_n$ , and  $D_p$  in the following way (for a general PN junction):

$$I_S = qn_i^2 A \left( \frac{D_p}{N_d W_n} + \frac{D_n}{N_a W_p} \right)$$

Intuitively, you should know that  $n_i$  increases with temperature (since more thermal energy allows more charge carriers to be intrinsically mobiler) and that  $D_n$  and  $D_p$  increase with temperature (diffusion is more rapid at higher temperatures). If you look up equations for these values, you'll find your intuition is correct, as  $n_i \propto e^{-E_g/2kT}$ ,  $D_n = \mu_n kT/q$ , and  $D_p = \mu_p kT/q$ .

Thus, a reasonable explanation for why  $I_C$  increases with temperature is that the increase in  $I_S$  outweighs the decrease in  $e^{qV/kT}$ .

3.1.7 Does  $\beta$  agree with the value listed in the datasheet? If not, explain why you might see discrepancies.

Discrepancies may come from fabrication variation, temperature dependence, and measurement error.

3.1.8 Set  $V_{BB}$  to 4 V and  $V_{CC}$  to 2 V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?

Saturation

$$I_B = 3.2 \text{ nA}$$

$$I_C = 0.363 \text{ mA}$$

$$V_{BE} = 0.596 \text{ V}$$

$$V_{BC} = 0.473 \text{ V}$$

3.1.9 Set  $V_{BB}$  to  $-3$  V and  $V_{CC}$  to 5 V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?

Cutoff

$$I_B = 0 \text{ A}$$

$$I_C = 0 \text{ A}$$

$$V_{BE} = -2.68 \text{ V}$$

$$V_{BC} = -7.33 \text{ V}$$

3.1.10 Swap the emitter and collector. Set  $V_{BB}$  to 4 V and keep  $V_{CC}$  at 5 V. Measure  $I_B$ ,  $I_C$ ,  $V_{BE}$ , and  $V_{BC}$ . What is the region of operation?

Reverse Active

$$I_B = 3.5 \text{ nA}$$

$$I_C = -0.0126 \text{ mA}$$

$$V_{BE} = -4.55 \text{ V}$$

$$V_{BC} = 0.492 \text{ V}$$

Use all of the data you've collected up to this point to fill out Table 1.

3.2.2 Attach the plot of the I-V curve to this worksheet. Label the two regions of operation and draw the boundary between them.

See Figure 1 for the BJT I-V curve.

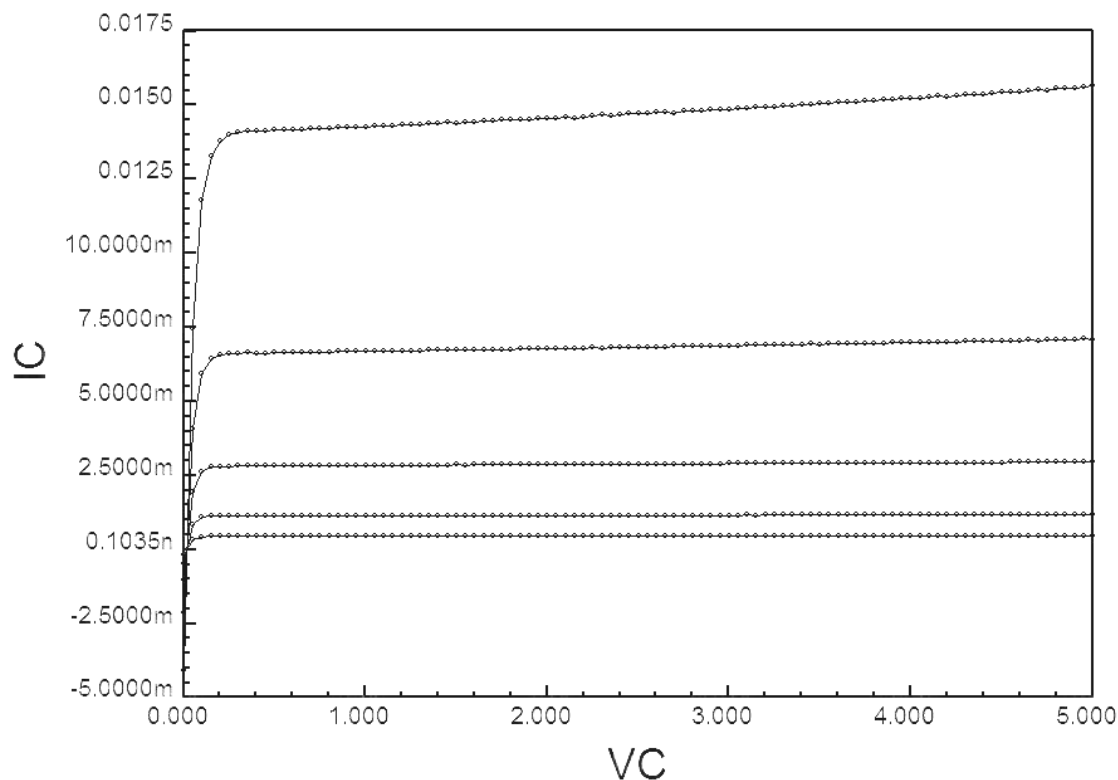


Figure 1: I-V curves for a BJT.

3.2.3 Use the I-V curve to determine  $V_A$ .

$$V_A = I_{C,SAT} \cdot r_o$$

$$r_o = \frac{1}{\text{Slope in Forward Active}}$$

$$V_A = 173.077 \text{ V}$$

3.2.4 Repeat your calculation of  $V_A$  for base voltages of 0.625 V, 0.65 V, 0.675 V, and 0.7 V (you can step the base voltage in ICS to get this data). Does  $V_A$  depend on  $V_B$ ? Why?

$V_A$  depends on  $V_B$ .  $V_A$  being constant with  $V_B$  is just an approximation. In reality, changing  $V_B$  (holding  $V_E$  constant) will change the quasi-neutral base width due to the change in depletion width in the base-emitter junction. Therefore,  $V_A$ , which captures the effect of the change in depletion width in the base-collector junction relative to the quasi-neutral base width, changes with  $V_B$  when  $V_E$  is


$V_B$	$V_A$
0.600 V	173.077 V
0.625 V	145.987 V
0.650 V	111.111 V
0.675 V	77.77 V
0.700 V	57.5 V

**Table 2:** Early voltage calculations

held constant.

3.3.2 Attach the plot of the I-V curve to this worksheet. What semiconductor device does this I-V curve look like?

See Figure 2 for the I-V curve. This device looks like a diode.

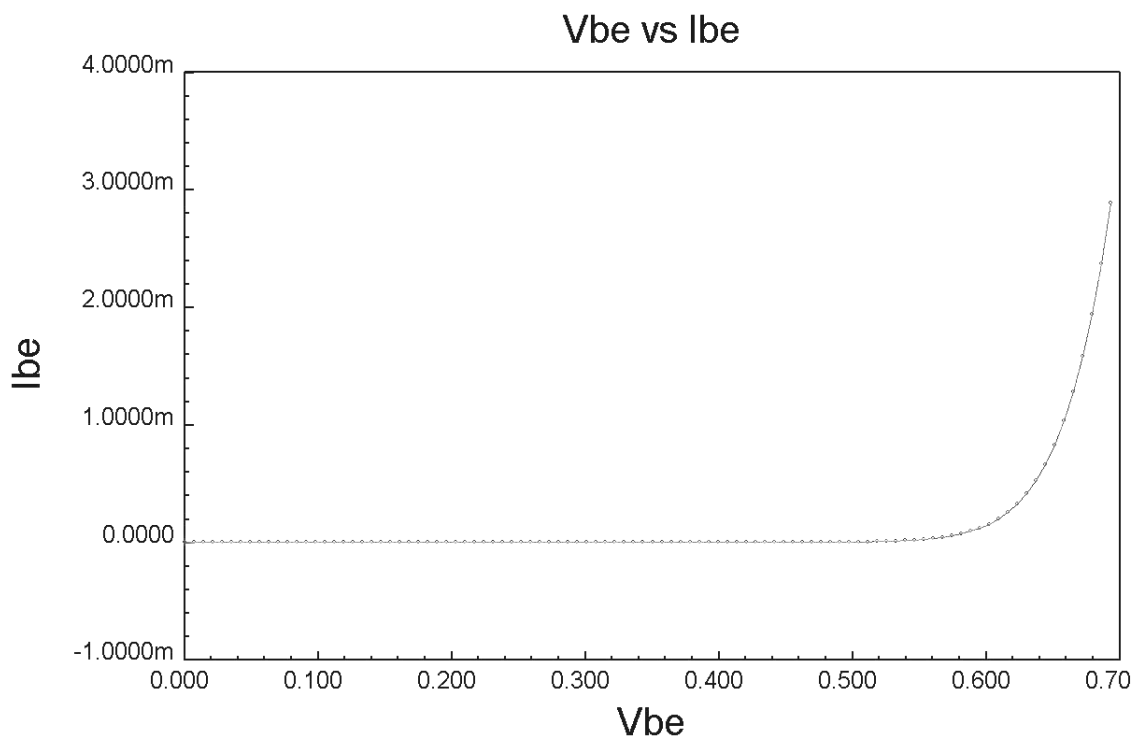

**Figure 2:** I-V characteristic of a diode-connected BJT.

3.4.2 Measure  $I_{B1}$ ,  $I_{C1}$ ,  $I_{B2}$ , and  $I_{C2}$ . Calculate  $\beta_1$  and  $\beta_2$ .

$$\beta_1 = \frac{I_{C1}}{I_{B1}} = \frac{0.0286 \text{ mA}}{0.3 \text{ nA}} = 95.33$$

$$\beta_2 = \frac{I_{C2}}{I_{B2}} = \frac{6.9 \text{ mA}}{0.0289 \text{ mA}} = 238.75$$

$$I_{B1} = 0.3 \text{ nA}$$

$$I_{C1} = 0.0286 \text{ mA}$$

$$I_{B2} = 0.0289 \text{ mA}$$

$$I_{C2} = 6.9 \text{ mA}$$

$$\beta_1 = 95.33$$

$$\beta_2 = 238.75$$

3.4.3 What is the overall current gain,  $\beta_{tot}$ ? Use the formula you derived in the prelab to calculate the total current gain from  $\beta_1$  and  $\beta_2$  and compare the calculation to your measurement.

$$\begin{aligned} \text{(Calculated)} \quad \beta_{tot} &= \beta_2(1 + \beta_1) \\ &= 238.75 \cdot (1 + 95.33) \\ &= 22998.79 \end{aligned}$$

Measurement error:

$$\frac{23000 - 22998.79}{22998.79} = 5.26 \times 10^{-5}$$

$$\text{(Measured)} \quad \beta_{tot} = 23000$$

$$\text{(Calculated)} \quad \beta_{tot} = 22998.79$$